

RADIO & TELEVISION NEWS

WTMJ's MOBILE TELEVISION UNIT

Page 53



Kills Two Birds with One Stone



The Mallory Midgetrol



You win *two* ways with the amazing Mallory Midgetrol.

First, it is ideal for servicing auto radios, portables and other sets requiring small size controls. Second, its husky electrical capacity allows you to use it in sets originally equipped with older, bulkier controls.

So when you stock the Mallory Midgetrol, you're actually able to handle more jobs with a smaller inventory. That's important these days.

LOOK WHAT THE MALLORY MIDGETROL OFFERS:

WIDER APPLICATION—The small size allows you to service portables, auto radios and small AC-DC receivers requiring $1\frac{5}{16}$ " controls.

SIMPLER INSTALLATION—The new and unique flat shaft design of the Mallory Midgetrol saves installation time with *all* types of knobs.

LESS INVENTORY—Electrical characteristics allow you to use the Mallory Midgetrol to replace $1\frac{1}{2}$ " as well as $1\frac{5}{16}$ " controls. Since no special shafts are required, you carry fewer controls in stock.

NEW SIZE
NEW DESIGN

NEW SHAFT
NEW EXTENSION

NEW SWITCH
NEW ELEMENT

NEW CONTACT
NEW TERMINAL

NEW TWO-POINT SUSPENSION

See your Mallory Distributor for this new standard in carbon controls

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS ... CONTROLS ... VIBRATORS ...
SWITCHES ... RESISTORS ... RECTIFIERS
VIBRAPACK* POWER SUPPLIES ... FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

NEW

I'LL TRAIN YOU FOR YOUR FCC LICENSE

A Federal Communications Commission Commercial Operator's License puts you in line for a good job in Radio or Television Broadcasting, Police, Marine, Aviation, Two-way, Mobile or Micro-wave Relay Radio. Mail coupon below for book and catalog (both FREE) about my NEW Communications course.

YOU BUILD THIS TRANSMITTER

with parts I send. This low-power broadcasting transmitter shows you how to put a station "on the air." You perform procedures demanded of Broadcast Station Operators, conduct many experiments, make many practical tests.

LEARN COMMUNICATIONS by PRACTICING at Home in Spare Time

with MANY KITS of

MODERN EQUIPMENT I SEND

Ever think HOW FAST Radio-Television Communications is changing, developing, growing? Have you considered what this amazing progress can mean to you?

In 1945, there were 943 Broadcasting Stations. Today 2,694 are on the air! Result—THOUSANDS OF QUALIFIED MEN STEPPED INTO GOOD JOBS. Only 19 Television Stations were on the air in 1947. Today there are more than 50 and experts say there will be 150 in a few months, 1,000 within three years. That means thousands of well-paid jobs for trained Operators and Technicians. Then add development of FM, Two-way Radio, Police, Marine, Aviation and Micro-wave Relay Radio! Think what all this means! New jobs, more jobs for beginners! Better jobs, better pay for experienced men!

Are you a beginner who wants steady work in this growing field? My NEW course can help you get an FCC License and prepare for the job you want. Are you a man with some training in Radio or Radar, or a Licensed operator? My NEW course modernizes, increases the value of your knowledge and experience!

MY COURSE INCLUDES TELEVISION

Course is New! Different!

Mail coupon now for facts about my NEW, intensely practical course in Radio-Television Communications. Let me send you FREE books. Read outlines of 78 lesson texts written for you by leading Communications experts, edited by my practical staff. See the nine big Kits of Parts I send that "bring to life" theory you learn. Read about the transmitter you build and operate, about the Electronic Multitester you get. All equipment yours to keep. My BRAND NEW course includes BOTH Theory and Practical Experience, with result-getting kits, in Radio-Television Communications. It's backed by N. R. I.—the world's oldest and largest home study Radio school.

Mail Coupon For Book FREE

Send today! See what my NEW course is like. Find out how I get you ready for a brighter future, better earnings, more security in Radio-Television. Send coupon now in envelope or paste on penny postal. NO OBLIGATION. NO SALESMAN WILL CALL! My books, sent to you FREE, tell the full story. J. E. SMITH, President, Dept. 9FR, National Radio Institute, Washington 9, D. C.

Servicing Training Also Offered by N. R. I.

If you prefer a good-pay job in Radio-Television Servicing . . . or your own money-making Radio-Television Sales and Service Shop, I'll train you at home. My famous Servicing Course also includes many Kits of Parts. You conduct experiments and tests with modern Radio and other circuits you build. I also show you how to make \$5, \$10 a week or more EXTRA MONEY fixing neighbors' Radios while training. Full information in my 64-page catalog. Mail coupon.

MAIL NOW-BOOK FREE

MR. J. E. SMITH, President, Dept. 9FR
National Radio Institute, Washington 9, D. C.

Mail me FREE Catalog and Book about Radio and Television Communications opportunities and training. (No salesman will call. Please write plainly.)

Name.....Age.....

Address.....

City.....Zone.....State.....

☐ Check if Veteran ☐ Approved Under G. I. Bill

YOU BUILD this Transmitter Power Supply used in the basic experiments in RF and AF amplifiers, frequency multipliers, buffers, etc.



YOU SET UP code amplitude and frequency modulation circuits (put voice, music, etc., on "electrical signal" you produce). You introduce, correct defects, learn how to get best performance.

YOU MEASURE current, voltage (AC, DC and RF), resistance and impedance in circuits with Electronic Multitester you build. Shows how basic transmitter circuits behave; needed to maintain station operation.



YOU BUILD this Wavemeter and use it to determine frequency of operation, make other tests on transmitter currents.

I TRAINED THESE MEN



"I am now Chief Engineer of Radio Station WOKD, in charge of four engineers. Owe all I know about Radio to N. R. I."—C. J. BURDETTE, Spartanburg, S. C.



"Thanks for splendid Home Study Radio Course, a large factor in my getting present position as Senior Radio Operator of Station WRGP."—C. LISTER, Pensacola, Fla.



"Hold a Radio telegraph Second Class License. Now with Civil Service as P-4 Electrical Engineer."—OTIS L. WRIGHT, Albuquerque, N. M.



"I have been in several kinds of Radio work. I am now specializing in Marine Radio telephone installations and service."—MURRAY DICKSON, Paducah, Ky.



"When I enrolled, I had no idea of entering Commercial Radio. Now Operator, Police Radio Station WASP and Highway Station WKSJ."—G. DERAMUS, Selma, Ala.



"Am now Chief Engineer at Radio Station WAGC. Still using my N. R. I. texts as well references."—CHAS. W. STOKLEY, Chattanooga, Tenn.

VETERANS

GET THIS TRAINING WITHOUT COST UNDER G. I. BILL. MAIL COUPON.

Editor
OLIVER READ, W9ETI

Managing Editor
WM. A. STOCKLIN

Technical Editor
H. S. RENNE, EX-W8PTS

Associate Editor
RAY FRANK, W9JU

Contributing Editor
ROBERT HERTZBERG, W2DJJ

Short-Wave Editor
KENNETH R. BOORD

Staff Artist
R. S. KUPJACK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager
JOHN A. RONAN, JR.

Art Director
HERMAN R. BOLLIN



COVER PHOTO: Equipped by RCA with a complete TV control room and portable cameras, the WTMJ-TV mobile unit goes "on location." (Staff photo by O. Read)

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
ARTHUR T. FULLEN

Vice-Presidents

MICHAEL H. FROELICH
Dir. Eastern Div.

H. J. MORGANROTH
Production Director

H. G. STRONG
Circulation Director

BRANCH OFFICES

NEW YORK (1)
Empire State Bldg., WI 7-0400

LOS ANGELES (14)
815 S. Hill St., Tucker 9273
Manager, WILLIAM L. PINNEY

TORONTO
21 King Street, East

ASSOCIATED WITH
Ziff-Davis, Ltd., Grampians Bldg.
Western Gate, London, England

RADIO & TELEVISION NEWS

First in
radio-television-electronics

Average Paid Circulation over 181,000

Radio News Trade Mark Reg. U.S. Pat. Office No. 378427

CONTENTS

JUNE, 1949

Radar Training in the Air Force.....	Major Chas. E. Spitz, W7JHS	29
Miniature 4 Tube Transceiver.....		33
A Low-Cost Bandswitching V.F.O.....	Robert Lewis, W8MQU	34
The Television Antenna.....	Gardiner G. Greene	36
Planning for Profit.....	Fred Merish	38
Modern Television Receivers, Part 15.....	Milton S. Kiver	41
A Three-Dimensional Reproducer System.....	Michael Wolfe	44
Audio Transient Distortion.....	Glen Southworth	46
A Simple Television Tuner.....	J. T. Goode	48
A Super-Modulated, Low-Power Phone Transmitter.....	Rufus P. Turner, K6AI	50
WTMJ's Mobile Television Unit.....	John E. Hubel	53
Build This Absorption Type Signal Marker.....	Guy Dexter	54
A Compact Low-Frequency Baffle.....	Donald Fort	56
The Beginning Amateur, Part 5.....	Robert Hertzberg, W2DJJ	58
Mac's Radio Service Shop.....	John T. Frye	60
A Miniature Phone-C.W. Transmitter for Portable or Mobile Use.....	Hal Bumbaugh, W6HI	61
Can 2,710,000 Television Sets Be Sold in '49?.....		66
Do You Know?.....	David Scott	72
Screen Modulated Final.....	J. D. Kline, W6CXM	110

DEPARTMENTS

For the Record.....	The Editor	8	AFCA News.....	80
Spot Radio News.....		14	MARS.....	90
Within the Industry.....		22	Manufacturers' Literature.....	100
Short-Wave.....	K. R. Boord	40	New TV Receivers.....	114
What's New in Radio.....		76	Technical Books.....	119
Letters from Our Readers.....		122		



COPYRIGHT 1949
ZIFF-DAVIS PUBLISHING COMPANY
185 North Wabash Ave., Chicago 1, Ill.
VOLUME 41 • NUMBER 6



Member
Audit Bureau of
Circulations

RADIO & TELEVISION NEWS is published monthly by the Ziff-Davis Publishing Company, 185 N. Wabash Ave., Chicago 1, Ill. Subscription Rates: in U. S. and Canada \$4.00 (12 issues), single copies 35 cents; in Mexico, South and Central America, and U. S. Possessions, \$4.00 (12 issues); in British Empire, \$5.00 (12 issues)—all other foreign countries \$5.00 (12 issues). Subscribers should allow at least 2 weeks for change of address. All communications about subscriptions should be addressed to: Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. Entered as second class matter July 21, 1948, at the Post Office, Chicago, Illinois, under the Act of March 3, 1879. Entered as second class matter at the Post Office Dept., Ottawa, Canada. Contributors should retain a copy of contributions and include return postage. Contributions will be handled with reasonable care but this magazine assumes no responsibility for their safety. Accepted material is subject to whatever revisions and by-line changes that are necessary. Payment made at our current rates, covers all authors' contributors' or contestants' rights, title, and interest in and to accepted material, including photographs and drawings.

RADIO & TELEVISION NEWS

Which Do You Want?



Better Pay



A Nice Home



A New Car



Greater Security



Happy Vacations
and Travel

Get Your FCC Ticket
Jobs leading to
\$3,000 to \$7,500
(Average Pay Reported by FCC
Nationwide Survey)
are opening up
right now for
FCC Licensed
Radiomen.

Add Technical Training to Your Practical Experience and

Get Your FCC COMMERCIAL RADIO OPERATOR LICENSE in a Few Short Weeks



**It's EASY if you use CIRE Simplified Training and
Coaching AT HOME in SPARE TIME**

Get your license easily and quickly and be ready for the jobs open to ticket holders that lead to \$3000 to \$7500. CIRE training is the only planned course of coaching and training that leads directly to an FCC license.

**YOUR FCC TICKET IS ALWAYS RECOGNIZED
IN ALL RADIO FIELDS AS PROOF
OF YOUR TECHNICAL ABILITY**

**CIRE Graduates Find
FCC License Pays Off**

"Transmitter engineering is great, especially in the job I am on. Thanks again for all you have done, and you can take the credit for the fact that my 'ticket' is now posted on the wall of a 1000 watt broadcast station."

Student No. 3678N12

"I now hold ticket P-10-3787, and holding the license has helped me to obtain the type of job I've always dreamed of having. Yes, thanks to CIRE, I am now working for CAA as Radio Maintenance Technician, at a far better salary than I've ever had before. I am deeply grateful."

Student No. 3319N12

"I took the FCC examination on March 4th, and received my second class radiotelephone license March 9th. I go to work for the Trans-Texas Airways in the maintenance department. Thanks for all the assistance."

Student No. 2394A1

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RN-6 4900 Euclid Bldg. Cleveland 3, Ohio
Approved for Veteran Training under "G.I. Bill of Rights"

GET THIS AMAZING NEW BOOKLET

1. TELLS OF THOUSANDS OF BRAND-NEW, BETTER-PAYING RADIO JOBS NOW OPEN TO FCC LICENSE HOLDERS.
2. TELLS HOW YOU WILL BENEFIT BY HOLDING AN FCC COMMERCIAL LICENSE.
3. TELLS HOW YOU CAN GET YOUR FCC COMMERCIAL RADIO OPERATOR LICENSE IN A FEW SHORT WEEKS—EASILY AND QUICKLY, BY USING CIRE SIMPLIFIED TRAINING AND COACHING AT HOME IN YOUR SPARE TIME.
4. TELLS OF HUNDREDS OF OUR SUCCESSFUL STUDENTS WHO NOW HAVE LICENSES AND NEW, BETTER-PAYING JOBS.
5. TELLS HOW WE PREPARE YOU TO PASS THE NEW FCC COMMERCIAL LICENSE EXAMINATIONS, WHICH NOW INCLUDE FM AND TELEVISION.
6. TELLS HOW WE GUARANTEE TO TRAIN AND COACH YOU UNTIL YOU GET YOUR LICENSE.
7. TELLS HOW WE HELP YOU TO GET A BETTER-PAYING LICENSED JOB, WITH OUR FREE AND EXCLUSIVE SERVICE WHICH PREPARES YOUR EMPLOYMENT APPLICATION FOR MAILING TO HUNDREDS OF EMPLOYERS, INCLUDING FM, AM AND TELEVISION BROADCAST STATIONS, RADIO MANUFACTURERS, POLICE RADIO STATIONS, AND RADIO-EQUIPPED TAXI, BUS AND PUBLIC UTILITY COMPANIES.



Get All 3 FREE Send Coupon Now!

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Desk RN-6, 4900 Euclid Building, Cleveland 3, Ohio
(Address to Desk No. to avoid delay.)

I want to know how I can get my FCC ticket in a few short weeks by training at home in spare time. Send me your FREE booklet "Money Making FCC License Information," as well as a sample FCC-type exam and FREE booklet, "How to Pass FCC License Examinations," (does not cover exams for Amateur License).

Name

Address

City.....Zone.....State.....

☐ Veterans check for enrollment information under G. I. Bill.
NO OBLIGATION—NO SALESMEN.

"KEN-RAD TUBES MEAN SATISFIED CUSTOMERS— INCREASED BUSINESS!"



H. A. GEORGE, Carr Radio & Appliance Store, 7604 South Cottage Grove, Chicago, Illinois, is another serviceman who knows by experience that Ken-Rad Tubes are fast, dependable sellers.

"We've sold a lot of Ken-Rad Tubes in our shop through the years, so I know what I'm talking about.

"Believe me, Ken-Rad Tubes have what it takes to keep customers satisfied. A satisfied customer is a steady customer—and steady customers mean faster turnover, more money in the till.

"There's no substitute for quality—that means there's no substitute for Ken-Rad Tubes!"

"KEN-RAD TUBES ARE TESTED OVER AND OVER AGAIN—TO GUARANTEE SATISFACTION!"

"From start to finish of production, Ken-Rad Tubes must pass one comprehensive test after another.

"These are based on work such as the special stroboscopic vibration check developed by General Electric engineers.

"Tubes are placed in a special spring-supported socket which is driven from a variable-frequency audio oscillator.

"A stroboscopic light then is used to illuminate the tube while it is studied for vibrating elements or loose parts under a high-power microscope.

"No wonder Ken-Rad Tubes satisfy customers!"



ROBERT W. FIELD, Circuit Engineer, is in charge of special stroboscopic vibration test (below). This helps to determine the numerous tests Ken-Rad Tubes must pass before being approved and shipped to dealers.



THE SERVICEMAN'S TUBE

... backed by profit-making sales aids which your Ken-Rad distributor gladly will show you. Phone or write him today!

KEN-RAD *Radio Tubes*

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

See how YOU may get
started toward an Exciting Future in

TELEVISION RADIO • ELECTRONICS!

MODERN CHICAGO LABORATORIES

Train quickly, using a wide variety of commercial equipment. D. T. I.'s new laboratories are among the finest of their kind. Ample instructors . . . every major training advantage. Write for details!

EMPLOYMENT SERVICE

When you complete your training, our effective Employment Service is available to you without extra cost—a grand aid to help you get started.



YOU ALSO
USE
**HOME
MOVIES**
a D.T.I.
Exclusive!

D. T. I., alone, includes the use of one of today's most effective training aids . . . MOVIES . . . to help you learn important fundamentals faster, easier, at home. What an advantage to see electrons on the march, and other fascinating "hidden action" — a remarkable home training advantage that speeds your progress.

OUR GREATEST OFFER IN 17 YEARS!

Here is your big opportunity to get started toward FASCINATING WORK . . . GOOD MONEY . . . a THRILLING FUTURE! Mail the coupon today. See how YOU may prepare to tie in your future with a field that includes one of America's fastest-growing new industries—Television. You'll find out, too, about the many other thrilling opportunities in FM Radio . . . Aviation and Broadcast Radio . . . 2-Way Taxi, Truck and Police Radio . . . Industrial Electronics . . . even the chance to start your own profitable Television-Radio Sales and Service business. And to top it all, you'll see that you don't need to know a thing about this subject at present—that NOW you can get the very training and starting help you need by means of our GREATEST OFFER IN 17 YEARS.

Send for **FREE** Information

See HOW—in your own home—DeForest's Training, Inc., now brings you one of today's most complete combinations of major home training aids. You (1) Learn-by-Reading from well-illustrated lessons. (2) You Learn-by-Seeing from D.T.I.'s exclusive instructive Home Movies. And (3), you set up your own HOME LABORATORY where you Learn-by-Doing from 16 shipments of Radio-Electronic parts which you use and KEEP to work over 300 instructive . . . fascinating projects. This includes building the valuable 6 tube "Superhet" RADIO and the commercial-type OSCILLOSCOPE, R-F SIGNAL GENERATOR, and Jewel-Bearing MULTIMETER, pictured at the right.

You may use this test equipment to help you earn real money—both in your spare time and later when working full time in the field. Get complete facts. Mail coupon today!



6-TUBE RADIO
RECEIVER



OSCILLOSCOPE

R-F SIGNAL
GENERATOR



MULTI-METER

OPPORTUNITY COUPON!

DeForest's Training, Inc.
2533 N. Ashland Ave., Dept. RN-F6
Chicago 14, Illinois

MAIL TODAY

Without obligation, send me complete facts showing how I may make my start in Television-Radio-Electronics.

Name Age

Street Apt.


City Zone State

DeFOREST'S TRAINING, INC.
CHICAGO 14, ILLINOIS

Affiliated with the DeVry Corporation,
Builders of Electronic and Movie Equipment.

READY... AIM...

SOLDER!

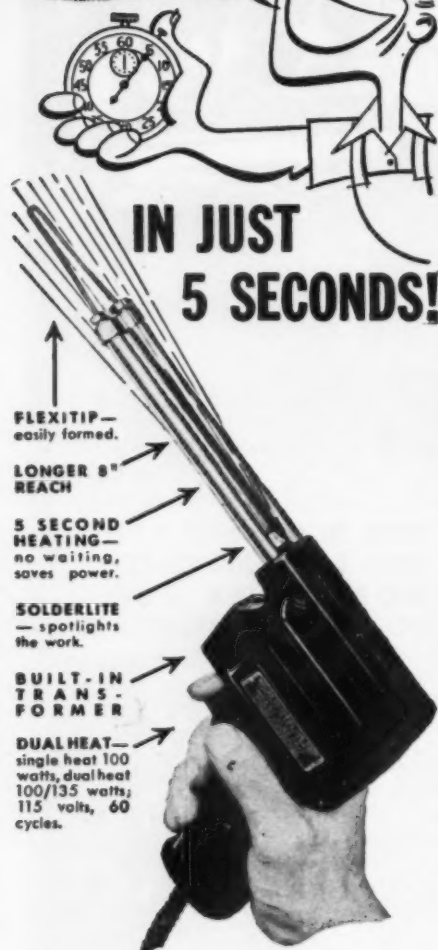

Pull the trigger switch, make contact, and you solder. Then release the trigger and off goes the heat—automatically. No wasted time. No wasted current. No need to unplug the gun between jobs. The Weller Gun's Flexitip heats only when in use—saves hours and dollars. Your Weller Gun will pay for itself in a few months.

Solderlite, extra length, and the easily shaped Flexitip mean real soldering ease. And because the transformer is built in—no separate—the Weller Gun is a complete, self-contained unit, compact, convenient.

For laboratory and maintenance work, we recommend the efficient 8" model—DX-8 with dual heat; or 4" types S-107 single heat and D-207 dual heat. Order from your distributor or write for bulletin direct.



Be sure to get your copy—**SOLDERING TIPS**, the new Weller Handy Guide to easier, faster soldering—20 pages fully illustrated. Price 10c at your distributor's.

WELLER
MANUFACTURING COMPANY

810 Packer Street • Easton, Pa.

For the **RECORD.**

BY THE EDITOR

PUBLIC ENTITLED TO TVI CONTROL

INTERFERENCE created by automotive ignition systems is playing havoc in many areas with television sets. In fact, automotive TVI is probably the Number One source of headache to the set owners. Distorted and torn pictures are commonplace in television service areas, especially in the large metropolitan centers, where the streets and highways are jammed with these hash-creating "transmitters." Amateur mobile radio operators and other communications services have long been able to cope with the problem and have equipped their vehicles with various forms of suppressors, filters, and other gadgets designed to forestall radiation from the ignition systems. It is generally believed by the public that the addition of such accessories hinders the proper working of the auto engine. On the contrary, there are few complaints of poor engine performance resulting from such equipment.

Amateur radio operators have, for the past two years, been severely criticized by television set owners for causing interference with their video reception. Actually, only a small percentage of these complaints has been fully justified.

The FCC is required by law to take action against transmitter licensees whenever justifiable complaints arise as a result of an improperly adjusted transmitter which causes interference, so why shouldn't *any* radiated signal, including that from automotive equipment, also be controlled by the FCC and other authorities? There are literally millions of automobiles cruising our city streets and travelling our highways. Nearly all of these are, in a sense, portable transmitters. Not only are they capable of, and guilty of, transmitting multiple signals, but as any technician knows, each vehicle can transmit many signals at different frequencies at the same moment. Radiation from diathermy machines and other signal producing devices is controlled by law, and shielding and other methods of hash control are required of the owners. Why shouldn't the same apply to car owners? The British recognize the need for such control and enforce strict regulations on offenders and demand filters and any other remedies that may be indicated to prevent radiation from automotive equipment. Many cities in the United States have enacted laws against the use of horns and other noise-producing sources, but America is far behind in

cleaning up the ever-present interference that is still plaguing all short-wave and television services.

Service technicians are being damned for improper installation and adjustment of television sets. In many cases, the disgruntled customer complains that the picture frequently streaks and otherwise distorts during a program. These technicians tell us that in most cases of this nature the interference was being caused by idling motors and from passing automobile traffic. Even with a highly efficient antenna installation the trouble often persists. Service technicians would save a large percentage of unnecessary calls if anti-hash legislation were enacted. Everyone would benefit, and the cost to the car owner would be a mere trifle by comparison. It's the job of the local newspaper press to present the facts accurately to its readers and insist that steps be taken by their local and state representatives to present this problem to the authorities and to demand concerted action, the same as was done in Britain. Television continues to grow in importance and in service and is expected eventually to replace many conventional radio services. It is about time something was done about this "hash" situation.

WARNING TO TELEVISION TECHNICIANS

AS WE go to press, an attempt has been made in Illinois to "railroad" an act to license and regulate the business of installing, servicing and repairing television receivers. A copy of this House Bill No. 702 has been obtained and studied by RADIO AND TELEVISION NEWS.

This bill, introduced *without any discussion* with the major elements of the industry, is in direct opposition to the welfare of television set owners and the industry. Representatives of this magazine will appear before the committee to argue the bill and to recommend major changes. Basically this bill favors certain "accredited television schools" inasmuch as the bill (as drafted) requires a minimum 36 weeks' course in television instruction.

Technicians should, in whatever state they reside, query their Representatives and find out whether or not similar bills are in the process of preparation within their states and, if they are, plan their attack accordingly. We will give you a further report on this bill in our next issue. O.R.

RADIO & TELEVISION NEWS

ALL THE NEWEST RELEASES

BIG MONEY-*SAVING* VALUES

**They're in your latest
ALLIED CATALOG!**

TOP VALUES IN QUALITY TV ANTENNAS



Knight Indoor TV Antenna


High efficiency indoor type—with length and direction easily adjustable for maximum TV reception. Covers all TV channels efficiently. Compact; fits on receiver cabinet or table, or mounts to wall. Ideal for use where roof antennas can't be installed. Shpg. wt. 2 lbs.
97-354. Only **\$325**



Knight TV All-Band Antenna

An excellent, low cost all-channel TV antenna. Has separate dipole and reflector for the high and low bands. Two-section 6 ft. mast of sturdy aluminum tubing, with dipoles and reflectors of aluminum also. Complete, less only lead-in line. Shpg. wt., 8 lbs.
97-355. Only **\$795**

NEW LOW-COST HIGH-QUALITY RECORDERS

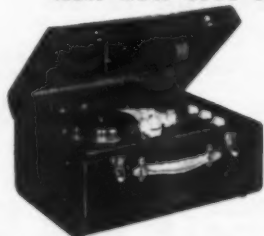

Knight Wire Recorder


Makes and plays high-quality wire recordings; plays any 10" or 12" 78 rpm disc recording; serves also as PA system or as wireless phono oscillator. Easy to operate. Ruggedly constructed. Complete in compact simulated leather case; with crystal hand mike, playback pickup, all tubes, and 2 half-hour spools of wire. For 105-125 v., 60 cy. AC. Shpg. wt., 29 lbs.
96-172. Only **\$9950**



Knight Tape Recorder

A top-grade tape recorder and playback unit at amazing low cost. May also be used as 6 watt PA system. Excellent frequency response. Easy to record; stable constant-speed mechanism. Exceptional playback quality. In sturdy portable case; with crystal hand mike, 600 ft. reel of tape, take-up reel, and all tubes. For 105-125 v., 60 cy. AC. Shpg. wt., 36 lbs.
96-187. Only **\$12750**

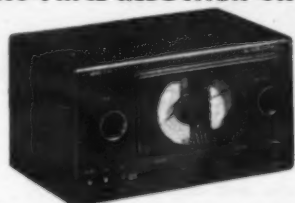BIG PRICE REDUCTION ON FAMOUS HALLICRAFTERS S-38



A new low price for this all-star, all-wave value! Covers 4 full bands continuous from 540 kc. to 32 mc. Full electrical bandspread; noise limiter; band selector; BFO pitch; voice-code switch; speaker-headphones switch; standby-receive switch; latest PM speaker. In handsome 12 x 7 x 8" furniture-steel cabinet. Complete with tubes. For 105-125 v. AC or DC. Shpg. wt., 15 lbs.
97-565. Only **\$3995**



FREE

Send for
Radio's Leading Buying Guide

Get the Radio Buying Guide that's used by thousands of expert servicemen, engineers, amateurs, soundmen, builders and experimenters. Get every buying advantage at ALLIED: widest selection of equipment at money-saving low prices—speedy, expert shipment—personal attention—complete satisfaction on every order. Get your latest ALLIED Catalog today—use handy coupon below!

NEW! 45 RPM Record Playing Equipment



Knight 45RPM Automatic Phono


First at ALLIED! Automatically plays ten of the new 7" 45 rpm records at one loading. Just push a button for 50 minutes of fine reproduction. Exceptionally reliable changer mechanism works with amazing speed. High-quality amplifier and built-in speaker deliver plenty of power and excellent fidelity. With tone control. In attractive portable case. With all tubes and precious-point needle. For 105-125 v., 60 cy. AC. Shpg. wt., 16 lbs.
96-284. Only **\$3995**



Knight 45 RPM Player

Plays the sensational new RCA 45 rpm records! Can be connected easily to any amplifier and speaker, or to any radio with phono connection. With special crystal pickup and precious-point .001" needle; dependable 45 rpm phono motor. In attractive, extremely compact cabinet, finished in furniture brown. Includes on-off switch and pickup arm rest. For 110-120 v., 60 cy. AC. Shpg. wt., 5 lbs. A real buy at our low price!
96-257. Only **\$1225**

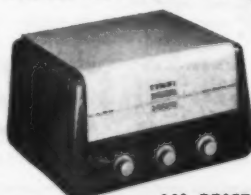Better Than Ever—Knight 20 Watt Hi-Fi Phono Amplifier



New styling—new features! The big high-fidelity value. Response ± 1 db, 20-20,000 cps. Less than 2% harmonic distortion at full 20 watts; hum way down—80 db below 20 watts; dual phono input with 78 db gain; matches anything—output impedances, 4, 8, 16, 250 and 500 ohms. There's nothing finer anywhere near this low price. In handsome new two-tone steel case. Complete with tubes. For 110-125 v., 60 cy. AC. Shpg. wt., 30 lbs.
93-320. Only **\$5995**

ALL PRICES NET F. O. B. CHICAGO

**FREE
CATALOG**

ALLIED RADIO CORP., Dept. 1-F-9
833 W. Jackson Blvd., Chicago 7, Illinois

☐ Send FREE ALLIED Catalog

☐ Enter order for.....

Enclosed \$..... ☐ Full Pay. ☐ Part Pay. (Bal. C.O.D.)

Name.....

Address.....

City..... Zone..... State.....

*Everything
in Radio
and Electronics*



**ALLIED
RADIO**

TRANSVISION TV KITS



Announcing— SMASHING PRICE REDUCTIONS

MODEL 12A-TV KIT with 12½" PICTURE TUBE

• FAMOUS TRANSVISION
TELEVISION KIT, giving the
finest television money can buy.

• NO INSTALLATION COST. You
can install assembled kit yourself in
about an hour.

\$199⁰⁰

less cabinet*



MODEL 12CL TV-FM KIT

200 Sq. In. PICTURE TV-FM KIT MODEL 12CL

Has DuMont Inputuner

IMAGE IS EQUAL to that of a 20" tube—even sharper and clearer—visible from all angles.

EQUIVALENT OF \$1000 SETS!

Price of the new Transvision 12CL electromagnetic kit includes these outstanding features:

- 12½" picture tube with special fitted built-in All-Angle Lens and color kit.
- DuMont TV-FM Inputuner
- Streamlined Console Cabinet

Includes Cabinet, Lens, Indoor or Outdoor Antenna, 60 ft. of Lead-in Wire.

\$349

TRANSVISION Model 15A TV KIT

This high-quality Transvision TV Kit has a 16" picture tube.
FREE ANTENNA: INDOOR or OUTDOOR type, with lead-in wire.


\$279 Less Cabinet*

*CHOICE of BEAUTIFUL CABINETS from \$29

For example, a "Modular" Console Cabinet, which can easily be assembled in about an hour, costs \$29.

ASSEMBLE Your Own CABINETS

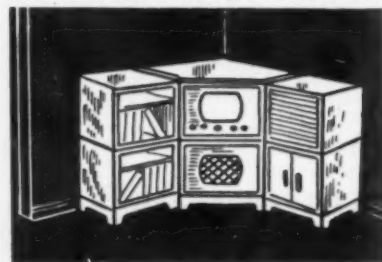Transvision's "MODULAR" Cabinets come in knock-down, unpainted units, offering an unlimited range of combinations, including even a bar. Finish them off to suit your taste and need.



Corner piece, shown above, has room for TV, Phone, Record Storage, and open Book Case. COMPLETE... \$84.00
For other units and prices, write for "Modular" Catalog.

FREE: 162 PAGE TV COURSE

... with purchase of any Transvision TV Kit... You don't need this course to assemble a Transvision Kit, because the job is easy enough and our instruction sheet is simple and clear. BUT, if you want a good introduction to Television Fundamentals as a basis for further study, the Transvision Television Home-Study Course is ideal. Remember, you pay nothing extra for this course.

TRANSVISION, INC., Dept. RN, NEW ROCHELLE, N. Y.

All Transvision Prices are fair traded, subject to change without notice. Prices 5% higher west of the Mississippi.

For FREE 20-page TV BOOKLET and CATALOG SHEETS, SEE YOUR TRANSVISION OUTLET!

NEW YORK, N. Y.
TRANSVISION OF MANHATTAN
75 Church St.

BRONX, N. Y.
TRANSVISION OF THE BRONX
1425 Boscobel Ave.

BROOKLYN, N. Y.
TRANSVISION OF BROOKLYN
485 Coney Island Ave.

LONG ISLAND, N. Y.
TRANSVISION OF LONG ISLAND
40-14 Greenpoint Ave.
Long Island City, N. Y.

WESTCHESTER, N. Y.
TRANSVISION OF WESTCHESTER
606 Central Park Ave.
Yonkers, N. Y.

NEWARK, N. J.
TRANSVISION OF NEW JERSEY
601 Broad St.

PHILADELPHIA, PA.
TRANSVISION OF PHILADELPHIA
235 North Broad St.

BOSTON, MASS.
TRANSVISION OF NEW ENGLAND
1306 Boylston St.

WASHINGTON, D. C.
STAR RADIO, 409 11th St., N. W.

CINCINNATI, OHIO
TRANSVISION OF CINCINNATI
Fourth and Plum Sts.

CLEVELAND, OHIO
TRANSVISION OF CLEVELAND
2001 Euclid Ave.

COLUMBUS, OHIO
TRANSVISION OF COLUMBUS
53 W. Norwich Ave.

CHICAGO, ILL.
TRANSVISION OF CHICAGO
1002 South Michigan Ave.

SYRACUSE, N. Y.
TRANSVISION OF SYRACUSE
517 Butternut St.

MIAMI, FLA.
TRANSVISION OF FLORIDA
10 Northeast Third Ave.

DALLAS, TEX.
TRANSVISION OF TEXAS
700 Commerce St.

HOLLYWOOD, CALIF.
TRANSVISION OF CALIFORNIA
8572 Santa Monica Blvd.

SAN FRANCISCO, CALIF.
TRANSVISION OF CALIFORNIA
3471 California St.

CANADA
TRANSVISION OF CANADA
465 Church St., Toronto, Ontario

TRANSVISION TV INSTRUMENTS



ELIMINATE the VARIABLES in Television Installation with the TRANSVISION FIELD STRENGTH METER

Improves Installations!!

Saves 1/2 the Work!!

Has numerous features and advantages, including—(1) Measures actual picture signal strength . . . (2) Permits actual picture signal measurements without the use of a complete television set . . . (3) Antenna orientation can be done exactly . . . (4) Measures losses or gain of various antenna and lead-in combinations . . . (5) Useful for checking receiver re-radiation (local oscillator) . . . (6) **12 CHANNEL SELECTOR** . . . (7) Amplitudes of interfering signals can be checked . . . (8) Weighs only 5 lbs. . . (9) **Individually calibrated** . . . (10) Housed in attractive metal carrying case . . . (11) Initial cost of this unit is covered after only 3 or 4 installations . . . (12) Operates on 110V, 60 Cycles, A.C.


Model FSM-1, with tubes . . . Net \$99.50



NEW LOW PRICE
TRANSVISION ALL-CHANNEL
TELEVISION BOOSTER
CONTINUOUS TUNING

To assure television reception in weak signal areas, or areas which are out of range of certain broadcasting stations, Transvision engineers have designed this new booster. It **increases signal strength on all television channels**. Tunes all television channels **continuously**. Can be used with any type of television receiver. Unusually high gain in upper television channels.

Model B-1 . . . List \$32.50

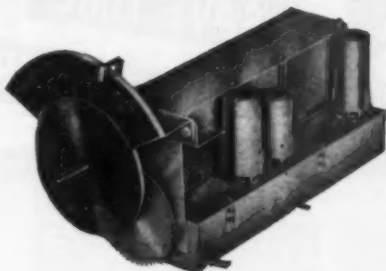

DuMont TV-FM

INPUT TUNER

The finest TV-FM Tuner on the market today! Distributed exclusively by Transvision.

- Covers all 12 channels, entire FM Range.
- Continuously tunes from 44 to 216 mc without a break. Requires no band switching for tuning from channel to channel.
- Complete with tubes and escutcheon.

Model IT-1 . . . List \$59.95

TRANSVISION ALL-ANGLE LENSES for ALL TV SETS

Give picture sizes up to 150 sq. in. Exclusive patented feature makes image visible from wide angle. Lenses come with adapter for installation on ANY 7" or 10" picture tube, and with color kits. **All-Angle Lens for 7" tubes (gives 75 sq. in. picture) . . . \$25.95**
All-Angle Lens for 10" tubes (gives 150 sq. in. picture) . . . \$37.50
For 12 1/2" tubes . . . \$49.50



GET INTO the TV BUSINESS
In a BIG WAY with the
TRANSVISION DEALER PLAN
WRITE FOR FOLDER D-1



TELEVISION and FM SWEEP SIGNAL GENERATOR

Complete frequency coverage from 0-227 MC with no band switching. . . Sweep width from 0-12 MC completely variable. . . Accurately calibrated built-in marker generator.

OUTSTANDING FEATURES: (1) Frequency range from 0-227 MC . . . (2) Dial calibrated in frequency . . . (3) Sweep width from 0-12 MC completely variable . . . (4) Self-contained markers readable directly on the dial to .5% or better. (No external generator required to provide the marker signals) . . . (5) Crystal controlled output makes possible any crystal controlled frequency from 5-230 MC . . . (6) Plenty of voltage output—permits stage-by-stage alignment . . . (7) Output impedance 5-125 ohms . . . (8) Directly calibrated markers, 20-30 MC for trap, sound and video IF alignment . . . (9) RF for alignment of traps for IF channels when a DC voltmeter is used as the indicating medium . . . (10) Unmodulated RF signal to provide marker pips simultaneously with the main variable oscillator . . . (11) Markers can be controlled as to output strength in the pip oscillator . . . (12) Power supply completely shielded and filtered to prevent leakage . . . (13) All active tubes are the new modern miniature type . . . (14) Phasing control incorporated in the generator . . . (15) Operates on 110V, 60 Cycles, A.C.

Model SG . . . Net \$79.50

REMOTE CONTROL UNIT
OPERATES ANY TELEVISION SET from a DISTANCE up to 50 feet.



Model TRCU Remote Control Unit, factory pre-wired and tested, with 25-ft. cable . . . \$69.00
Also available without cabinet . . . \$5.00

IF YOU ARE NOT NEAR A TRANSVISION OUTLET

USE THIS COUPON

MAIL TO: TRANSVISION, INC., NEW ROCHELLE, N. Y.

Please ship the following Transvision Products **THROUGH YOUR NEAREST LOCAL OUTLET—** RN-6

I am enclosing 10% DEPOSIT in the amount of \$. . . balance C.O.D.

☐ I want to get into the Television Business. Send me details of your Dealer Plan.

Name . . . City & Zone . . .

(please print)

Address . . . State . . .

PHOTOFACT Publications

The Books that Help You

SAVE TIME

SAVE WORK

EARN MORE

LEARN MORE



NEW TELEVISION BOOKS

TELEVISION COURSE

Gives you a clear, complete understanding of TV principles, operation and practice. Covers: Beam Formation and Control; Beam Deflection Systems; Beam Modulation and Synchronization. Full analysis of the Cathode Ray tube, voltage supplies, control functions, antenna circuits, RF and IF systems, AGC, video amplification, contrast, etc. 216 pages; 8½ x 11"; profusely illustrated; sturdily bound. **\$3.00**

TELEVISION ANTENNAS

All you need to know about TV antennas. Written by Donald A. Nelson; based on actual field experience. Shows you how to select antenna, how to install it, how to solve troubles. Many short-cuts help you save time and earn more. Chapters cover: antenna principles; construction; analysis of all types of commercial units; installation data; problems and trouble-shooting. 192 pages; 124 illustrations. **\$1.25**

THE RED BOOK

Tells you in one volume all you need to know about replacement parts for 17,000 receivers made from 1938 to 1948. Eliminates wasteful hunting through dozens of incomplete manuals. Includes full, accurate listings of all 9 major replacement components; lists correct replacement parts made by 17 leading manufacturers. Gives original parts numbers, proper replacements and valuable installation notes on: Capacitors, transformers, controls, I.F.'s, speakers, vibrators, phono-cartridges, tube and dial-light data, battery replacement data. 448 pages; 8½ x 11"; sewed binding. **\$3.95**

RECORD CHANGER MANUALS

Volume 2, 1948. Covers 45 models made in 1948, including new LP and dual-speed changers, plus leading wire and tape recorders. Complete accurate data—based on actual analysis of the equipment. Gives full change cycle data, adjustment information, needle landing data, hints and kinks, parts lists, exclusive "exploded" diagrams. A time-saving, money-making book. Over 400 pages; 8½ x 11"; deluxe bound. **\$6.75**

Volume 1, 1947. Covers over 40 different post-war models up to 1948. Includes full, hard-to-get data on leading wire, ribbon, tape and paper disc recorders. 400 pages; fully illustrated; 8½ x 11"; hard binding. **\$4.95**



SPECIALIZED SERVICE DATA VOLUMES

Post-War Auto Radios. Covers everything you need to know on over 100 post-war models (practically every auto radio made since 1946); represents the products of 24 different manufacturers. Makes auto radio servicing easy. Over 360 pages; profusely illustrated; each model treated uniformly, completely, accurately—based on actual study of the equipment. Sturdy binding. 8½ x 11". **\$4.95**

Post-War Audio Amplifiers. Invaluable data for custom-builders, audio men and sound engineers. Covers a wide variety of well-known audio amplifiers and FM and AM tuners, plus data on important wire and tape recorders. Presents a complete analysis of each unit. A "must" for all sound men and custom installers. 352 pages; 8½ x 11"; sturdily bound. **\$3.95**

Post-War Communications Receivers. Complete technical analysis of more than 50 of the most popular communications sets on the market. An invaluable service aid, a perfect buying guide for purchasers of communications receivers. All data is accurate and authoritative, based on actual examination and study of each unit. 264 pages; profusely illustrated; 8½ x 11"; durably bound. **\$3.00**

"MUSTS" FOR EVERY SERVICE BENCH

Radio Receiver Tube Placement Guide. Shows you exactly where to replace each tube in 5300 radio models, covering 1938 to 1947 receivers. Clear, accurate diagram for each tube layout. Saves time—eliminates risky hit-or-miss methods, especially where tubes have been removed from the set. Indispensable in the shop or on calls. 192 pages. **\$1.25**

Dial Cord Stringing Guide. The book that shows you the one right way to string a dial cord. Here, in one handy pocket-sized book, are all available dial cord diagrams covering over 2300 receivers; 1938 through 1946. Makes dial cord restringing jobs quick and easy. Nothing like it. Order copies today for your tool kit and shop bench. **\$1.00**



PHOTOFACT SERVICE MANUALS

Here's the radio service data that's invaluable—that saves you time and helps you earn more! Preferred and used daily by thousands of Radio Service Technicians. Complete, accurate—based on analysis of the actual equipment. Uniform treatment for each model: includes Standard Notation Schematics; full chassis photo coverage; alignment, stage gain, voltage and resistance analysis; parts numbers and proper replacements; disassembly notes; oscilloscope wave forms; record changer analysis—everything you need for quick, profitable servicing. Covers all post-war radios; in semi-annual deluxe bound volumes, over 1000 pages each. 7 volumes cover receivers made to Oct. 1, 1949. **\$18.39**

Each Volume in Deluxe Binder

"The Recording and Reproduction of Sound"

by Oliver Read

The first complete reference book that gives the right answers on all phases of SOUND. Written by the editor of Radio News. Authoritative, complete information on recording and reproduction. Nothing else like it. Order now.


320 Pages
Deluxe Bound **\$5.00**

Published by **HOWARD W. SAMS & CO., INC.** • INDIANAPOLIS 1, INDIANA

Better! Stronger! Last Longer!

Because  Flat Cell "B" Batteries Are

INTERLOCKED

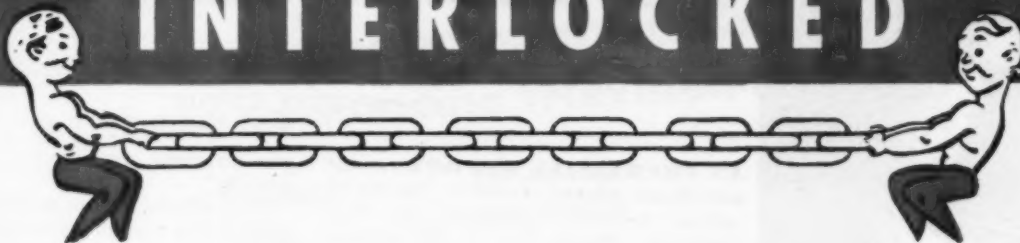

The principle of *interlocking* is simple—and complete assurance of maximum strength. For example, you'd naturally prefer a tire chain which is *interlocked* with equally strong links to one with its links taped or tied together. For the same reason

both you . . . and your customers . . . will prefer OLIN flat cell "B" batteries since they have triple-sealed, equally-strong, *interlocked* flat cells . . . instead of ordinary cells bound together with paper tapes or other types of wrapping.

They Are The ONLY Flat Cell Radio "B" Batteries in Which Each Cell Is



"Greatest development in 20 years for battery radios" say radio manufacturers. And backing up their judgment OLIN

interlocked flat cell "B" batteries are recommended as standard or replacement equipment by leading radio manufacturers.



Look What It Means


Each cell holds only power-producing chemicals with no waste space.

Triple sealing, under fixed pressure, insures against power leakage.

Up to 91% fewer soldered connections greatly reduce battery "hum" or failure—give longer life.


We guarantee these . . . the ONLY radio batteries with *interlocked* flat cells . . . to give more listening hours, and clearer reception under normal conditions.

See How It's Done

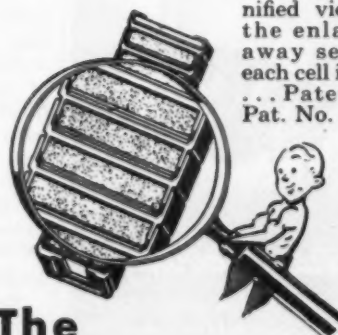

Note in the magnified view showing the enlarged cut-away section how each cell is *interlocked* . . . Patented U. S. Pat. No. 2416576.

Available Only In The

WINCHESTER and  **Lines**

of OLIN INDUSTRIES, INC., Electrical Division, New Haven 4, Connecticut.

Mr. RETAILER: Order From Your Wholesaler's Salesman Today To Be Ready For The Vacation Selling Season!

Spot Radio News

★ Presenting latest information on the Radio Industry.


By RADIO & TELEVISION NEWS'

WASHINGTON EDITOR

MINIMUM SPACE...
MAXIMUM PERFORMANCE

Specify Type BH6

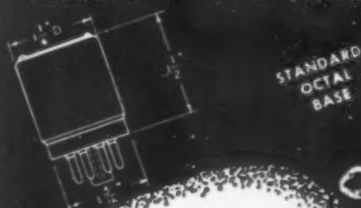This miniaturized crystal unit is available in the frequency range 1 mc to 100 mc with tolerances to meet all commercial or military specifications.



STANDARD
OCTAL
BASE



TYPE
TCO-1
OPER. TEMP. 75°C
RATING 6.3V, 0.5W

For Extra Stability

... down to $\pm .0001\%$ between -55°C and $+70^{\circ}\text{C}$, specify BH6 units in TCO-1 (single) or TCO-2 (dual) temperature controlled ovens.

For over 19 years... foremost in frequency control applications.

Bliley
CRYSTALS

BLILEY ELECTRIC COMPANY
UNION STATION BLDG. • ERIE, PA

AN IMPRESSIVE REPORT on the significant advancements in communications services, presented by FCC chairman Wayne Coy at the annual luncheon-meeting of the Armed Forces Communications Association in Washington, revealed that motorists and train, ship, and plane passengers can now telephone to practically anywhere in the nation, thanks to the two-way radiotelephone systems. Coy said that 7000 cars are now equipped with two-way apparatus providing tie-ins with regular telephone switchboards and contact to any telephone in the country, fourteen trains have phone service, and 11,000 vessels and 150 planes also have two-way units, which provide local and long-distance communications.

The use of the two-way setups by the utilities and petroleum industries was also emphasized by Coy, who pointed out that there are more than 26,000 two-way equipped utility trucks which have consistently demonstrated the invaluable aid provided by the field and office radio link by accelerating repair to damages in water and gas mains and electric and telephone lines. The oil companies not only have radio-equipped trucks, but walkie-talkies and two-way plane service to patrol their pipelines and provide immediate dispatching of crews in case of leaks or explosions.

"In all, we have authorized two-way radio for some 200,000 vehicles," said Coy.

Amateur radio received quite a bit of applause, too, at the Washington luncheon-meeting, Coy declaring that ham service, which has served the nation so well in past disasters and has been such an effective training school for military and industry personnel, is growing steadily. Today there are 78,000 active hams, an increase of 18,000 since the war.

Describing how these new and expanding services can benefit the nation during an emergency, Coy said that an unparalleled closely-woven link could be rapidly established in hamlets, towns, cities, and states from coast to coast via the fixed and mobile stations which now span the country. He pointed out that... "No nation in history has ever been so well equipped with civilian communications facilities—facilities to promote our efficiency, comfort, and enjoyment in peace and

our national security in the event of attack."

In a tribute to the outstanding services of the wartime government agencies, Coy praised the famous RID (Radio Intelligence Division), which was headed by George Sterling, now a FCC Commissioner, and which played so vital a role in tracking down clandestine transmitters. He cited the case of the secret transmitter hidden in the German Embassy in Washington which the RID located, and the hundreds of other unlicensed transmitters traced and taken off the air. At its peak during the war RID had twelve primary stations and ninety secondary setups in this country, Puerto Rico, Alaska, and Hawaii. Today the FCC has ten primary stations, eleven secondary stations, and seventeen mobile direction finders, which are very active. Coy reported that the monitors are now locating illegal transmitters at the rate of about 150 a year. Horse racing gamblers appear to be giving the FCC monitor boys plenty of headaches. The monitors have also been of assistance to pilots, last year over 170 lost planes obtaining their bearings from the FCC posts. Captain William Odom, on his sensational light-plane flight from Honolulu to Newark, N. J., also benefited from the FCC monitor service. According to Coy, as a result of the FCC monitor fix, Odom discovered that he was 300 miles off his course while he was in the middle of the Pacific.

Listening in to Coy's spirited comments were the nation's outstanding government and industry radio specialists: Major General F. L. Ankerbrandt, U. S. Air Force Director of Communications; Brig. General David Sarnoff, chairman of the board of RCA; Rear Admiral E. E. Stone, U. S. Navy Chief of Naval Communications; Major General Spencer B. Akin, Chief Signal Officer of the Army; Fred R. Lack, vice president of Western Electric and president-elect of AFCA; and the internationally-famous communications legislator, Senator Wallace H. White, who retired last June.

AT THE ANNUAL NAB conference in Chicago, the FCC chairman appeared at a luncheon-meeting of broadcasters, disclosing this time the progress achieved by TV.

RADIO & TELEVISION NEWS

PREFERRED

by these outstanding television set makers..

Admiral



*Andrea
Automatic
Radio*

*Bendix
Radio*

CROSLLEY

DEWALD

*Emerson
Radio*

**FADA
Radio**

Furnsworth
GAROD RADIO

GLOBE
hallicrafters

Hoffman

Magnevox



Motorola
NATIONAL

Olympic
radio and television

Packard Bell
PHILCO



Regal

Sentinel

Silvertone

Spartan

**STROMBERG
CARLSON**

Tele-tone



TRAV-LER

Westinghouse

ZENITH
RADIO



Sylvania's outstanding television picture tubes

When 32 nationally known television set makers specify Sylvania television tubes for their sets, you have a sure indication of their excellent quality.

If you wish full information about the entire line of Sylvania Cathode Ray Tubes, made by the manufacturers of highest quality radio tubes for many years, write Sylvania Electric Products Inc., Cathode Ray Division, Emporium, Pa.

SYLVANIA ELECTRIC

CATHODE RAY TUBES; RADIO TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS; PHOTOLAMPS
June, 1949

For Clearer Television!




TV-FM ANTENNA ROTATOR

- Sharper Pictures
- Wider Range
- Peak Reception!

This antenna rotator turns your TV antenna instantly as needed—"aims" it at the station—keeps image clear—overcomes interference and distortion! In multi-station and fringe areas Tenna-Rotor *brings in that station you couldn't get before*—increases selectivity, directivity and range!

Weather-proof enclosed electric rotor unit, (size 7" x 8") fits antenna mast—is quick and easy to install—self-lubricated for long life! Smart, plastic remote-control case plugs into 110-volt house circuit. Price \$39.95. (Slightly higher west of Rockies.) Complete assembly, rotor and control case, weighs 12 lbs. End your "fixed position" antenna worries—ask your dealer or service shop!

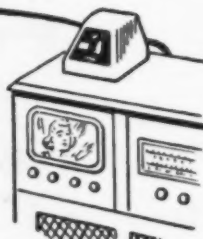Ask for Alliance 4-Conductor Cable made especially for Tenna-Rotor!




ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO

Export Department; 401 Broadway, New York, N. Y., U. S. A.

ARE YOU RECTIFIER-WISE? WIN A VALUABLE PRIZE

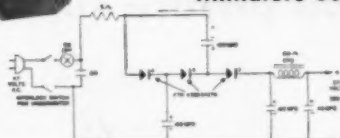With your Circuit Designs Using Federal's
Miniature Selenium Rectifiers



Here is your opportunity to convert your circuit ingenuity into a useful and valuable prize. Federal, the originator of the Miniature Selenium Rectifier, is interested in your ideas on the use of this revolutionary circuit element.

A multitude of circuits have been built around the outstanding characteristics of Federal's complete line of Miniature Selenium Rectifiers—audio amplifiers, home radios, television receivers, 'ham' transmitters, FM adapters, phonograph amplifiers and many other electrical and electronic circuits. They all capitalize on the long life, high current capacity, instantaneous starting and great efficiency of these rectifiers. This compact, lightweight television power supply is typical.

These are but a few applications. The uses of these Miniature Rectifiers are almost unlimited. Get your idea down on paper and send it in today. It may be a prize winner!

CONTEST DETAILS


1. All entries must be original circuits.
2. All entries become the property of Federal Telephone and Radio Corporation.
3. Federal engineers will judge entries on basis of novel and useful applications and select winning circuits.
4. Five winners will be selected from the entries received during each month of the contest. A grand prize will be awarded to the outstanding entry of the contest.
5. All entries for this month's judging must be received by June 30. Entries for the final month of the contest must be received by July 31st. Contest closes July 31st.
6. Winners will be announced.

FIVE MONTHLY PRIZES AND A GRAND PRIZE

The five monthly winners will each receive, FREE, a Federal FTR-1342-AS Selenium Rectifier Power Supply-Battery Charger. This compact unit, with its 6-volt, 6-ampere DC output, has many uses in home and shop. It comes equipped with a handy under-dash mounting socket for automobile battery charging.



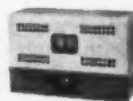The grand prize, a Federal FTR-3246-BS Radio Service Power Supply, is invaluable as a source of heavy duty, filtered DC power. Its 6-volt, 10-ampere DC output will handle auto radio testing and many other test and permanent power requirements. List price \$74.50.



MAIL YOUR ENTRY TO: MINIATURE RECTIFIER CONTEST
Federal Telephone and Radio Corporation

SELENIUM INTELIN DIV. • 900 PASSAIC AVENUE • EAST NEWARK, NEW JERSEY

"The trend is toward television . . . and there is no doubt that TV and sound are entering into a period of intensive competition," Coy declared.

Coy reported that television is the dominant medium of broadcasting in the future. "It is a new force unloosed in the land," he said.

Continuing with his enthusiastic comments on TV, Coy stated, "I believe it is an irresistible force. It is a technological discovery that the people want and demand. It is not something that you have to high-pressure the people into buying. In metropolitan areas, television has met with sensational acceptance.

"But don't think that the people outside of the metropolitan areas are going to be content to grow old gracefully while TV passes them by," Coy warned the broadcasters. "The day of the hinterland, the provinces, the backwoods, and the 'sticks' has passed in America. Radio itself helped hurry that process. The wartime prosperity and the dispersion of our industrial plants took us further along the road toward greater equality of opportunity."

And then Coy drove into the topic that has been a headline for many, many months, the ultra-highs, with the chairman disclosing that before many months, there'll be ultra-high allocations which will open up a new frontier of the spectrum . . . "so that it may be possible, given imaginative leadership . . . to take television service to all of America."

In a previous talk at Baltimore, Coy reemphasized his comment that the standard twelve-channel very-high band would remain, with the statement: "Present television sets available on the market will get service from these channels continuously. . . . I think the question of obsolescence of television receivers is something of a tempest in a teapot. I do not think that any one buying a television set today will have a fraud perpetrated upon him. I can assure them that wherever a television signal is available from a very-high transmitter, their sets will render them fine service for many years."

Amplifying Coy's opinions, Dr. Thomas T. Goldsmith, Jr., director of research for DuMont, reported at the NAB Chicago meeting, that if and when the ultra-highs come, the public will be able to buy, at a moderate price, converters which will bring the additional channels to their sets. He reported that such converters have been developed and found very satisfactory during tests.

Discussing the characteristics of ultra-high reception, Goldsmith said that ultra-high pictures will probably be of a higher quality because of the reduction in man-made interference and ghosts at these frequencies.

During an interview, Goldsmith stated that ultra-high stations, allocated on a 300-mile separation basis now, could provide an immediate service.

(Continued on page 128)

The Success Story of Bill Smith... OR YOU!



Mails coupon to National Schools in Los Angeles, and receives Free Lesson and book of information about Radio, Television and Electronics training.



Enrolls... studies in spare time. Finds personal attention from instructors, interesting material and practical equipment, all increase his interest.



Builds actual units as part of Course. Earns money doing spare time repair and installation work.



Completes Course and receives Diploma... is now a qualified Radio, Television and Electronics Technician.



Applies for—and GETS—a good pay, full time job in industry. Finds that employers know National Schools and like to hire their graduates.



Or he opens own profitable Service Shop, with valuable counsel and aid from National Schools. Now for real happiness and success!



GET INTO RADIO, TELEVISION and ELECTRONICS by NATIONAL SCHOOLS SHOP METHOD HOME TRAINING

THIS PRACTICAL, TECHNICAL RESIDENT TRADE SCHOOL TRAINS YOU AT HOME FOR BIG RADIO OPPORTUNITIES!

Never in history has such rapid progress been made as in the great Radio, Television and Electronics Industry today! This exciting, fast-moving development means new and greater opportunities for the trained, skilled man—for you—in Television and Radio Broadcasting, Installing, Servicing; in Frequency Modulation; in Applied Electronics in many industries; in a business of your own!

National Home Training is Practical
Your National Schools Course fully covers basic, advanced and specialized instruction in all phases, including basic radio principles, receivers, am-

plifier systems, transmitters, television, aviation radio, electronics. You get complete instruction material, including shop manual, tube manual, job sheets, radio dictionary, special laboratory experiment lessons, experimental equipment. You receive complete, modern television lesson texts.

Your Home Study is supervised by our staff of highly trained instructors who daily teach our resident students here. Let the Free Books shown below tell you more about National Home Training. Use coupon today!

APPROVED FOR VETERANS

You Build This Superheterodyne Receiver With Parts We Send

You receive complete standard equipment, including latest type High-Mu Tubes, for building various experimental and test units. You progress step by step until you build a complete Superheterodyne Receiver. It is yours to use and keep.


Professional Multitester Included!

This portable instrument (see right) enables you to perform many practical tests, make delicate adjustments and do service work. Complete with test leads.

You receive a series of special laboratory experiment lessons to guide your practical exercises with your equipment. These lessons have been prepared with a special technique of illustrating radio principles by numerous easy-to-understand examples.

Both Resident and Home Study Courses Offered

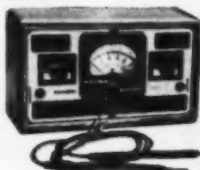Send Coupon Today for These Two Valuable Free Books



NATIONAL SCHOOLS

LOS ANGELES 37, CALIF. • EST. 1905

FIND OUT NOW... MAIL COUPON TODAY

National Schools, Dept. 5-RN
4000 South Figueroa Street
Los Angeles 37, California

(Mail in envelope or paste on postcard)


Mail me FREE the book, "Your Future in Radio," and a sample lesson of your course.

NAME _____ AGE _____

ADDRESS _____


CITY _____ ZONE _____ STATE _____

☐ Check here if veteran of World War II

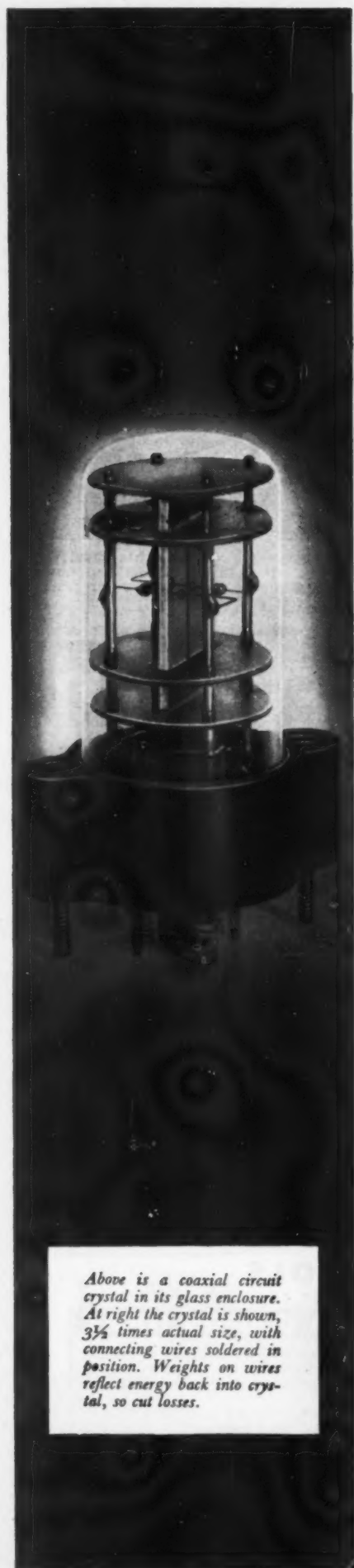

Above is a coaxial circuit crystal in its glass enclosure. At right the crystal is shown, $3\frac{1}{4}$ times actual size, with connecting wires soldered in position. Weights on wires reflect energy back into crystal, so cut losses.

Key to a Crystal Gateway

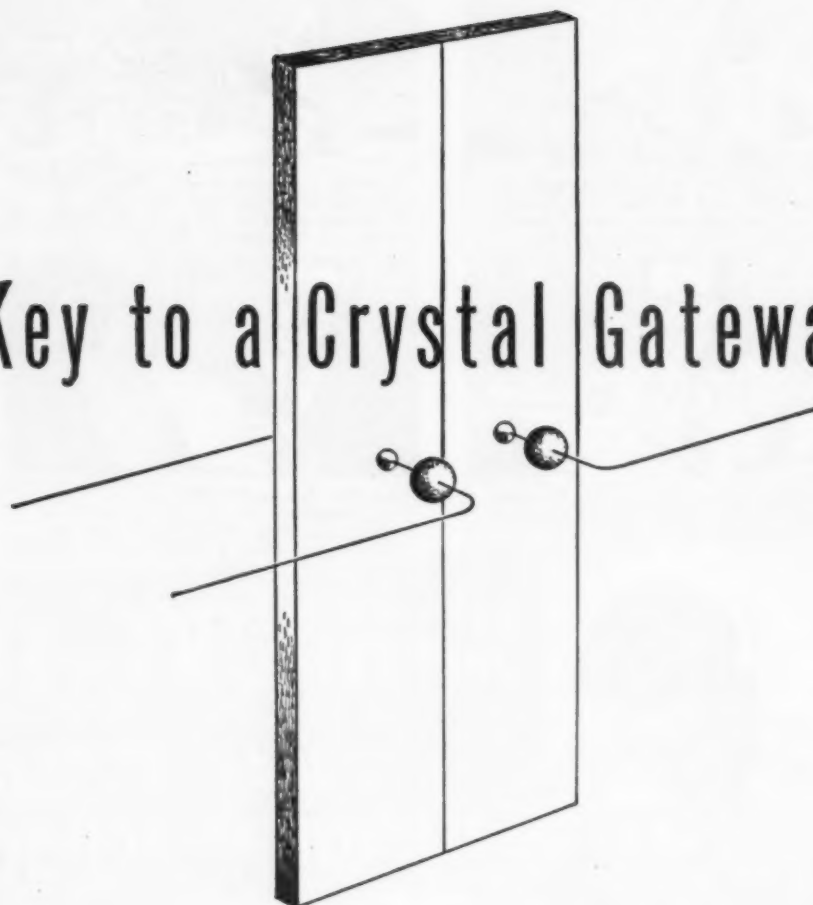

How would you solder a wire to a crystal? This must be done for most of those wafer-thin plates of quartz used in electrical circuits. They play a big part in the myriad-channel telephone system that utilizes coaxial cables.

This is how Bell Laboratories scientists solved the problem: A spot of paste containing silver is deposited on the crystal and bonded to it by oven heat. The crystal is then vapor-plated with a thin layer of silver. Then a fine wire is soldered to the spot by a concentrated blast of hot air. The result

is a rugged electrical connection to the surface of the crystal which does not interfere with its vibrations.

Sealed in glass tubes, the crystals are precise and reliable performers in the telephone system. Each is a crystal gate to a voiceway, separating *your* conversation from the hundreds of others which may be using a pair of coaxial conductors, at the same time.

This spot of paste, this tiny wire, this puff of air are among the tremendous trifles which concern Bell Telephone Laboratories in finding new ways to improve your telephone service.

BELL TELEPHONE LABORATORIES

EXPLORING AND INVENTING, DEVISING AND PERFECTING, FOR
CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE



NOW! T. A. C. AGAIN SCOOPS THE INDUSTRY!

**TELEVISION
ASSEMBLY CO.**
Subsidiary of

**Builders of America's Finest
Television Kits Now Offers—**

**DIRECT VIEW AND
PROJECTION**

COMPLETED SETS!



T.A.C. "CHAMPION" 12"-TUBE DIRECT VIEW

BIG 74 Square Inch Picture without lenses or gadgets. Exclusive T.A.C. designed handsome, modern-styled Select-Grain Cabinet in Walnut, Mahogany or Blonde. 30 Tubes, including BIG 12-inch Picture Tube. Manufactured by the nationally accepted Leader in Custom-Built Television. Licensed by Radio Corporation of America. The ideal home Television and FM Receiver! Remarkable performance and value! A miracle of Television engineering as well as a rich, beautiful furniture piece.

LIST **\$425*** PLUS INSTALLATION
IN BLONDE \$435.00*

"AUDITORIUM" 520 SQ. IN. PROJECTION TELEVISION



Optical system by Bausch and Lomb and Eastman Kodak. 37 tubes. 12" High-Fidelity Speaker. 20" by 26" screen for BIGGER-THAN-LIFE-SIZE, bright, steady, clear pictures. Can be viewed by an audience as large as 750 people. For home recreation rooms, institutions, schools, clubs, commercial establishments and offices.

\$1495.00*
PLUS INSTALLATION

Combination TV and ALL FM Sets

DuMont Inputuner for continuous tuning of ALL TELEVISION and ALL FM channels with utmost sensitivity and stability.

Exclusive T.A.C. "VIVIDeo" Feature PAT. PENDING

Renowned I.F. Picture and Sound Strip with 5½ stages of Cathode-Coupled Grounded-Grid Video I.F. Amplification that brings television reception to a new high standard of quality.

FREE!

Complete Service Data Manual SB-1 on the "VIVIDeo" feature, contains all information needed to thoroughly understand and service this unique high-gain I.F. Strip. Write for it today or ask your local jobber for it.

"Studio Quality Picture"

Until you've seen and enjoyed T.A.C.'s "Studio Quality Picture" you haven't really viewed television at its best. Here is a new standard of video quality. It's a NEW KIND of picture and we know you will agree it's the best yet.

Finest Obtainable Components

Combination of RCA, DuMont and highest rated nationally advertised components.

**AMERICA'S GREATEST
TELEVISION VALUE
PER SQUARE INCH
OF PICTURE!**

GUARANTEE

All T.A.C. receivers and their components are of the highest quality and are guaranteed under the Standard RMA Guarantee.



T.A.C. "SPORTS-VIEW" 15"-TUBE DIRECT VIEW

128 Square Inches. Amazingly bright, steady and clear! 30 tubes, including BIG 15" Picture Tube. Large 12" Heavy-Duty PM Speaker for fidelity sound. Licensed by Radio Corporation of America. Manufactured by the nationally accepted Leader in Custom-Built Television. Leatherette covered cabinet in choice of colors. Perfect for commercial installations and all large audience viewing. Special—Controls under Lock and Key!

LIST **\$550*** PLUS INSTALLATION

**DISTRIBUTED THROUGH NATIONAL
PARTS DISTRIBUTORS**

**DISTRIBUTORS! DEALERS! WRITE FOR
LITERATURE AND CONFIDENTIAL
PRICE INFORMATION TODAY!**

**TELEVISION
ASSEMBLY CO.**
Subsidiary of

**540 BUSHWICK AVE.
BROOKLYN 6, N. Y.**

* 5% Higher West of the Mississippi.
Prices subject to change without notice.

Centralab Announces the

New KOLORDISK (BC) HI-KAP...



**is Smaller
than a Dime**

Kolordisk (BC) Hi-Kap

WHAT IT IS!

Centralab's amazing new KOLORDISK BC HI-KAP is a versatile, dependable disc-type capacitor — seven times smaller than ordinary capacitors of similar capacity. Just 19/32 of an inch in diameter and .174 inches thick, it's actually smaller than a dime. And you'll like KOLORDISK's sturdy construction as much as its miniature size. The new KOLORDISK BC HI-KAP is made of metallic silver electrodes, bonded to a sturdy disk of tough Ceramic-X whose tensile strength is 3000 pounds per sq. in. In addition, KOLORDISK's minimum capacity is guaranteed

to .005 mmf. Yes — when you use this reliable new capacitor in your work, you'll agree its positive low internal inductance makes KOLORDISK ideal for TV, AM, FM, HF and AF circuits . . . just the capacitor you need for VHF and UHF applications, too. What's more, with KOLORDISK there's no mistaking capacity values. The complete value is clearly stamped on each capacitor. And, to make recognition simpler, the first digit of each CRL KOLORDISK's capacity is accurately indicated by the capacitor's red, brown or green body color.

WHAT IT DOES FOR YOU!

Centralab's new KOLORDISK BC HI-KAP is just what you need to replace obsolete, old-type by-pass or coupling capacitors. Its fine, sturdy Ceramic-X construction gives you exceptional mechanical stability . . . eliminates the possibility of shorts, opens or intermittent operation. There's no doubt about it — when you use Centralab's KOLORDISK BC HI-KAP, you'll agree it's rugged and efficient. Yes, you'll find

KOLORDISK will give you years of dependable service . . . service that will match the life expectancy of any unit on which it's installed. For all the facts on the KOLORDISK BC HI-KAP — the best capacitor, see your Centralab Distributor. Or write for Bulletin 42-16.


(Note: KOLORDISK BC HI-KAPS are not recommended for resonant or tuning applications.)

Ask Your Distributor for These CRL Parts




CONTROLS

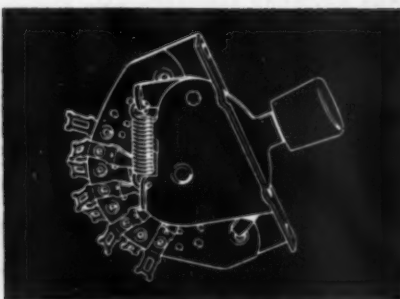MODEL "M" for voltage-divider, antenna shunt and "C" bias control, tone control, AF grid control. Model "1" for all miniature applications; rated at 1/10 watt, actually smaller than a dime. MODEL "R", wire wound, for voltage divider, antenna shunt, "C" bias, AF grid or tone control circuits.



SWITCHES

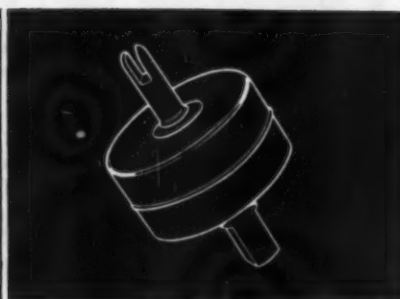ROTARY for band change, meter, intercom circuits; made in ceramic and phenolic models. ROTARY SPRING RETURN for meter selection, intercom, phono-radio applications. MEDIUM DUTY for band changing in low power exciter-transmitters and receivers. LEVER ACTION for intercom, speaker, microphone and other applications.



CAPACITORS

TC HI-KAPS for correcting temperature drift in TV, FM, AM, VFO circuits. BC HI-KAPS for by-pass and coupling applications in non-resonant, TV, AM, FM, AF, HF, VHF and UHF circuits. HI-VO-KAPS for TV power supplies. CERAMIC TRIMMERS for padder application in TV, AM, FM and HF circuits.

Centralab

Division of GLOBE-UNION INC., Milwaukee

Choose
PYRAMID
ELECTROLYTICS

for
Top performance
at 85°C



Pyramid Type 457M Capacitors are now in volume production for leading TV-receiver manufacturers throughout the U.S.A. and Canada.



PYRAMID
CAPACITORS

PYRAMID ELECTRIC COMPANY

155 Oxford Street
Paterson, N. J., U.S.A.

TELEGRAMS: WUX Paterson, N. J.
CABLE ADDRESS: Pyramidelec

Within the INDUSTRY

RUFUS SCHAGER, a tool and die maker for *Sylvania Electric Products, Inc.*, was awarded \$3950.00 for his suggestion for improving small metal parts. This is the highest award yet made by the Emporium, Pa., radio tube plant, and according to J. C. Farley, general manager, the idea received the top award because it has materially reduced shrinkage in radio tube production, increased production, and shortened the time required for a basic small parts operation.

The suggestion system was started in *Sylvania* plants seven and a half years ago, and since then, \$18,594.00 has been paid for 809 ideas adopted.

HAROLD HEINDEL, associated with the *Andrea Radio Corporation* for twenty-five years, has been appointed secretary of the organization.

Mr. Heindel, an outstanding figure in the development of both radio and television, was responsible for designing the first radio speakers for the *Andrea* radio sets.

Along with his new duties, Mr. Heindel will continue in his capacity of Chief Engineer for the corporation, manufacturers of the *Andrea* "sharp focus" television sets.

WARD LEONARD ELECTRIC CO., Mount Vernon, New York, announces that its general office has been moved from the factory building at 31 South St. to a new office building at 115 S. MacQuesten Parkway, Mount Vernon, New York. **TINNERMAN PRODUCTS INC.** has moved its New York district office from 620 Lexington Ave., New York City, to new and larger quarters at 75 Roseville Ave., Newark, New Jersey.

MICHAEL L. KAPLAN is president-elect of the newly formed Television Manufacturers' Association, which is now officially incorporated under the laws of New York State.



Mr. Kaplan, who is also president of *Sightmaster Corporation*, made the announcement after the initial meeting of the group. Ways and means by which the TV industry's service to the public can be bettered and increased are among the aims of TMA. The members realize that success in business is dependent on the public, and therefore the association will aim to reform and prevent abuses which have hurt the industry, such as the misuse of technical information employed to confuse and mislead the public.

Since the initial meeting of TMA, there has been steady activity in the group, and Mr. Kaplan has been contacted by many firms who report that an organization such as this has long been needed in the industry, and who have expressed their full support.

EVERETT GILBERT has been promoted to the position of vice-president of engineering at the *Radio Frequency Laboratories, Inc.*, Boonton, N. J.



Mr. Gilbert, a graduate of the University of Colorado, although only 28 years old, has been special projects engineer since 1945 and was previously with *General Electric Company* as a member of a development group on the Manhattan Project. His accomplishments at *RFL* include development of a new electronic metal detector for industrial processing lines. He is a member of several engineering societies, including IRE.

EDWIN J. SHERWOOD has been appointed television promotional manager of *Admiral Corporation*; his principal duty will be to conduct, in cooperation with *Admiral* regional sales managers, television sales training programs for distributors in the present thirty-five TV markets, as well as for those distributors in markets where television is just around the corner. **DR. ROBERT L. JOHNSON**, president of Temple University, is a newly elected director of the *Avco Manufacturing Corporation*. **DR. JOHNSON** is a trustee of the International YMCA, and is affiliated with many educational and charitable organizations; he was recently named chairman of the Citizens' Committee to press for favorable action on the proposals of the Hoover Commission. **R. T. PENNOYER** will succeed the late R. O. Poag as manager of the *General Electric Company's* Buffalo tube works. He will be concerned mainly with the manufacture of television picture tubes, the chief product of the company's Buffalo plant. *Lear, Incorporated*, at the annual meeting of stockholders, elected three new directors: **HAROLD R. BOYER** of Detroit, Mich., **COL. THOMAS N. BELSHE**, *Lear's* representative at Washington, D. C.; and **O. C. HALL** of Grand Rapids, Mich. The recent appointment of **JAMES J. SUTHERLAND** as general manager of the Electronics Division of *Sylvania Electric Products, Inc.*, was announced by H. Ward Zimmer, vice-president. To meet the demands of increased pro-

RADIO & TELEVISION NEWS

PRACTICAL HOME-STUDY

RADIO COURSE



"FINEST, UP-TO-DATE," TRAINING COURSE USED IN MANY SCHOOLS

"The radio training course is the finest up-to-date easy to understand course. . . . This course outlines practical work. We are using this course in our Topeka High School. It is wonderful." *Henry Ward, Jr., 622 Filmore St., Topeka, Kans.*



WORTH MUCH MORE

"You should get more money for your Course. The first week I studied it, I made \$10.00 repairing sets. I built my own test outfit from details given in this course. I have repaired 100 radios to date. . . ."

Signed: *Robert C. Hammel, 120 W. 13th, Davenport, Iowa.*



I COMPLETED COURSE IN ONLY 8 WEEKS

"I am very satisfied with the course. When I was at the twelfth lesson I started repairing radios. It took me two months to master your course." From a letter written by *Roger Langlois, 1679 Poupart St., Montreal, Canada.*



MODERN, UP-TO-DATE

"Your course is modern and up-to-date. There is not one page in the whole course which anyone can afford to miss. Your course started me on the road to a well paid job and has repaid me many times." *Charles Alspach, 433 Elm St., Reading, Pa.*

AMAZING BARGAIN OFFER

Here is your chance to take advantage of the most sensational offer in radio education. In this large course-manual of lessons you have all the topics covered by the best \$150.00 radio correspondence course. Learn important fundamentals. Speed-up radio servicing. Includes hundreds of circuits, thousands of repair hints, pages of practical short-cuts.

RADIO TRAINING FOR HOME-STUDY

This practical home-study course will show you how to repair all types of sets faster and better, tell you how to open your own shop and run the business. The lessons are well illustrated, interesting to read, easy to understand and apply. No special previous knowledge is needed. The early lessons explain important principles. Other lessons cover test equipment, trouble-shooting, circuit tracing, television, and every important topic of radio.

SERVICING METHODS SIMPLIFIED

Learn new speed-tricks for radio fault-finding, case histories, servicing short-cuts, extra profit ideas. Included are many large lessons on the use of regular test equipment, explanation of signal tracing, oscilloscope, transmitters, P.A., television, recorders. Let this information save for you enough time on a single job to pay the full price of \$2.50 for the complete course of 22 money-making lessons.

SOME OF THE TOPICS

Circuits, Auto Sets, P.A., Tube Characteristics, A.C., Fidelity, Using Charts, Amplifiers, Tracking, I.F., Phase, T-V, Reactance, Impedance, Modulation, A.V.C., Photo-cell, Review Questions, Crystals, Test Equipment, Meters, Analyzers, Tube Testers, Signal Tracing, Oscilloscope, Ohmmeters, Accuracy, Graphs, and hundreds of other radio and T-V topics.



IN MANUAL FORM

\$2.50
COMPLETE

SPECIAL OFFER
READ THE DETAILS

EASY TO UNDERSTAND AND APPLY

The practical lessons making up this course-book are easy to follow and apply to actual radio jobs. Hundreds of radio facts that puzzled you will be quickly cleared up. You will find yourself doing radio repairs in minutes instead of hours—quickly finding the faults or making needed adjustments. Every new radio development of importance and thousands of time-saving radio facts are packed into this complete course-manual.

SATISFACTION GUARANTEED

Use the "no-risk" coupon at the bottom of this page to order the complete Course for a 10-day examination. Look over the lessons, read a few sections, apply some of the hints to a few service jobs. Only then decide to keep the lessons at the bargain price of \$2.50 (full price), or return the material and receive a cash refund. Like other Supreme Publications listed below, this Course is available to you without risk, on a 10-day, satisfaction guaranteed, trial basis.

SUPREME DIAGRAM MANUALS



1949	1948	1947	1946	1945	1944	1943	1942	1941	1940	1939	1938	1937	1936	1935	1934	1933	1932	1931	1930	1929	1928	1927	1926-38
NEW												DIAGRAMS											
Manual												240 Pages											
\$2.50												Price \$2.50											

You can speed-up and simplify radio repairs with Supreme Publications manuals. Service all radios faster, better, easier, save time and money, use these most-often-needed diagram manuals to get ahead, earn more per hour. For the remarkable bargain price (only \$2 for most volumes) you are assured of having in your shop and on the job, needed diagrams and other essential repair data on 4 out of 5 sets you will ever service. Every popular radio of all makes, from old-timers to new 1949 sets, including F.M. and Television, is covered. Clearly printed circuits, parts lists, alignment data, and helpful service hints are the facts you need to be an expert in radio servicing. Save hours each day, every day, begin to earn more by making repairs in minutes instead of hours. Let these manuals give you diagrams for 80% of all sets. There is no need to spend large sums for bulky, space-wasting manuals of other publishers, or to buy additional drawings every few weeks; be wise, use SUPREME Manuals to get the most in diagrams and service data for the smallest cost. Select manuals wanted and rush "no-risk" coupon.

NO RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 3727 W. 13th St., Chicago 23, ILL.

Ship manuals checked on 10-day trial under your guarantee of satisfaction or money back.

- ☐ Radio Servicing Course-Book.....\$2.50
- ☐ 1948 Television Servicing Manual.....3.00
- ☐ 1947 F.M. and Television Manual.....2.00
- ☐ Simplified Radio Servicing.....1.50
- ☐ Post-War Record Changers.....1.50

☐ I am enclosing \$....., send postpaid.


☐ Send C.O.D. I am enclosing \$.....deposit.

- ☐ 1949 Manual, \$2.50
- ☐ 1948
- ☐ 1947
- ☐ 1946
- ☐ 1945
- ☐ 1944
- ☐ 1943
- ☐ 1942
- ☐ 1941
- ☐ 1940
- ☐ 1939
- ☐ 1926-1938 — \$2.50

PRICED AT ONLY \$2 EACH

Name:

Address:

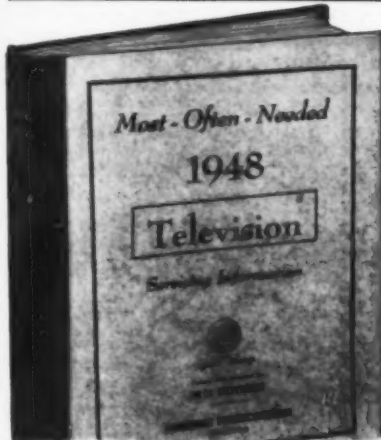

1948 TELEVISION

New, giant volume of 1948 Television factory data covers every popular make. Gives description of circuits, pages of test patterns, response curves, alignment facts, oscilloscope waveforms, voltage charts, service hints, many diagrams in the form of double-spread blueprints, test points, everything to bring you up to date and make you expert in T-V repairs. Large size: 8 1/2 x 11", manual style binding, flexible covers, price only **\$3**

1947 F.M. and Television Manual

Manual of instructions for trouble-shooting, repairing, and alignment of all popular 1947 F.M. and Television sets. Covers every popular make; includes F.M. tuners, AM-FM combinations, and all types of T-V receivers. This is the material you need to adjust and fix any modern F.M. and T-V set. Data on 192 large pages, 8 1/2 x 11". Sturdy, manual style binding. Your price, only..... **\$2**

SIMPLIFIED RADIO SERVICING

New, revolutionary different comparison technique permits you to do expert work on all radio sets. Most repairs can be made without test equipment or with only a volt-ohmmeter. Many simple, point-to-point, cross reference circuit suggestions locate faults instantly. Covers every radio set—new and old models. Over 1,000 service hints, 63 job-sheets, 26 large trouble-shooting blueprints, 114 tests you can make using a 5¢ resistor. Complete..... **\$1.50**

Post-War Automatic RECORD CHANGERS

Service expertly all modern (1945-48) record changers. Includes every popular make. Just follow simplified factory instructions to make needed adjustments and repairs. Hundreds of photographs and exploded views. Large size: 8 1/2 x 11 inches; 144 fact-filled pages. At your radio jobber or postpaid, special bargain price, only..... **\$1.50**

Supreme Publications

ONE OF A SERIES

GUARANTEED ACCURACY

WHY BURLINGTON PANEL INSTRUMENTS PROVIDE UTMOST RELIABILITY . . .




All Burlington instruments are calibrated with precision laboratory standards, which are periodically checked against a prime standard. All ranges AC and DC available in rectangular or round case styles and are guaranteed for one year against defects in workmanship or materials.

Refer inquiries to Dept. K-59.

Burlington INSTRUMENT COMPANY
BURLINGTON, IOWA



TELEVISION RECEPTION PROBLEM—No. 4 of a series

REDUCING "SNOW" OR IGNITION EFFECTS

The Workshop's Super-High-Gain, Six-Element Arrays will furnish strong, clear and snowless pictures even when weak signals have to compete with local electrical disturbances. This is due to the exceptionally high signal-to-noise ratio . . . the result of its sharp directional pattern coupled with the use of shielded coax line.

Send for the new Workshop TV Catalog (No. 49)

THE WORKSHOP ASSOCIATES, Inc.
Specialists in High-Frequency Antennas
62 NEEDHAM STREET, NEWTON HIGHLANDS 61, MASSACHUSETTS



duction at *Workshop Associates, Inc.*, Newton Highlands, Mass., **FRANK O. STAVES** has been appointed to the position of plant superintendent, bringing to his new post many years of experience in the field of plant management.

FLOYD MAKSTEIN has been named television field engineer for *Emerson Radio and Phonograph Corporation* and will serve as adviser to *Emerson* distributors throughout the country on television servicing and installation procedures.



Mr. Makstein joined *Emerson Radio* in January, 1945, upon his release from the armed services. For several years he worked with the television engineering staff and then was assigned to the company's subsidiary, the *Emerson Television Service Corporation*, working on the development of the service organization.

In rejoining the national manufacturing organization, Mr. Makstein will introduce an educational program for technical personnel of both distributors and dealers.

EUGENE B. LUCAS, well known to the radio industry, has been appointed sales manager of *Walco, Inc.*, maker of *Walco* standard and micro-groove phonograph needles, *Tele-Vue* lens, and *Walco* Television Filters. **YOUNG & MYERS**, 539 Jewel Ave., Kirkwood 22, Mo., will be the sales representatives in Eastern Mo. and Southern Illinois for the line of resistors, controls, and resistance devices made by *Clarostat Mfg. Co., Inc.*, of Dover, New Hampshire. **ALBERT M. BAEHR** is the new sales representative in Ohio for *C. P. Clare & Co.*, Chicago relay manufacturer; his offices will be at 11621 Detroit Ave., Cleveland 2, Ohio. With the addition of the **NEAL BEAR CORPORATION** of Peninsula, Ohio, and **ED OSSMANN**, Rochester, New York, *Hermon Hosmer Scott, Inc.*, will attain virtually complete national sales representative coverage. They will serve jobber and industrial accounts throughout their respective territories. The appointment of **ROY BOSCOW** as general sales manager was announced recently by the *Magnavox Company*. Mr. Boscov brings to his *Magnavox* position much valuable experience acquired while serving in responsible capacities with various large corporations. *Motorola, Inc.*, Chicago has appointed **ELLIS L. REDDEN** as its director of advertising and sales promotion. Mr. Redden has acquired a good deal of background in his field, having served in that capacity with *Borg-Warner*, *McCann-Erickson*, and latterly, with the *Avco Manufacturing Corp.* **ROBERT C. HOFFMAN** has been transferred from industrial engineer to Chicago distributor

(Continued on page 148)

RADIO & TELEVISION NEWS



TV Offers YOU Good Pay, Security and Bright Future

CREI On-the-Job Training Can Give You the Technical Ability to Step Ahead of Competition and Get the Better Job You Want

GET IN and get ahead in Television! You can make your own opportunity if you start preparing now. No need to tell you how fast Television is expanding—or, of the great number of jobs that are being created. One of industry's leaders predicts: *1 Million Persons in TV within 4 Years!* He estimates 12 Million TV sets by 1953—40 Million by 1958.

If you are now in radio, and wish to get in Television, CREI offers the very training you need to go after—and get—a good TV job.

CREI can show you the way with convenient spare-time study at home that gives you the up-to-date technical background and understanding you *must* have for Television. CREI courses are designed to give you a thorough grounding in basic principles and take you step-by-step through the more advanced subjects of TV and its related fields. It must

VETERANS: CREI TRAINING AVAILABLE UNDER G.I. BILL. FOR MOST VETERANS JULY 25, 1951, IS THE DEADLINE — ACT NOW!

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have the training you need to qualify for a better radio job. To help us answer intelligently your inquiry—please state briefly your background of experience, education and present position.



Capitol Radio Engineering Institute

An Accredited Technical Institute Founded in 1927

Dept. T16A, 16th and Park Road, N. W., Washington 10, D. C.

Branch Offices: New York (7) 170 Broadway • San Francisco (2) 760 Market St.

be remembered that all new electronic developments have their roots in past techniques. That's why your own radio experience is so important and worth while when coupled with modern CREI training. You will find CREI basic and helpful right from the start. You will learn about and understand such subjects as: Optics, Pulse Techniques, Deflection Circuits; RF, IF, AF and Video Amplifiers; FM; Receiving Antennas; Power Supplies; Cathode Ray, Iconoscope, Image Orthicon and Projection Tubes; UHF Techniques, Television Test Equipment, etc.

Don't wait another day. Television won't wait for you. In all our 22 years of association with professional radiomen we know that the man who acts promptly is the man who succeeds. The facts about CREI, our courses, and what we can do for you, are described in our 32-page booklet. It is well worth reading. Send for it now.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

16th & Park Road, N. W., Dept. T16A, Washington 10, D. C.

Gentlemen: Please send your free booklet, "Your Future in the New World of Electronics," together with full details of your home-study training. I am attaching a brief resume of my experience, education and present position.

Check field of greatest interest:

- | | |
|---|---|
| <input type="checkbox"/> PRACTICAL RADIO ENGINEERING | <input type="checkbox"/> PRACTICAL TELEVISION ENGINEERING |
| <input type="checkbox"/> AERONAUTICAL RADIO ENGINEERING | <input type="checkbox"/> TELEVISION, FM & ADVANCED AM SERVICING |
| <input type="checkbox"/> BROADCAST RADIO ENGINEERING (AM, FM, TV) | <input type="checkbox"/> ADVANCED ELECTRONICS COMMUNICATIONS |
| | <input type="checkbox"/> RADIO-ELECTRONICS IN INDUSTRY |

NAME _____

STREET _____

CITY _____ ZONE _____ STATE _____

☐ I AM ENTITLED TO TRAINING UNDER G. I. BILL.

2 GREAT NEW TUBES FOR

WITH television racing ahead to new records in popularity—to ever higher figures in dollar volume—choice of picture tubes takes priority with designers and builders of receivers. The picture tube is the heart of the TV set. Cost, picture size, brightness—these must be carefully weighed in the light of the particular market at which a new receiver is aimed.

Good news to designers is G.E.'s introduction of the two tubes shown here. One—the 8½-inch type (8AP4)—dovetails with requirements of the low-priced receiver market where costs must be scrutinized down to the last penny. The 12½-inch aluminized tube (12KP4) matches the needs of that field of sale—also large—where picture size and quality come first.

Both tubes are G-E-designed to embody tomorrow's advanced engineering concepts. Both tubes are G-E-built to highest precision standards of quality!



CHARACTERISTICS

	8AP4	12KP4	MAX. RATING DESIGN CENTER VALUES	
Max. bulb diameter	8 11/16 inches	12 9/16 inches	8AP4	12KP4
Min. inside case width	7 1/4 inches	11 inches	Max. Voltage	10,000 V.
Max. weight	6.3 lbs.	12.5 lbs.	Grid No. 1	1000
Max. length	10 1/2 inches	14 1/2 inches	Grid No. 2	1000
Max. base diameter	1 1/2 inches	1 1/2 inches	Grid No. 3	1000
Max. base length	1 1/2 inches	1 1/2 inches	Grid No. 4	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 5	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 6	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 7	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 8	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 9	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 10	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 11	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 12	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 13	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 14	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 15	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 16	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 17	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 18	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 19	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 20	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 21	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 22	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 23	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 24	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 25	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 26	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 27	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 28	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 29	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 30	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 31	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 32	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 33	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 34	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 35	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 36	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 37	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 38	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 39	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 40	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 41	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 42	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 43	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 44	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 45	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 46	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 47	1000
Max. base height	1 1/2 inches	1 1/2 inches	Grid No. 48	1000
Max. base depth	1 1/2 inches	1 1/2 inches	Grid No. 49	1000
Max. base width	1 1/2 inches	1 1/2 inches	Grid No. 50	1000

MASS TELEVISION MARKETS

TYPE 12KP4-A 12½-inch cathode-ray tube, all-glass construction. Aluminized screen. Offers the *brightest picture*—93 percent brighter (average) than a standard tube at 11,000 volts! Offers a *big picture*—95 square inches when the entire tube face is scanned; 75 sq. in. when standard raster of 3-by-4 aspect is employed. These areas are nearly half again as large as with the popular 10-inch type. . . . Here's the tube for TV-set manufacturers who put quality first, who wish to build consumer acceptance based on superior performance, on a larger, brighter, sharper picture. . . . Here's the tube that's setting the pace in 1949 television!

TYPE 8AP4—An 8½-inch cathode-ray tube with metal-cone envelope. Has plenty of picture area—47 square inches when the entire tube face is scanned; 36¼ sq. in. when standard raster of 3-by-4 aspect is used. . . . *Half the weight* of an all-glass tube, so ideal for small TV receivers that are lifted and moved about. . . . *Shortness of tube* (14½ inches) saves valuable space for the cabinet designer . . . *Requires a simpler, less costly circuit*, because the 8AP4's triode construction does away with need for a Grid-No.-2 voltage supply. . . . *Low in price*, up-to-the-minute in design—a combination that's putting this tube in first place with builders of small TV sets.

Size, responsibility, wide facilities for research, for manufacture—these identify a top source of supply for any manufactured article. Your source for picture tubes need be no exception. General Electric is actively engaged in every phase of television—has pioneered many important TV developments—brings to each tube type the knowledge gained from designing and building picture tubes for years in the field in which it is best known.

of picture tubes to the receiver you may be designing. Your phone-call, wire, or letter will bring immediate, helpful response. General Electric's distributor-dealer facilities for replacing picture tubes in picture sets are nationwide; your sales agents and customers can count on this service that is fast and reliable. Space-saving picture tubes for your quality television sets—General Electric has the best and most complete line of picture tubes available.





**MODEL
666-R
\$24⁵⁰**

U. S. A. Dealer Net

**A New TRIPLETT
POCKET-SIZE
VOLT-OHM-MIL-AMMETER
with self-contained Resistance
Ranges to 3 Megohms**

**Note the special
features of this New
handy-size tester**

- (1) **RESISTANCE RANGES** from 0-3000 Ohms (.5 Ohm low reading) to 3 Megohms, self-contained. Also A.C.-D.C. Volts to 5000, 10 ranges; and 3 Direct Current ranges.
- (2) **ENCLOSED SELECTOR SWITCH**, molded construction. Keeps dirt out, and retains contact alignment permanently.
- (3) **UNIT CONSTRUCTION**—Resistors, shunts, rectifier, batteries are housed in a molded base integral with the switch. Direct connections without cabling. No chance for shorts.
- (4) **RESISTORS** are precision film or wire-wound types, each in its own compartment.
- (5) **BATTERIES EASILY REPLACED**—Positive grip coil spring assures permanent contact. Makes replacement of batteries a simple procedure.
- (6) **STREAMLINED STYLING**. Handsomely designed, pocket-size case. Only two controls, both flush with panel.

*For Detailed Information
See your Radio Parts Distributor or write . . .*

TRI-PLETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.

In Canada: Triplett Instruments of Canada, Georgetown, Ontario



RANGES:

D.C. VOLTS: 0-10-50-250-1000-5000, at 1000 Ohms/Volt

A.C. VOLTS: 0-10-50-250-1000-5000, at 1000 Ohms/Volt

D.C. MILLIAMPERES: 0-10-100, at 250 Millivolts

D.C. AMPERES: 0-1, at 250 Millivolts

OHMS: 0-3000-300,000
..... (20-2000 at center scale)

MEGOHMS: 0-3
..... (20,000 Ohms center scale)

(Compensated Ohmmeter circuit for greatest accuracy over wide battery voltage variations.)

Precision first...to Last



RADIO & TELEVISION NEWS

Radar

By
MAJOR CHAS. E. SPITZ,
W7JHS

Radar Dept., Keesler Air Force Base, Miss.

**Complete radar training—
from basic principles to
actual working experience
—is covered at the Keesler
Air Force Base in Biloxi.**

THE Mississippi Gulf Coast, long famous for its shrimp, "place of worship" for the followers of Izaak Walton, and general vacation land for people who like to bask in its sunny breezes, is the site of one of the Air Force's large technical schools. Keesler Air Force Base, one of the finest of the Air Force Training Command Installations, is also the home of Radar Training.

One of the bright spots of the ARRL Delta Division Convention, held at Biloxi, Mississippi, on September 19 to 21, was the tour of the Radar Department with its whirling antennas, crackling sparks, and flashing oscilloscopes.

Radar, of course, is no longer one of the dark secrets of the past and much has been published on the subject; however, radar does exemplify some phases of radio at its peak efficiency, and every radioman who has had radar training has found his radio knowledge vastly strengthened. Radar antennas are of extremely high gain (and rotary, of course, as in the best amateur technique), receivers have such high gain and so low a signal-to-noise ratio that even some of the tubes used were bound to be adopted by the radio fraternity, where they now grace converters and pre-selectors in ham shacks throughout the country as the "hot" 6AK5 and 6J6, and QRM-less frequencies so high as to be barely tapped by communications people. It might easily be said that the commonplace in radar today is a view of the future in communications.

Radar training starts with fundamentals, way back at the beginning, both for men who can't hook up a doorbell and "oldtimers" alike. For the latter, it is a highly desirable refresher about many things long since forgotten, or skipped. For the begin-

Training in the Air Force



Student adjusting a feedline on an aircraft warning radar.

ner, it represents an introduction into the mysteries of electricity and an electronics career in the bud. The pace is fast, with six solid hours a day packed chock full of theory and lab; the general theme is to learn by doing, but you must understand what you do.

The course for a general airborne or ground radar mechanic is 42 weeks. Various specialist courses take different periods of time, depending on


the scope and complexity of the work. The study of d.c. with the necessary accompanying mathematics starts the ball rolling. If you can assimilate the material contained in a text such as Cooke's "Mathematics for Electricians and Radiomen," you shouldn't have much difficulty. The student studies electrostatics, electrodynamics, and the circuit analysis of multiple generator and network circuits, magnetic induction, motors, generators and elec-




Radar training starts with fundamentals.



It includes six solid hours of theory.

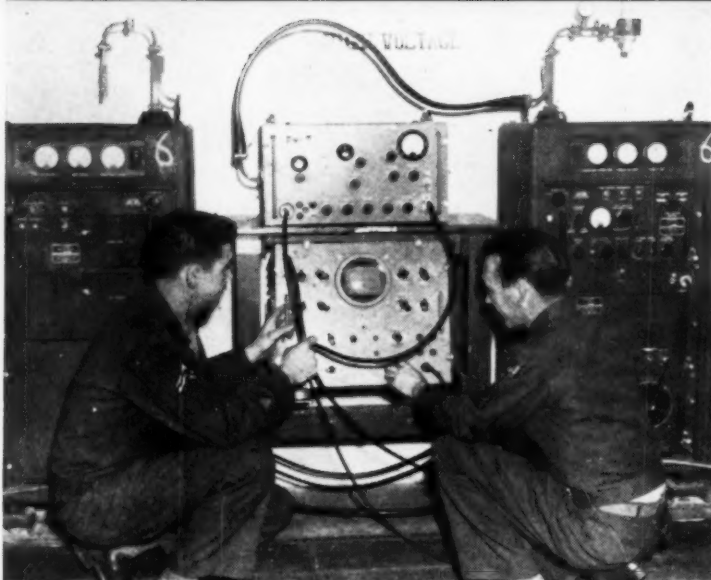

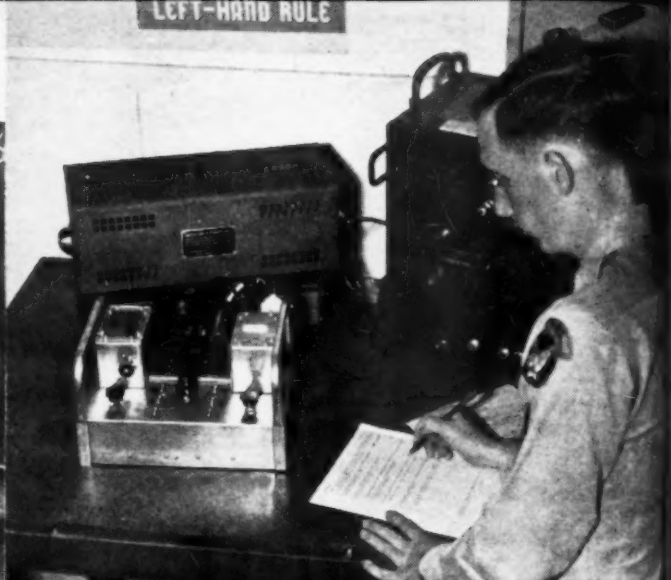Complete laboratory training is included.



Students perform experiments on circuits studied.



What makes the mutivibrator tick?



Students perform projects in Servo mechanisms.

trical measuring instruments which in turn are mastered before continuing to alternating current and its behavior in all types of reactive circuits. Intensive lab work is done where the student works projects in alternating current circuit analysis, resonance, and transformers. Particular emphasis is placed on vector analysis of alternating current networks and factors affecting magnitude and phase of circuit currents.

It gets even more interesting as you go along, for at this point electronics begins. Electronic emission, vacuum tube construction, characteristics of gas and cathode-ray tubes are studied concurrently with all types of rectifier power supplies and regulators. Enough equipment is provided so that each student performs experiments on each circuit studied, working independently of his classmates during the laboratory sessions. Amplifiers and oscillators come in for their share of scrutiny as do transients and non-sinusoidal alternating currents. Limiters, clippers, and sweep generators, common terms to the television people, are also subjects for study. One of the more interesting student experiments in this phase is the determination of the effect of coupling, staggered tuning, and loading of i.f. amplifiers. Laboratory exercises include tracing one- and two-stage amplifier and oscillator circuits and determining the effect of variable factors on gain, bandpass, frequency stability, etc. Using Thévenin's theorem, amplifiers are studied quantitatively by breaking down their complicated mass to equivalent circuits, which makes for ease of understanding and learning.


By now the student feels as though he has mastered a good deal, and he surely has. An oscilloscope is constructed by each student, and he completes this phase of training with further oscilloscope analysis, servo me-

chanisms and electronic timers. In the conclusion of electronic fundamentals, the principles of AM and FM modulation are studied, together with generation, transmission and propagation of microwave energy, impedance matching, how to convey the energy to the antenna by means of various transmission lines, and how to radiate it by various forms of antennas in or-

der to produce desired directive patterns.

Six months of intensive work have gone into the making of our future radar man in order to ground him well in basic concepts, and both he and the Air Force have reason to be proud of his accomplishments so far. In order to apply this knowledge, whole sets and systems are studied and operated, and trouble shooting is practiced for periods of eight to sixteen weeks. The sets studied range from small, compact, relatively simple systems, to bulky and complex blind landing and aircraft warning equipment weighing tons and numbering literally hundreds of operating tubes and circuits. The student is taught to calibrate, tune, adjust, inspect, and repair each set he is studying. The main objective is

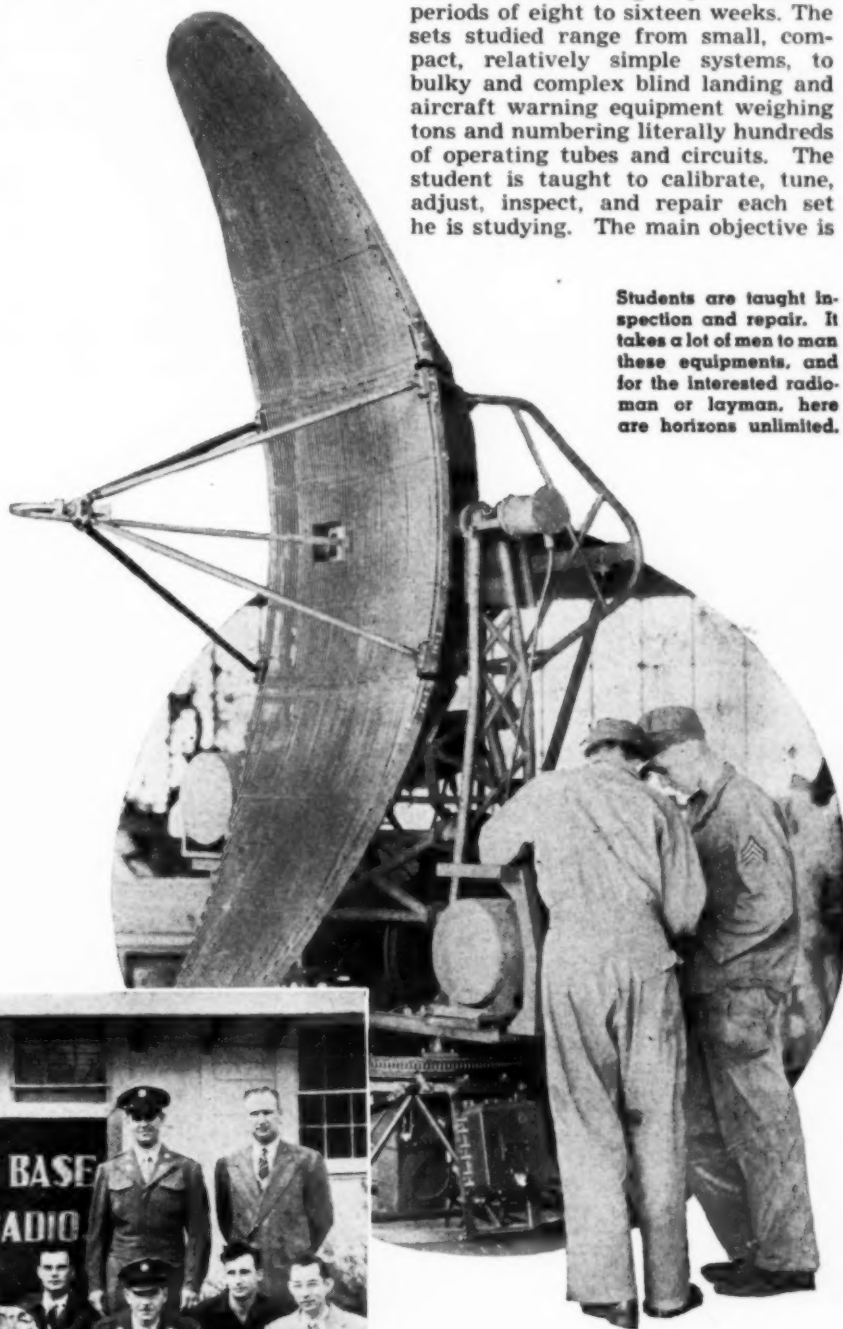Students are taught inspection and repair. It takes a lot of men to man these equipments, and for the interested radio-man or layman, here are horizons unlimited.



Typical club meeting of the Keesler Air Force base amateur radio club. Front row (left to right): 1st Lt. Paul W. Ridenour; Mr. Charles E. Spitz, W7JHS; 1st Lt. James S. Mays, W5PDS; S/Sgt. Lawrence K. Hulett; S/Sgt. Gilbert Becklin; Capt. James B. Sanders, W5LKI; T/Sgt. Marion T. Atkins; Sgt. Robert J. Townsend, Jr.; Mr. Ancil Z. Arseneau, W50PR. Rear row (left to right): Capt. B. E. Tillotson, W5PDW; 2nd Lt. Arvid E. Hamer, W4KJ1; 1st Lt. N. B. Ostrye, W5PDV; WOJG, R. A. Champagne, W4KQW; Lt. Col. Francis R. Delaney.



Even small, compact, and simple systems are tried.

The student is taught to tune, calibrate, and adjust.



Problems in trouble shooting.

to understand the principles of electronics underlying the various circuit combinations peculiar to each set, enabling it to do the job for which it was designed. Many different types of equipments are incorporated into the courses, and the student soon

learns that specialized uses require specialized sets. Therefore, with a maximum of practical work, equipments taught are representative of those used for altimeters, bombardment, gun-laying, navigation, weather observation, search, height finding, blind landing, and air traffic control.

A typical section of the course deals with a simple radar system, such as a high-altitude altimeter, and by means of it, introduces the student to the kind of maintenance work he would be expected to do. This includes training on the sort of tools he will have to work with, such as test equipments, hand tools, and technical manuals. He also learns the basic circuits necessarily incorporated into a simple functional radar. Stress is placed on how these circuits are oriented with respect to each other, and the specific way these circuits are used to enable them to do the job for which they are intended. Most radars consist basically of the units found in the first one studied. Typically, these are the power supply, synchronizer, transmitter, antenna system, receiver, indicator and control panel. The usual relationship of these units to each other is best shown by a simple block diagram such as the one in Fig. 1, with the indicator

arrows radiating from each source.


Some equipments are similar to FM radio, but because of their use, for example, a typical low-altitude altimeter, they are treated as radar. The set studied has widespread popularity, and does its job of measuring height above the ground so efficiently, it is used in a great many types of aircraft and by most airlines. One typical radar studied may seem rather large for airborne equipment, being a little more than a quarter of a ton, and consisting of no less than nineteen units connected by seven miles of wire! Other courses deal with aircraft warning radar. These giants, delicate though they be, indicate the movement of aircraft, telling of speed, direction and height, and some are so large they even have their own telephone system.

It takes a lot of men to handle these equipments, and for the interested radioman or layman, here are horizons unlimited; new circuits, techniques, and methods that stir the imagination. Here truly are careers awaiting men.

Recreation facilities are plentiful, and the average radio man or amateur is interested in the Keesler Air Force Base Radio Club, co-sponsor of the Delta Division 1948 ARRL Convention. Enthusiasm in the club mounts high. The clubhouse is a pretty white cottage, with two 600-watt transmitters, a four-element rotary on 10 meters, and fixed antennas on other bands. Many of the students and school faculty have their own rigs operating in barracks or quarters, and their calls are known throughout the world, wherever there are amateurs.

Many graduates leave to become well known DX stations, and it is not unusual to have D4, KG, and J hams arrive as students or instructors, both military and civilian. We like it here, know that you would, too, and hope some day to have the pleasure of welcoming you as one of us!

Fig. 1. Most radars consist basically of the following units: power supply, synchronizer, transmitter, antenna system, receiver, indicator, and control panel. Block diagram shows the usual relationship of these units to each other.

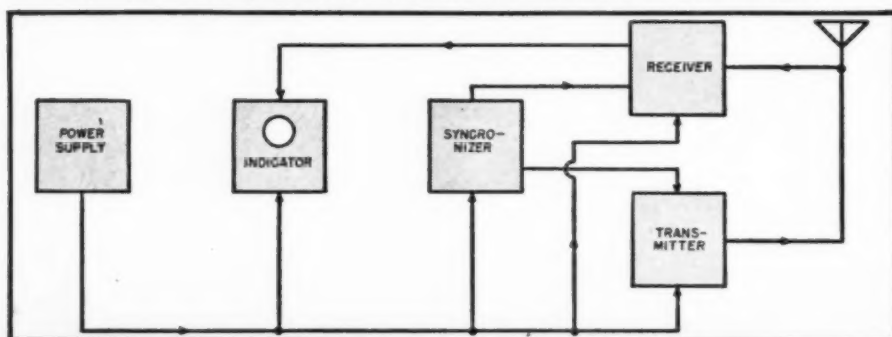



George S. Colman, Coles Signal Lab. Eng., who designed experimental model transceiver, demonstrates operational technique.

MINIATURE 4 TUBE TRANSCEIVER

Miniaturization in the extreme—yet this recently developed Signal Corps unit will find many practical uses.

EX-GI's who lugged around heavy communications equipment during the war will be interested to learn that the Signal Corps is working on a four-tube transceiver small enough to fit comfortably in a shirt pocket. The accompanying photos show an experimental model that weighs only eleven ounces *complete with batteries*.

Intended only for voice operation, this midget-midget permits reliable conversation over distances of about 200 yards. Depending on terrain and other circumstances, much greater distances can be covered. The major part of the design work on this new set was done by George S. Colman, a civilian engineer employed by the Signal Corps Engineering Laboratories, Fort Monmouth, N. J.


Except for a two-foot plug-in antenna which collapses to toothpick dimensions, there are no external wires, connections, or accessories. Both microphone and loudspeaker are built into the top of the case and are accessible to the mouth and the ear, respectively, when the lid is pushed up. With the lid closed, the device looks much more like a cigarette box than a radio set. Its actual size is $3\frac{1}{2}$ by $2\frac{1}{4}$ by 1 inches.

Unit sub-assemblies with plug-in connections greatly simplify both initial construction and subsequent servicing. "Repair" is almost entirely a matter of pulling out one sub-assembly and sliding in a new one.

The filament battery is a single round cell of the mercury type. Two flat "B" batteries are used. All three batteries snap into place without wires.


Aside from demonstrating the model illustrated, and emphasizing that it is only experimental, the Signal Corps is not releasing any technical circuit data. However, from the dimensions of the r.f. coils that appear in the open in the plug-in tuning units, it is fairly safe to guess that operation on the medium-high frequencies, rather than the very-high frequencies, is intended. Tiny crystals about the size of a tack head are used to assure proper "netting" of several "stations."

-30-

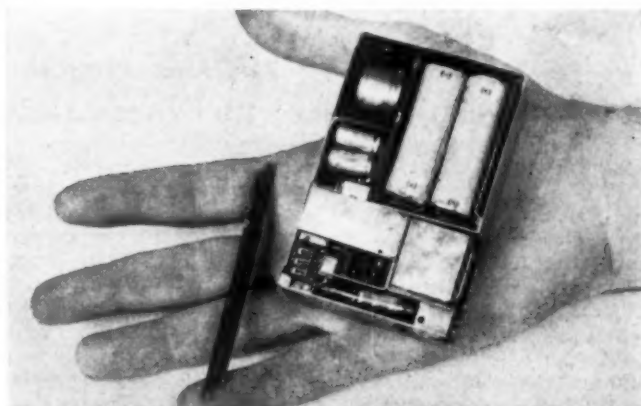

No idle space—the sub-assemblies nest together perfectly.

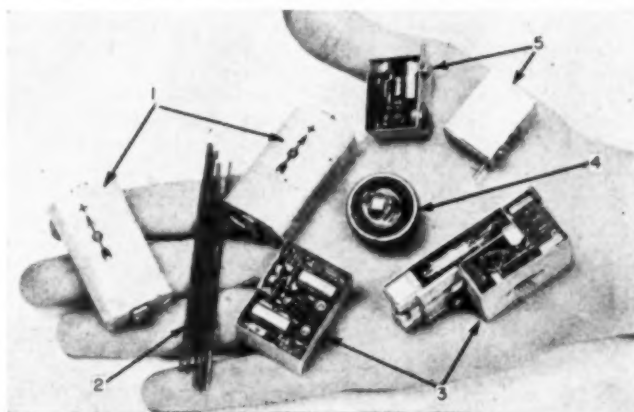The watch-like parts used in the new Signal Corps 11-ounce transceiver do not even cover the palm of a hand. (1) "B" batteries. (2) Antenna, collapsed to six 4" pieces. (3) Main sub-assemblies, containing r.f. and a.f. components. (4) Mercury type battery. (5) Plug-in r.f. tuning units, used one at a time.



A Low-Cost Bandswitching V.F.O.

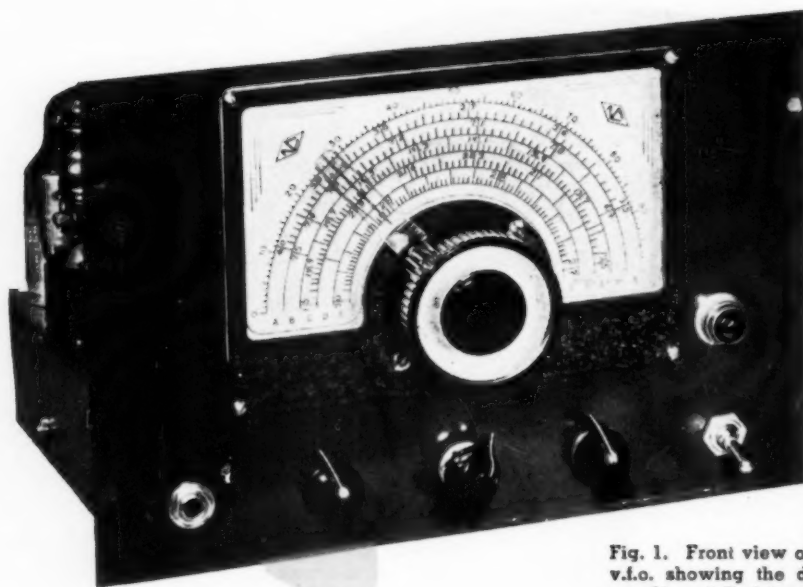


Fig. 1. Front view of the v.f.o. showing the direct reading full-vision dial.

By **ROBERT LEWIS, WAMQU**

A high-stability v.f.o. featuring fundamental three-band output with either v.f.o. or crystal.

EVER since the variable frequency exciter unit became popular, hundreds of ideas have come out of the amateur ranks, and reams of material have been written on the subject. The chances of digging up something new that has not been thought of before appear to be rather remote. Therefore, no claims are made on that score regarding the unit described herein.

The specific purpose in mind when this v.f.o. was designed was to produce an exciter that could be used to drive an existing crystal oscillator stage which would operate on the fundamental frequency or harmonics. It was desired to make the unit cover all bands below 30 mc. with a single external multiplier stage. Bandswitching and compact construction were to be incorporated, combined with maximum possible stability, all at the lowest possible cost consistent with good workmanship.

There are many manufactured v.f.o.'s on the market today, and at reasonable cost, too. Therefore, this article is written for hams who like to build, as well as operate, their own equipment.

A look at the diagram will show that the oscillator resembles the Colpitts circuit. Literature in recent ham publications setting forth claims of

high stability for this circuit prompted the writer to try it out. At first an oscillator circuit was built using a 7A4 triode. This circuit had a grounded plate, with output being taken from the cathode. However, it was desired to use the following stage as a doubler, and it was found that insufficient driving power was available from the 7A4. Therefore, a 7C5 was substituted for the 7A4, with output now being taken from the plate as in any electron-coupled circuit.

The second stage in this v.f.o. unit incorporates a single 7C5 tube as a doubler. It could be operated straight-through, but in view of the fact that the unit was to be operated with output on the 20-meter band, it was deemed advisable to operate the oscillator no higher than the 7 mc. band. With a plate voltage of about 275 on the 7C5 and a screen voltage of 150, sufficient power output can be obtained to drive a small beam-power tube as a straight amplifier or multiplier.

Oscillator screen and plate voltage is maintained at 150 by means of a voltage regulator tube. The high-voltage rectifier is a 5Y3GT, which was chosen because of its small physical size. The power supply uses regular receiving-type components and with the ratings as given, temperature rise within the cabinet is normal.

First plans were to use plug-in coils, but after some consideration it was concluded that coil switching could be conveniently used at a negligible increase in cost. Rather than utilize a tapped-coil arrangement, separate coils for each band were used, in conjunction with a ceramic selector switch. A two-gang condenser tunes the oscillator and doubler simultaneously. Prior to beginning construction, plans for the entire unit were drawn up on paper. All the coils were calculated on an inductance-capacity slide rule. However, as might well be expected, they all had to be more or less changed after testing began. In most instances, a few turns had to be removed from the coils. More time was spent in getting the tuning of the v.f.o. adjusted than in the actual construction.

Band No. 1 covers a frequency of 3450 to 4050 kc. The fundamental output frequency of band No. 2 is about 6900 to 7500 kc. By using an external tripler circuit, output in the 21 mc. band can be obtained. For 20-meter fundamental drive, band 3 covers 13,500 to 15,000 kc. Operating the following stage in the rig as a doubler results in 11- or 10-meter output. Thus all the lower-frequency amateur bands can be covered with three sets of coils and one external beam-power tube operating as buffer, doubler, or tripler.

A 7x8x10 inch steel cabinet was used to house the v.f.o., in conjunction with a 2x7x9 inch steel chassis. The cabinet and chassis were both refinished in smooth gray lacquer in preference to the original black crackle. The main objection to crackle finishes is the difficulty in keeping dust from

accumulating and becoming embedded in the paint. A word here might not be amiss regarding the painting of electro-zinc plated chassis. Some hams may already have known about this, but it was something new to the writer; this is the fact that lacquer does not adhere well to zinc-plated chassis, even when a good lacquer primer is used. In the case under consideration, the problem was solved by grinding off most of the zinc with a power sanding machine.

Observation of the photographs will show that all power supply components are mounted at the rear of the chassis. The coils are mounted vertically under the chassis with oscillator coils on the left and doubler coils on the right. Padding condensers are mounted alongside each respective coil. The band-change switch is mounted at the center of the chassis to facilitate wiring to both oscillator and doubler stages. First consideration regarding the tuning dial was to use one having a 0-100 scale in conjunction with calibration charts. However, after comparing the relative merits of that type, and the type having a calibrated scale, the National SCN dial got the nod. Controls along the lower edge of the front panel are: key jack, test switch, band switch, send-standby switch and power switch. Above the power switch is a "power-on" pilot light.

On the rear drop of the chassis is mounted a 6-terminal Jones strip to which are connected receiver cut-off circuit, transmitter relay circuit, and 117-volt supply line. Also mounted on the rear of the chassis are a fuse holder and output coaxial connector.

It will be noted that the v.f.o. incorporates a crystal socket and a single-pole, double-throw toggle switch S_2 , providing crystal control at will. The 7C5 doubler stage then operates as the crystal oscillator, with output

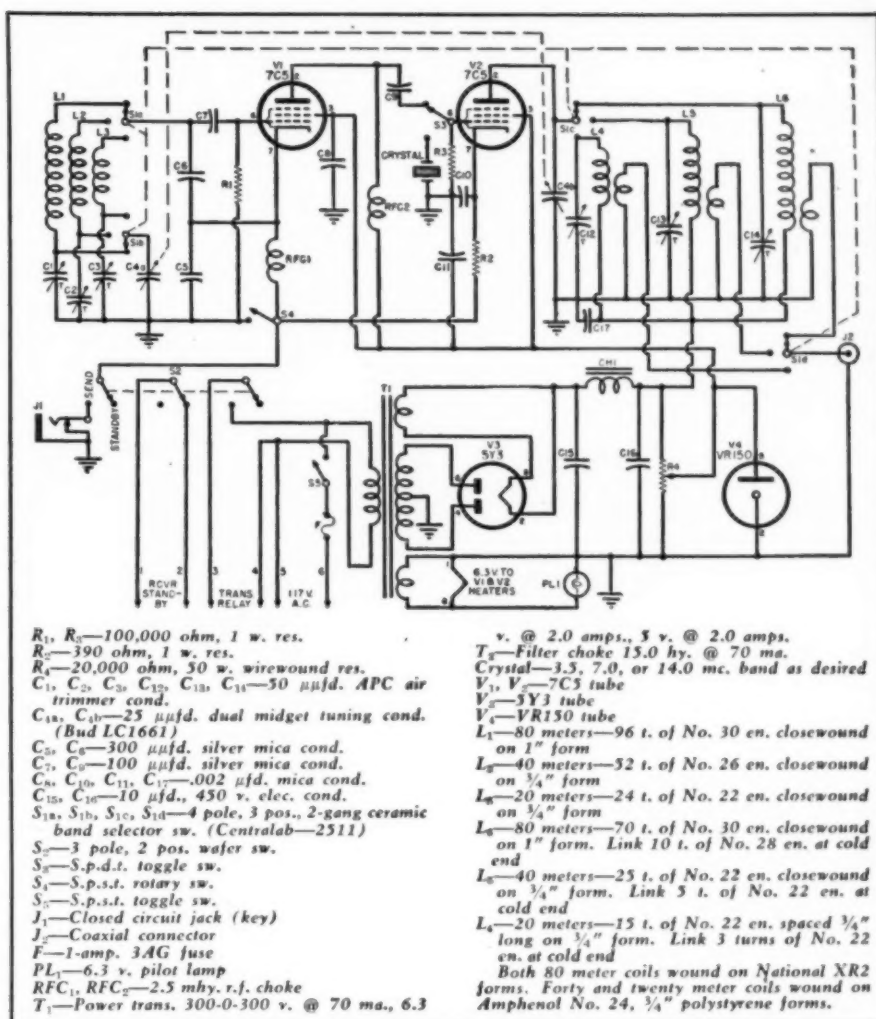


Fig. 2. Schematic diagram of the completed v.f.o. Provision is made to control external circuits. A two-gang condenser tunes the oscillator and doubler simultaneously.

on the fundamental frequency of the crystal. When using crystal control, the tuning is set to the high-frequency

end of the band in which the crystal is located.

(Continued on page 120)

Fig. 3. Top view. S_2 is to the right of the tuning condenser.


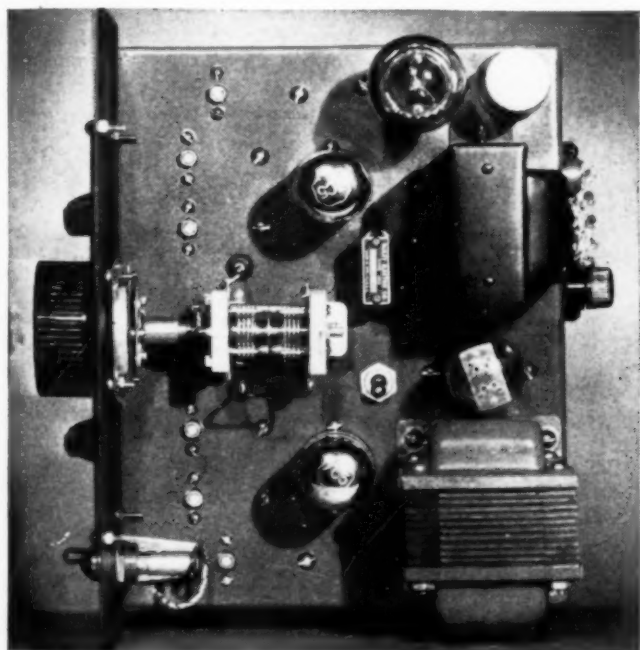


Fig. 4. Bottom view. Padding condensers are near front edge.

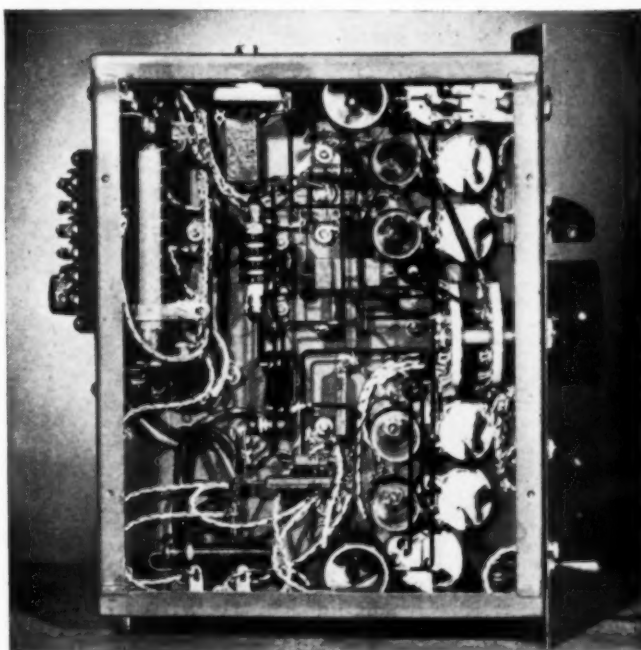

The Television ANTENNA

By
GARDINER G. GREENE

Pres., The Workshop Associates

Do not attempt your own TV installations without understanding the basic fundamentals involved in antenna-matching networks

TO GET the most out of the television installation, the installer must thoroughly understand the fundamentals involved in antenna-matching networks.

A television installation consists of a television antenna, transmission line, and television receiver. The maximum is realized from the installation of these three components when they are all of like impedance. Under the conditions of a perfect match at both ends of the transmission line, it is impossible for standing waves to develop on the transmission line. Standing waves cause a power loss and develop reflections which mar the television picture.

While it is true that there will be no standing waves on the line when

Fig. 2. Horizontal pattern in power for horizontally polarized three-element parasitic array. This pick-up pattern is for the antenna illustrated in Fig. 1 above.

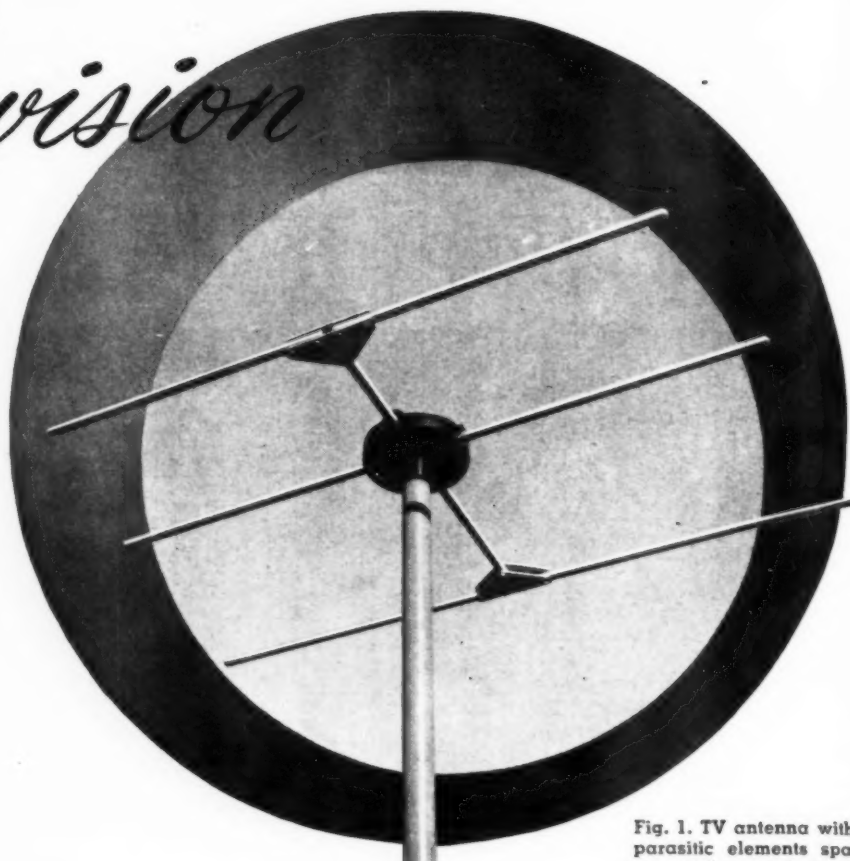
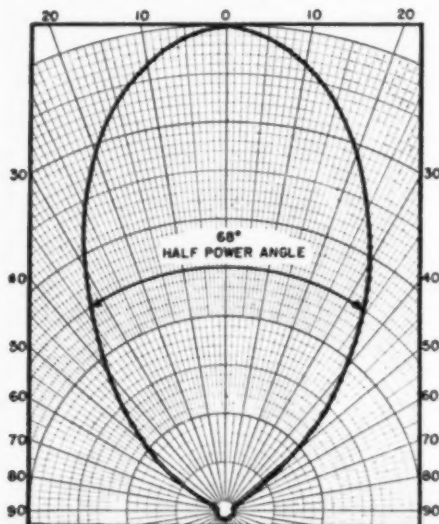


Fig. 1. TV antenna with its parasitic elements spaced to match coaxial cable.

the television receiver impedance matches the transmission line, it is very difficult for some manufacturers to make their receivers a fixed impedance over the wide TV spectrum from 54 to 216 megacycles. Therefore, should there be an appreciable mismatch at the receiver input, a perfectly-matched antenna and line will re-radiate whatever signal is reflected up the transmission line due to this receiver mis-match. In some systems employing long, low-loss lines, where there is an appreciable mis-match at both antenna and receiver, a large share of the reflected signal will not be re-radiated, but will return to the receiver with a total time delay sufficient to register ultimately as a "ghost" on the video display.

If the line is not low-loss, it may attenuate the weaker reflected signal to the extent that it will not be perceived; a shorter line possessing a small transit time may not produce a "ghost," but will certainly create a fuzzy, indistinct image. Therefore, good engineering practice makes it mandatory to preserve impedance matches throughout the complete system.

As a transmission line, coaxial cable is preferred over balanced twin lead because of its higher signal-to-noise ratio characteristic, and with some types, such as RG-8/U and RG-11/U, it has lower loss. While coaxial cable is more expensive, it requires less time and care to install and it guarantees the stability and longevity of the installation. Many installers have dis-

regarded coaxial cable, although they realize its value, because they were unable to connect it to the common type of television receiver which has a 300-ohm balanced input. This problem has been solved by the new, inexpensive impedance-matching transformer shown in Fig. 7. This transformer permits quick and easy connection to a transmission line and television receiver in the manner shown in Fig. 4. This unique transformer also solves two perplexing installation problems: (1) Increasing signal strength, and (2) Elimination of "leading ghosts" caused by direct pickup.

The transformer (Fig. 7) increases the signal level 2 to 1 in voltage. This voltage step-up in certain signal areas may be just the amount necessary to remove the "snow" from the TV picture. Another advantage in weak signal area installations is that the transformer permits the use of coaxial cable to match a 300-ohm receiver and thereby enables the installer to realize a greater signal-to-noise ratio by virtue of the shielded nature of the coaxial cable.

When coaxial cable is employed in an installation, a perfect match and maximum transfer of power from the antenna to the receiver can be accomplished by use of the TV antenna shown in Fig. 1. This beam antenna has its elements so spaced that its impedance at the TV channel to which it is adjusted approximates the impedance of the coaxial cable. The narrow beam pickup pattern shown in Fig. 2 raises the signal-to-noise ratio, since

It rejects spurious signals transmitted from devices located at the rear and side of the antenna's installed position, and increases the TV signals received by 5 db., relative to the response of the conventional one-half-wave dipole.

Fig. 5 shows further applications of this matched antenna in a stacked array which further increases the signal-to-noise ratio.

While the antennas shown in Figs. 1 and 5 cannot be used singly for 12-channel reception, it is possible to realize the benefits of efficiently matched antennas by circuiting several of these antennas to a TV receiver through a coaxial switch (Fig. 6) in the manner shown by Figs. 4 and 8. An antenna of the type shown in Fig. 1 offers a close match for coaxial cable on adjacent channels, e.g., an antenna cut for channel 3 will have a good match to the coaxial transmission line on channels 2 and 4. An antenna cut for channel 8 is a close match to the coaxial line on channels 7 and 9, etc. Therefore, a 6-channel high-gain installation could be made up with two antennas (Fig. 8).

Any one metropolitan area will not have active adjacent channels. A spectator living approximately midway between two fairly well-separated cities *may* be in a position to receive three consecutive channels as suggested in the foregoing. However, in congested areas served with TV signals of varying strength and from many directions, it is usually wiser to select, initially, the stronger channels carrying network programs of definite appeal to the spectator. Consequently, a few well chosen antennas can be used to render reliable and consistent signals in the manner of the multiple array configuration displayed in Fig. 3.

One of the most difficult TV installation problems to solve in strong signal areas is "leading or positive

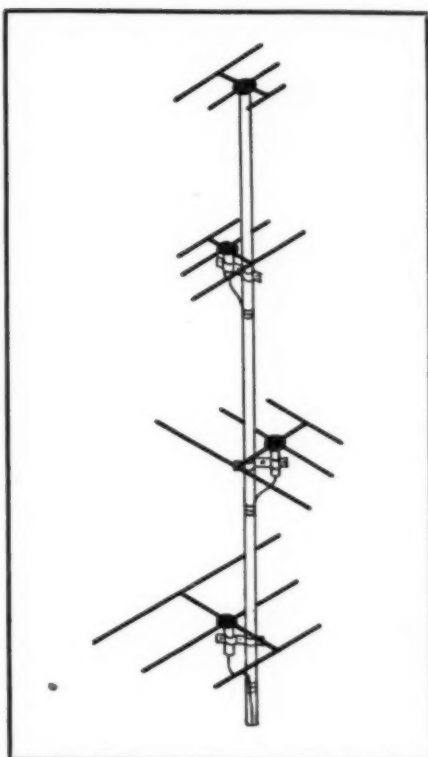


Fig. 3. A multiple-channel array which will permit reception on as many as ten channels.

ghosts" which are created by TV signals, picked up by the unshielded conductors of 300-ohm "twin lead," and which arrive at the input terminals of the television receiver sooner than the TV signals from the antenna. The time delay involved makes the signal arriving from the antenna the second pattern on the screen. A "leading ghost" will mar the picture as badly as the common "lagging" or "negative ghost."

The "leading ghost" problem can be

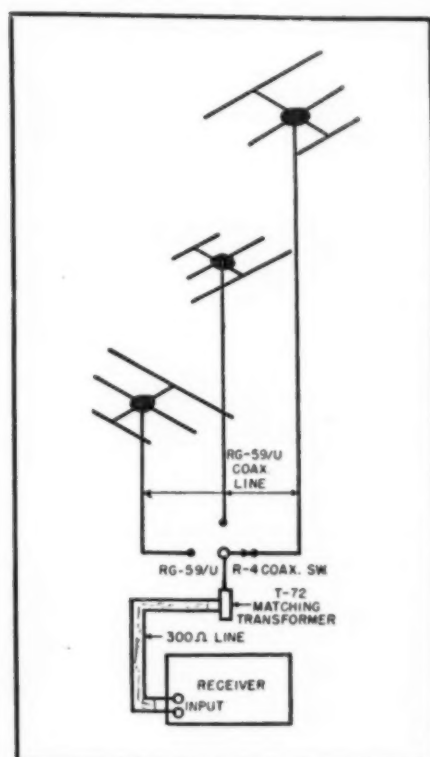


Fig. 4. Circuit of coaxial switch allowing one TV set to connect to three antenna lines.

anticipated in strong signal areas by checking the television receiver to be installed without an antenna connected to its input terminals. If the TV pictures are strong and of high definition, a completely shielded installation is advised. To solve the "leading ghost" problem with a shielded installation, a coaxial line must be installed with a high-gain antenna. The high-gain antenna should favor the TV channel which indicates the strongest direct
(Continued on page 112)

Fig. 5. Six-element high-gain array. It has a higher signal-to-noise ratio than the antenna shown in Fig. 1.

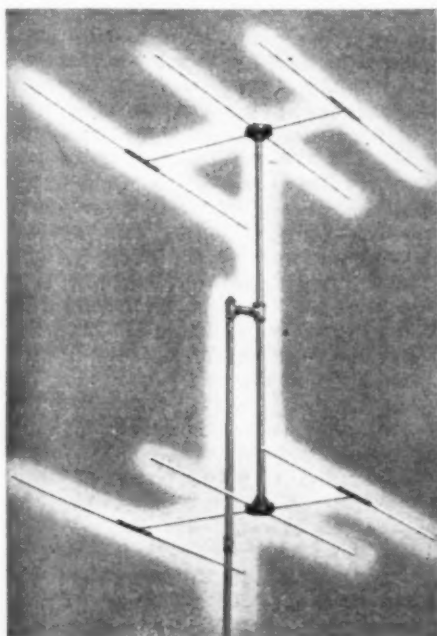


Fig. 6. A conventional coaxial switch that is used to connect a single TV receiver to any of four TV antennas.

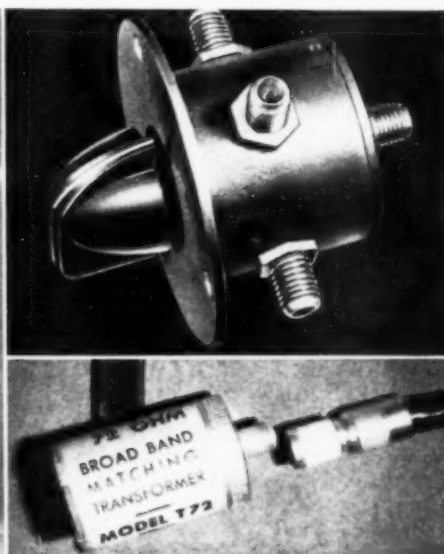


Fig. 7. Television matching transformer. Unit provides a voltage step-up ratio of 2:1 over the entire television spectrum.

Fig. 8. Typical high and low band television antennas mounted on a single mast for efficient four-channel operation.



Planning for Profit

By
FRED MERISH



A budget can start any month in the year—the sooner the radio and television dealer starts budgeting, the more actual profits he will show.

MANY are aware that 1949 has ushered in a buyer's market.

In some fields the pipelines are full, inventories are at the highest level in history, and prices have softened. The day is over when the retailer can buy or sell with little or no thought to planning. From now on, he must plan his work and work his plan if he expects to earn maximum profits.

The way to plan successfully is to use a budget which is a forecast of sales, cost of sales, margin, overhead expense, and net profit for a forthcoming period, the estimated figures being checked against actual results with all substantial variances investigated.

A budget is set up in reverse. In other words, the dealer estimates his overhead expense first, then the desired net profit, arriving at the sales volume figure last. In setting up his overhead expense estimate, the dealer should use prior-period figures as the base, adjusting them in line with future plans.

Say that a review of experience figures for the prior twelve months shows that the ratios in relation to sales were as shown in Table 1.

These ratios are merely illustrative,

and are not necessarily indicative of any dealer's experience figures.

When the ratios based upon sales have been determined by a review of experience figures, the next step is to budget, or estimate, the overhead outlay in dollars and cents. If this figure is set at \$17,500, covering rent, light, office expense, insurance, etc., and if the overhead ratio to sales is customarily thirty-five per-cent, as shown on the foregoing table, divide 35 into \$17,500 to get one per-cent, or \$500; then multiply by 100 to get the budgeted sales volume (sales are always considered 100 per-cent), in this case \$50,000.

With the sales figure budgeted, a dealer can easily fill in the remaining figures as shown in Table 2.

This is the basic formula for setting up a budget. If a dealer is not satisfied with a five per-cent net profit and wishes to increase the percentage, he must deduct the differential from the overhead, or cost of sales percentage, and then arrive at the dollars-and-cents estimate. No counsel can be given as to desirable ratios. This is entirely up to the dealer to decide, upon reviewing experience records and using his own judgment as to reason-

able income, outgo, and net profit. Once the dealer fixes the budgetary figures, he should try to approximate them; hence, he must be realistic and not attempt the unattainable.

In arriving at the overhead outlay in dollars and cents, a dealer should consider, not only the outlay for the prior period, but any changes that future plans may make in the figure. If a dealer plans to increase his advertising outlay, or his selling expense, he must increase this estimate on the budget; if he plans to buy certain depreciable assets, he must include a depreciation charge for them. Every sensible businessman has a fairly good idea of what he intends to do along these lines over a coming period, and he adjusts prior-period figures on overhead expense accordingly.

The dealer will arrive at a sales volume figure based upon overhead expense, that can be used as a guide to profitable operation in a subsequent period; but this is a volume figure for the period as a whole, and, to be of value, it must be broken down to monthly totals. Sales volume varies during the year in accordance with seasonal business, selling efficiency, promotional activity, and consumer demand. Past experience figures, however, will be a good guide to these sales fluctuations.

For example, if January sales for a prior year, or a number of prior years, were 3.5 per-cent of total sales, the current budget is set up accordingly,

When budgeting for a subsequent period, a dealer should use the foregoing monthly ratios to set up his monthly quotas, the monthly percentage multiplied by the total sales volume, as estimated, to get the monthly sales figure in dollars and cents. To get the monthly figures for the cost of sales, overhead expense, and net profit, use the ratios shown on the foregoing tables. For example, the budgeted figures for January would be those shown in Table 4.

The dealer cannot expect to match estimated with actual results each month, or for the year as a whole, but a budget will give him some semblance of constructive control. The fact that in any month there may be a big difference between estimated figures and actual results does not negate the value of a budget as a check-sheet on operations. All budgets require a certain degree of flexibility, and the figures set at the beginning of a period may be changed if conditions warrant.

Budgeting may start any month and cover any period from a month to a year. If a business year ends in December, and a dealer starts budgeting in May, estimates may be forecast to December and budgeted from January to December thereafter, the budgets being kept in a looseleaf binder for comparative analysis so that the dealer can determine the accuracy of his estimates from period to period. If a dealer wants to budget quarterly or semi-annually, he forecasts each period as detailed here, getting experience figures from similar periods in the past, adjusting the figures, wherever necessary, to current conditions, and breaking down the total figures to monthly figures by referring to the customary results experienced in the months on his budget. At first, estimates may vary widely from actual results, but with the passing months, paying close attention to the figures, the dealer will find himself doing a better job of forecasting.

Some businessmen assume that because their operations are complex in certain phases, budgeting is impracticable, but this assumption does not square with the experiences of business men in general. Many concerns producing hundreds of different products budget operations with success.

One weakness in this field is lack of budgetary control. In our public accounting work, we find very few radio and television dealers who forecast operations. Such negligence from now on will prove more costly than in bygone years. Because of variables and uncertainties, operations will be hard to forecast, but this is no excuse for not budgeting, although some dealers do decry the efficacy of a budget for this reason. They contend that they do not know what the morrow will bring, so how can they budget for an ex-

[illegible]

When the figures for the budget have been compiled, they should be recorded on a budget sheet similar to the one shown above. The estimated sales should be checked against actual sales, likewise, the cost of sales, margin, overhead, and net profit, the results being entered in the proper column and month. Many dealers do not budget because they assume that it is an intricate process. The formula given in this article is easy to follow and can be applied to all businesses in this field, large or small.

Sales	100%
Cost of sales—purchased goods sold	60
Margin on sales	40%
Overhead expense	35
Net profit on sales	5%

Table 1.

Sales	\$50,000	100%
Cost of sales—purchased goods sold	30,000	60
Margin on sales	\$20,000	40%
Overhead expense	17,500	35
Net profit on sales	\$ 2,500	5%

Table 2.

tended futurity. Such businessmen do not understand the underlying purpose of a budget, which is to provide a jumping-off place from which to get perspective on future operations.

In checking our research work sheets covering prewar operations in the retail field, we find that ninety per-cent of the dealers using budgets made, or exceeded, anticipated profits, ten per-cent dropped below anticipated profits by an average of only eight per-cent, while none lost money. Of those not using budgets, only thirty per-cent made or exceeded anticipated net profit, forty-five per-cent did not make the net profit hoped for, the deficiency averaging twenty-two per-cent, and twenty-five per-cent lost money, even though they used a pricing formula that looked profitable on paper. It is only reasonable to conclude from these field studies that budgetary control in prewar years was essential to the attainment of maximum

January	\$ 1,750—	3.5%
February	1,600—	3.2
March	4,750—	9.5
April	5,000—	10.0
May	5,300—	10.6
June	4,600—	9.2
July	3,500—	7.0
August	2,500—	5.0
September	3,050—	6.1
October	5,700—	11.4
November	5,750—	11.5
December	6,500—	13.0
Totals	\$50,000—	100.0%

Table 3.

profits; and, certainly, if this business control gadget was needed in a more placid day, how much more imperative is its use in this postwar period, when business is "needed" by high costs, high taxes, inflation, and the threat of a buyer's market.


Table 4.

Sales	\$1,750.00—100%
Cost of sales—purchased goods sold	1,050.00—60
Margin on sales	\$ 700.00—40%
Overhead expense	612.50—35
Net profit on sales	\$ 87.50—5%



International SHORT-WAVE

Compiled by KENNETH R. BOORD

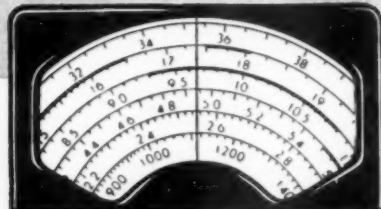

IT IS a pleasure this month to dedicate the *ISW Department* to "The International Goodwill Station," OTC, of the Belgian National Broadcasting Service, Leopoldville, Belgian Congo, and to its unique OTC Club. Thanks go to John J. Gaynor, California, for supplying us with this current information received by him from Leopoldville.

OTC is now operating on 9.767 (30.71 m.) with 50 kw. power and is scheduled as follows:

First transmission—1300-1400 Belgium calling the Netherlands and South Africa (Dutch); 1400-1415 (Dutch) and 1415-1430 (French) Belgium calling her countrymen in the world; 1430-1530 (English) Belgium calling Great Britain in the British Territories in Africa, with news 1432, news headlines 1527, and "Amongst Friends" (answering listeners' letters) 1445; 1530-1540 (French) Belgium calling her countrymen in France; 1540-1700 (French) Belgium calling France, Switzerland, and the French Union; 1700-1845 (French and Dutch) for the Belgian seamen and their French and Dutch friends; 1845-1900 closedown for change in transmitters to North and South America.

Second transmission—1900-2030 (French) Belgium calling Canada; 2030-2045 (French) Belgium calling countrymen in the world; 2045-2100 (Dutch); 2100-2300 (English) Belgium calling the United States and Canada, news 2102, news headlines 2255, and "Amongst Friends" (answering listeners' letters) 2115. On Wednesdays around 2115, DX items for SWL's and radio amateurs, including radio club information, are presented. On Friday of each alternate week, from last January 7, at 1445, there is a special "Amongst Friends" edition in Swedish, in answer to letters from Swedish listeners. A preview of the coming week's musical programs is broadcast each Sunday 1445 in the first transmission and 2115 in the second.

At present, verification appears to be by mimeographed letter, but may also send out QSL cards.

Data on the OTC Club as sent out by the station is:

(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.)

"Listeners will be pleased to hear that the OTC Club has been formed, and that any time from now on applications for membership can be made. Membership tokens, in the form of a membership card and a small badge, will be forwarded to those of our friends who send us (1) one dollar (U.S.A. and the dollar zone), or, (2) five shillings (Europe and Africa), or, (3) five Swedish kronen (Scandinavian countries). This small charge is meant to defray printing and postage costs, but it is hoped that there will be a small surplus which will go to the benefit of the widows and orphans of members of the famous Underground Radio Resistance group, 'Samoyede,' which did such fine work in Belgium during the war.

"*'Samoyede'* was conceived and created by a Belgian patriot, a reporter of the Belgian National Broadcasting Service, who was arrested by the Gestapo and interned in the infamous concentration camp at Breen-donck. Having talked the idea over with other radiomen, he was lucky enough to escape to Great Britain and to work it out. Soon a man whose task it was to organize the underground ra-

dio net by getting in touch with former leading people of the *Belgian Radio*, was parachuted over Belgium, and it was the appearance of this parachutist that suggested the name of the underground group. As a matter of fact, his cheek bones were prominent as they are with the Northern Samoyede people.

"Membership in the OTC Club, therefore, brings closer contact between YOU and US and makes you an active promoter of friendship and international goodwill.

"In conclusion, we would like to point out that it is *not* essential to become a member of the club in order to get a reply to your letters; the club is the formal part of what is in reality an informal club group of OTC friends and listeners throughout the world. Nevertheless, we hope you will come forward to give active support to the OTC Club and its objectives. Our address is International Goodwill Station O.T.C., P.O. Box 505, Leopoldville, Belgian Congo."

The Belgian Congo (*Congo Belge*) has an area of 902,082 square miles, and the 1942 population was 10,383,929. The Congo Free State had its origin in the vision of King Leopold II of Belgium, who, roused by Stanley's discoveries in Africa, realized the great economic possibilities in the development of the vast territory reached by the Congo. The International Association of the Congo, which he founded and largely financed, sent Stanley back (1879). He founded the first station, VIVI, in February 1880 and, in all, twenty-four before he returned in 1884. The territory was formally ceded to Belgium by treaty in 1908.

The average mean temperature is 80.6 F. but only 70 degrees in the high country constituting the rim of the Congo Basin, and the average rainfall is 43.27 inches. The native religion is gross fetishism, but there are 3,117 Catholic and 835 Protestant missionaries (1946) in the country. About one-quarter of the native population has been Christianized. Leopoldville, of course, is the capital city.

Vast, sunless, and well-nigh impenetrable tropical forests fill the upper reaches of the Congo River, covering about 25,000 square miles. Principal products of the Congo are palm-oil, (Continued on page 103)

Short-wave listener C. F. Bachman of Reading, Pennsylvania, believes that with patience and perseverance, real DX can be heard on comparatively simple equipment. Using a Hallicrafters S-20R receiver, and a ten-foot antenna, single-wire, running north and south, he has had verifications from Chungking, Radio SEAC, Radio Saigon, Radio Australia, All India Radio, and Honolulu, along with many others.



Modern Television Receivers

By
MILTON S. KIVER



The Motorola Model VT-71. This receiver is only one of the many commercial types available designed around Intercarrier system.

Part 15. Additional notes on Intercarrier television systems, including advantages and disadvantages

THE Motorola Model VT-71 was one of the first Intercarrier receivers to appear commercially. The circuit contains several unusual features which merit special attention, aside from its operation as an Intercarrier television sound receiver. The set, Fig. 1, is provided with an 8-position station selector switch. Thus, although there are 12 television channels, the allocation is such that no more than 7 will normally be available in any one locality. This receiver can be aligned for the reception of any 8 stations.

The front-end section of the receiver consists of a 6AG5 r.f. amplifier, one-half of a 12AT7 as an r.f. oscillator and the other half as the mixer. The input terminals are so arranged as to provide input impedances of 75 ohms and 300 ohms. The 300 ohm terminals connect to each end of a center-tapped coil, whereas the 75 ohm terminals connect to one end and the coil center tap. The reason for this stems from the fact that the inductance of a coil varies as the square of the number of turns. Thus, a coil possessing twice as many turns as another coil has four times the inductance and, at the same frequency, four times the impedance. Since 300 is four times 75, the arrangement shown in Fig. 1 can be employed.

The incoming signals are transferred from the antenna terminals to

the tuned grid circuit of the 6AG5 r.f. amplifier through an antenna coupling line. In the grid circuit, coil L_1 is for channel 2 or 3, L_2 is for channel 4, L_3 is for channel 5, and L_4 is for channel 6. In any one locality, L_1 would be tuned to the channel (either 2 or 3) which was occupied. Only one of these can be allocated in any one locality. These coils are selected by switch S_{1A} and transferred to switch S_{1B} where the coils for the upper channels are located. While any one of the channels from 2 to 6 are in use, the energy passes through the high band coils (L_1 to L_4) all of which are connected in series. For the high band (channels 7 to 13), coil L_5 tunes to channel 7, L_6 to channel 8 or 9, L_7 to channel 10 or 11, and the remaining inductance in the circuit tunes to channel 12 or 13 when the wafer switch S_{1B} is switched to its final position. A separate coil is not shown for this position because actually only a small length of straight wire is used. For channels 7 to 13, the "Q" of the circuit is 6 and the bandwidth is of the order of 15-25 mc. The bandwidth being so great, no special core tuning is necessary, and it becomes readily possible to receive two adjacent channels at each switch position. Since adjacent channels in the upper television band are not assigned in the same community, this arrangement is satisfactory. Each coil of switch S_{1A} and S_{1B} is tuned to the

video carrier of its channel, while the corresponding coil of switch S_{1C} and S_{1D} is tuned to the audio carrier of the channel. This produces a flat-topped input response of the proper bandwidth. The oscillator tube, in conjunction with the coils of switch S_{1A} and S_{1B} , provides the proper oscillator frequencies to produce the intermediate frequency. (Because of the wide bandwidth on the upper channels, it is only the setting of the local oscillator frequency which determines the station to be received.)

Before we progress any further, it should be pointed out that the output of the power supply in this receiver is divided into two sections. One section is connected between "B—" and half the total available power supply voltage. In the diagram this positive point is known as "B+." The other section is connected between the "B+" and a higher positive voltage labeled "B++." "B+" is approximately at 125 volts with respect to chassis ground and "B++" is approximately at 250 volts. Thus we have what amounts to a three-wire system, with some sections of the receiver connected between "B+" and "B—," others between "B+" and "B++," and still others between "B++" and "B—." For those stages that are connected between "B++" and "B+," the "B+" point may be considered as being equivalent to ground and the "B++" as being lowered to 125 volts. Thus, in the diagram, if the plate receives "B++" voltage, then the grid and cathode would connect to "B+." This explains why the r.f. amplifier plate connects to "B++" and its grid

Fig. 1. A partial schematic of the Motorola VT-71 receiver.

A second unusual feature of this system is the manner in which the automatic gain control network is tied in with the contrast control, R_1 . The contrast control network, Fig. 3, consists of R_2 , potentiometer R_3 , and resistor R_4 , all connected in series from the high-voltage side of the detector load resistor R_4 to the grid of the clipper tube. The contrast control R_1 has its movable contact connected through R_5 to the grid of V_4 . A condenser, C_1 , bypasses r.f. currents so that the a.g.c. circuit is not affected thereby.

One lead going to the contrast control comes from the high voltage side of the video detector. The voltage developed across the detector load resistor depends upon the signal strength and the type of image being transmitted at that particular moment. This voltage is always negative (in this circuit) and varies from a large negative value for a solid black picture to a small negative voltage on a solid white picture. The other side of the contrast control connects to the grid of the clipper tube. Now, the voltage at the grid of the clipper tube is always negative, and its amplitude is determined only by the peak value of the sync pulses. This is so because sufficient grid-leak bias is developed at this tube to prevent plate current from flowing except at the peaks of the sync pulses. This grid-leak bias is about ten times as large as the video detector voltage. Resistors R_1 , R_2 , and the contrast control form a voltage divider network, with each of the foregoing voltages having some effect on the voltage at any point along the divider. In actual practice the diode load voltage will have an average value of 1 to 1½ volts and the clipper grid will be held at an average value of from 10 to 18 volts. Since the voltage developed at the clipper grid depends upon the tips of the sync pulses and these, in turn, depend upon the amplitude of the incoming signal, the voltage developed at the clipper grid will serve nicely as an a.g.c. voltage. This a.g.c. voltage is fed to the grid of V_1 and controls the gain of this tube and V_2 .

It may be wondered why the contrast control does not receive all of its a.g.c. voltage from the grid of the clipper tube since this is 10 times greater than the voltage the contrast control receives from the video detector. The reason is this: If the end of the contrast control now connected to the video detector were grounded, then it may happen that, in switching from a weak to a powerful station, the grid of the 6AU6 video amplifier will block due to the particular combination of time constants found in the grid circuit of this tube. Prior to the switching, the set is operating at full gain, due to the weak signal, and after switching, a powerful signal may readily overload the video amplifier before the a.g.c. voltage has had a chance to increase. As a result of the video amplifier blocking, the picture will momentarily disappear from the screen, the set will lose sync control and the negative voltage at the grid of the clipper tube will decrease to zero, permitting the i.f. amplifiers to continue operating at full gain. This will tend to further aggravate the situation. To guard against this occurring, the negative video detector voltage is fed to the other end of the a.g.c. network. Now, if a powerful signal should suddenly reach the set the average negative voltage at the detector will instantly rise, reducing the gain of the i.f. system and preventing overload of the video amplifier.

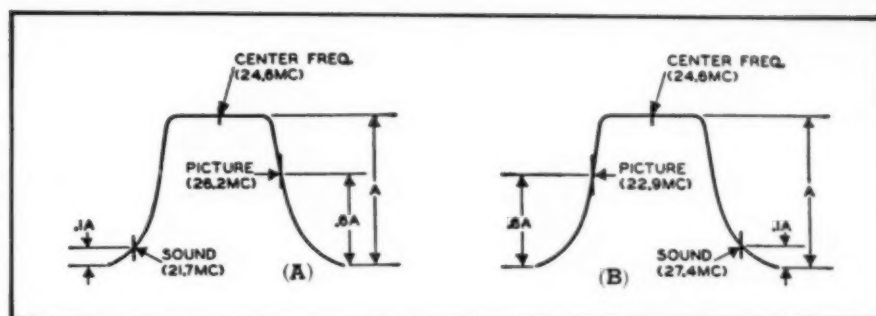


Fig. 2. (A) Over-all response curve of mixer transformer and i.f. amplifiers for channels two to six. (B) Over-all response curve of mixer transformer and i.f. amplifiers for television channels seven to thirteen.

CHANNEL NUMBER	CHANNEL FREQUENCY	CARRIER PICTURE FREQ.	SOUND CARRIER FREQ.	RECEIVER R.F. OSC. FREQUENCY
2	54-60	55.25	59.75	81.45
3	60-66	61.25	65.75	87.45
4	66-72	67.25	71.75	93.45
5	76-82	77.25	81.75	103.45
6	82-88	83.25	87.75	109.45
7	174-180	175.25	179.75	152.35
8	180-186	181.25	185.75	158.35
9	186-192	187.25	191.75	164.35
10	192-198	193.25	197.75	170.35
11	198-204	199.25	203.75	176.35
12	204-210	205.25	209.75	182.35
13	210-216	211.25	215.75	188.35

Table 1. Signal and local oscillator frequencies for each television channel.


Thus we see that while the voltage fed into the a.g.c. system from the video detector is ordinarily unimportant, it does become important if the video frequency amplifier should become blocked by a sudden rise in the signal voltage.

The video detector uses a 1N34 germanium crystal as its rectifier. The crystal also functions as a converter, providing the 4.5 mc. difference frequency which contains the audio in-


telligence. A low pass filter is included to prevent i.f. voltages from reaching the amplifier.

The signal output of the detector is fed to a video-frequency amplifier which is designed to function, too, as a partial limiter tube. The output of the video detector is in the negative direction and noise peaks drive the video amplifier beyond cut-off, thus being clipped. The 4.5 mc. beat note
(Continued on page 84)

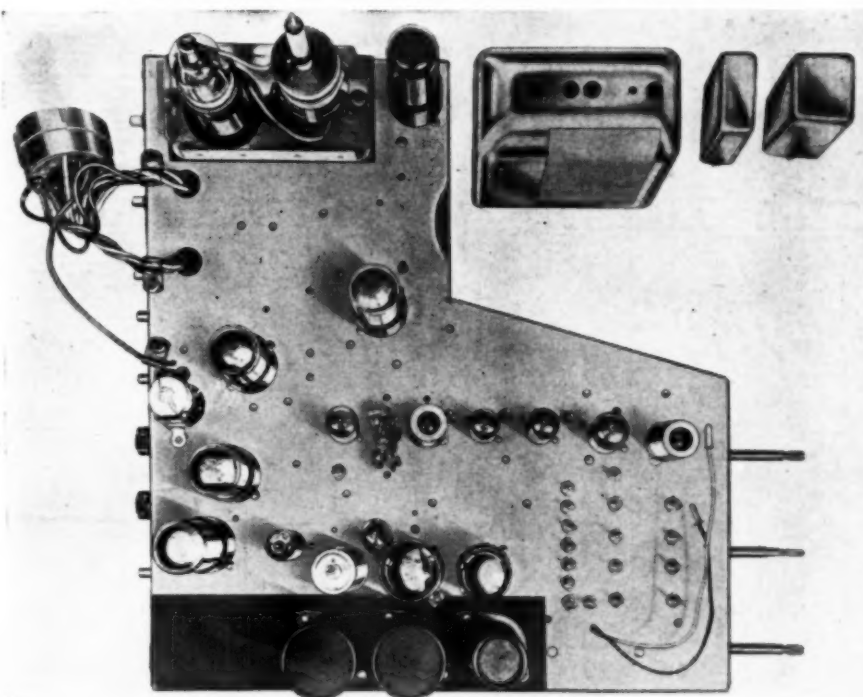Top chassis view of the Motorola VT-71 Inter-carrier Television receiver.



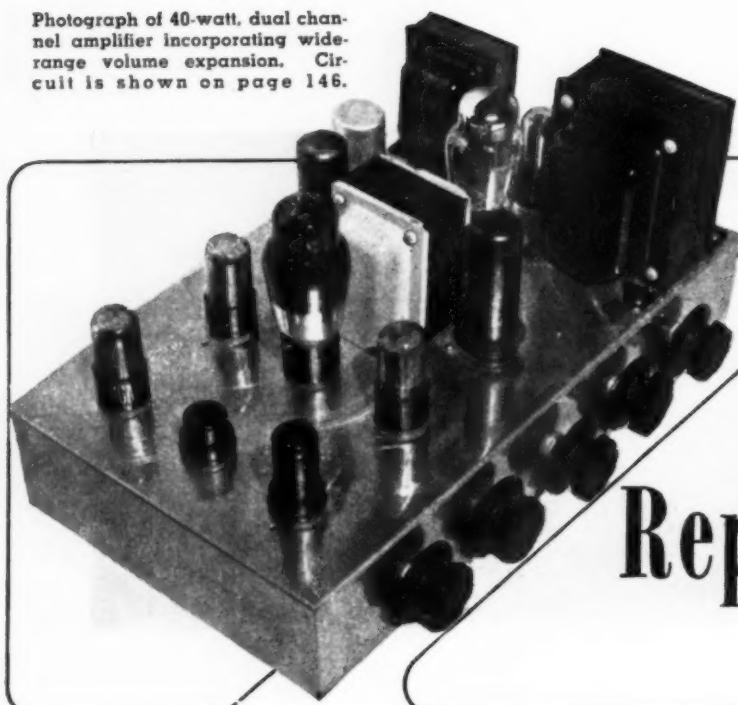Photograph of 40-watt, dual channel amplifier incorporating wide-range volume expansion. Circuit is shown on page 146.



A Three-Dimensional Reproducer System

By MICHAEL WOLFE

By adding volume expansion-compression and dual channel operation, you can attain greater "depth" in your audio.

ALTHOUGH the binaural nature of sound is seldom mentioned in discussions of high fidelity, it offers an important and fascinating field of experimentation to the audio enthusiast.

Binaural perception means the ability to perceive the direction from which a sound is coming. A few moments' reflection is enough to estab-

lish how unnatural it is to have a wide variety of sounds, such as those produced by a ninety-piece orchestra, issue from a fixed source of perhaps twelve inches in diameter.

Ideally, a separate channel of reproduction would be used for each instrument with a multiplicity of loudspeakers spread about in proper locations, though in common practice two or


three channels are sufficient to give very excellent reproduction.

Commercially, binaural transmission and recording has been almost ignored due to the greatly increased cost of multiple channel operation, but recently, systems have been developed to achieve a very interesting effect of binaural reproduction from conventional single channel sources.

As far back as 1930, it was suggested that greater naturalness might be achieved from ordinary transmissions by placing a loudspeaker on either side of the room, with the low notes fed to one speaker and the highs to the other. In orchestral music, this would tend to separate the string basses, kettledrums, and other low-register instruments from the high-register instruments, such as flutes, piccolos, and triangles. An arrangement of this nature is quite easy to construct and operate. A dual channel amplifier like the one described later is recommended for flexibility and ease of control, and for the most desirable results the operating ranges of the two channels should overlap to a certain degree to prevent sudden discontinuities.

As human ears can tell the direction of a sound by measuring the relative phase difference between the vibrations striking each ear, a somewhat similar system may be built by the deliberate introduction of phase distortion into two amplifier-speaker systems. A thousand-cycle note coming from a right angle will represent a phase difference to the two ears of nearly 180 degrees and zero degrees difference when coming from straight ahead. With sound coming at an angle, the phase difference at low frequencies is very small but increases with an increase in frequency.

Fig. 1. Diagram of three-tube volume expander (A) and a wide-range compressor (B).

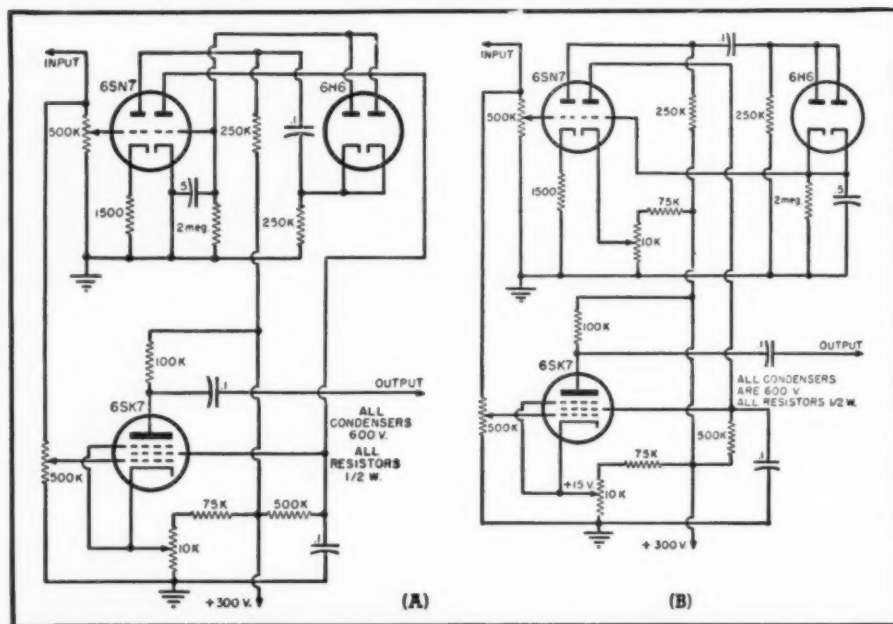

By making use of this effect, results are obtainable that can be achieved in almost no other way. If two amplifiers are used having similar frequency characteristics but different phase shift characteristics, and the outputs are applied to identical speakers placed on either side of the room, acoustic images are formed at various frequencies, giving the effect of a large number of reproducers around the room. A variable phasing control was included in an experimental set-up, with the result that it was possible to change the apparent position of the string section of an orchestra over a distance of ten feet. When the phase shift is relatively great over a narrow frequency range, the very unusual effect of a rapidly moving sound source is obtained during orchestral passages where a particular instrument falls within this range.

Although ideal from several standpoints, this system has the drawback that careful attention must be paid to controlling the phase shifts, not only in the amplifier and associated apparatus, but in the speakers and room acoustics as well. Wall reflections may generate large amounts of phase distortion, making the problem one of designing a system for a particular speaker and listener location, and for this reason no detailed circuits will be given here.

A third effective system for achieving binaural reproduction makes use of the dynamic characteristics of music — automatically distributing sound to various portions of the room in accordance with the energy or frequency content.

This system rests on the use of volume compressors and expanders capable of ratios of more than twenty to one with relatively low distortion. Two amplifiers are employed in the simplest form: a small, low-powered amplifier, to carry the quiet passages, and a higher power amplifier fed through a volume expander that comes into operation during the high level passages and feeds a speaker placed on the opposite side of the room. During quiet passages usually only one or a few instruments will be playing, and they will appear to come from one side of the room. As the volume level increases the other amplifier will operate, giving the effect of other instruments joining in from the opposite side of the room. If desired, a compressor may be used to cut out the first amplifier altogether at high volume levels. Using these basic elements a great number of variations are possible. The frequency range of the low power amplifier may be limited to cut off scratch and turntable rumble providing dynamic noise suppression, and other forms of dynamic frequency variation may be achieved through the use of tone networks on the two amplifiers. Special gating systems may be used to operate separate amplifiers when only high frequencies, low frequencies, or a combination are present.

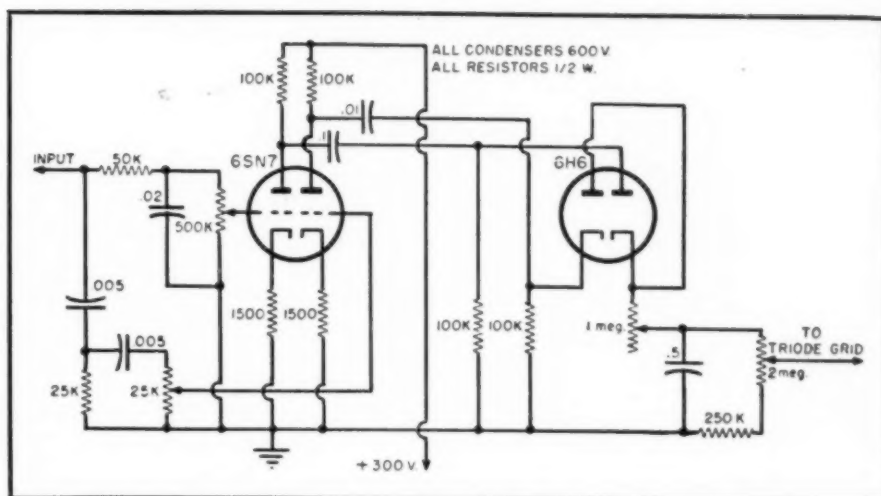


Fig. 2. Diagram of frequency discriminator system to be used in conjunction with an expander or compressor. Circuit can be used to expand highs or compress lows. Low-frequency expansion or high-frequency compression may be achieved by reversing the two diode sections. Unit also features variable attack and release controls.

The compressor-expander circuits used differ from conventional types in that the control signal is applied to the screen grid of a variable mu pentode. This has the advantage that relatively low filtering of the signal voltage is needed and the fact that the expander circuit cannot be overdriven by the control voltage. The operation of either circuit is effected by varying the plate resistance of a low mu triode, the plate of which is connected to the screen grid of a variable mu pentode. An appropriate d.c. voltage is applied to the grid of the triode, changing its effective plate resistance which, through a voltage divider action, changes the screen voltage of the pentode, consequently changing the transconductance.


Distortion introduced by this circuit is desirably low and consists almost entirely of second harmonic distortion that can be eliminated through using two pentodes in push-pull if desired. For single ended operation, distortion is greatest at maximum compression,

and measurements showed that eight per-cent second harmonic distortion could be expected at a compression ratio of twenty to one, with a one-half-volt input to the grid of the 6SK7. Halving either the compression or the input voltage will halve the distortion. In practice, the circuit functions smoothly from inaudibility to full power output.


The time constants of the compressor-expander circuits will generally represent a compromise of several factors. If the time constants are small, the switching action may be unpleasantly jerky. If the time constants are large, a smooth switching results, but sharp dynamic effects may suffer. In the system presently used by the author a time delay of about one-half second is used. On percussive passages this gives the effect of two sets of instruments, with one set taking the first beat and the other set finishing the passage.

Schematics of the compressor and
(Continued on page 146)

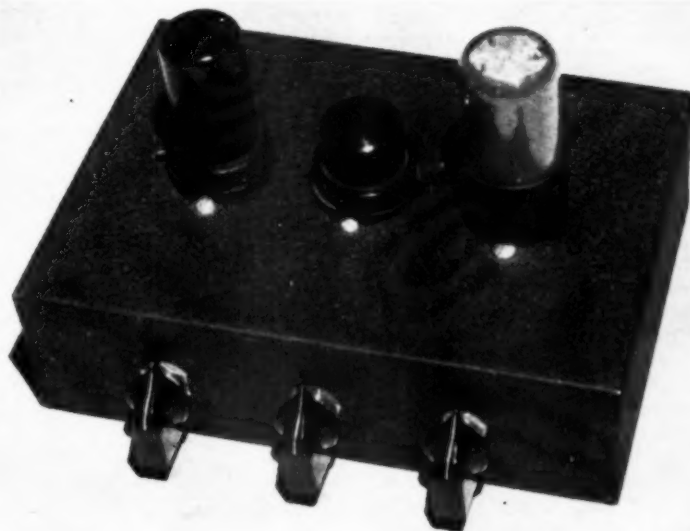Photograph of a compact expander unit that may be used with existing equipment.



AUDIO TRANSIENT DISTORTION

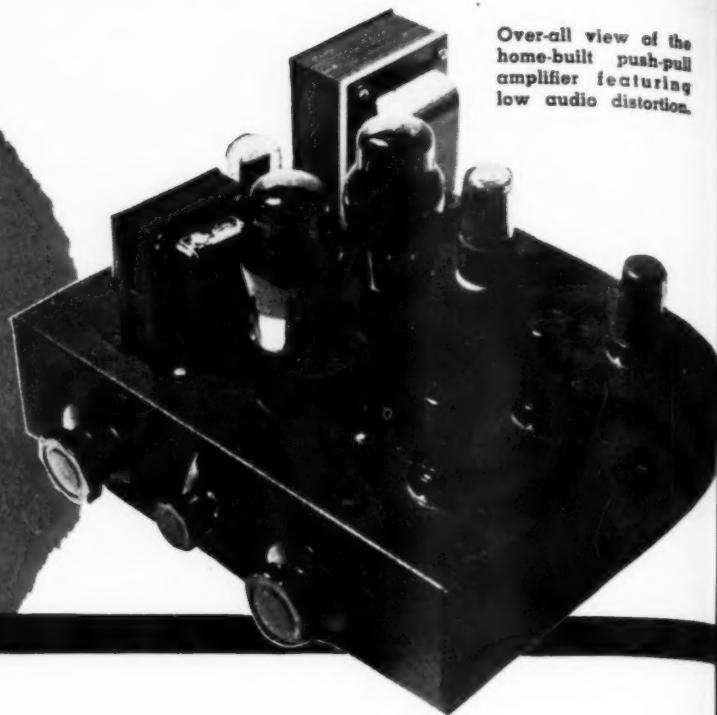

Over-all view of the home-built push-pull amplifier featuring low audio distortion.

By
GLEN SOUTHWORTH

A loudspeaker correction system is incorporated in a novel amplifier that has good transient response.*

GOOD transient response is important, not only in equipment designed for high-quality musical reproduction, but as a factor to be seriously considered by the radio amateur, communications man, and public address operator. In the case of musical reproduction, good transient response means the ability to respond readily to complex wave patterns with low distortion and the corresponding ability to reproduce complicated instrumental passages clearly with a minimum of spurious tones generated by the equipment itself, while in communications or public address work, the operator will find himself repaid with higher intelligibility by paying careful attention to the design of his audio system.

Although serious transient distortions may occur in almost any part of audio equipment, the worst distortions usually are discovered in electromechanical devices, such as pickups or speakers, due to the physical inertia of these devices. A considerable amount of material on various types of pickups has been generally available in recent years, including both commercial and home constructed types; however, there are several factors worth noting. A number of excellent pickups on the market today are capable of wide-range, low-distortion output but can cause excessive record wear. Stiff moving elements

and worn or chipped needles are usually the worst offenders and may cause a great deal of noise and distortion on loud passages or certain tones due to the needle's digging into the side of the record groove; surface noise or scratch will often be greatly increased on the playback by a defective needle, due to the lessened damping effect of the groove. For these reasons, many people have in the past preferred to use cactus or soft steel needles, even in connection with wide-range equipment. However, the present trend in pickup manufacture is toward lightweight pickups with high needle compliance, thus combining low distortion and record wear with wide-range reproduction. Transient distortions in pickups usually occur in the upper audio ranges and may often be detected by using a sweep frequency record in connection with an oscilloscope, as this approximates the interrupted tone technique described in the preceding article.

For several reasons, little detailed information is generally available on the subject of loudspeakers, but the effects of various types of speaker baffles and enclosures are quite well known, and a considerable amount of excellent material has been published

* The author presents herein a practical construction type article based on his theoretical analysis of audio transient distortion presented in the April, 1949, issue of *RADIO & TELEVISION NEWS*.

on this subject. The fact that loudspeaker performance may be greatly influenced by the type of amplifier used with it is also quite well known, but considerable controversy has existed on this subject in recent years.

A loudspeaker may be considered a motor-generator having one or more resonant elements. These resonant elements will not only cause an increase of sound pressure at certain frequencies but will continue to oscillate after the exciting impulse has ceased. If resistance is inserted into a resonant circuit, the "Q" of the circuit will be lowered, these oscillations will die out more rapidly, and the sound pressure variations will not be so great. This resistance may be mechanical in nature, due to the speaker construction, or acoustic resistance, obtained by proper loading of the speaker by the associated enclosure. A third method relies on the fact that the speaker acts as a generator and produces a back e.m.f. When this voltage is developed across a relatively low impedance, such as provided by a triode output amplifier, a considerable braking effect may take place with consequent damping of speaker oscillations. It is important to note, however, that this braking effect will be dependent upon the loudspeaker efficiency, and for good results, speakers with very heavy magnetic fields and capable of attaining efficiencies three or four times that of common speakers may be used in high-quality installations. The apparent low-impedance output of triodes may be achieved by multi-element tubes in several ways. The simplest of these is to place a high-wattage resistor of low value in parallel with the speaker voice coil. A more common method is to use fairly large amounts of inverse feedback over the output stage of the

amplifier. This system has the disadvantage that the voltage reflected by the speaker will be in-phase at only two points in the frequency range. Fortunately, one of these points is the primary resonant frequency and relatively good damping can be achieved at this point. In the high frequency ranges, however, the voltage developed by the speaker may be greatly out-of-phase with the amplifier output and lead to dynamic instability in some instances.

The importance of inverse feedback has long been recognized in dealing with electrical distortions, and with proper care it can be used to reduce mechanical distortions occurring in conventional loudspeakers. Advantage may be taken of the fact that the speaker acts as a generator as well as a motor. In this case, an electrical replica of the physical vibration of the loudspeaker will appear at the amplifier output and may be fed back into the amplifier to provide electrical compensation for speaker defects. In doing this, two problems must be overcome. First, the voltage developed by a speaker of ordinary efficiency will be only a small fraction of the amplifier output, and a means must be found of separating this small voltage, or excessively heavy feedback with its attendant problems will be required. Second, the voltage developed by the speaker will vary greatly in phase over the audio range and high-frequency phase correction should be used in the feedback loop. A simple solution to these problems is shown in the circuit illustrated in Fig. 1. A bridge circuit is used to balance out most of the voltage developed by the amplifier, leaving the out-of-phase voltage developed across the loudspeaker, plus any voltages that may be developed by impedance variations of the speaker. The output of the bridge is then passed through a simple phase shifting network and applied to one of the amplifier voltage stages. In most conventional, single radiator speakers, phase shift increases in a positive direction with ascending frequency, and resistance capacitance phase-shifting systems may be used with little difficulty.

The results attainable with speaker compensation of this nature are very good indeed, performance of conventional twelve-inch speakers being comparable with expensive, two-way speaker systems using horn loading. Although use of large diameter radiators for reproducing high frequencies is unconventional in high-quality sound systems, excellent results were achieved by the author, with high-intensity, wide-range reproduction being obtained from a single speaker with a minimum of distortion. Musical reproduction with high-frequency intensity at levels of near physical sensation have been experienced for periods up to six hours, with a minimum of listening fatigue. Excellent reproduction of instruments with sharp transients, such as piano, kettledrums, chimes, cymbals, etc., is achieved.

This circuit has been tested with a variety of different amplifiers and speakers with marked improvement in every case, but for best results it is recommended that the constructor get a speaker with reasonably good performance to start with and preferably with as heavy a field or magnet as possible. A speaker of high efficiency will permit more effective adjustment of the feedback loop. Although this system has been designed primarily for use with a single speaker, excellent results may be achieved by using two speakers in series. Of course they should be of proper phasing and, if of different manufacture, should be tried in different connections for best results.

The circuit of a low-powered amplifier using bridge type feedback is shown in Fig. 2. This circuit incorporates several interesting features such as a variable feedback and phasing control and provision for triode or beam power output tubes. This circuit makes a decided improvement in reproduction when using either triodes or multi-element tubes, and with full feedback the difference in operation is unnoticeable. However, in some instances it may be desirable to provide a moderate amount of "hangover" in

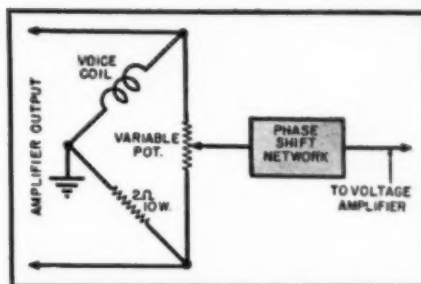



Fig. 1. Diagram of basic bridge circuit that may be incorporated in existing equipment. Care should be taken to maintain the proper phase relations throughout the circuit.

the bass frequencies in order to achieve an effect of live acoustics, or to soften hard tones or a number of other effects; the high resistance output tubes, such as 6L6's, make a wider range of control possible and provide extra power output.

Several factors should be noted in connection with the feedback loop. First, the polarity of the amplifier output must be correct, and the out-of-phase voltage should appear across the side of the bridge containing the loud speaker. Second, in designing a feedback loop, the constructor may have

(Continued on page 92)

Fig. 2. Diagram of amplifier using bridge-type feedback with provision for variable feedback control and triode or beam power output tubes. The 6B4 or 6L6 power tubes are interchangeable. The same pin connections on the tube sockets can be used. The screen and cathode connections are left floating, with 6B4 operation.

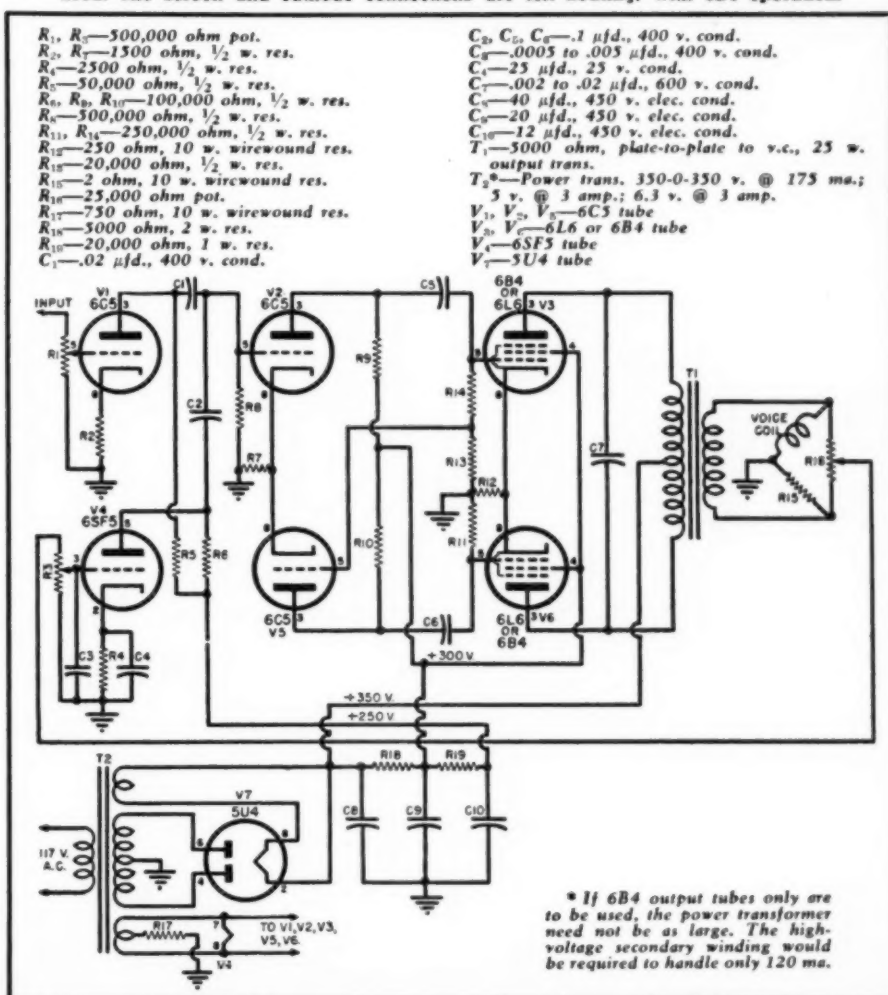

A Simple *Television* TUNER

By J. T. GOODE

Television receivers that cover only the low frequency band need not be obsoleted. Add this low cost tuner to your present set and obtain 5-channel coverage—two high band and three low band, or your choice.

MANY of the early television kits covered only the low band with the result that their owners have only limited reception. The tuner described here will enable these owners to add the high band to these sets, making a total coverage of five channels. The details of construction will vary with the particular set being altered, but every effort should be made to keep all leads as short as possible.

The tuner described will permit your present receiver to tune to two of the high band channels and three of the low band. With the necessary alterations on the coils specified, it is possible to place any of the five channels in either the high or low band as desired, or any desired combination.

To alter the coils, some experimenting will be necessary to determine the proper number of turns. Due to the frequencies involved, with the attendant importance of lead lengths and parts placement, it is not possible to give the specifications for these different coils.

The tuner is designed to replace the present tuner in sets covering only the low-frequency channels. The old tuner and its associated parts should be removed and replaced with this new unit. If your television receiver will now tune all twelve channels, the author does not recommend building this to replace the one now in service. Although this tuner may in some respects operate more satisfactorily than your present one, the difference will be in the order of a few db. that may not be noticed in actual operation.

The circuit of this tuner is extremely simple. It consists of a 7F8 dual triode using one-half for the oscillator and the other half as a mixer. The antenna is fed into the grid of the mixer. The plate of the mixer feeds into your present i.f. channel.

This television tuner requires a minimum of parts and is comparatively simple to construct. The use of a signal generator to adjust the coils will simplify the problem, but if a generator is not available the coils can be adjusted on a received signal.

The antenna input circuit consists of condenser C_1 and load resistor R_1 . Con-

denser C_1 feeds the antenna circuit to the grid of the mixer stage. The mixer grid circuit consists of a series coil arrangement, whereby L_1 is attached to number one contact on the switch and fed to the grid through coupling condenser C_2 . This condenser breaks the d.c. path allowing injection voltage to develop across grid resistor R_2 . Condenser C_3 couples the oscillator to the mixer grid.

The arm of the switch connects to ground. When the switch is in number one position, only one coil will be in the circuit and this will be tuned to the highest frequency channel. The first and second contacts are tied together with number 20 wire. This will set the inductance for the next high-frequency channel. Three low-frequency channels are covered by L_3 , L_4 , & L_5 . The plate of the mixer connects to the primary of the first i.f. transformer. Condenser C_4 is the oscillator grid condenser, and resistor R_3 is the grid leak. R_4 is the oscillator plate filter resistor.

A Colpitts oscillator circuit is used. Normal Colpitts construction consists of a split stator condenser shunting the oscillator inductance with the rotor going to ground, forming a capacity center tap. The capacity center tap of this circuit is formed by condensers C_5 , C_6 , and C_7 .

Condenser C_8 is a 5 μ fd. variable condenser which is used for the oscillator and is available from the front panel. By connecting C_8 in series with this capacity, a rather long lead can run between the bandswitch and the oscillator condenser which must be on the front panel without upsetting the oscillator coils. By using the leads attached to C_8 a span of two or three

inches can be tolerated. L_6 and L_7 are the high-frequency oscillator coils. L_8 , L_9 , and L_{10} are the low-frequency coils.

The lowest frequency oscillator coil is shunted by condensers C_9 , C_{10} , and C_{11} . These condensers were added to this low-frequency channel to reduce the number of turns in L_{10} . A coil with more than twenty turns presents a mounting problem on the band switch.

Coil Construction

L_1 . Three turns of number 20 copper tinned wire with an i.d. of 3/16ths, spacing between turns 1/16th.

L_2 . Short switch contacts with number 20 wire.

L_3 . Seven turns of number 24 silk enamel wire close-wound.

L_4 . Five turns of number 20 copper wire spaced 1/32.

L_5 . Five turns of number 20 copper wire spaced 1/32.

L_6 . Two turns of number 16 copper wire spacing 1/16th.

L_7 . Three turns of number 16 copper wire spacing 1/16th.

L_8 . Thirteen turns of number 24 silk enamel closewound.

L_9 . Twenty turns of number 24 silk enamel closewound.

L_{10} . Twenty turns of number 24 silk enamel closewound.

All coils with the exception of L_1 are 1/4 inch i.d. The coils are wound on a 1/4 inch rod and then slipped off the form. The closewound coils should be dipped in coil dope and allowed to dry before mounting.

The bandswitch is a standard two-deck, four-pole five-position switch. One section is not used. Notice when the switch is rotated to one extreme the amount of inductance in the switch arm is minimum. When rotated to the

other extreme the arm inductance is maximum. Number one contact will be the contact nearest the arm contact. The mounting of the mixer coils is shown in Fig. 1.

Connecting the coils to the switch in this manner is important. L_6 has only two turns of wire. Connecting L_6 to number five switch contacts would result in even less wire to hit the highest frequency channel. The oscillator coils are mounted on the back switch deck. One end of the coils connects to one set of contacts and the other end of the coils to the other set of switch contacts. Fig. 2 shows the details of this mounting.

The mixer grid coils also connect directly to the front switch deck. By mounting oscillator coils on both sides of the rear switch deck, adequate space is available. Mount the coils in such a way that they are available for adjustment. The location of the 7F8 tube socket must be close to the channel switch and, if possible, directly under it. This will keep all critical lead lengths to a minimum.

Keep all leads as short as possible. The cathodes of the 7F8 should be grounded right at the socket. The ground lead going to the mixer switch arm should be number 16 wire grounded at the same point as the cathodes. All fixed condensers should be ceramic. Zero temperature coefficient condensers will reduce oscillator drift, and are recommended.

Tuning Procedure

Due to the high frequencies involved, the lead length in wiring will undoubtedly necessitate coil adjustment. The coils described cover channels 2, 4, 5, 9, and 13 in a receiver using the old low-frequency i.f. channels, approximately 12 mc. If your receiver has a high-frequency channel, approximately 25 mc., it will be necessary to reduce the inductance of the oscillator coils slightly. Since the coils must be adjusted this presents no hardship.

First determine the oscillator frequencies required to cover five channels. Add the i.f. frequency to the channel frequency which will give the proper oscillator frequency. This must be done for each channel. Use the center frequency of each channel for this calculation.

Turn on your receiver and proceed to adjust each oscillator coil so that it covers the desired frequency range when condenser C_6 is in center position. This adjustment consists of spreading turns or pushing turns closer together. If the frequency is too low it may be necessary to remove a turn from the coil. On the other hand, if the frequency is too high it will be necessary to wind a new coil with an additional turn.

If a calibrated signal generator is available, the oscillator coil adjustment can be made with very little effort. Connect the generator to the antenna terminals and adjust the oscillator coils to cover the desired frequencies.

(Continued on page 111)


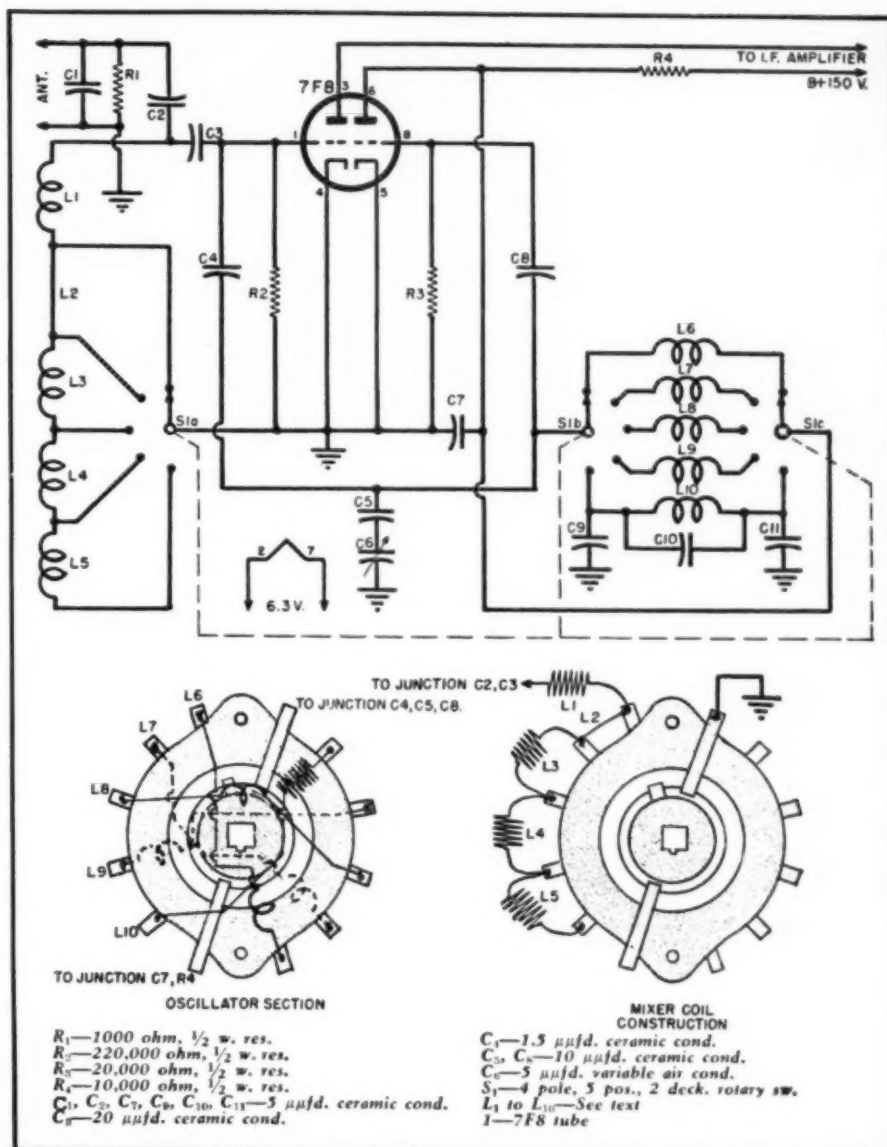


Fig. 1. Schematic diagram of TV tuner. A conventional Colpitts oscillator circuit is used.

Fig. 2. Underchassis view—tube socket is mounted over switch while trimmer condenser is mounted to front panel. It is important to keep all the leads as short as possible.

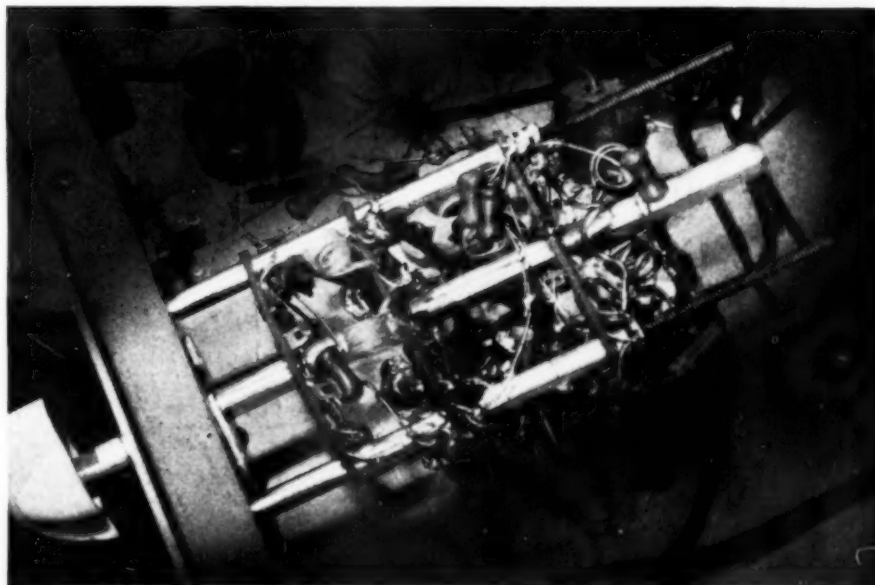

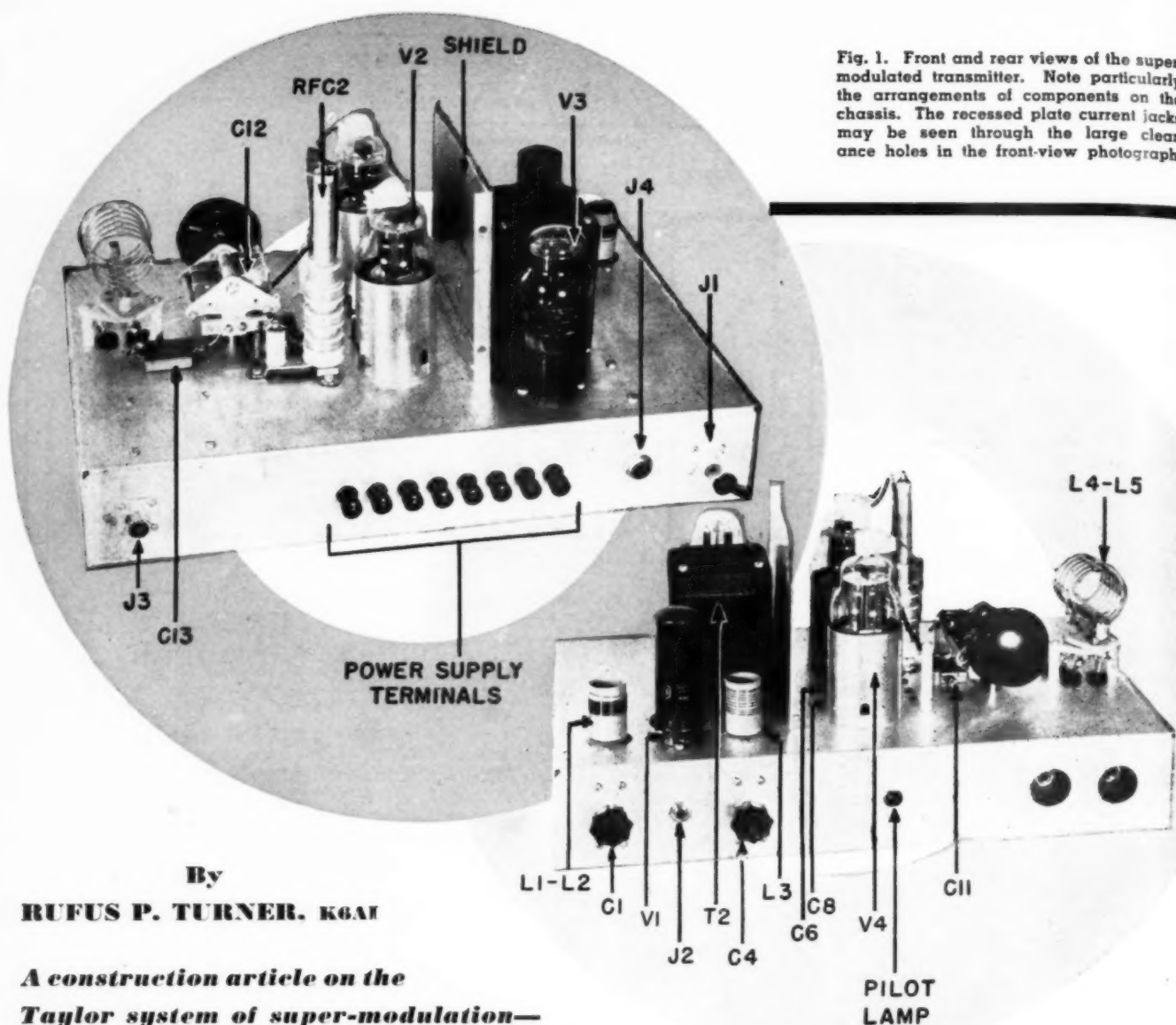


Fig. 1. Front and rear views of the super-modulated transmitter. Note particularly the arrangements of components on the chassis. The recessed plate current jacks may be seen through the large clearance holes in the front-view photograph.

By
RUFUS P. TURNER, K6AT

**A construction article on the
Taylor system of super-modulation—
it has many advantages over conventional rigs.**

THE Taylor system of super-modulation certainly is worth the attention of every ham who wants the best in amplitude modulation but neither cares to run a veritable audio powerhouse to get it, nor put up with the poor efficiency of grid, screen, or cathode modulation.

The patented Taylor system¹ disposes of the high-powered audio stage and its power supply, the costly high-level modulation transformer, and the necessity of impedance matching between modulator and final amplifier. At the same time, this new system affords outstanding advantages which include the following.

(1) The final r.f. amplifier tube may be run at its full c.w. input rating, since the modulation process does not increase the plate input. This permits the fullest use of small tubes which ordinarily are unattractive in AM transmitters.

(2) The carrier is reduced automatically during modulation, reducing heterodyne interference at the receive-

ing location and narrowing bandwidth. At the same time, the side bands are emphasized, yielding a characteristic "punch" which other types of amplitude modulation (all other things being equal) do not exhibit. A super-modulated signal is easily picked out by its surprising loudness and sharp tuning.

(3) During positive modulation, the plate input power to the final amplifier actually is reduced, giving this tube a cooling interval similar to the key-up period in c.w. transmission.

(4) In the Taylor circuit, the modulator is an audio-operated r.f. stage, not the power audio stage of conventional AM modulation. The modulator is triggered into operation by the audio wave to feed additional r.f. energy to the final amplifier tank. This additional energy brings the r.f. output up to the level of positive amplitude modulation. (For example, the

modulator will boost the original carrier to twice its value in 100 per-cent modulation).

(5) Little r.f. and audio exciting power are required. The r.f. excitation is intermediate between c.w. and plate-modulated phone requirements for a given tube.

(6) The final r.f. amplifier and modulator are operated from the same high-voltage power supply, resulting in a considerable saving.

(7) Plate efficiency is the high value obtained heretofore in c.w. and conventional plate modulation.

Considerably more "talk power" is discerned in a signal from a super-modulated transmitter than from conventional AM rigs of the same plate power input. This particular advantage of super-modulation, while beneficial at all power levels, is of special interest to users of low and medium-power transmitters in power-competitive amateur channels.

For a detailed explanation of super-modulation circuit operation, the

¹ The Taylor "Super-Modulation" Principle. R. E. Taylor RADIO & TELEVISION NEWS, September, 1948, p. 42. Part 2 in the October, 1948, issue, page 44.

A SUPER-MODULATED, LOW-POWER PHONE TRANSMITTER

reader is referred to Mr. Taylor's two articles.¹

The super-modulated transmitter described in this article has been developed around type 807 tubes in the r.f. amplifier and modulator, since we believe these tubes are representative of the popular inexpensive, low-powered, low-excitation group. In designing the rig, we have recognized that most amateurs have an external power supply, speech amplifier, and exciter (v.f.o. or crystal) of some kind which may be connected easily to the super-modulated rig. Satisfactory terminals and jacks accordingly have been provided for feeding in low-level audio and r.f. and for connecting the power supplies. If an individual builder chooses, however, he may include the power supplies, one or two additional speech amplifier stages, and an oscillator and one doubler on the same chassis. These additional stages will be entirely conventional.

Description

Fig. 2 is a complete circuit schematic of the super-modulated transmitter. The following paragraphs describe the various portions of the circuit separately.

One of the 807 tubes, V_2 , is the final r.f. amplifier. This tube operates in a conventional manner, except that its grid bias voltage is somewhat higher than ordinarily is used in Class-C operation. The second 807, V_1 , is the modulator tube and its plate is connected across a portion of the tank coil, L_1 .

The r.f. from the 6L6 driver stage is fed to both 807 grids through the capacitance-coupling network consisting of C_6 , C_7 , and C_8 . The grid of V_4 is connected to the midpoint of the capacitive network. The condensers in this network act as a radio-frequency voltage divider. Through voltage divider action, different values of r.f. excitation voltage are applied to each 807 grid. Condensers C_6 and C_8 are made variable so that the operator may select optimum r.f. voltage for each grid. At the correct setting of C_6 and C_8 , r.f. excitation to the amplifier tube, V_2 , will be reduced sufficiently during positive modulation to "knock down" the input of V_2 and accordingly reduce the carrier. Before audio voltage is supplied by the secondary of transformer T_2 , tube V_2 supplies most of the r.f. energy to the final tank, C_{12} - L_4 . Tube V_4 is highly biased and accordingly supplies very little.

The 6L6 r.f. driver stage acts as a straight-through neutralized amplifier


on 80 meters and as a doubler on the two other phone bands, 20 and 10 meters. This stage has sufficient r.f. reserve capability to meet the demands of the super-modulated final amplifier.

From an external low-level exciter unit 80, 40, or 20-meter input is fed into the r.f. input jack, J_1 , to give operation on 80, 20, or 10 meters.

The audio driver stage employs a 6B4-G tube, chosen for its good regulation which is essential in this application. This stage is operated Class-A₁. Low-level audio input voltage is delivered to the 6B4-G through the line-to-grid transformer T_1 , the primary of which is connected to the audio input

jack, *J.*. The primary of *T*₁ may be designed either for a 200 or 500-ohm line. The output transformer in the external speech amplifier must have a secondary impedance of the same value. For most amateur crystal microphones, the external speech amplifier need not be more complicated than a high-gain pentode input stage followed by one or two resistance-coupled triodes. These speech stages may be incorporated into the external exciter or v.f.o. unit to make a compact desk-top control unit. If *T*₁ has a 200-ohm primary, a carbon microphone and battery may be connected directly to Jack *J*₁ to give satisfactory performance.

Fig. 2. Diagram of super-modulated transmitter. A separate power supply is required.

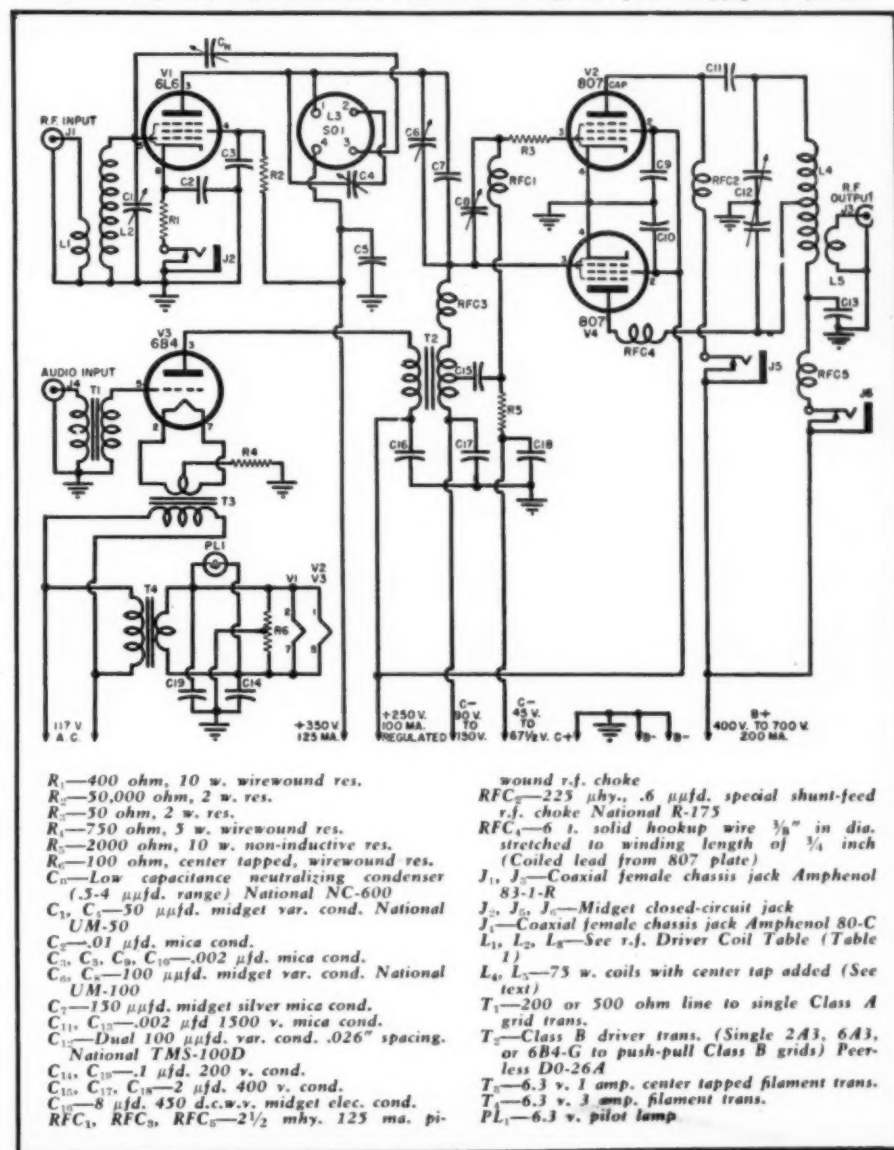

	L_1	L_2	L_3
80 METERS	2 turns No. 20 enamelled wirewound self-supporting around inside of coil form near cold end of L_2 .	50 turns No. 26 enamelled wire on 1"-diameter form. Winding length 1 inch.	50 turns No. 26 enamelled wire on 1"-diameter form. Winding length of 1 inch. Top 25th turn. USE BASE CONNECTION A.
40 METERS	Same as for 80 meter coil.	22 turns No. 24 enamelled wire closewound on 1"-diameter form.	NONE
20 METERS	Same as for 80 meter coil.	12½ turns No. 24 enamelled wire on 1"-diameter form. Winding length of ¾ inch.	12½ turns No. 24 enamelled wire on 1"-diameter form. Winding length of ¾ inch. USE BASE CONNECTION B.
10 METERS	NONE	NONE	5½ turns No. 24 enamelled wire on 1"-diameter form. Winding length of ¾ inch. USE BASE CONNECTION B.

80
METER COIL
(A)

20 & 10
METER COILS
(B)

Table 1. Winding details for all coils covering the 80, 40, 20, and 10-meter bands.

For maximum efficiency, plug-in coils have been employed throughout. The driver coils may be wound according to specifications given in Table 1 (the r.f. Driver Coil Table). The final amplifier coils are manufactured items, except in the case of the 10-meter inductance.

As will be seen from (Table 1), separate grid and plate coils are required in the 6L6 stage. These coils are not interchangeable. Each input coil (L_2) has a link input winding (L_1). The plate coils (L_3) have no link windings. The 80-meter plate coil is center tapped for neutralization. By observing the L_3 base connections given in the coil table, the neutralizing condenser will be disconnected automatically from the circuit, when the 10

and 20-meter coils are plugged in, and "B+" will be connected to bottom of the coil at the same time. For 80-meter operation, plug the 80-meter, L_1 - L_2 coil into the 6L6 grid circuit and the 80-meter, L_3 , coil into the plate circuit. For 20-meter operation, plug the 40-meter, L_1 - L_2 , coil into the 6L6 grid circuit and 20-meter L_3 coil into the plate circuit. For 10-meter operation, plug the 20-meter L_1 - L_2 coil into the 6L6 grid circuit and the 10-meter L_3 coil into the plate circuit.

Mechanical and Electrical Construction

The transmitter (See Figs. 1 and 3) is built on a 17"x11"x3" metal chassis. A 5½"x7" metal baffle shield (Bud No. IS-1246) is mounted between the

amplifier-modulator and r.f. audio driver sections.

The r.f. driver stage is assembled near the left-front edge of the chassis (Fig. 3). The two r.f. coils (L_1 - L_2 and L_3) are wound on 1-inch phenolic forms (National XR-1) which plug into standard 4-prong tube sockets mounted on each side of the 6L6 tube. As will be seen from (Table 1), six of these driver coils are required to cover the 80, 20, and 10-meter bands (two 80's, one 40, two 20's, and one 10). Ceramic-insulated driver tuning condensers, C_1 and C_2 , are recessed behind the front lip of the chassis so as to be as close as possible to the coil sockets.

Driver audio transformer T_1 and the 6B4-G tube are mounted to the rear of the r.f. driver stage. Audio input transformer T_1 is mounted under the chassis between the 6B4-G tube and audio input jack J_4 . The latter is mounted through the rear lip of the chassis.

The two variable r.f. coupling condensers, C_3 and C_4 , are mounted below the chassis with their shafts extending up through wide clearance holes between the two 807 tubes. The shafts are provided with sawed slots for screwdriver adjustment during the initial tuning-up of the rig.


The two 807 tubes are provided with external shields 2½" in diameter and 2¾" high. These shields are necessary for stable operation of the 807's and must not be omitted. The special shunt-feed r.f. choke (National R-175), RFC_1 , is mounted on top of the chassis near the 807 amplifier (V_1) to which it is connected. A portion of the plate lead of the 807 modulator (V_2) is coiled (See RFC_1 in Fig. 2) to provide a parasitic suppressor choke. This coiled lead is visible in the photograph in Fig. 1.

A milliammeter jack (J_1) is connected in series with the 6L6 cathode resistor. This jack may be seen along the front lip of the chassis, in Fig. 1, between the two r.f. driver tuning knobs. Jacks J_5 and J_6 for the r.f. amplifier and modulator plates respectively are mounted on a bakelite sub-panel recessed for safety behind the front lip of the chassis. Large clearance holes (1½" in diameter) permit insertion of the meter plug without danger of contacting the live jacks with the fingers. These clearance holes may be seen on the right-hand front end of the chassis in Fig. 1 (right). The recessed jack panel is visible in the left-hand lower portion of Fig. 3.

Coaxial cable connects r.f. input jack J_1 to the coil socket holding L_1 - L_2 . A similar cable connects the output tank coil link winding, L_3 , to the r.f. output jack, J_3 . A short length of insulated hookup wire covered with shield braid connects the primary of transformer T_1 to the audio input jack, J_4 . The shield braid around this lead, as well as the outer sheath of the two coaxial lines just described, must be

(Continued on page 96)


Fig. 3. Under-chassis view showing components and wiring. Condensers C15, C17, and C18, were removed for this photograph, as they would hide much of the wiring.

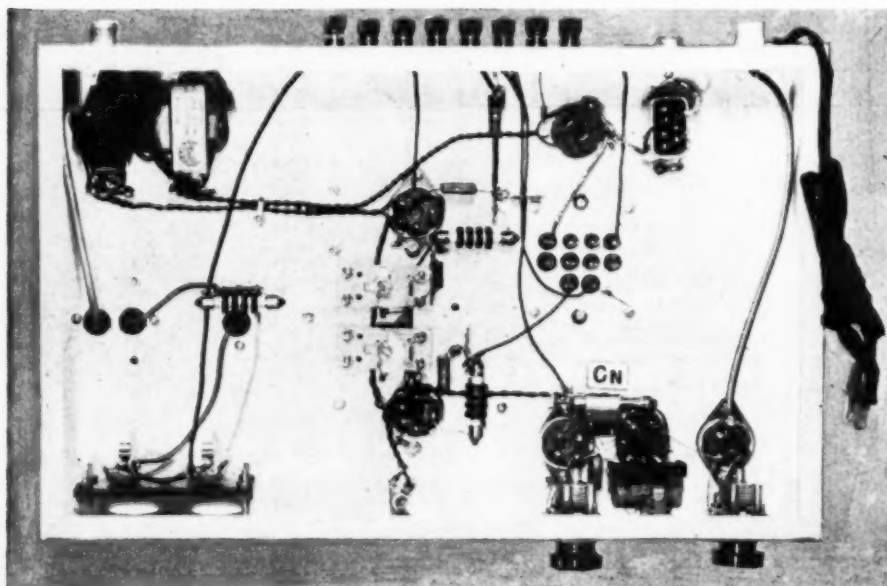

WTMJ's Mobile TELEVISION UNIT



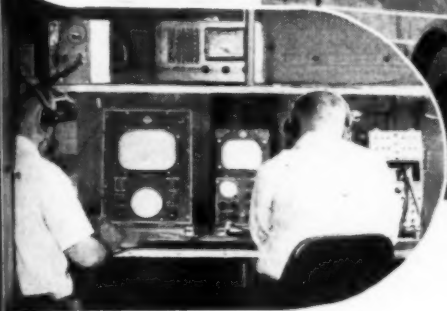Mobile TV truck, costing \$10,000, houses all equipment necessary for remote pickups. (Left) The rear part of the truck is a complete television control room.



Remote pickups are not simple—it takes a crew of five to ten men and two tons of equipment and cable.

By JOHN E. HUBEL

WHEN WTMJ-TV, The Milwaukee Journal station, does a remote broadcast, such as a football game far from studio transmitters, it's a speedy, efficient, though big, operation. During the weeks of trial period before going on the air on December 3, 1947, however, it was a difficult task to get the TV equipment to "location." Several trucks were used to carry the heavy units to the spot, and the programs were put on with all the attendant difficulties of gathering together and loading the TV broadcast facilities.

Now, the WTMJ-TV mobile unit is often a familiar sight; it's on the spot and on the job just as soon as anything worthwhile turns up, no matter how far from the studios. This unit, a Chevrolet truck, was ordered months ago, especially constructed for television by RCA at Boyertown, Pa. It cost \$10,000 and weighs 9500 pounds.

To the weight of the truck, itself, is added about two tons of television equipment when taken out on location. When covering an assignment, one and one-half tons of equipment stay in the truck, and a half-ton of equipment is on cables 1000 feet long, so that it can be moved at will to the place where the pictures are to be taken. The truck has a hole in the

roof on which there is a deck reached by a ladder from inside, and when necessary, television cameras can be moved to the top.

Three portable cameras may be used with this mobile unit. They are assembled before each broadcast and dismounted when it is over. The inside rear of the truck is a complete

television control room, with wide panels of glass installed on three sides to permit broad vision from inside the control room. Television cameras are set up on a table stretching across the room, with three revolving seats provided for WTMJ-TV engineers. Above the table is a shelf for sound equipment, while down in front there is room for the cables to be run to the scene of the pictures.

In the central part of the truck are numerous cabinets to house equipment for amplifying as well as for television equipment not being used for the particular picture in work. There is also space for the microwave transmitter used to send the picture back to the microwave receiver at station WTMJ-TV, and space is also provided for the metering equipment used to measure the amount of electricity consumed.

Before a broadcast, the microwave transmitter must be set up on a roof or some other high point and be lined up with the microwave receiver on the tower of Radio City in Milwaukee on a line-of-sight basis. The sound portion of a television broadcast

(Continued on page 153)

Gordon Thomas of WTMJ-TV does an interview at the Wisconsin State Fair Park.



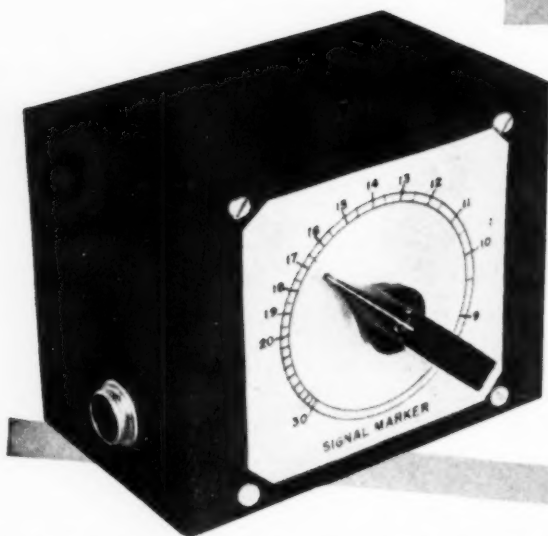


Fig. 1. External view of the completed unit. Coaxial input and output jacks are provided. The frequency dial reads from right to left in this particular unit.

Build This Absorption Type SIGNAL MARKER

By GUY DEXTER

Construction details of a simple tubeless marker device which places frequency-determined "inverted pips" on an oscilloscope alignment pattern. It is ideal for the visual alignment of AM, FM, and television receivers.

VISUAL alignment is an important time-saver in the testing of AM, FM, and television receivers. The response curves reproduced instantaneously on an oscilloscope screen in a visual alignment test would take many minutes of painstaking effort to draw by the slow point-by-point method. A number of excellent articles telling how to use frequency-modulated signals for visual alignment with an oscilloscope have appeared on these pages. For that reason, the techniques will not be reviewed here.

One difficulty of the visual alignment method, often expressed by service technicians who attempted visual alignment of AM receivers, is the inability to distinguish frequencies readily at points along the selectivity patterns. This has been overcome in modern television signal generators by means of self-contained marker devices which produce a frequency-calibrated pip or dip at one or more selected points on the image. However, a number of frequency-modulated signal generators and test oscillators now in use have no such provision.

An auxiliary oscillator is needed to produce an upright pip on the image. Some technicians already have used a separate oscillator for this purpose. As the second oscillator is tuned, the pip moves along the curve, and its frequency position (that is, the frequency it marks) at any point may be determined from the setting of the auxiliary oscillator with respect to the main

oscillator frequency. Thus, the total width of the curve can be measured, or the frequency at any point on the curve can be determined.

An inverted pip—or more precisely, a *dip*—can be produced on the image more simply by means of an absorption circuit (nothing more than a direct-reading wavemeter) connected between the signal generator and the receiver (or stage) under test. The absorption-type marker uses no tubes and accordingly requires no power supply. The latter advantage will recommend this particular device to numerous servicemen bent on improving their present visual alignment equipment.

Any serviceman can build and calibrate an absorption-type signal marker inexpensively. The marker shown in this article cost \$3.50, using all brand-new parts. An inspection of Fig. 4 will show that most of the required components can be retrieved from the junk box. The time required for the construction and calibration should not exceed a couple of hours under the worst conditions.

Signal Marker Specifications

The tuning range of the signal marker shown in the accompanying illustrations is 8.7 to 30 megacycles. This range includes the FM and television intermediate frequencies. Other frequencies may be provided by using other coil-tuning condenser combinations. For example, a 400-to-1000 kc.

range might be more serviceable to the serviceman who concentrates on broadcast receivers with intermediate frequencies of 455, 456, and perhaps 465 kc.

The tuned circuit, which is the heart of the device, is comprised by the tuning condenser C_1 and coil L_1 (See Fig. 4). It will be noted that, except for a ground connection from the condenser rotors, the tuned circuit is inductively coupled to the signal generator output and receiver input. The coupling is rather loose. This arrangement affords somewhat better selectivity than is possible with an absorption circuit simply connected in series with one leg of the signal generator output, and produces a sharper dip on the oscilloscope image.

Since most signal generators now are provided with concentric-line output cables, concentric-type input and output jacks have been included in the marker. Concentric cables between the generator, marker, and receiver insure good shielding and low signal leakage. If *Amphenol* type 80-C connectors (J_1 and J_2 in Fig. 4) are employed, one matching type 80-M plug may be connected to the end of the signal generator output cable, another to the end of the cable from the receiver-circuit input terminals. If no other variety of flexible concentric line is available, regular microphone cable may be employed in this application.

The 8.7-30-mc. coil, L_1 , is wound on a $\frac{1}{2}$ -inch-diameter polystyrene form which, in the interest of short leads, is mounted directly on the frame of the tuning condenser. (See Fig. 5.) The *National* PRD-2 coil form used by the writer has one closed end with a central hole for a 6-32 mounting screw. This type of form is suited to the type of assembly shown in Fig. 5.

A straight-line frequency tuning

condenser should be used, otherwise the dial scale will be too crowded at its high-frequency end to permit accurate reading. The condenser employed by the writer turns counter-clockwise to reduce capacitance. That is why the high frequencies are at the left instead of right-hand end of the scale (See Fig. 1). A condenser with clockwise rotation will give the more conventional left-to-right scale.

The marker unit is built into a 5"x4"x3" metal box (I.C.A. No. 3811). The frequency scale is drawn on a 3½"x3½" card of white Bristol board held to the box by means of thinly spread rubber cement, and covered with a plate of transparent plastic to prevent soiling. The long finger-grip knob (I.C.A. No. 1155) permits close setting without a vernier.

An individual builder may follow any other preferable assembly pattern. The simplicity of the electrical part of the marker gives the builder considerable freedom in the mechanical arrangement. The marker may even be built into a signal generator if there is sufficient room.

Wiring is very simple, as Fig. 4 shows. The only care necessary in construction of the marker is to keep all leads as short as practicable. Scrape the metal sides of the box clean of all paint directly around the jack (J_1 and J_2) mounting holes to insure good electrical contact, and take up the mounting nuts of these jacks tightly. Likewise, clean the paint from around both sides of the mounting hole for the tuning condenser and mount this component tightly. The ground connection shown between the lower end of the tuned circuit and the instrument case in Fig. 4 will be made automatically by mounting the tuning condenser on the metal panel.

Calibration Procedure

After the marker unit has been assembled and its wiring verified, proceed with the frequency calibration as follows:

(1) Connect an amplitude-modulated signal generator or test oscillator, the signal marker, and a receiver capable of tuning from 8 to 30 megacycles, as shown in Fig. 2. Interrupt the a.v.c. in the receiver. It will be helpful to employ an output meter (any rectifier-type a.c. voltmeter connected across the loudspeaker voice coil will be satisfactory); but if one is not available, the speaker signal will serve as a less accurate audible indicator.

(2) Set the signal generator to 8.7 mc. and tune-in the signal on the receiver. Be sure to tune "on-the-nose," as indicated by the exact peak in the receiver output.

(3) Swing the marker tuning condenser to its maximum capacitance setting. As the marker is tuned to 8.7 mc., a reasonably sharp dip should take place in the receiver output, due to the wavetrap action of the marker. If the 8.7 mc. frequency cannot be reached, carefully bend the two outside rotor plates in toward the stators

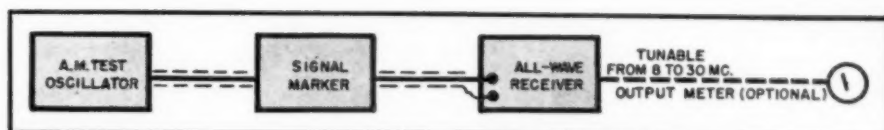


Fig. 2. Block diagram shows arrangement of miscellaneous equipment for calibrating unit.

to increase the high capacitance, until the signal is reached. When a good dip in receiver output is obtained, mark this point 8.7 on the marker dial scale.

(4) Set the signal generator to 9 mc. Tune-in the signal on the receiver and adjust the marker tuning for a sharp dip in the receiver output. Mark this point 9 on the marker dial scale.

(5) Repeat the procedure at 10, 10.5, 11, 11.5, 12, 12.5, 13, 13.5, 14, 14.5, 15, 15.5, 16, 16.5, 17, 17.5, 18, 18.5, 19, 19.5, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, and 30 megacycles. Additional intermediate points may be checked and added to the dial scale, if the operator desires.

Using the Marker

The signal marker unit may be used to identify frequency points on any image whose dimensions are within the marker tuning range. Such images include i.f., r.f., and discriminator response patterns. The marker dip may be "slid" along the curve simply by tuning the marker unit, and the position of the dip (in megacycles) may be read on the marker dial scale.

Typical selectivity images obtained with a frequency-modulated (sweep) signal generator are shown in Fig. 3. In Fig. 3A, the marker dip has been moved to the low-frequency end of the selectivity curve by tuning the marker unit. The frequency represented by this point on the curve may be read directly from the marker dial. Similarly, in Fig. 3B, the dip has been moved to the peak (center-frequency or resonant frequency) of the curve. And in Fig. 3C, the dip has been moved to the high-frequency end of the curve. With this movable dip, the operator can literally put his finger on any point anywhere on the curve and read the frequency of that point directly from the marker dial.

In use, the marker unit is connected


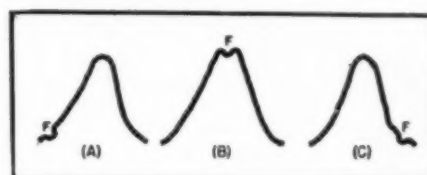


Fig. 3. Illustrating use of marker dip to determine frequencies along a typical visual alignment pattern. See text for details.

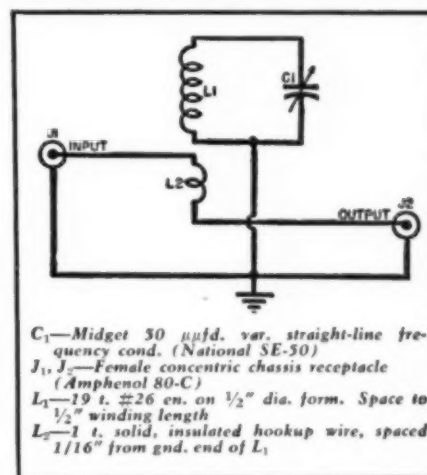

C_1 —Midget 50 μ fd. var. straight-line frequency cond. (National SE-50)
 J_1, J_2 —Female concentric chassis receptacle (Amphenol 80-C)
 L_1 —19 t. ± 26 en. on $\frac{1}{2}$ " dia. form. Space to $\frac{1}{2}$ " winding length
 L_2 —1 t. solid, insulated hookup wire, spaced $\frac{1}{16}$ " from gnd. end of L_1


Fig. 4. Complete circuit of signal marker.

between the frequency-modulated signal generator and the receiver or receiver stage under test. The connections are similar to those shown in Fig. 2.

It is possible to construct a marker unit for frequency coverage other than that afforded by the instrument shown in this article. Either higher or lower frequency bands may be covered by using values of C_1 and L_1 other than are shown in Fig. 4. The 50- μ fd. tuning condenser will be adequate for all frequencies up to about 75 megacycles. At higher frequencies, it will be ad-

(Continued on page 141)

Fig. 5. (Left) Inside view of the home-built marker unit showing simple wiring and the few components required. (Right) A close-up of the tuning assembly. For short leads and simplicity of construction, the coil should be mounted directly on the frame of the tuning condenser, as graphically illustrated.

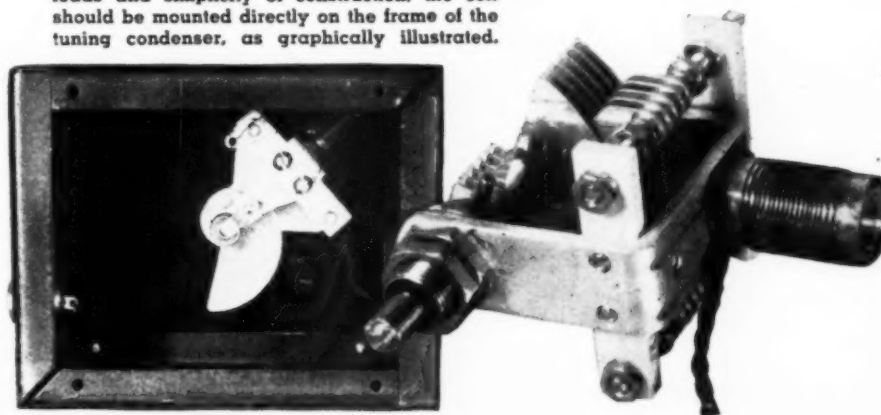

A COMPACT LOW-FREQUENCY BAFFLE

By DONALD FORT

***You don't need any particular woodworking skill
to construct this simple yet effective housing.***

COMMERCIAL baffles with good bass response are usually quite bulky, often occupying from five to ten cubic feet. Such baffles are satisfactory when there is plenty of room, but when space is at a premium a much smaller baffle must be used. It should preferably be small enough to fit within an existing radio-phonograph cabinet, or to set on a shelf where, if necessary, the unbeautiful product of the amateur woodworker can be hidden behind a thin curtain. Such a baffle, occupying less than two cubic feet and giving a smooth bass response down to below 60 c.p.s., is described here. While it compares favorably with much larger conventional bass reflex baffles in frequency range, it is somewhat inferior in efficiency and in maximum power output at low frequencies. It is therefore advocated chiefly for home use, where economy of space is often essential and where only moderate sound levels are necessary. With all its shortcomings, however, it can still give a cheap twelve-inch speaker, driven by a ten-watt amplifier, enough woof to rattle the china.

The baffle combines the features of the acoustic labyrinth and the so-called "infinite" baffle. The usual acoustic labyrinth* consists of a folded absorbent-lined column, one end of which is coupled to the rear of the speaker, the other end being open to provide a release for back pressure. The proposed baffle differs from the usual labyrinth only in that the end of the column is *closed*. It thus resembles the infinite baffle in that the back of the speaker is completely enclosed, the front surface of the speaker diaphragm being the only sound source. The reason for this design is explained below.

The lower limits of the bass response of a baffle are set by the fundamental resonant frequency of the enclosed air mass, the response falling off rapidly below this point. For conventional bass reflex and infinite baffles the desired resonant frequency is

obtained by making the volume of the speaker enclosure sufficiently large. The resonant frequency of the open-ended labyrinth depends on the length of the column, the wavelength at resonance being twice the column length. The column cross-section can be reduced sufficiently so that the bulk of the labyrinth is considerably less than that of bass reflex or infinite baffles of the same resonant frequency. There is a limit to this reduction in bulk, however, for if the column cross-section is constricted too much, very little sound can pass through the column, and back pressure will build up behind the speaker diaphragm, impeding its motion and thereby reducing the sound output. The proposed design effects a further saving in bulk, however, by cutting the column *length* in half, and *closing* the end of the column. This leaves the fundamental resonant frequency unchanged, for the wavelength at resonance is four times the column length for a closed column, as compared with twice the column length for the open column. The volume is thereby reduced to approximately half that of the conventional open-ended labyrinth with the same column cross-section and same resonant frequency.

The reduction in bulk is not accomplished without cost, however. With the open-ended labyrinth (and also the bass reflex baffle), back radiation is emitted through a separate port. With the proposed baffle, as with infinite baffles in general, sound can be emitted only through the speaker diaphragm. Thus, at resonance the back radiation travels the length of the column and is reflected back in the proper phase to reinforce the motion of the diaphragm, so that the back radiation is, in effect, emitted through the diaphragm. For a given total sound output, the amplitude of motion of the diaphragm must be greater when all the sound is coming from the dia-

phragm, than when part of the sound is coming from a separate port. But at large amplitudes the cone suspension system departs from linearity, resulting in harmonic distortion. Thus our baffle, in common with other infinite baffles, cannot put out as much "undistorted" sound power as can a baffle with a port for releasing back pressure. Furthermore, much of the back radiation is absorbed by the labyrinth walls. Also, the cross-section of the column is sufficiently small to offer appreciable opposition to the passage of sound, so the motion of the speaker cone is restricted somewhat. This baffle, like other labyrinth baffles, is therefore less efficient than a bass reflex baffle.

The labyrinth is lined with sound-absorbing material partly to cut down and spread out the fundamental resonant peak, and partly to damp out higher harmonics and anti-resonances. (The open labyrinth gives even harmonics, the closed labyrinth odd harmonics.) If the labyrinth walls are non-absorbent, a pronounced peak is obtained at fundamental resonance, with a series of lesser peaks and dips at higher frequencies. The latter fluctuations are not as noticeable to the ear as one might expect, however. For that reason some experimenters may find a non-absorbent baffle reasonably satisfactory.

A typical baffle design is shown in Fig. 2. The dimensions and general layout may be varied within limits to fit various sizes and shapes of speaker compartments. The volume of the baffle is slightly over $1\frac{1}{2}$ cubic feet.

Design Notes

1. *Acoustic Lining.* For best results the lining should have a high absorption coefficient at middle and high frequencies, and moderately good absorption at low frequencies. Dense mats of mineral fiber, such as rock wool or glass, fiber, meet these requirements. (Do not use *thermal* insulation, as it is not nearly dense enough). It is a good idea to look at a table of the absorption characteristics of various materials for different frequencies before choosing the material. You may be impressed, as I was, with the scarcity of materials with good low-frequency absorption.

Material in the form of rigid sheets is the easiest to work with, since it supports itself and can therefore be used by itself to form the baffle plates.

*Olney: Journal Acoustical Society of America, Vol. 8, No. 2, 1936, page 104.

I used *Johns-Manville "Airacoustic"* sheets, one inch thick (rigid sheets for lining air-conditioning ducts). Thinner sheets are available, but the thicker ones have better low-frequency absorption as well as greater mechanical strength. Sheets of glass fiber or other material with similar properties should work just as well. The sheets are used both to line all surfaces of the speaker compartment and to form the interior baffle plates.


The baffle plates should preferably be mounted vertically as shown, as this simplifies the problem of keeping them in place. If they are cut for a tight fit, they will stay in place without being fastened, unless the cabinet is tipped over. If necessary they may be pegged securely in place with a few finishing nails, as shown in Fig. 1C.

2. Column Dimensions. The effective length of the baffle shown here is over 5 feet, which means a resonant wavelength of over 20 feet, or a resonant frequency somewhat below 60 c.p.s. The choice of resonant frequency depends on the type of over-all response desired, and on the characteristics of the other audio components, in particular the resonant frequency of the speaker. It is very easy to experiment with different column lengths by varying the number or arrangements of baffle plates until the desired response is obtained.

The baffle shown is believed to be about as small as is practicable. Since the acoustic material takes up a sizable fraction of the total volume, any further reduction in bulk would necessitate a relatively great decline in the air space. This would mean a substantial reduction in either column length or cross-section, at the expense of performance. By the same reasoning, it is advisable to make the baffle larger than shown, if space permits. This baffle, however, seems to be a reasonably satisfactory compromise between performance and compactness.

The front baffle plate has a hole which fits snugly over the speaker field housing, permitting the plate to be mounted close to the front of the speaker. This is necessary to provide proper coupling between the speaker and the column. If the arrangement of Fig. 1B were used instead, the coupling would be very poor because of the great contrast between the cross-section of the column and that of the chamber immediately surrounding the speaker. Most of the back radiation would be trapped in the latter chamber, setting up a resonance, not adequately damped by the lining, resulting in a very annoying peak in the middle voice frequencies.

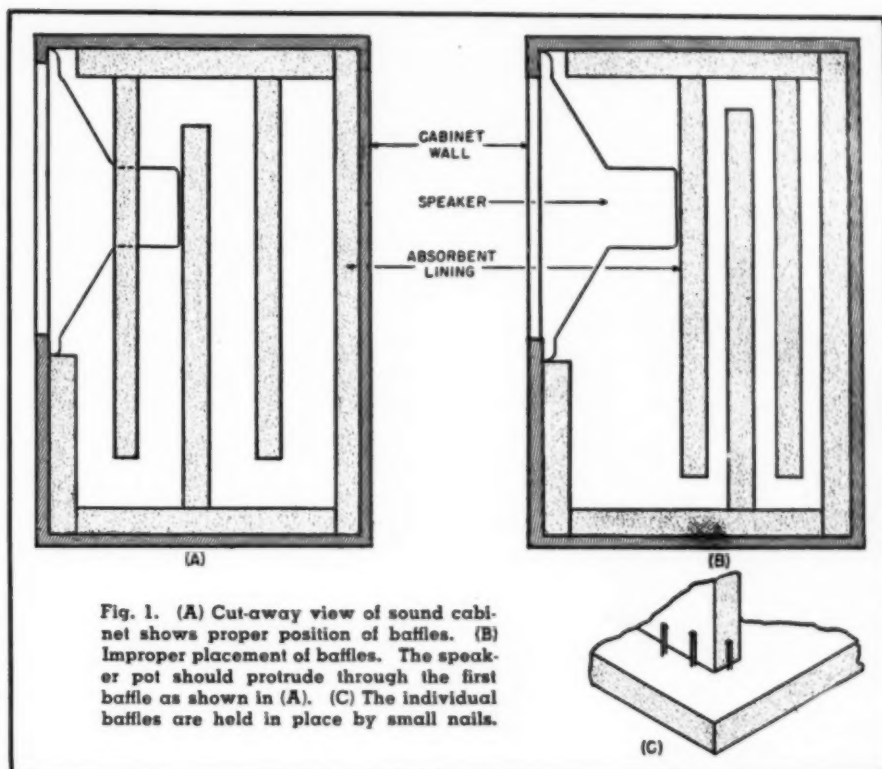3. Speaker. In the open-ended labyrinth and bass reflex baffles much of the low-frequency output comes from the port rather than directly from the speaker diaphragm. It is thus possible to obtain satisfactory bass response using a relatively small diameter speaker. With our baffle, however, as with all types of infinite baffles, it is essential to use a large speaker, since




the front of the speaker diaphragm is the only sound source. A six or eight-inch speaker is entirely unsatisfactory for this type of baffle. A twelve-inch speaker will do, and a fifteen-inch speaker is still better. The larger speaker is superior in having a lower resonant frequency as a rule, but the chief advantage is in the greater maximum undistorted sound output at low frequencies. This is particularly important, for high power output is most needed at low frequencies.

The marked dependence of bass response upon speaker size is evident from the theoretical equations of speaker performance. Assuming the cone to

move as a piston, the sound power output at a given frequency is proportional to the area of the cone, the radiation resistance per-unit-area, and the square of amplitude of vibration of the cone. But the area of the cone varies as the square of its diameter, and so does the radiation resistance per-unit-area, at low frequencies. And the maximum excursion the cone can make, without excessive distortion due to non-linearity of the suspension system, is presumably roughly proportional to the cone diameter. For there is usually a rough correlation between the dimensions of the cone and the dimen-

(Continued on page 112)

Fig. 2. Over-all view of speaker case with top lining removed.

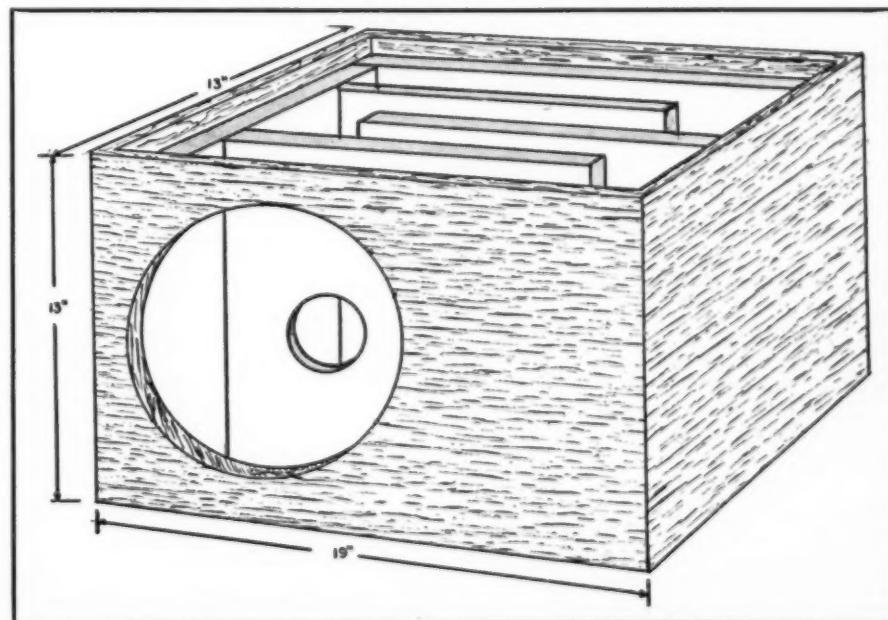



The Beginning Amateur

By
ROBERT HERTZBERG,
W2DJJ

YOU now have a ham license, a receiver (described in the April, 1949 issue of RADIO & TELEVISION News), and a burning desire to go on the air. Where do you start? How much, or rather how little, must you spend for a transmitter?

You'll be rather surprised to learn, right off, that a basic c.w. transmitter is simpler in design and construction than a receiver. The foolproof rig pictured herewith can easily be assembled in about three or four hours, at a cost of \$20 to \$25. The parts, with the exception of the main tuning coil, L_n , are standard receiving-type components and can be bought at bargain prices. If you start the project in the morning and allow yourself an hour

Part. 5. You're on the air—if you've followed this series you should have your ham license and receiver—here are the construction details for your transmitter.


or so after lunch for the antenna installation, you will be pounding brass by supper time. The likelihood is that you'll forget all about supper when some other ham answers your first CQ!

The transmitter was designed as a companion unit for the receiver, and uses a chassis and a front panel of the same dimensions. If you have access to a manual training shop in school, or have the necessary woodworking tools at home, you can dress up the outfit considerably by enclosing both receiver and transmitter in a simple

cabinet. Provide a hinged top for the receiver so that you can change plug-in coils readily.

Note that this is a c.w., not a phone transmitter. Sure, you'll go on phone eventually, but you need preliminary experience in tuning procedures, the handling of radio-frequency energy, etc., and a c.w. rig gives it to you painlessly and inexpensively. Phone is fun, but also a bit more costly. Check the cost of microphones, speech amplifiers, and modulation transformers, and you'll agree that c.w. is a smart beginning for your ham career;

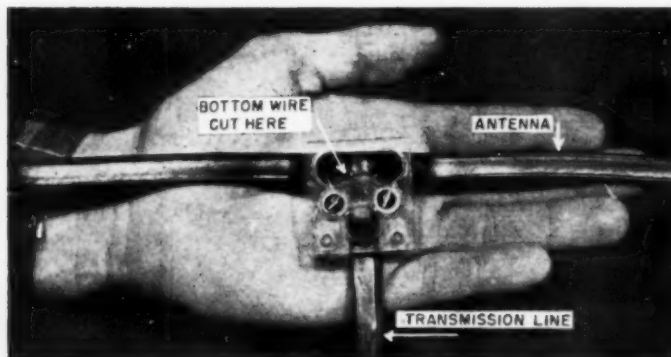(Left) The photograph shows how the transmission line joins the center of the antenna. One wire of the antenna is cut, and the two ends thus formed go to the ends of the transmission line, under the heads of machine screws.
(Right) The free ends of the antenna are joined and soldered where they pass through one hole of the insulator.



and when you discover how readily you can work DX with low power, you'll appreciate c.w.'s long-standing popularity with hams the world over.

The transmitter uses one tube, a 6L6, as an oscillator, or generator of radio-frequency energy, and a second, a 5Y3, as a high-voltage rectifier to supply direct current to the plate of the 6L6. The actual radiating of the radio signals into space is done by an antenna of the popular "folded dipole" type, made of inexpensive twin lead wire. This is the same stuff used for television aerial lead-ins. There is only one tuning control, and once you set it for a particular frequency you leave it alone.

After you look over the diagram of the transmitter, the parts list, and the construction photographs, you'll probably remark, "Heck, there's nothing to this." Study the layout carefully before you drill any holes. It has been worked out to produce short, direct connections, which are helpful in any short-wave transmitter. No detailed layout drawings are given because parts vary in dimensions, but follow the general plan and you'll experience no difficulty.


On the chassis proper are mounted the power transformer, T_1 , and its associated rectifier tube, V_2 , and filter condensers, C_5 and C_6 ; the sockets for the oscillator tube, V_1 , the crystal, and the plug-in coil, L_1 . The front panel holds only the tuning condenser, C_4 , the line switch, S_1 , and the panel light, PL_1 .

Because the tuning condenser, C_4 , is part of the high-voltage supply circuit, it must be insulated completely from the panel. Mount it on a piece of bakelite, fiber, or even well dried hard wood measuring about 1 x 3 inches. Drill a center hole in the panel large enough to clear the condenser mounting stud and nut by about $\frac{1}{8}$ inch, and fasten the insulating strip to the panel, from the back, by a couple of short 6-32 screws and nuts. Fit the protruding shaft, on the front side, with a bakelite pointer knob. Make a simple dial from white paper and attach it to the panel by means of rubber cement, airplane dope or Scotch tape.

The sockets for V_1 and L_1 are raised above the top surface of the chassis by brass or fiber spacers, or piles of washers, to a height of about $\frac{1}{2}$ inch. This arrangement keeps the high-voltage leads in the open air and reduces the possibility of flashovers to the grounded chassis. The crystal socket sits flush against the chassis. Only two of the five pins of this socket are used to take the prongs of the crystal holder.

The underside of the chassis holds the filter choke, CH_1 , and the few small resistors and condensers. The wiring is very simple and shouldn't take you more than thirty minutes.

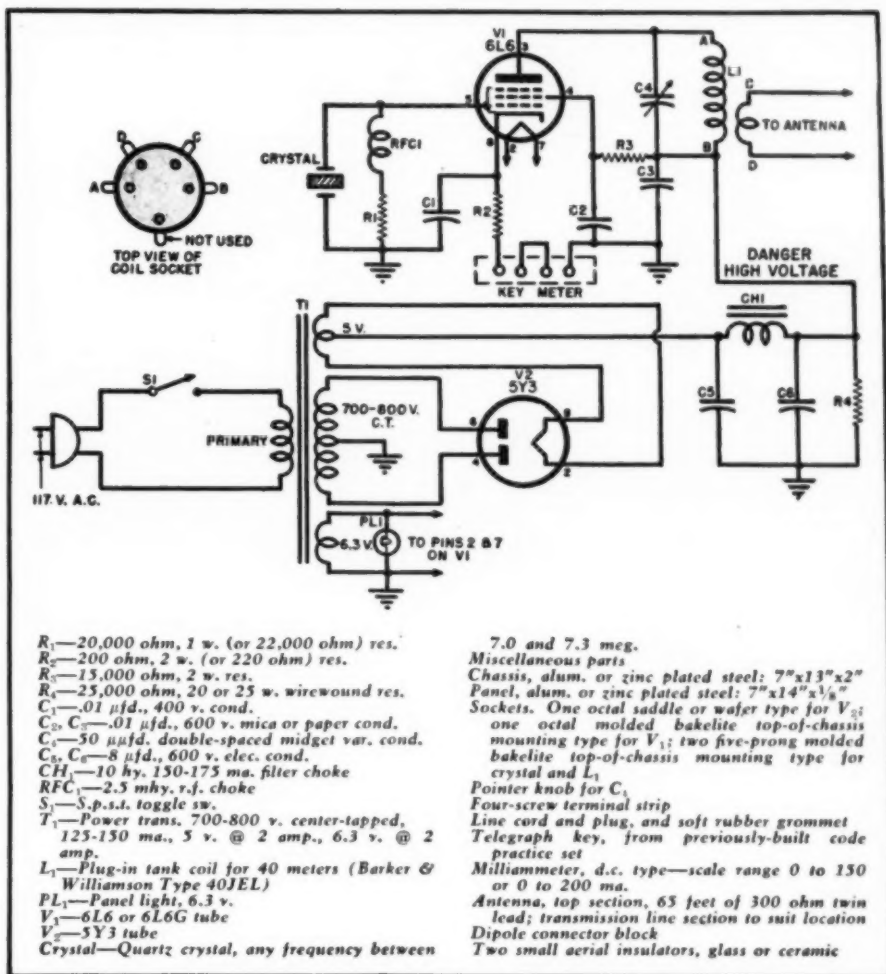Connections for the key and a plate circuit milliammeter are made at a four-terminal strip on the back of the chassis. Space this away from the



Complete schematic diagram of transmitter. Only two tubes are required.


metal surface by collars, to give access to the soldering lugs.

I strongly recommend that you go on the air initially on the so-called 40-meter band. This extends from 7000 to 7300 kilocycles (7 to 7.3 megacycles), is devoted exclusively to c.w., permits wonderful DX contacts, and requires only a simple antenna. Surplus Army and Navy crystals for this range are available by the thousands, at give-away prices. To play safe,

keep away from the extreme edges of the band. Any frequency higher than 7000 and lower than 7300 is satisfactory. I selected a crystal cut for 7150 kilocycles because it can be used later to control a phone transmitter on 28.6 megacycles, in the 10-meter phone band. (For this purpose, the circuits are arranged to quadruple the crystal frequency: 7150 times 4 equals 28,600 kilocycles, or 28.6 megacycles.) Used


(Continued on page 142)

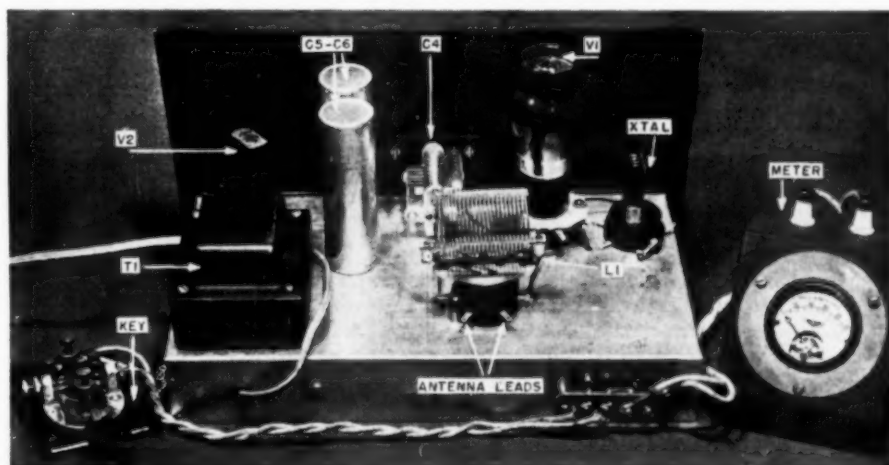The complete amateur transmitting station: key is on the left, the transmitter is in the center, and the plate meter is on the right.



Mac's RADIO SERVICE SHOP

By JOHN T. FRYE

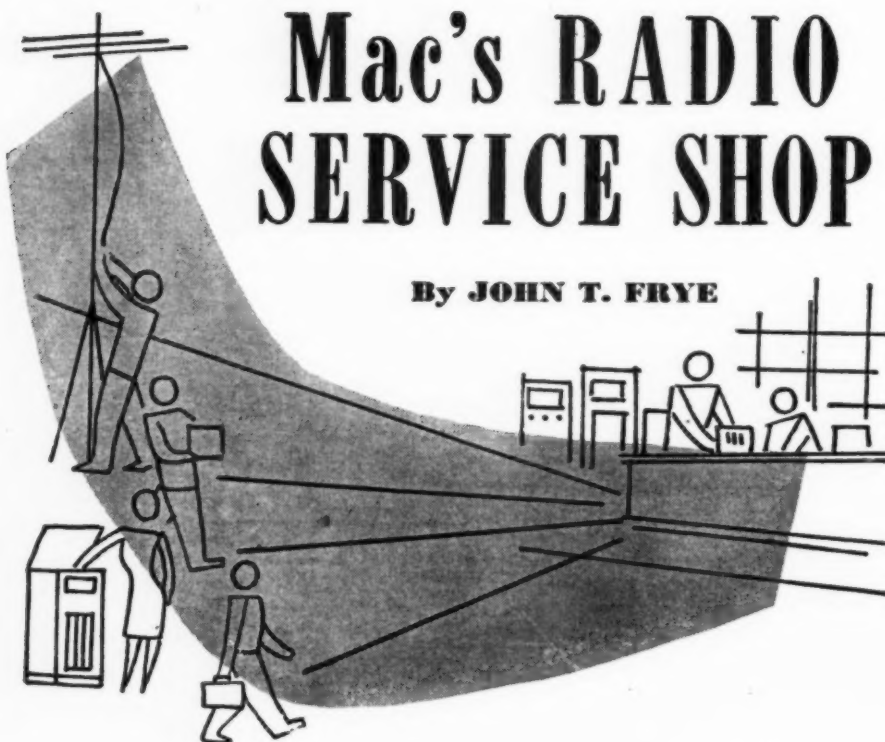

BARNEY AND THE BOOSTERS

AFTER having had that young Irishman, Barney, as an assistant in his radio service shop for over a year, Mac thought he was pretty well prepared for anything the boy might do; but he was still somewhat taken aback when one bright June day the lad came dashing and sliding into the service department after his lunch hour, yelling at the top of his voice, "Your-a-kay! Your-a-kay!"

Instantly Mac grabbed up the atomizer-bottle of cleaning fluid used to brighten up dial glasses and squirted a couple of shots at Barney's fiery red hair.

"Calm down! Calm down!" he ordered. "And what's this 'your-a-kay' business?"

"You know: 'your-a-kay,'" Barney said impatiently. "It is what Archimedes said when he discovered the law of flotation. It's Greek and means 'I have found it.'"

"I always thought the word was pronounced 'Eureka,'" Mac said mildly; "but what particular 'it' have you found this time?"

"I've just solved the problem of how to get good TV reception in the fringe areas," Barney announced importantly.

"I told you not to run around in this hot sun without your hat on," Mac muttered, "but tell me more! I, and about fifty million other Americans, are strangely interested."

"Like all great inventions, it is really quite simple," Barney said modestly. "You know that an airplane flying overhead reflects a signal down to the set; right?"

"Check."

"My idea is simply to paint the outside of a spherical balloon with metal-

lic paint, so that it will reflect TV waves and then to send it up a thousand feet or so on the side of town farthest from the TV station. Because of the spherical shape, it will reflect the signals passing high overhead down into every part of the town, and there will always be some point on its curved surface that will reflect the signal to a given spot, no matter how much the balloon turns or bobs around."

"Perhaps if you were to lie down there on the bench for a while and if I were to place cool, moist compresses on your head," Mac mused, "or maybe squeeze your head just a little bit in the vise—?"

"All right! All right! They laughed at Marconi, too," Barney said: "but I am going to try it all the same—just as soon as I can get hold of a suitable balloon."

"What brought on this unusual attack of deep thinking?" Mac asked curiously.

"The gang over at the hash-house was arguing about fringe-reception in general and boosters in particular. Some said boosters were next to worthless; others swore by them. How do you feel about boosters?"

"Well, that's a good bit like asking what you think about blondes. In both cases the answer might well be: 'There are lots of different kinds, and even the same kind behaves differently in different situations.'"

"Is that why there is so much disagreement about blondes—I mean boosters?"

"I think so. One thing you have to remember is that the booster has to have something to boost. Unless the antenna can deliver some sort of sig-

nal to it, it has nothing to work on. The results are about the same as when a small boy reaches the bottom of his soda. He keeps on trying, but about all his straw delivers is noise.

"And speaking of noise," Mac went on, "the important thing to a booster is not how much signal you have, but how much signal you have in comparison with the noise level. In a very quiet location, the booster can take a noise-free signal of only a few microvolts and push it up to where it will make a good picture. In another location where a much stronger signal is available but where it is accompanied by an equally-strong noise, the booster is helpless, for it cannot boost the one and not the other. In the latter case, the owner of the TV set could truthfully say that a booster did not help him, for the gain of his unaided receiver would be sufficient to reach down to his high noise level."

"What could he do about it?"

"Well, he would have to make changes in the kind, orientation, or location of his antenna, or in the type or path of his lead-in so as to produce a more favorable signal-to-noise ratio. He could do this by increasing the signal strength, decreasing the noise, or by raising or lowering both, non-uniformly, so that the signal has the better of it. Once he has that signal sticking up out of the noise level, the booster can take hold of it and raise it to picture-making strength."

"In other words, if the signal in your antenna is well above your noise level, the booster can do a good job on it; if not, the thing to do is not to cuss the booster but to work on the antenna."

"Go to the head of the class, Junior."

"What does it take to make a good booster?"

"The perfect booster," Mac said slowly, "would be one that would amplify uniformly the full six megacycle width of each of the twelve channels and nothing else. It would contribute no noise of its own, would be completely stable, would not upset the impedance of the lead-in into which it was inserted, and would have high amplification."

"How close can we come to that?"

"Not too close. Tight coupling to the antenna and resistor loading of the tuned circuits flatten out the response curve but only at the expense of gain; and we still cannot achieve the straight-sided flat-topped response curve we'd like. What's more, every booster contributes some noise of its own to that picked up by the antenna, and it is difficult to achieve both high gain and low noise."

"What does too narrow a bandpass do?"

"Shows up as a lack of detail in the picture or, in the case of a weak signal, difficulty in getting both the picture and the sound at the same time. By tuning the narrowband booster, you can peak up one or the other, but not both." (Continued on page 140)

RADIO & TELEVISION NEWS

A Miniature Phone-C.W. Transmitter for Portable or Mobile Use



Fig. 1. The r.f. section (left) and the modulator portion (right) are housed in interlocking war surplus metal cabinets.

By HAL BUMBAUGH, W6HI

A deluxe type portable or mobile transmitter which offers all of the desirable features of a home rig.

THE design of small transmitters for portable or mobile use resolves itself usually into a struggle for simplification and compactness. While, in general, these are definitely necessary requisites they are all too frequently obtained at the cost of power output, stability, and completeness of control.

If there is one type of transmitter in which every fraction of a watt should be conserved within the transmitter and every possible watt obtained at the output it is the small portable or mobile job.

It is the purpose of this article to describe a transmitter in which every feature to be found in the home shack kilowatt rig is retained, one which has adequate output for DX work on phone or c. w. on all amateur bands, and yet can be comfortably housed in a small metal carrying case.

All-band operation can be had on either phone or c. w. with only three crystals in the 80 meter region, and the rig may be powered either with a 6 volt battery, a 12 volt battery, or a conventional a. c. power pack.

Use is made of presently available items on the surplus market which permit the building of a complete transmitter at a very reasonable cash outlay.

The two principal items entering into such a design are, first, tubes, and second, power supply.

The power tube used in the final stage of the transmitter and in the output stage of the modulator is the 815. This is a tube which is one of the best dollars-and-cents buys available to the amateur but one whose watts-per-dollar value is, unfortunately, little recognized by amateurs. The general design of the tube is such that it lends itself well to external short leads and compact construction. It is a double beam tube built into a short, sturdy glass envelope and requires extremely low grid driving power—either r. f. or a. f.—for full power output. Its construction also makes it ideal for push-pull operation where the length of the external leads may be brought down to the irreducible minimum, thus making for extremely high efficiency and stability. For example

the grid leads in the rig to be described are one inch in length while the plate leads are one half inch long.

The other half of the team is a PE 103 dynamotor of the type which gave such excellent service during the last war and which is now available on the surplus market at an extremely low figure. One of these new dynamotors should take care of all future mobile problems—as well as some portable ones—for the amateur for some years to come. They are very ruggedly built and will deliver several times their rated output without damage. Furthermore they can very readily be adapted to amateur use as will be seen later.

The surplus market is again called on to provide a carrying case for the transmitter and the modulator. These cases were used by Collins to house their small communications units known as the MBF. These aluminum cabinets, with carrying straps and lock-on lids, are available at a very reasonable figure and come in pairs which lock together, thus making an ideal set-up for housing the transmitter and modulator to be described. The individual cases measure 14 inches by 9 inches by 8 inches. If these cases cannot be obtained, commercial cabinets approximating these dimensions may be used.

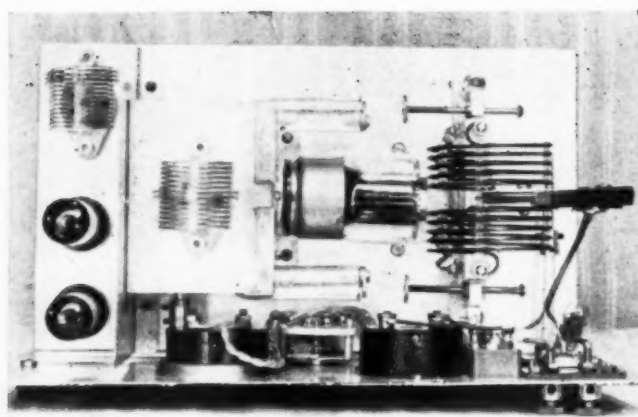


Fig. 2. Top chassis view of r.f. portion. Neutralizing condensers, C_{11} , C_{12} , may be seen at ends of tank coil, L_1 , L_2 .

Standard commercial chassis measuring 12 inches by 7 inches by 3 inches are just right for these cases as can be seen in the photographs.

Front panels may be of any desired metal and thickness to suit the constructor as they will be finished in black crackle lacquer when completed. Panel dimensions are $13\frac{1}{4}$ inches by $8\frac{1}{8}$ inches.

Transmitter

Fig. 4 is the circuit diagram of the r. f. section.

While a great deal of latitude is permitted the designer in the choice of oscillator circuits it is the author's belief that the circuit shown is probably the best all-around circuit since it is easily set up, never fails to start re-

gardless of the load, can work straight-through with no possible damage to the crystal, and has extremely high harmonic output up to the fourth harmonic. There are no adjustments other than that of the load circuit tank. As will be seen, the circuit is inherently a Colpitts with the voltages apportioned by the condensers in the grid circuit. The load is electron coupled for the fundamental or any of its harmonics.

While almost any of the conventional tubes used as oscillators may be used in this circuit, the 6AG7 (basically a television video tube) is the best because of its extremely small interelectrode capacities and its excellent inherent shielding which is an aid in holding crystal current to a minimum

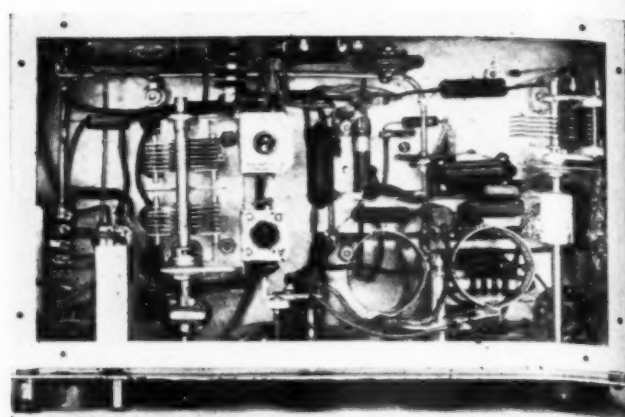


Fig. 3. Bottom view of unit. The two toggle switches near center of chassis are phone-c.w. and microphone supply switch.

and protecting the oscillator from reflected changes in the output or load circuit.

For the above reasons another 6AG7 was chosen to function as a buffer-doubler tube since it functions equally well for this purpose, the doubling efficiency being very high.

As a load circuit for the 6AG7 oscillator and a coupling medium to the 6AG7 buffer-doubler a Barker & Williamson 2-A "Band-Hopper" coil was chosen and can be seen in Fig. 3. Its taps are available through the medium of the switch built into the assembly, the shaft of which extends through the front panel, and it is the second control from the left in the lower row in Fig. 1.


The load circuit L_2 of the 6AG7 buffer-doubler is a plug-in "Baby Type" Barker & Williamson coil with end link (type MEL). It is tuned by a $100\text{ }\mu\text{fd.}$ condenser, C_5 .

A very important feature of the buffer-doubler stage is the 50,000 ohm potentiometer, R_4 , which functions as an excitation control for the final. Not until one has had experience with such a control is it realized what extended voltage excursions of screen and plate voltage are required to maintain rated grid milliamperes in the final stage under conditions of doubling or buffer action in the second stage. From the standpoint of maintaining optimum conditions and efficiency in the transmitter, this is probably the most important single control.

A very short section of 72 ohm flat line connects the link on the buffer-doubler coil with the center link of another "Baby" Barker & Williamson coil, L_1 , in the grid circuit of the final (type MCL). To avoid unwanted coupling this link is grounded thus restricting the coupling to magnetic only.

The grid circuit of the final is tuned with a two-section 100-100 $\mu\text{fd.}$ condenser, C_6 , positioned directly under the grid coil and adjacent to the base pins of the 815 thus making for short leads. As a matter of fact the one inch grid leads are really made up of 10 ohm resistors R_{10} , R_{11} with 7 turns of #20 tinned wire wrapped around them to form the parasitic suppressors L_3 and L_4 , and are completely effective

Fig. 4. Circuit diagram of the r.f. portion of the portable-mobile transmitter.

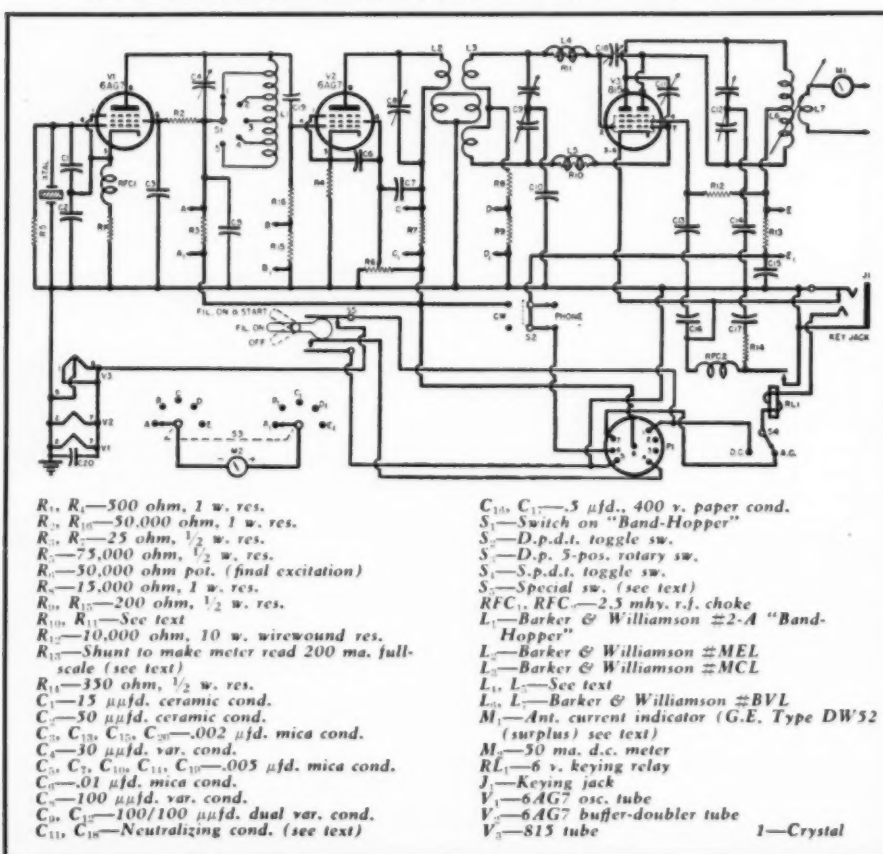

since no parasitics exist in the rig.

The output circuit of the 815 is the conventional push-pull set-up tuned by a 100-100 μ fd. split-stator condenser, C_{15} , while the coils used are larger Barker & Williamson "Air Inductor" type equipped for swinging link (Type BVL). The shaft on which the swinging link is positioned is carried through the front panel and controlled by a knob mounted near the right hand end of the panel. The adjustment of this link is very important in getting optimum performance out of the transmitter, especially on phone where the loading must be adjusted to provide the proper impedance match for the secondary of the modulation transformer. The pickup coil of the link is connected through a few inches of 72 ohm flat line to a small G. E. antenna current meter and associated rectifier (Type DW 52) which is available on the surplus market. This meter has a full scale reading of .75 amp. and the scale is divided into ten parts. Many small r.f. meters of similar type are available on the surplus market. From the meter the leads then go to a pair of binding posts on the front panel. In parallel with these posts is a coaxial fitting which permits connection to the antenna through the medium of flat lines, twisted pairs, or coaxial cable.

Since the small job was to have the same metering facilities as the largest rig—and had only one meter—a metering switch was indicated and this was connected as shown on the wiring diagram. In view of the fact that in the five circuits to be metered the lowest reading was to be about five milliamperes and the highest (in the final plate circuit only) about 150 milliamperes—the others being intermediate—a 0-50 milliamperere Weston Model 506 meter was chosen. Thus it will read all circuits directly with the exception of the 815 final plate circuit. For this circuit a piece of nichrome wire from an old resistor was put across the meter terminals (with the meter reading full scale from a battery and potentiometer) and shortened until the meter read $\frac{1}{4}$ full scale. This shunt was then applied to the plate resistor R_{15} in the transmitter diagram. Thus

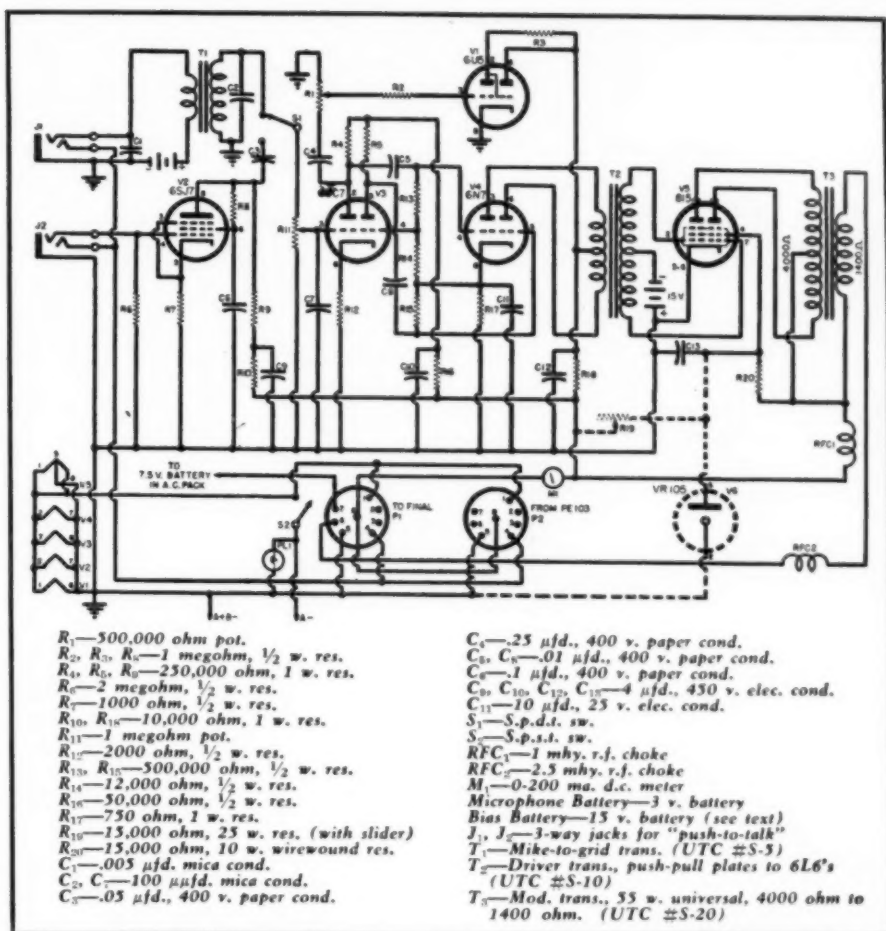


Fig. 5. Schematic diagram of the audio and modulator portion of the transmitter.

the final plate current is four times the milliamperere reading on the meter.

While the 815 may be used for some purposes and under some conditions without neutralization complete mastery of the circuit could be obtained only if there was complete and stable neutralization under all conditions. Hence the small neutralization set-up, consisting of C_{11}, C_{15} , as shown in Fig. 2 was installed. The grid circuit is "crossed over" and the leads brought out along polystyrene stand-offs as shown. The dimensions of the end plates on these leads are approximately $\frac{5}{8}$ " by $\frac{3}{8}$ " with rounded cor-

ners and edges. The other plates of the condenser are $\frac{3}{8}$ " diameter washers soldered on the end of 8-32 brass screws 3" long. Adjustment is made by screwing the assembly in or out. While the spacing will depend on the mechanical and electrical set-up adopted by the individual constructor the spacing used in this case is $\frac{13}{16}$ inches. This was the setting obtained for the ten meter band and will serve for all lower frequency bands. The final neutralizes easily and is perfectly stable with this arrangement.

In Fig. 2, just over the shaft extension for the swinging link, is shown a

Fig. 6. Bottom view of the audio section. The battery for "C" bias may be seen at the upper left hand corner of the chassis.


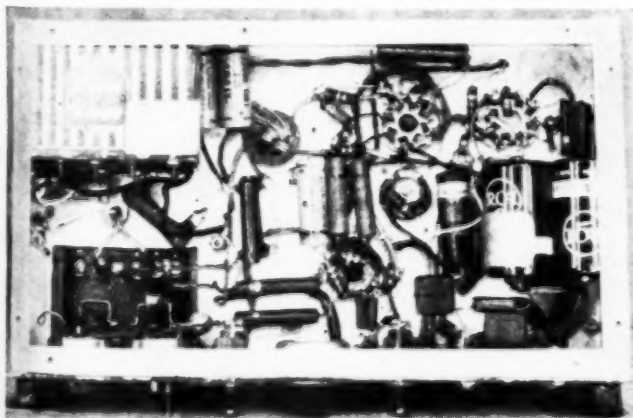


Fig. 7. Top view of the audio chassis. The 6U5 tube used for modulation indication may be seen at the lower left of photo.

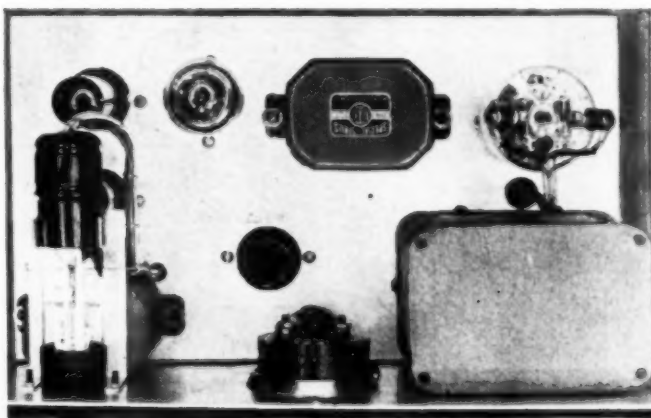

Band	Xtal. No.	Sw. S ₁	Buffer or Doubler	Excitation R ₁	Xtal. Tune C ₁	Buff.-Doub. Tune, C ₂	Final Grid Tune, C ₃	Final Plate Tune, C ₁₂	Freq. (kc.)
80 c.w.	1	5	B	15	50	48	63	70	3,525
80 ph.	3	5	B	15	49	55	62	51	3,925
40 c.w.	2	5	D	40	48	42	46	34	7,130
20 ph.	2	3	D	65	42	27	27	26	14,260
20 c.w.	1	3	D	65	58	30	28	20	14,100
10 ph.	2	1	D	85	30	41	26	18	28,520
10 c.w.	1	1	D	85	30	44	26	19	28,200

Table 1. Typical tuning chart showing approximate settings of the various controls.

¼ watt neon tube in a screw holder. Although all circuit adjustments are made by meter under normal conditions this neon tube was included in the rig so that in the event of trouble in the field the source of the difficulty could be readily found.

The crystal holder is on the top of the chassis directly under the milliammeter case and immediately adjacent to the base of the 6AG7 oscillator (the tube nearest the front panel).

Three crystals in the 80 meter region cover all amateur frequencies on which a rig of this type is likely to be used. Both phone and c. w. are provided for as follows: 3525 kc.—c. w. on all bands; 3565 kc.—40 c. w., 10 and 20 phone; 3925 kc.—80 meter phone.

No chassis layout is given for the transmitter or modulation chassis since the present layout is shown in the photographs and the individual constructor will no doubt prefer to improve upon the layout and substitute available components. This may be done with assurance since the circuits are very stable.

Switch S₁, shown in Fig. 1 immediately adjacent to the power plug,

is another surplus item which lends itself perfectly to the present rig. It is a W. E. SW 185 and the positions are shown on the r. f. schematic (Fig. 4). In its "up" position it functions similarly to the push-to-talk button on a crystal or carbon microphone so that the r. f. circuits may be heated up for adjustment without using the microphone switch. It is also used on c. w. where the transmitter may be on for extended periods of time. The other positions are explained on the diagram.

Keying is accomplished, as seen in Fig. 4, through the medium of a small 6 volt d. c. relay, RL₁, again from the surplus market. This relay may be seen in the upper left hand corner of the transmitter chassis in Fig. 3. It will be observed that this relay is not in the circuit until the key is inserted in the keying jack.

When the transmitter is used with an a. c. power pack a small 7½ volt battery must be supplied for use on the d. c. keying relay winding since this relay will not work satisfactorily on a. c. This small battery has its "+" side connected to one leg of the 6 volt a. c. filament circuit and its "-"

side connected to pin #7 in the cable going to the modulator and transmitter panels. It will of course be necessary to provide an adapter between the standard P. E. 103 cable and the a. c. power pack. The small toggle switch labeled "A.C.-D.C." in Fig. 3 (when set for "A.C.") transfers the minus side of the relay winding to pin #7 and a. c. operation on c. w. may then be employed. Of course for phone operation on a. c. such a battery is not needed since the keying relay is not involved.

In Fig. 1 the controls shown are: top row, (left to right) final grid tuning, meter switch, excitation control, and (hidden by corner of audio cabinet) variable link adjustment.

On the bottom row (left to right) are shown the buffer-doubler plate tuning, crystal harmonic output selector (2-A "Band-Hopper" coil and switch assembly), 2-A tuning condenser, final plate tuning, keying jack, J₁, filament control switch S₂, and power input plug P₁.

For ease and rapidity in changing bands the author made up a log giving all the pertinent data involved and, for the benefit of those desiring to make up a similar one, this log is reproduced in Table 1.

Fig. 3 shows a small toggle switch labeled "Phone—C.W." In the "phone" position the output of the modulator secondary is connected to the plates and screens of the 815 in the final. In the "C. W." position the modulator transformer secondary is disconnected and "B+" taken straight through to the plates and screens of the 815.


Modulator

The modulator unit is conventional in every respect. The schematic is shown in Fig. 5.

Two 3-pole jacks are used for the crystal and carbon microphone inputs, the 6SJ7 not being in the circuit when the carbon microphone is used. The additional contacts on the jacks are for the PE 103 starter circuit in conjunction with the push-to-talk switches. The surplus market may again be called on to furnish a crystal or carbon microphone. Any type will be satisfactory as the modulator has adequate gain to take care of even the lowest microphone input. The diagram is self-explanatory, but two items might be elaborated upon. The first is the VR 105-30 tube shown in dotted lines on the drawing. From the theoretical point of view the simultaneous modulation of plate and screen grid (as in the 815) requires a very well regulated screen supply such as might be furnished by the part of the circuit pertaining to the VR 105-30. While it is agreed that the theory is correct at this point the added circuit drain due to such a set-up is undesirable in mobile or portable use and, furthermore, experience has shown that in a well constructed and controlled circuit such voltage regulation is not absolutely necessary. The present transmitter

(Continued on page 144)

Fig. 8. Performance curves for the PE 103A dynamotor under various loads.

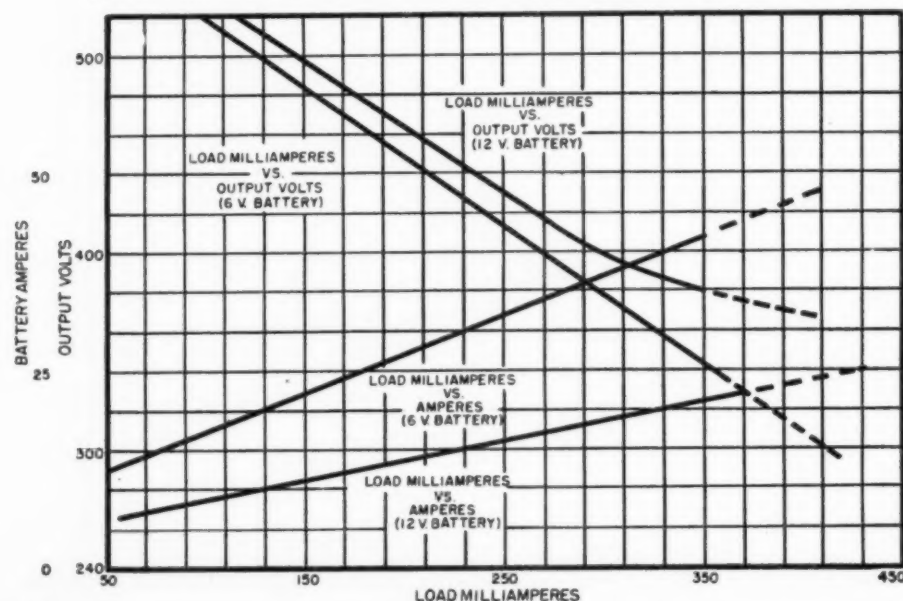


PERFORMANCE-ENGINEERED AT ELECTRONICS PARK




SMALL-SIZE SPEAKERS

**That Talk in Terms of
GREATER SERVICE SATISFACTION
To 65% of Your Trade!
Because they deliver more—**


**POWER
SENSITIVITY
FIDELITY**

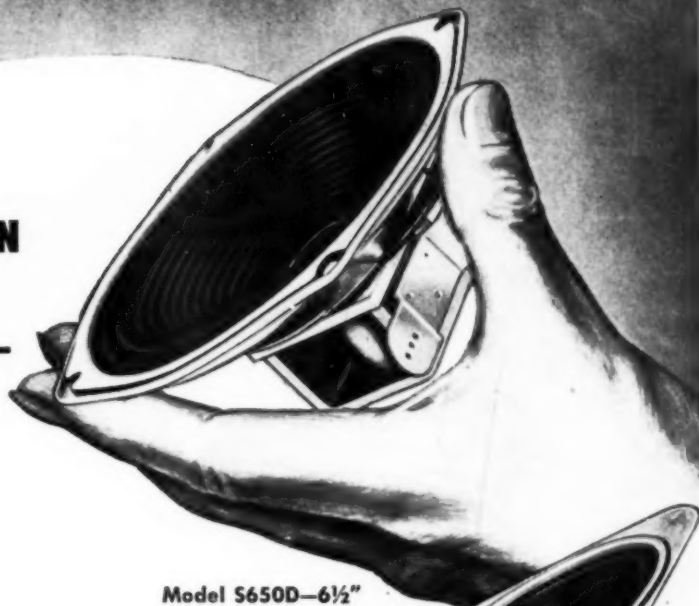

Model S650D—6½"

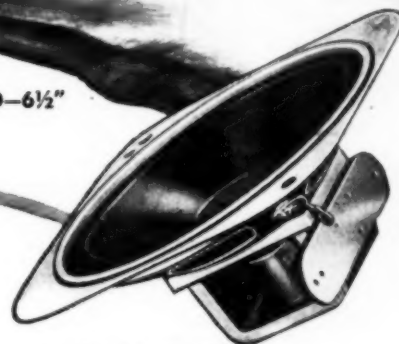

Model S525D—5¼"

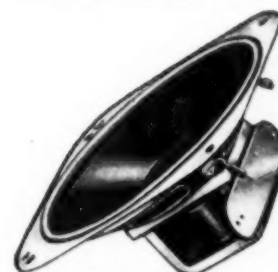


Model S400D—4"

A RECENT SURVEY shows that 65% of all speaker service requirements are on sets using 4 to 6 inch speakers! Remember—even the smallest General Electric speaker is rated at 4 watts... General Electric speakers, with sturdy all-weld construction, give you higher sensitivity because each G-E Alnico 5 magnet is fixed so firmly in the yoke that hundreds of pounds of pressure cannot budge it!

It costs no more to give your customers the finest! The G-E Speaker family is headed by the famous 1201—grand-daddy of 'em all. Build your reputation on the General Electric Value Line! Send for FREE BULLETIN on G-E speakers:

General Electric Company,
Electronics Park,
Syracuse, New York.

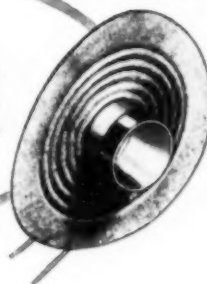**Yes—Even the Smallest G-E Speaker
Uses the Aluminum Foil Base Voice Coil**
—not subject to warping resulting from high
humidity. Provides much higher wattage
handling capacity.



You can put your confidence in—


GENERAL



ELECTRIC

COMPLETE TRAINING

FOR BETTER JOBS
in Radio-Electronics

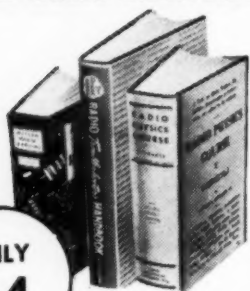

ONLY
\$14

5 MONTHS TO PAY!

Here are three world-famous books so thoroughly covering radio theory, troubleshooting and servicing methods; so clearly explaining every phase of the work that, with a minimum of time, you'll soon be able to handle repairs on any type of Radio-Electronic Equipment and qualify for better jobs, bigger pay checks! You couldn't get a finer, more complete or easier to understand training course AT ANY PRICE. Remember! These are the same Ghirardi books that were more widely used for wartime radio-electronic training than any other books or courses of their type!

Ghirardi's BIG-3 RADIO SERVICING LIBRARY

These three big books contain a total of 3016 pages and 1214 illustrations covering the complete range of basic radio-electronic and service subjects:

1—RADIO PHYSICS COURSE

Complete basic training for beginners. Makes even the most difficult subjects easy to understand! 972 pages, 508 illus. Price \$5.00.

2—MODERN RADIO SERVICING

The 1300-page book that teaches you to work by truly professional methods. Explains all about test instruments, how to use them, circuit analysis, component replacements and dozens of other subjects. 1300 pages, 706 illus. Price \$5.00.

3—RADIO TROUBLESHOOTER'S HANDBOOK

The great Ghirardi book that cuts service time in half on most jobs. Tells what to do, exactly how to do it in making quick repairs on over 1800 specific radio models. 744 manual-size pages. \$5.00.

Let A. A. Ghirardi train you for Radio-Electronics—AT ABSOLUTE MINIMUM COST! Starting with the fundamentals of basic electricity, these 3 books take you step-by-step through the efficient radio testing, adjustment and repair procedures that mean time saving and more profitable work. Hundreds of working data on tubes, color codes, transformers, resistors capacitors, record changers and other components help you solve job snags in record time.

NEW LOW PRICE . . . Easy Terms

Bought singly, the books in this fact-packed library would cost you \$15. Under this special offer, you save \$1 and also have the privilege of paying in easy monthly installments, while you use the books. No waiting for monthly lessons. You learn fast—and you learn right!

10 DAYS' FREE EXAMINATION

Dept. RN-69, MURRAY HILL BOOKS, INC.,
232 Madison Ave., New York 16, N. Y.

Send me Ghirardi's Big-3 Radio-Electronics Library for 10 days' examination on approval. In 10 days, I will send you \$2 plus a few cents postage, and \$3.00 a month for four months—or return books postpaid. Postage paid on orders accompanied by \$2.00, same return privilege. (Books sent on approval in U. S. only.)

Name.....

Address.....

City, Zone, State.....

Occupation.....

CAN 2,710,000 TELEVISION SETS Be Sold in '49?

Sylvania's TV market analysis reveals new facts regarding customer thinking on prices, screen sizes, brands, etc.

DURING 1949, television sets will be purchased by at least 1,580,000 families, but as many as 2,710,000 sets may be sold by the industry if it improves its selling techniques.

This was one of the conclusions reached by *Sylvania Electric Products, Inc.*, researchers as a result of the latest in a series of surveys undertaken by company management to forecast demand and market conditions in the changing television field.

The interviews indicated that 2,710,000 families in television areas may purchase a set in 1949, which is a figure far in excess of the most optimistic guess now being made by the television industry. Frank Mansfield, Director of Research, explained, however, that under present conditions of salesmanship, promotion, programming, and the confusion regarding pricing, frequencies, and screen sizes, the figure of 1,580,000 should be considered the more probable.

The survey disclosed a "terrific increase in latent interest in, and knowledge of, television since a previous analysis made in 1945." At that time, about 9,603,000 families, at most, could be considered prospective owners of television sets at some time in the future. With today's findings, the number of prospects is easily projected at about 16,600,000, or an increase of around seventy per-cent. The current survey indicates that three out of four families in TV areas have purchased, intend to purchase, or are favorable toward television; whereas in 1945, less than half had a comparable interest.

The study further reveals that only eleven per-cent of the people in television areas have not seen television, indicating the great impact of the new medium. In 1945, only sixteen per-cent had seen television, as contrasted with the present-day figure of eighty-nine per-cent. This new knowledge is not merely casual, for by far the greatest bulk of people who have seen it are doing so frequently in homes of friends or relatives, in stores, and other public places.

That television has made a favorable impression on most of those who have seen it is shown by the three out of four people who expressed opinions

ranging from enthusiastic to moderately favorable. At least one member of the family is favorable in ninety-one per-cent of the total interviewed. A closer analysis of these latter figures shows that the presence of children in the family has an important effect on the interest in television; if a family has children, the chances of its being interested is about fifty per-cent greater. The husband is found to be the moving influence in most of the interested families, however, the wife being the motivating factor less often.

The 4,600,000 families who have considered purchasing television make up twenty-eight per-cent of all non-owners in television areas, and these are pretty serious about obtaining sets. The greatest part of the potential prospects, seventy-seven per-cent, earn less than \$100 a week, thus placing the future of television with the great middle-income or "mass" market, according to the survey.

When asked why they have not yet bought sets, the families considering purchase replied that they are "waiting for a cheaper set" or "I can't afford it right now." These two reasons were given by sixty-six per-cent of that group. Minor reasons given are "waiting for a larger variety of programs," and "waiting for better quality programs."

Of the twenty-eight per-cent, the "definitely interested" prospects, (4,600,000 families), those who said they would probably buy or may buy in 1949 number 2,700,000. To check the attitudes of these families, the researchers (1) found out what type of set the respondent wanted to buy, then asked what he would pay for it, and (2) showed the types of sets and screen sizes available at the "about-right" prices. The resultant figure shows 1,580,000 very good prospects for television sales in 1949.

Although the *Sylvania* interviews reveal how people think, rather than how they will finally act to affect the industry, it also indicates that improved selling—which the previous survey showed is lacking—better promotion and merchandising, and the clearing up of some confusions about television, can overcome the reasons given for not purchasing a set. —

RADIO & TELEVISION NEWS



ELECTRONIC BARGAINS for EXPERIMENTERS and HOBBYISTS

ORDER NOW ALL QUANTITIES LIMITED

PE101C BC645 POWER SUPPLY
NO. 273. Complete power supply for BC 645. Operates from 12 or 24 Volts. Supplies both AC and DC required. Shipping Wgt. 13 lbs. Each **\$3.95**

DM 35 12 VOLT DYNAMOTOR
NO. 274. New input 12 Volt at 18.7 Amperes. Supplies 675V at 275 MA or 1/2 above voltage from 6 volts. Excellent for auto use. Shipping Wgt. 11 lbs. Each **\$7.50**

HOME WORKSHOP GRINDER KIT

NO. 230. Easily assembled 110V AC or DC ball bearing fully enclosed motor from Army surplus dynamotor. Purchaser to make simple changes and shaft extensions, detailed instructions and all parts supplied. Motor approximately 5,000 R.P.M. Ideal for tool-post grinder, flexible shaft tool, model drill press, saw. Shipping Weight 6 lbs. **\$3.95**

COLLINS AUTOTUNE CONTROL HEAD

NO. 278. Brand new controls used on the ART/13, 100 Watt, Transmitter. Types 7, 8, 10, and 11 available. Get a spare while available as new cast is over \$22.00 each. Shipping Wgt. 3 lbs. Price any type (mention when ordering). Each **\$4.50**

300 MA SELENIUM RECTIFIERS
NO. 209. Rated 300 MA at 36 Volts, complete with mounting brackets. Shipping Wgt. 1 lb. **3 FOR \$1.00**

1N90 FEED THROUGH INSULATOR

NO. 276. Heavy duty feed through, 2" diameter 4" long, complete with brass hardware and gasket. Shipping Wgt. 2 lbs. **2 FOR \$1.00**

1N86 STRAIN INSULATOR

NO. 277. Husky army type 1 1/4" diameter, 5 1/4" long. Brown porcelain. Shipping Wgt. 4 lbs. **4 FOR \$1.00**

G.E. BC 306 ANTENNA TUNING UNIT

NO. 231. Matches any aerial to 150 Watt transmitter, used on BC 375. Brand new. Add postage for 20 lbs. **\$2.95**

G. E. 1,000 VOLT 350 MA DYNAMOTOR

NO. 213. An ideal dynamotor for mobile operation in taxicabs, police cars, sound systems and amateur stations. Supplies above voltage from 12 Volts or 500V. at 350 MA from 6 Volts. Complete with starting relay, and fuses. New. Our Dynamotor A. Shipping Weight 72 lbs. **\$5.95**

POWER TRANSFORMER *Specials*

NO. 226. Primary 117V. 60 cycle. Secondaries supply 746 V.C.T. at 220 MA, 6.3V. at 4.5 A., and 5V. at 4A. Will handle 13 tube radio receivers. Supply is limited, order early. Shipping Weight 11 lbs. each. **\$3.95 . . . 3 for \$9.95**

T32 TABLE MICROPHONE

NO. 210. One of the Army's best. Built by Kellogg, ideal for factory call system, public address, amateur use. Brand new in original cartons. Add postage for 5 lbs. **\$2.95**

MINIATURE ELECTRIC MOTOR

NO. 211. Tiny Delco motor only 1" x 1 1/4" x 2" 10,000 RPM. Operates from 6 to 24 V. Excellent for models. Add postage for 1 lb. **\$2.95**

OUTPUT TRANSFORMER

NO. 227. Push pull 6V6's to 6-8 ohm voice coil excellent characteristics. **3 for \$1.95**

RCA SATURABLE REACTOR TRANSFORMER

NO. 246. New RCA No. CKV30531 AC current 750 MA DC current 2 Amperes. Rated 1.75 henries. Shipping Wgt. 4 lbs. Each **\$1.00**

12.6V POWER TRANSFORMER

NO. 247. New cased 110 V 60 cy. Power Transformer. Supplies 440V C.T. at 60 MA, 6.3V at 2A., and 12.6V at 1 Amp. Excellent for military sets. Shipping Wgt. 6 lbs. Each. **\$1.95**

RCA INPUT TRANSFORMER

NO. 248. Heavy duty RCA No CKV-30529. Input has primaries 600 to 200 and 25 ohms secondary 250,000 ohms C.T. Shipping Wgt. 2 lbs. Each **\$1.00**

FEDERAL POWER TRANSFORMER

NO. 252. New cased 110V 60 cy. Power Transformer. Supplies 480V C.T. at 50 MA and 6.3 V at 2.1 Amps. A beautiful transformer. Shipping Wgt. 4 lbs. Each **\$1.50**

MILITARY POWER TRANSFORMERS

NO. 229. Convert your military receivers without rewiring the filament. "A" type supplies 500 VCT at 50 MA, 5V. at 2A. and 24V. at 1/2 A. "B" type supplies 500 VCT at 50 MA, 5V. at 2A. and 12V. at 1 Amp. State whether A or B type desired. **\$2.95** Shipping Weight 4 lbs.

WALKIE TALKIE TRANSFORMER


NO. 744. Carbon microphone input transformer and output to head-phone transformer, all in one case, excellent for building your own. Shipping Wt. 1 lb. **4 for \$1.00**

LOW PASS FILTER UNIT

NO. 637. 3000 cycle cutoff consists of 3 inductances and 4 capacitors in network, 500 ohms in and out. Excellent for clipping all frequencies above 3000 cycles. Drawn steel case, shipping Wt. 5 lbs. **\$2.50**

FM PUSH BUTTON TUNER

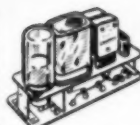NO. 224. Brand new ten push button tuning assembly from Army FM receiver. Contains 4 gang 100 MMF silver plated tuning condenser. Add postage for 10 lbs. **\$2.50** EACH



BC 746 TUNING UNIT
NO. 257. Plug in transmitter tuning unit from army Walkie Talkie. Contains antenna and tank coils, tuning condenser, transmitting and receiving crystals. Ideal transmitter foundation. Shipping Wgt. **\$1.00** 1 lb. Each (Same as above except transmitter crystal in 80 meter amateur band \$2.50 each)

T30 THROAT MICROPHONE

NO. 258. Makes excellent contact microphone for musical instrument or vibration pick-up. Shipping Wgt. 1 lb. **\$1.00** each Extension cord with switch for above **\$.50** each

BC731 CONTROL BOX

with Weston Model 476 AC Voltmeter
NO. 208. Excellent buy in motor control box. Size 8"x10"x5 1/2". Contains Weston 0-150V. AC 3 1/2" voltmeter, motor starting switch, 28 fuses all 30 Amp 110V. and 8 fuse holders. Fuses and holders alone worth the price. Shipping Weight 18 lbs. **\$7.95**

METER SPECIAL

NO. 237. Brand new DeLur Model 312 0-800 M.A. D.C. Square 3" 0-10 M.A. basic meter with built in shunt. Probably the best buy ever offered in a surplus meter. Shipping Weight 1 lb. **\$2.95**

HEARING AID HEADPHONES

NO. 216. The Army's best — eliminate flat ears and outside noise. Complete with transformer for conversion from low to high impedance. With cord and plug complete. Add postage for 1 lb. **\$1.00**

BC 451 CONTROL BOX

NO. 236. Control box for 274N transmitters. Contains proper c.w. voice switch, 4 channel switch, power switch, mike jack and telegraph key. Add postage for 2 lbs. **\$1.95**

100 MA FILTER CHOKE

NO. 641. Heavy 1.5 henry choke in drawn steel case. 50 ohm resistance, conservatively rated at 100 MA. Shipping Wt. 1 lb. **50c**

FILAMENT TRANSFORMER

NO. 922. 220V. 60 cy. primary supplies 12.6V. at 3.5 Amps, 15.6V at 1 Amp. Supplies 6.3 at 3.5 Amps and 7.8V. at 1. Amp from 110V. Shipping Wt. 8 lbs. **\$1.50**

PANEL METER

Burlington 0-300 VAC Meter
NO. 290. Model 32XA 3 1/2" round AC Voltmeter 0-300 VAC full scale. Scale also calibrated 0-600V. Bakelite case. A beautiful meter in original carton. Shipping Wt. **\$3.95**

DRIVER TRANSFORMER

NO. 651. Couples 3000 ohm plate to push pull parallel grids hermetically sealed. Ship. Wt. 1 lb. **\$1.00**

OUTPUT and MODULATION TRANSFORMER

NO. 745. Companion transformer to above driver. A push pull output, 3000 ohms to 3.2 ohm voice coil, or to 1250 ohms at 80 MA. A high quality cased unit. Shipping Wt. 2 pounds. **\$1.00**

HOW TO ORDER . . . GIVE PART NUMBER AND DESCRIPTION . . . ADD POSTAGE FOR WEIGHT SHOWN. NO ORDERS UNDER \$2.00 . . . WE WILL SHIP C.O.D.

The HEATH COMPANY
... BENTON HARBOR 15, MICHIGAN

*It's a
Natural*

BUILD YOUR OWN

Heathkit SINE AND SQUARE WAVE AUDIO GENERATOR KIT



\$34.50

*Nothing
ELSE TO BUY*

Experimenters and servicemen working with a square wave for the first time invariably wonder why it was not introduced before. The characteristics of an amplifier can be determined in seconds compared to several hours of tedious plotting using older methods. Stage by stage, amplifier testing is as easy as signal tracing. The low distortion (less than 1%) and linear output (\pm one db.) make this Heathkit equal or superior to factory built equipment selling for three or four times its price. The circuit is the popular RC tuning circuit using a four gang variable condenser. Three ranges 20-200, 200-2,000, 2,000-20,000 cycles are provided by selector switch. Either sine or square waves instantly available at slide switch. All components are of highest quality, cased 110V. 60 cycle power transformer. Mallory F.P. filter condensers, 5 tubes, calibrated 2 color panel, grey crackle aluminum cabinet. The detailed instructions make assembly an interesting and instructive few hours. Shipping Wt., 15 lbs.

New Heathkit TELEVISION ALIGNMENT GENERATOR KIT



\$39.50

*Nothing
ELSE TO BUY*

Everything you want in a television alignment generator. A wide band sweep generator covering all FM and TV frequencies 0-110 and 165 to 220 Megacycles, a marker indicator covering 19 to 43 Megacycles, AM modulation for RF alignment—variable calibrated sweep width 0-30 Mc.—mechanical driven inductive sweep. Husky 110V. 60 cycle power transformer operated—step type output attenuator with 10,000 to 1 range—high output on all ranges—band switching for each range—vernier driven main calibrated dial with over 45 inches of calibration—vernier driven calibrated indicator marker tuning. Large grey crackle cabinet 16 1/8" x 10 3/8" x 7-3/16". Phase control for single trace adjustment. Uses four high frequency triodes plus 5Y3 rectifier—split stator tuning condensers for greater efficiency and accuracy at high frequencies—this Heathkit is complete and adequate for every alignment need and is supplied with every part—cabinet—calibrated panel—all coils and condensers wound, calibrated and adjusted. Tubes, transformer, test leads—every part with instruction manual for assembly and use. Actually three instruments in one—TV sweep generator—TV AM generator and TV marker indicator. Also covers FM band.

1949 MODEL Heathkit VACUUM TUBE VOLTMETER KIT

Features

New 200 ua Meter

24 Ranges

New Accessory H.V. Probe makes
Heathkit a kilovoltmeter. (Extra)

New Accessory R.F. Probe extends range
to 100 megacycles. (Extra)

A new Model V2 Heathkit VTVM with new 200 microampere meter, four additional ranges—full scale linear ranges on both AC and DC of 0-3V., 10V., 30V., 100V., 300V. and 1,000V. Accessory probe listed elsewhere in ad extends voltage range to 3,000 and 10,000 volts D.C. New model has greater sensitivity, stability and accuracy—still the highest quality features—shatterproof plastic full view meter face—automatic meter protection, push pull electronic voltmeter circuit, linear scales—db. scale—ohmmeter measures 1/10 ohm to 1 billion ohms with internal battery—isolated DC test prod for dynamic measurements—11 megohm input resistance on DC—AC uses electronic rectification with 6H6 tube. All these features and still the amazing price of only \$24.50. Comes complete with cabinet—panel—three tubes—new Mallory switches—test prods and leads, 1% ceramic divider resistors and all other parts. Complete instruction manual for assembly and use. Better start your laboratory with this precision instrument. Shipping Wt., 8 lbs.




\$24.50

Heathkit RF SIGNAL GENERATOR KIT


\$19.50

Nothing ELSE TO BUY

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110V. 60 cycle transformer operated power supply. 400 cycle audio available for modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Shipping Wt., 4 1/2 lbs.

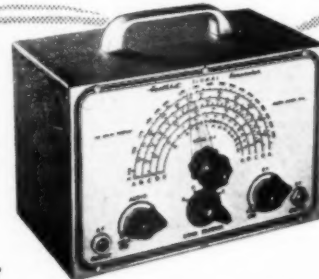

New Heathkit FM TUNER KIT

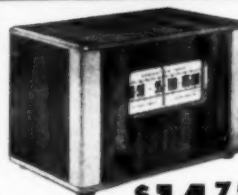

\$14.75

CABINET EXTRA

A truly fine FM Tuner with the coils ready wound, all alignment completed—all that is necessary is wiring and it's ready to play—uses super regenerative circuit—110V. 60 cycle transformer operated—two gang tuning condenser—slide rule calibrated dial—two tubes—complete instructions including pictorial enable even beginners to build successfully. Shipping Wt., 4 lbs.

Beautiful mahogany cabinet for FM Tuner (shown above) extra \$3.75




The HEATH COMPANY

... BENTON HARBOR 15,

MICHIGAN

with **HEATHKITS...**

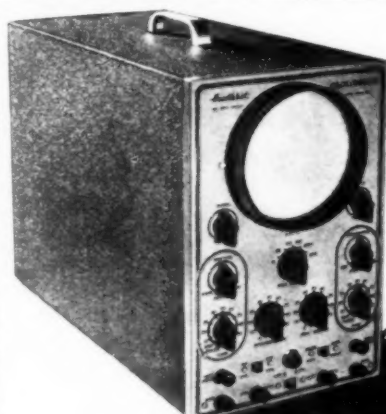HAVE THE FUN
Save THE DIFFERENCE
WITH HEATHKITS



Heathkit 5" OSCILLOSCOPE KIT

Features

Instant switching to plates or amplifier from front panel.
Sweep generator supplying variable sweep 15 cycles to 30,000 cycles.
All controls on front panel.
Cased electrostatically shielded 110V. 60 cycle power transformer.
AC test voltage on front panel.
External synchronization post on front panel.
Deflection sensitivity .65V. per inch full gain.
Frequency response $\pm 20\%$ from 50 cycles to 50 Kc.
Input impedance 1 Megohm and 50 MMF.

The Heathkit 5" Oscilloscope fulfills every servicing need. The husky cased power transformer supplies 1100 Volts negative and 350 Volts positive. Tubes supplied are two 6SJ7 amplifiers, 884

sweep generator, two 5Y3 rectifiers and 5BP1 CR tube. Grey crackle aluminum cabinet and beautiful grey and maroon panel. Chassis especially designed for easy assembly.


An oscilloscope provides endless sources of experimentation in radio, electronics, medicine and scientific research.

Detailed instructions make assembly fun and instructive. Shipping Wt., 24 lbs. Express only.

Nothing
ELSE
TO BUY

\$39.50

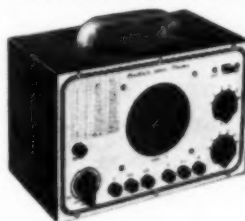NEW Heathkit SIGNAL TRACER AND UNIVERSAL TEST SPEAKER KIT



\$19.50

Nothing
ELSE
TO BUY

The popular Heathkit signal tracer has now been combined with a universal test speaker at no increase in price. The same high quality tracer follows signal from antenna to speaker—locates intermittents—defective parts quicker—saves valuable service time—gives greater income per service hour. Works equally well on broadcast—FM or TV receivers. The test speaker has assortment of switching ranges to match push pull or single output impedance. Also test microphones, pickups—PA systems—comes complete—cabinet—110V. 60 cycle power transformer—tubes, test probe, all parts and detailed instructions for assembly and use. Shipping Wt., 8 lbs.

Heathkit

ELECTRONIC SWITCH KIT

DOUBLES THE UTILITY OF ANY SCOPE

\$34.50

Nothing
ELSE TO BUY



An electronic switch used with any oscilloscope provides two separately controllable traces on the screen. Each trace is controlled independently and the position of the traces may be varied. The input and output traces of an amplifier may be observed one beside the other or one directly over the other illustrating perfectly any change occurring in the amplifier. Distortion—phase shift and other defects show up instantly, 110V. 60 cycle transformer operated. Uses 5 tubes (1 6X5, 2 6SN7's, 2 6SJ7's). Has individual gain controls, positioning control and coarse and fine sweeping rate controls. The cabinet and panel match all other Heathkits. Every part supplied including detailed instructions for assembly and use. Shipping Wt., 11 lbs.

Heathkit CONDENSER CHECKER KIT

\$19.50

Nothing
ELSE
TO BUY



Features

- Bridge type circuit
- Magic eye indicator
- 110 V. transformer operated
- All scales on panel
- Power factor scale
- Measures resistance
- Measures leakage
- Checks paper-mica-electrolytics

Checks all types of condensers, paper-mica-electrolytic-ceramic over a range of .00001 MFD to 1000 MFD. All on readable scales that are read direct from the panel. NO CHARTS OR MULTIPLIERS NECESSARY. A condenser checker anyone can read without a college education. A leakage test and polarizing voltage for 20 to 500 volts provided. Measures power factor of electrolytics between 0% and 50%. 110V. 60 cycle transformer operated complete with rectifier and magic eye tubes, cabinet, calibrated panel, test leads and all other parts. Clear detailed instructions for assembly and use. Why guess at the quality and capacity of a condenser when you can know for less than a twenty dollar bill. Shipping Wt., 7 lbs.



The HEATH COMPANY

... BENTON HARBOR 15, MICHIGAN

Heathkits
ARE COMPLETE

HEATHKITS are QUALITY



Only
\$69.50

Nothing ELSE TO BUY

New Heathkit IMPEDANCE BRIDGE KIT

A LABORATORY INSTRUMENT NOW WITHIN
THE PRICE RANGE OF ALL

Measures Inductance from 10 microhenries to 100 henries capacitance from .00001 MFD to 1000 MFD. Resistance from .01 ohms to 10 megohms. Dissipation factor from .001 to 1. "Q" from 1 to 1000.

Ideal for schools, laboratories, service shops, serious experimentors.


An impedance bridge for everyone — the most useful instrument of all, which heretofore has been out of the price range of serious experimentors and service shops. Now at the lowest price possible. All highest quality parts. General Radio main calibrated control. General Radio 1000 cycle hummer. Mallory ceramic switches with 60 degree indexing — 200 micro-amp zero center galvanometer — 1/2 of 1% ceramic non-inductive decade resistors. Professional type binding posts with standard

3/4" centers. Beautiful birch cabinet. Directly calibrated "Q" and dissipation factor scales. Ready calibrated capacity and inductance standards of Silver Mica, accurate to 1/2 of 1% and with dissipation factors of less than 30 parts in one million. Provisions on panel for external generator and detector. Measure all your unknowns the way laboratories do — with a bridge for accuracy and speed.

Internal 6 volt battery for resistance and hummer operation. Circuit utilizes Wheatstone, Hay and Maxwell circuits for different measurements. Supplied complete with every quality part — all calibrations completed and instruction manual for assembly and use. Deliveries are limited. Shipping weight, approximately 15 lbs.

Heathkit HIGH FIDELITY AMPLIFIER KIT

Build this high fidelity amplifier and save two-thirds of the cost. 110V. 60 cy. transformer operated. Push pull output using 1619 tubes (military type 6L6's), two amplifier stages using a dual triode (6SL7), as a phase inverter give this amplifier a linear reproduction equal to amplifiers selling for ten times this price. Every part supplied; punched and formed chassis, transformers (including quality output to 3-8 ohm voice coil), tubes, controls, and complete instructions. Add postage for 20 lbs.

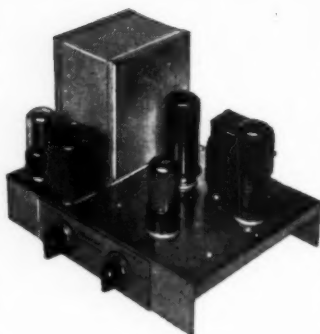

\$14.95

Nothing ELSE TO BUY

12" PM Speakers for above \$6.95

Mahogany Speaker Cabinet, 14 1/2" x 14 1/2" x 8" \$8.75

New Heathkit BATTERY ELIMINATOR KIT


Now a bench 6 Volt power supply kit for all auto radio testing. Supplies 5 - 7 1/2 Volts at 10 Amperes continuous or 15 Amperes intermittent. A well filtered rugged power supply uses heavy duty selenium rectifier, choke input filter with 4,000 MFD of electrolytic filter. 0 - 15 Volt meter indicates output. Output variable in eight steps. Excellent for demonstrating auto radios. Ideal for servicing — can be lowered to find sticky vibrators or stepped up to equivalent of generator overload — easily constructed in less than two hours. Complete in every respect. Shipping Wt., 18 lbs.



\$22.50

Nothing
ELSE TO BUY

Heathkit 3-TUBE ALL WAVE RADIO KIT

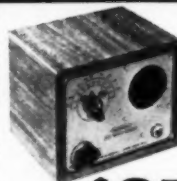

\$8.75

CABINET EXTRA

An ideal way to learn radio. This kit is complete ready to assemble, with tubes and all other parts. Operates from 110V AC. Simple, clear detailed instructions make this a good radio training course. Covers regular broadcasts and short wave bands. Plug-in coils. Regenerative circuit. Operates loud speaker. Shipping Wt., 3 lbs.

H530 Headphones per set \$1.00
2 1/2" Permanent Magnet Loudspeaker 1.95
Mahogany Cabinet 2.95



The **HEATH COMPANY**

... BENTON HARBOR 15, MICHIGAN


RADIO & TELEVISION NEWS

TITONE
picks
up
profit
NOW!

**Now! A
\$10 SALE**

**for every
record-player
in your area!**

LIST PRICE \$7.50

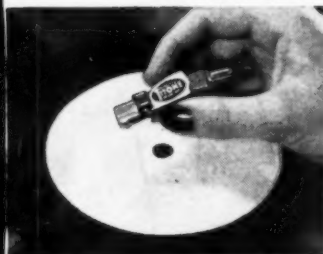

**SELL NEW
TITONE
PICKUP
to every customer!**

Here's a way to quick profit from every player owner who visits your shop! Have your salesmen "plug" it on every service call! First basic pick-up advance in over 10 years—the original piezoelectric ceramic pickup, made by SONOTONE, famous makers of hearing aids and miniature tubes!

- SELLS ITSELF IN A 2-TO-5-MINUTE CALL! Fits all tone arms. Let all your customers hear TITONE. They'll say "SOLD!" because—
- TRANSCRIPTION TONE QUALITY! Full frequency to 10,000 cycles! Real high fidelity! Bell-like supertone makes even old players thrilling!
- SURE-FIRE IN HUMID CLIMATES! Utterly unaffected by climate, moisture, fungus! Booms sales, wins back customers.
- DOUBLES RECORD LIFE AND PLEASURE! Gives "ordinary" records sparkling quality—revives worn favorites. Will play down to 1/2 normal pressure. NO "needle talk"!
- RUGGED! PERMANENT! No crystals, magnets, filaments to fail! No pre-amplifiers. Ceramic TITONE performs perfectly for years!


**NO TONE LIKE
TITONE**
CALL YOUR JOBBER—
or write now to
SONOTONE, Box T-2 Elmsford, N. Y.

DO YOU KNOW?

By DAVID SCOTT

63. Draw a simple schematic diagram of an electron deflection system.

A.

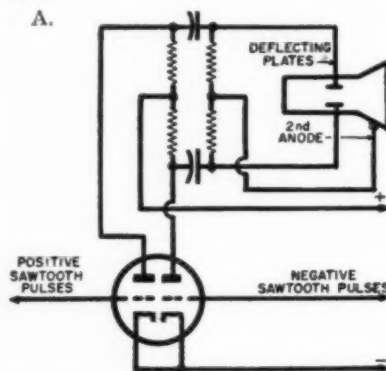


64. What are some of the important design considerations in magnetic deflection systems?

A. In magnetic deflection systems the same design considerations as in electric deflections systems are necessary. (See question 61). However, added attention must be given to insulation of the coils due to the high peak voltage surges which develop and the distributed capacitance which lends itself to the formation of spurious oscillations.

65. Draw a simple schematic diagram illustrating and explaining how undesired spurious oscillations may be damped out of magnetic deflection systems.

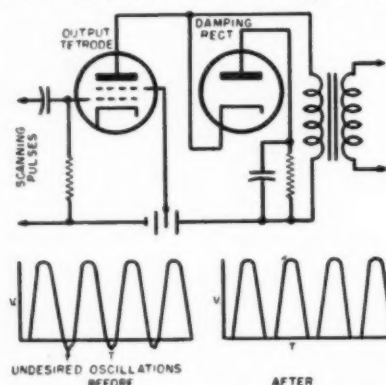A. Spurious oscillations due to the inductance of deflection coils, their distributed capacitance, and high peak voltage surges, which give rise to irregularities in the scanning motion, can be eliminated with a damping circuit, i.e., a rectifier tube in series with a shunt capacitance resistance combination, the whole circuit being shunted across the primary or secondary of the transformer. The rectifier has



a very low impedance to the portion of the oscillation which makes its anode positive, and this energy is

absorbed in the tube. The waveform is thereby damped so far as the high-frequency oscillations are concerned, and the current has the required linear form.

66. What is the function of the discharge tube in a saw-tooth generator system?


A. The discharge tube is the part of the saw-tooth generator which suddenly removes the charge from the condenser across which the saw-tooth wave is built up.

67. What is the function of an impulse generator?

A. The impulse generator causes the discharge tube to act by the application of a sudden positive voltage pulse on its grid. If this pulse is very sharp, i.e., of large amplitude and small duration, the discharge tube will assume a correspondingly low impedance for a comparatively short time.


68. Draw a simple diagram of a dynatron.

A.

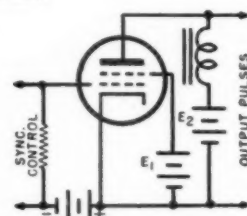


69. Draw a simple diagram of a multivibrator.

A.

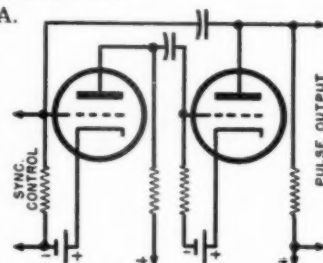

70. Draw a simple diagram of a blocking oscillator.

A.

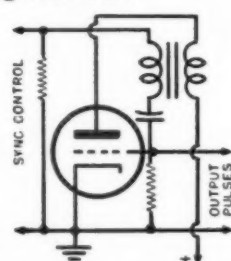

71. What are the two types of frequencies in sync action?

A. In sync action, there is a free frequency and the sync frequency. (To be continued)

ST. GEORGE WIRE RECORDER MECHANISM \$22.95



Majestic Wire Recording Radio
Chassis, St. George Mechanism,
Mike, Etc., As Pictured \$49.95

★ REGULAR \$75.00 LIST ★ BRAND NEW

Brand new Wire Recorder. Play back mechanism. Same as those used on the majestic radio wire recorder. This unit has 78 RPM Turntable for recording on wire from a phono record. Records up to 1 Hour on standard Webster Recording Wire. This wire recording mechanism is offered to you at a fraction of the regular net. Space required 9x13x3 1/2" below board. Each unit is furnished with Oscillator Coil and a diagram to show how to wire a 2-Tube Osc. (We furnish special Osc. coil not small part for Oscillator) and how to adapt the wire recorder to any radio or amplifier. Ready punched for crystal phono pick up. St. George wire record head with Osc. Coil and diagram. Stock No. X93, weight 15 lbs. Net \$22.95.
Crystal Pickup Arm for Playing 78 RPM record \$2.95 extra.
Webster Recording Wire, 15 Min. \$1.30, 30 Min. \$1.95, 1 Hr. \$3.25. Bullet Stand Shure Crystal Mike \$4.95.

★ RECORDS FROM 78RPM RECORDS

This complete radio Wire Recorder combination includes the St. George Wire Recorder Mechanism, Majestic Broadcast Receiver Chassis and Wire Recording oscillator. The receiver is a 2 Gang Superhet with 2 slide rule dial 1120KHz. Tube complement 12SA7, 12BK7, 12SJ7, 12SQ7, 50L6, 50B5, 35W4. The oscillator for wire recording is built on a 500 Ohm to 5000 Ohm variable capacitor. Each unit has plugs and sockets for easy quick connection. Brand new wire in the majestic factory for use in their \$200.00 radio wire recorder. Everything you need to record on wire from the radio, mike or phono record is furnished. Crystal mike, 15 Minute Spool of Wire, Majestic wire recording radio, 6" speaker and St. George Wire Recorder Play back Mechanism, all for only \$49.95. Weight 30 lbs. Extra recording wire, 15 Min. \$1.30, 30 Min. \$1.95, 1 Hr. \$3.25.

100 RADIO TUBES \$29.95

250,000 Tubes for fast sale. Tremendous value. Tubes up to \$3.00 list. 100 Cartoned and branded Hyvac Miniature Tubes for \$29.95. Over a million sold. Guaranteed full replacement. 34c Each in smaller quantities.

12A5	12BE8	12AU8	65U7	12S8
12A6	12AT6	12BF6	6AQ5	9001
12A7	35W4	6BA6	6AQ8	9002
38A	35B5	6BE6	6C4	6BH6
155	50B5	6AT6	6X4	11723
39A	12AT7	6AL5	6A5	1074
30A	12AU7	6AQ3	6AG3	6BJ6
36A	12AX7	6BF6	6AU6	6AT6
12BA6	12BA7	6AU7	6BG6	

\$2995

for 100

34c each

Popular GT Tubes, individually cartoned and branded Hyvacs, \$35.00 per hundred, 34c Each in smaller quantities.
125F7 125N7 32L7 39c each
65J7 65L7 35c each
125J7 35c each
125K7 35c each
125L7 35c each
125M7 35c each
125N7 35c each
125O7 35c each
125P7 35c each
125Q7 35c each
125R7 35c each
125S7 35c each
125T7 35c each
125U7 35c each
125V7 35c each
125W7 35c each
125X7 35c each
125Y7 35c each
125Z7 35c each
126A7 35c each
126B7 35c each
126C7 35c each
126D7 35c each
126E7 35c each
126F7 35c each
126G7 35c each
126H7 35c each
126I7 35c each
126J7 35c each
126K7 35c each
126L7 35c each
126M7 35c each
126N7 35c each
126O7 35c each
126P7 35c each
126Q7 35c each
126R7 35c each
126S7 35c each
126T7 35c each
126U7 35c each
126V7 35c each
126W7 35c each
126X7 35c each
126Y7 35c each
126Z7 35c each
127A7 35c each
127B7 35c each
127C7 35c each
127D7 35c each
127E7 35c each
127F7 35c each
127G7 35c each
127H7 35c each
127I7 35c each
127J7 35c each
127K7 35c each
127L7 35c each
127M7 35c each
127N7 35c each
127O7 35c each
127P7 35c each
127Q7 35c each
127R7 35c each
127S7 35c each
127T7 35c each
127U7 35c each
127V7 35c each
127W7 35c each
127X7 35c each
127Y7 35c each
127Z7 35c each
128A7 35c each
128B7 35c each
128C7 35c each
128D7 35c each
128E7 35c each
128F7 35c each
128G7 35c each
128H7 35c each
128I7 35c each
128J7 35c each
128K7 35c each
128L7 35c each
128M7 35c each
128N7 35c each
128O7 35c each
128P7 35c each
128Q7 35c each
128R7 35c each
128S7 35c each
128T7 35c each
128U7 35c each
128V7 35c each
128W7 35c each
128X7 35c each
128Y7 35c each
128Z7 35c each
129A7 35c each
129B7 35c each
129C7 35c each
129D7 35c each
129E7 35c each
129F7 35c each
129G7 35c each
129H7 35c each
129I7 35c each
129J7 35c each
129K7 35c each
129L7 35c each
129M7 35c each
129N7 35c each
129O7 35c each
129P7 35c each
129Q7 35c each
129R7 35c each
129S7 35c each
129T7 35c each
129U7 35c each
129V7 35c each
129W7 35c each
129X7 35c each
129Y7 35c each
129Z7 35c each
130A7 35c each
130B7 35c each
130C7 35c each
130D7 35c each
130E7 35c each
130F7 35c each
130G7 35c each
130H7 35c each
130I7 35c each
130J7 35c each
130K7 35c each
130L7 35c each
130M7 35c each
130N7 35c each
130O7 35c each
130P7 35c each
130Q7 35c each
130R7 35c each
130S7 35c each
130T7 35c each
130U7 35c each
130V7 35c each
130W7 35c each
130X7 35c each
130Y7 35c each
130Z7 35c each
131A7 35c each
131B7 35c each
131C7 35c each
131D7 35c each
131E7 35c each
131F7 35c each
131G7 35c each
131H7 35c each
131I7 35c each
131J7 35c each
131K7 35c each
131L7 35c each
131M7 35c each
131N7 35c each
131O7 35c each
131P7 35c each
131Q7 35c each
131R7 35c each
131S7 35c each
131T7 35c each
131U7 35c each
131V7 35c each
131W7 35c each
131X7 35c each
131Y7 35c each
131Z7 35c each
132A7 35c each
132B7 35c each
132C7 35c each
132D7 35c each
132E7 35c each
132F7 35c each
132G7 35c each
132H7 35c each
132I7 35c each
132J7 35c each
132K7 35c each
132L7 35c each
132M7 35c each
132N7 35c each
132O7 35c each
132P7 35c each
132Q7 35c each
132R7 35c each
132S7 35c each
132T7 35c each
132U7 35c each
132V7 35c each
132W7 35c each
132X7 35c each
132Y7 35c each
132Z7 35c each
133A7 35c each
133B7 35c each
133C7 35c each
133D7 35c each
133E7 35c each
133F7 35c each
133G7 35c each
133H7 35c each
133I7 35c each
133J7 35c each
133K7 35c each
133L7 35c each
133M7 35c each
133N7 35c each
133O7 35c each
133P7 35c each
133Q7 35c each
133R7 35c each
133S7 35c each
133T7 35c each
133U7 35c each
133V7 35c each
133W7 35c each
133X7 35c each
133Y7 35c each
133Z7 35c each
134A7 35c each
134B7 35c each
134C7 35c each
134D7 35c each
134E7 35c each
134F7 35c each
134G7 35c each
134H7 35c each
134I7 35c each
134J7 35c each
134K7 35c each
134L7 35c each
134M7 35c each
134N7 35c each
134O7 35c each
134P7 35c each
134Q7 35c each
134R7 35c each
134S7 35c each
134T7 35c each
134U7 35c each
134V7 35c each
134W7 35c each
134X7 35c each
134Y7 35c each
134Z7 35c each
135A7 35c each
135B7 35c each
135C7 35c each
135D7 35c each
135E7 35c each
135F7 35c each
135G7 35c each
135H7 35c each
135I7 35c each
135J7 35c each
135K7 35c each
135L7 35c each
135M7 35c each
135N7 35c each
135O7 35c each
135P7 35c each
135Q7 35c each
135R7 35c each
135S7 35c each
135T7 35c each
135U7 35c each
135V7 35c each
135W7 35c each
135X7 35c each
135Y7 35c each
135Z7 35c each
136A7 35c each
136B7 35c each
136C7 35c each
136D7 35c each
136E7 35c each
136F7 35c each
136G7 35c each
136H7 35c each
136I7 35c each
136J7 35c each
136K7 35c each
136L7 35c each
136M7 35c each
136N7 35c each
136O7 35c each
136P7 35c each
136Q7 35c each
136R7 35c each
136S7 35c each
136T7 35c each
136U7 35c each
136V7 35c each
136W7 35c each
136X7 35c each
136Y7 35c each
136Z7 35c each
137A7 35c each
137B7 35c each
137C7 35c each
137D7 35c each
137E7 35c each
137F7 35c each
137G7 35c each
137H7 35c each
137I7 35c each
137J7 35c each
137K7 35c each
137L7 35c each
137M7 35c each
137N7 35c each
137O7 35c each
137P7 35c each
137Q7 35c each
137R7 35c each
137S7 35c each
137T7 35c each
137U7 35c each
137V7 35c each
137W7 35c each
137X7 35c each
137Y7 35c each
137Z7 35c each
138A7 35c each
138B7 35c each
138C7 35c each
138D7 35c each
138E7 35c each
138F7 35c each
138G7 35c each
138H7 35c each
138I7 35c each
138J7 35c each
138K7 35c each
138L7 35c each
138M7 35c each
138N7 35c each
138O7 35c each
138P7 35c each
138Q7 35c each
138R7 35c each
138S7 35c each
138T7 35c each
138U7 35c each
138V7 35c each
138W7 35c each
138X7 35c each
138Y7 35c each
138Z7 35c each
139A7 35c each
139B7 35c each
139C7 35c each
139D7 35c each
139E7 35c each
139F7 35c each
139G7 35c each
139H7 35c each
139I7 35c each
139J7 35c each
139K7 35c each
139L7 35c each
139M7 35c each
139N7 35c each
139O7 35c each
139P7 35c each
139Q7 35c each
139R7 35c each
139S7 35c each
139T7 35c each
139U7 35c each
139V7 35c each
139W7 35c each
139X7 35c each
139Y7 35c each
139Z7 35c each
140A7 35c each
140B7 35c each
140C7 35c each
140D7 35c each
140E7 35c each
140F7 35c each
140G7 35c each
140H7 35c each
140I7 35c each
140J7 35c each
140K7 35c each
140L7 35c each
140M7 35c each
140N7 35c each
140O7 35c each
140P7 35c each
140Q7 35c each
140R7 35c each
140S7 35c each
140T7 35c each
140U7 35c each
140V7 35c each
140W7 35c each
140X7 35c each
140Y7 35c each
140Z7 35c each
141A7 35c each
141B7 35c each
141C7 35c each
141D7 35c each
141E7 35c each
141F7 35c each
141G7 35c each
141H7 35c each
141I7 35c each
141J7 35c each
141K7 35c each
141L7 35c each
141M7 35c each
141N7 35c each
141O7 35c each
141P7 35c each
141Q7 35c each
141R7 35c each
141S7 35c each
141T7 35c each
141U7 35c each
141V7 35c each
141W7 35c each
141X7 35c each
141Y7 35c each
141Z7 35c each
142A7 35c each
142B7 35c each
142C7 35c each
142D7 35c each
142E7 35c each
142F7 35c each
142G7 35c each
142H7 35c each
142I7 35c each
142J7 35c each
142K7 35c each
142L7


FAMOUS CAPEHART-2 POST AUTOMATIC RECORD CHANGER \$19.95

★ THIS IS THE SAME CHANGER INCORPORATED IN THE \$600.00 CAPEHART RADIOS

★ FURNISHED WITH EXTRA TONE ARM AND THREE CARTRIDGES, CRYSTAL V.R. AND TRUE TIMBER

★ NOW YOU CAN COMPARE ALL CARTRIDGES AT LOW COST TO YOU

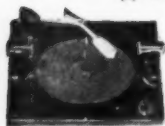★ WE BOUGHT A SOLID CARLOAD TO BE ABLE TO MAKE THIS LOW \$19.95 PRICE



CAPEHART TWIN POST \$19.95

We made an outstanding purchase of genuine Capehart Twin Post Automatic Record Changers. This is the changer that was incorporated in the famous Capehart Radios selling in the \$600.00 bracket. Do not confuse this with ordinary \$20.00 or \$30.00 changers. This one is of super heavy-duty construction. Made of heavy parts with easy accessible adjustments. Base size 14 1/2 x 14 1/2. Positive action twin post design plays 10-12" or 12-10" 78 RPM records automatically. We are passing our lucky purchase on to you.

This changer is equipped with the True Timber transparent plug in cartridge with permanent needle. (Requires same gain as Variable Reluctance Cartridge.) We also offer at no added cost to you an extra tone arm with two spare cartridges. The famous Caltron Variable Reluctance Broadband quality

cartridge as well as a standard output crystal cartridge. This deal gives you a changer with all types of cartridges. Only a limited quantity of these changer deals are available, so get your order in now. Schematic diagrams furnished for all types of cartridge inputs. You get Capehart Two Post Changer with True Timber Cartridge, extra tone arm with Caltron Variable Reluctance Cartridge and Standard Output Crystal Cartridge all for \$19.95. Shipping weight 23 lbs. If you desire we will throw in a General Electric RPX-010 Variable Reluctance Cartridge for \$2.50 extra. Capehart Changer with True Timber Cartridge, extra arm, Crystal & VR Cartridge, \$19.95; with RPX-010 G.E. Cartridge added, \$22.45 net.



ELECTROLYTICS UPRIGHT ALUMINUM CANS

Save half on these genuine aluminum can upright screw mounting. Fresh Stock One year guarantee.

RS213	8 mfd. 450V. 1 x2 1/2"	\$0.49
RS215	12 mfd. 450V. 1 x2 1/2"	.54
RS223	30 mfd. 450V. 1 1/2 x3"	.59
RS262	8x8 mfd. 450V. 1 1/2 x3 1/2"	.59

Type TCS Aluminum tubes with paper insulating tubes. Separate sections with lugs. Buy a good supply of these at over half off. Fresh stock. One year guarantee.

TC845	20x20 mfd. 150V. 1x2 1/2"	\$0.39
TC847	30x30 mfd. 150V. 1x2 1/2"	.44
TC848	40x40 mfd. 150V. 1x2 1/2"	.49
TC852	10x10 mfd. 250V. 1x2 1/2"	.29
TC855	20x20 mfd. 250V. 1x2 1/2"	.34

Type TCD Dual with Common Neg. and 3' Leads.

TC'D55	20x20 mfd. 250V. 1x2"	\$0.34
TC'D52	10x10 mfd. 250V. 1x2"	.29
TC'D65	20x20 mfd. 350V. 1x3"	.34

St., 2N, 3N, 4N. Cardboard Tubes with metal tabs for vertically or under chassis mounting. Fresh Stock. One year guarantee.

ST595	8 mfd. 450V. 1/2 x2 1/2"	\$0.29
ST597	16 mfd. 450V. 1 x2 1/2"	.34
ST598	20 mfd. 450V. 1x2 1/2"	.44
ST599	30 mfd. 450V. 1x3 1/2"	.49
2N500	20x20 mfd. 150V. 1x2 1/2"	.49
2N518	8x8 mfd. 450V. 1x2 1/2"	.49
2N556	30x30 mfd. 150V. 1x2 1/2"	.44
3N533	30x30 mfd. 150V. 20x25V.	.54
3N579	8x8 mfd. 450V. 20x25V.	.54
	1 1/2 x2 1/2"	
3N584	8x8x8 mfd. 450V. 1 1/2 x2 1/2"	.69

GENERAL ELECTRIC RPX-010

REGULAR \$7.95 LIST VARIABLE RELUCTANCE PICK-UP CARTRIDGE ON SALE FOR \$2.95

The widely publicized and nationally advertised General Electric RPX-010 Variable Reluctance pick-up Cartridge for standard 78 RPM records. Permanent sapphire needle. Made to sell to the dealer at \$4.45. A lucky purchase! We are passing this low price of only \$2.95. Packed 18 to a master carton. Better stock up now.

Kit to build a G.E. type pre-amplifier with wiring diagram and 6SC7 tube, \$2.49 extra. \$2.95. A lucky purchase! We are passing this low price of only \$2.95. Packed 18 to a master carton. Better stock up now.

Crystal Cartridges

We have 'em, \$1.39 and UP EVERY XTAL GUARANTEED

3 Cartridges—95% ON Your Need \$1.79 Each, 10 for \$15.00

Astatic L-40 or equal, with rest clip, replaces the following: L-41, L-75, Webster C-5, E-9, P-3, N-5, or N-7. \$1.79 each; 10 for \$15.00.

Astatic L-70 or equal, with rest clip, replaces the following: L-71, L-76, or Shure P-88, P-89, W-40, W-59 or Webster, IX-6, IX-2, N-4, E-4, etc. \$1.79 each; 10 for \$15.00.

Astatic L-72 or equal, with rest clip, replaces the following: L-24, L-46, Shure P-89 and Webster, N10P5, a 3 Volt output that will drive single tube record players and put extra power in any player. The most universal crystal built. \$1.79 each; 10 for \$15.00.

Caltron V.R. Cartridge, \$2.95

Caltron Variable Reluctance Standard size cartridge as used in broadcast stations. Has permanent needle. A \$15.00 cartridge for only \$2.95.

Micro Groove pick-up with permanent needle for L. P. Records, \$3.95.

COMPLETE PICK-UP ARM, \$1.95.

Standard plastic pick-up with 3 1/2 Volt Cartridge, Webster made, \$1.95.

Standard pick-up, light weight, with either 1 Volt or 3 1/2 Volt Cartridge, \$2.29.

Micro Groove pick-up with permanent needle for L. P. Records, \$3.95.

Solar Wet Electrolytics

Genuine Solar Screw Mounting Wet Electrolytics.

8 mfd. 500 Volt wet. Solar.....\$0.87

16 mfd. 500 Volt wet. Solar.....1.23

20 mfd. 500 Volt wet. Solar.....1.32

8 mfd. 600 Volt wet. Solar.....1.32

16 mfd. 600 Volt wet. Solar.....1.80



TYPE "AT" N.U. TUBULAR ELEC. ALUMINUM WITH SEALED ENDS

National Union Type AT Electrolytic. Housed in sealed metal tubes in spun-end cardboard sleeves. Bare wire leads. Standard package of 10 condensers. Save over half. This is your every day need in condensers. One-year guarantee.

AT 10 MFD.	25 Volt	11/16x1 1/4"	15c
AT 25 MFD.	25 Volt	11/16x1 3/8"	20c
AT 50 MFD.	25 Volt	11/16x1 3/8"	20c
AT 100 MFD.	25 Volt	11/16x1 3/8"	25c

AT 5 MFD.	50 Volt	11/16x1 3/8"	10c
AT 10 MFD.	50 Volt	11/16x1 3/8"	15c
AT 25 MFD.	50 Volt	11/16x1 3/8"	20c
AT 50 MFD.	50 Volt	11/16x1 3/8"	20c
AT 100 MFD.	50 Volt	11/16x1 3/8"	25c

AT 4 MFD.	150 Volt	11/16x1 3/8"	10c
AT 8 MFD.	150 Volt	11/16x1 3/8"	15c
AT 12 MFD.	150 Volt	11/16x1 3/8"	20c
AT 16 MFD.	150 Volt	11/16x1 3/8"	25c
AT 20 MFD.	150 Volt	11/16x1 3/8"	25c
AT 24 MFD.	150 Volt	11/16x1 3/8"	25c
AT 30 MFD.	150 Volt	11/16x1 3/8"	30c
AT 40 MFD.	150 Volt	11/16x1 3/8"	35c
AT 50 MFD.	150 Volt	11/16x1 3/8"	35c
AT 80 MFD.	150 Volt	11/16x1 3/8"	35c

AT 8 MFD.	250 Volt	11/16x1 3/8"	20c
AT 16 MFD.	250 Volt	11/16x1 3/8"	25c
AT 20 MFD.	250 Volt	11/16x1 3/8"	25c
AT 24 MFD.	250 Volt	11/16x1 3/8"	25c
AT 30 MFD.	250 Volt	11/16x1 3/8"	30c
AT 40 MFD.	250 Volt	11/16x1 3/8"	30c
AT 50 MFD.	250 Volt	11/16x1 3/8"	30c

AT 4 MFD.	450 Volt	13/16x1 3/8"	20c
AT 8 MFD.	450 Volt	13/16x1 3/8"	20c
AT 12 MFD.	450 Volt	13/16x1 3/8"	20c
AT 16 MFD.	450 Volt	13/16x1 3/8"	20c
AT 20 MFD.	450 Volt	13/16x1 3/8"	20c
AT 24 MFD.	450 Volt	13/16x1 3/8"	20c
AT 30 MFD.	450 Volt	13/16x1 3/8"	20c
AT 40 MFD.	450 Volt	13/16x1 3/8"	20c
AT 50 MFD.	450 Volt	13/16x1 3/8"	20c
AT 80 MFD.	450 Volt	13/16x1 3/8"	20c

AT 4 MFD.	450 Volt	13/16x1 3/8"	25c
AT 8 MFD.	450 Volt	13/16x1 3/8"	25c
AT 12 MFD.	450 Volt	13/16x1 3/8"	25c
AT 16 MFD.	450 Volt	13/16x1 3/8"	25c
AT 20 MFD.	450 Volt	13/16x1 3/8"	25c
AT 24 MFD.	450 Volt	13/16x1 3/8"	25c
AT 30 MFD.	450 Volt	13/16x1 3/8"	25c
AT 40 MFD.	450 Volt	13/16x1 3/8"	25c
AT 50 MFD.	450 Volt	13/16x1 3/8"	25c
AT 80 MFD.	450 Volt	13/16x1 3/8"	25c

AT 4 MFD.	450 Volt	13/16x1 3/8"	30c
AT 8 MFD.	450 Volt	13/16x1 3/8"	30c
AT 12 MFD.	450 Volt	13/16x1 3/8"	30c
AT 16 MFD.	450 Volt	13/16x1 3/8"	30c
AT 20 MFD.	450 Volt	13/16x1 3/8"	30c
AT 24 MFD.	450 Volt	13/16x1 3/8"	30c
AT 30 MFD.	450 Volt	13/16x1 3/8"	30c
AT 40 MFD.	450 Volt	13/16x1 3/8"	30c
AT 50 MFD.	450 Volt	13/16x1 3/8"	30c
AT 80 MFD.	450 Volt	13/16x1 3/8"	30c

NATIONAL UNION ALUMINUM CAN "TWIST TAB" TYPE TT

National Union Type TT Electrolytic Condensers. Aluminum can F.P. Type Twist Tab mounting common negative grounded to chassis. Individually cartoned in green N.U. boxes. Each condenser supplied with 1 bakelite insulating plate and 1 metal grounding plate. Save over half on these. All sizes and one-year guarantee.

TT 250 MFD.	25 Volt	1x2-1/16"	19c	TT 20-20-20 MFD.	450 Volt	1 3/8x3"	65c
TT 500 MFD.	25 Volt	1x2-9/16"	19c	TT 20-20 MFD.	150 Volt		
TT 10 MFD.	450 Volt	1x2-1/16"	25c	100 MFD.	25 Volt	1x2-1/10"	45c
TT 20 MFD.	450 Volt	1x2-1/16"	30c	TT 40-40 MFD.	150 Volt		
TT 30 MFD.	450 Volt	1x3 1/8"	40c	95 MFD.	95 Volt	1x2-9/16"	40c

THE FINEST IN "WIDE RANGE SPEAKERS" ARE AVAILABLE AT MCGEE



MODEL CR-13X 12" COAXIAL P.M. \$12.95
 MODEL 5-15X 15" COAXIAL P.M. \$24.95
 MODEL 15-LS 15" 50 WATT P.M. \$16.95
 MODEL 15-KR 15" JUKE BOX \$9.95
 MODEL A-50 12" 50 WATT P.M. \$14.95

DELUXE 12" COAXIAL MODEL CR-13X \$12.95
 15" DELUXE 50-WATT P.M. SPEAKER \$16.95

• RESPONSE 40 TO 17,000 C.P.S.
 • FINE CONSTRUCTION
 • GREY FINISH
 • REGULAR \$32.50 LIST
 Newly designed by one of America's finest speaker builders. Made for FM and AM high fidelity radios and record players. This speaker is incorporated in radius of the 500 dollar bracket. It has an especially designed 12" 6.8 ohm Alnico V Magnet PM for the low range woofer and a coaxially built in 3" Alnico V tweeter for the extended high range. The high pass filter is concealed under the pot cover. Just hook to any 8 Ohm output transformer. Will work in place of any home radio speaker as most speakers have an 8 Ohm Voice Coil, only 2 wires to connect. Will handle 18 Watts peak. Wide range response 40 to 17,000 Cycles. This speaker should sell for \$35.00. Why buy any ordinary speaker when we offer a 12" Coaxial PM for only \$12.95. Shipping weight 8 lbs. Model CR-13X, \$12.95. Two for \$24.95.

STANDARD 12" COAXIAL P.M. CR-12X \$10.95
 Standard Model 12" Coaxial PM Model CR-12X. Same as model CR-13X except 4.64 ohm. Mag. in woofer response 50 to 17,000 CPS. Will handle 12 Watts output. Shipping weight 7 lbs. Stock No. CR-12X, \$10.95. Two for \$20.95.

15" "KING COAX" P.M. SPEAKER \$24.95
 "IT WOOF AS IT TWEETS"
 The King Coax. A 21.5 oz. 15 inch Alnico V PM speaker with a built-in high frequency tweeter. Will respond from 50 to 12,000 cycles. This is a ruggedly built speaker with a curvilinear one piece molded cone. Built-in high pass filter. Just hook to any coil with 6.8 ohm voice coil. This speaker has a retail list of over \$60.00. We offer you our 5-15X 15 inch coax for only \$24.95. Shipping weight 16 lbs.

CURVELENIER "WIDE RANGE SPEAKER LINE" MOLDED HIGH FIDELITY CONES—6", 8" AND 12" SIZES

Designed to meet the ever-growing demand for finer reproduction of sound. Wide range 6 and 8 inch models offered for the first time. These speakers feature heavier moving parts assembly. One piece molded high fidelity curvilinear cones with 45 M.M. reinforcing ribbed buttons. This reinforcement adds to the high frequency response and overall speaker efficiency. Cone movement is piston-like with more unified action. All models have 1" diameter 8 ohm voice coils, with 6.8 ohm Alnico V magnets. Even ordinary radios will sound better with these speakers.

Model 6L-1. Wide range 6 1/2" PM 12 Watt. Shipping weight 4 lbs., response 90 to 12,000 CPS, \$4.95.
 Model 8L-1. Wide range 8" PM 12 Watt. Shipping weight 5 lbs., response 90 to 12,000 CPS, \$5.95.
 Model 12L-1. Wide range 12" PM 12 Watt. Shipping weight 7 lbs., response 50 to 12,000 CPS, \$7.95.

BUY COMPLETE AMPLIFIER KITS \$6.95 UP

TM-4-5 WATT KIT \$6.95
 Kit Model TM-4. 5 Watt Amplifier Kit. Ideal for beginner construction. Has features of higher priced amplifiers. Inputs for phono pick up or mike. Compensation for G.E. Variable Reluctance pick up. Push-pull output gives good tone quality. Output matches 8 ohm Voice Coil. Variable tone control and fader control. Ready punched chassis. This makes a top quality AC-DC Audio Amplifier. Priced complete with diagram and photos. 2-50B5, 2-12AX7, plus selenium rectifier. Weight 3 lbs. Stock No. TM-4, \$6.95. Crystal mike and utility desk stand \$4.95 extra. TM-4 custom wired and tested \$3.00 extra.

TM-8-8 WATT KIT \$8.95
 Kit Model TM-8. 8 Watt Amplifier Kit for utility use, record playing, or paging. Matched component parts. Ready punched chassis. Variable tone control. One control fades from mike to phono. Input compensation for G.E. Variable Reluctance pick up. Output matches 8 ohm Voice Coil. 75 Mill Power Transformer. Price includes tubes, diagram and photos. Push-pull 6AQ5, 2-12AX7, plus rectifier. Kit Model TM-8. Weight 8 lbs. Net \$8.95. Crystal mike and utility desk stand \$4.95 extra. TM-8 custom wired and tested \$3.00 extra.

TM-12-12 WATT KIT \$10.95
 Kit Model TM-12. 12 Watt Amplifier Kit. Ideal for a high quality record player as a P.A. System or recording amplifier. Matched component parts ready punched chassis. One control fades from phono to mike. Input compensation for G.E. Variable Reluctance pick up. Output matches 8 ohm Voice Coil. 100 Mill Power Transformer. Complete with tubes, diagram and photos. 2-6V6, 2-12AX7, plus rectifier. Variable tone control. Kit Model TM-12. Weight 10 lbs. Net \$10.95. Crystal utility mike and desk stand \$4.95 extra. TM-12 custom wired and tested \$4.00 extra.

TM-20-20 WATT KIT \$15.95
 Kit Model TM-20. A high quality 20 Watt Audio Amplifier with 125 Mill Power Transformer and push-pull 6L6's. Inputs for mike or phono pick-up. Compensation for G.E. Variable Reluctance pick up. Tone and fader controls. Has heavy duty universal output transformer, to match 4-8-16, 250, 500 Ohm. Ready punched chassis. Price includes tubes, diagram and photos. 2-6L6, 2-7N7, 7Z4. Frequency response 50 to 9,000 Cps. Kit Model TM-20. Weight 20 lbs. Net \$15.95. TM-20 custom wired and tested \$5.00 extra.

PUSH BUTTON TUNER KIT
 Complete kit of parts to build a 5 station push button tuner for PA system and record players. Small chassis push button only no condenser gang. 456 L.P. Furnished with diagram and tubes 6BA6, 6BE6, 6AT6, 6X4, B and A voltage. From your arm. Stock No. FA-3. Weight 2 lbs. Net \$5.95

\$59.50 VALUE MUSICAL AMP. \$24.95
 8 watt Musical Amplifier. 4 tube AC transformer type. Proper gain for all instrument pickups. Housed in leatherette case with built-in 8" speaker. Gain and tone controls. Made by a large manufacturer to sell for \$59.50. Stock No. XB-3. Weight 25 lbs. Net Price, \$24.95

15" JUKE BOX P.M. SPEAKER \$9.95

Model 15-KR—Pre-War or Post-War, you never bought a speaker like this for such a scoop price. Made by a nationally known builder of fine speakers. A full 15" 12 1/2 oz. Alnico V magnet speaker of juke box quality. Has standard 8 ohm voice coil. Will take up to 18 watts average or 25 watts peak. Here is a speaker that will bring out those low notes. Latest 1948 production; not line through-outs. Every speaker is guaranteed new and perfect. We may not be able to continue this offer for long, so place your order now. Stock No. 15-KR. INCLUDE POSTAGE. Wt. 10 lbs. A \$35.00 value for only \$9.95

50-WATT 12" SUPER HEAVY DUTY P.M. \$14.95

Model A-50—12" 50 watt super heavy duty permanent magnet speaker. Has 1 1/2" 8 ohm treated voice coil and one piece molded cone. Heavy half inch machined pot, with bolt secured 2 1/2 oz. Alnico V magnet. Frame is of heavy construction with metal pot cover. Finished in silver-grey enamel. This speaker is the best value possible today. Efficiency is two to three times that of ordinary speakers. Especially recommended for all public address systems and high quality home audio systems. Will handle 35 watts with ease and 50 watts peak or short lengths of time. Its retail value is \$50.00. But, by our large purchase, we are able to offer it to you for only \$14.95. Do not confuse this speaker with surplus merchandise. This is the latest production. Model A-50. Shipping weight 13 lbs. Net \$14.95, 2 for \$29.00

PHILCO MIKE SALE BRAND NEW WITH 20 FT. OF CABLE
 \$9.95 \$14.95 \$14.95
 High imp. dynamic mike made for Philco. 20 ft. cable. Reg. \$26.00 list. Sale price \$9.95, 3 for \$26.95
 High imp. dynamic mike made for Philco. 20 ft. cable. Reg. \$36.50 list. Sale price \$14.95, 3 for \$41.95
 High imp. dynamic mike made for Philco. 20 ft. cable. Reg. \$40.00 list. Sale price \$14.95, 3 for \$41.95
 Wide range response. 20 ft. cable. Regular \$59.90 list. Sale price \$24.95

Why pay \$40.00 to \$60.00 to buy parts for a good audio amplifier. Our engineering department designed this Kit to give you 20,000 CPS response and have inputs for any variable reluctance pick up. FM tuner or mike and regular crystal pick up cartridge. 3 Tone controls, fader control, high fidelity compound filled output. Transformer matched 4-8-16 Ohm PM Speakers and 250-500 Ohm lines. Push-pull 6AQ5 (name as 6V6). Gives 15 Watts of wide range audio. This kit is complete with photo, diagram and tubes. 12AX7, 3-6C4, 2-6AQ5, 5Y3. Ready punched chassis. Everything furnished. Weight 16 lbs. Kit Model ME-15R. Net \$24.95. Custom wired and tested \$10.00 extra. We recommend our CR-13X 12" Coaxial PM Speaker with this kit \$12.95.

Kit Model ME-34R. Similar to Kit ME-15R except has 2-6L6 tubes in output giving 34 Watts Audio. Kit ME-34R \$34.95. Weight 25 lbs. Custom wired and tested \$10.00 extra.

Challenger (Bogan Built) CC-18, 18 Watt Amplifier. Input for 3 mike, 1 phono. Regular \$63.75 list. Net \$37.50.
 Model CC-30, 30 Watt, 2 Mike inputs. \$60.00 list. Net \$47.00.
 Model CC-618, 6V DC, 110 AC, 18 Watts. 1 Mike, 1 phono input. List \$128.00. Net \$75.30.
 12" Walnut Wall Baffles. Net \$4.95 Each. For PM Speaker see elsewhere on page.
 University 25 Watt drive and PH horn. List \$54.00. Net \$33.72.
 Write for Bogan Challenger and University laboratory circular.

PRICES F.O.B. K.C. Send 25% with order. Bal. Sent C.O.D. With parcel post orders include postage.

OUTPUT TRANSFORMER HIGH FIDELITY 20-20,000 C.P.S. SCOOP PRICE \$6.95 EACH

6600 OHMS PLATE TO PLATE
 Why pay \$20.00 or \$30.00 for an output? Supreme quality and high fidelity output transformer. Designed to match push-pull plates 2-6L6, 2-6V6, or 2-6AQ5 class AB, to 4-8-15-250 and 500 ohm with 10% feedback winding. Housed in a compound filled case: 3 1/2 x 4 1/2 x 3 1/2. Actual net weight, 6 lbs. If you want the best quality from your audio system, order this transformer. Response essentially flat from 20 to 20,000 cycles. We have tried several high fidelity outputs in our lab and find this to be the best value. Even though your amplifier only puts out 10 or 15 watts, this 34 watt job is what you should have. Connecting instructions are furnished. Stock No. A-403, shipping weight 8 lbs. Net price \$6.95.
 10 Watt High Fidelity Output similar to above A-403, only for push-pull 50L6 tubes (4000 ohm plate to plate) to 3.2 or 8 ohm voice coil. A high fidelity amplifier diagram furnished for your convenience. Stock No. H-201. Weight 5 lbs. Net \$3.95

CONSOLE BASS REFLEX SPEAKER BAFFLE \$24.95

6 Cubic Foot Utility Base Reflex Speaker Baffle. Size 22x22x16. Heavy construction with curved pleasing lines. Celotex lining assures non-rattle reproduction. Finish is an attractive brown wrinkle paint. Chrome front trim. Specify when ordering whether for use with a 12" or 15" speaker. Weight 40 lbs. This is an ideal baffle for our deluxe Coaxial model CR-13X. Baffle Stock No. NA-12. Net \$24.95. CR-13X 12" Coaxial PM Speaker and NA-12 Baffle both for \$34.95. You will be pleased with the fine tone of this construction.

12" P.M. FOR UTILITY USE 5 P.M. SPEAKERS ONLY \$22.50

Nationally known 12" 6.8 ohm Alnico V Magnet PM speaker made by voice coil. Will take 15 watts. Grey finish. Our leading 12" speaker.
 Stock No. CH-12. Net \$4.95.
 5 for \$22.50
 12 1/2 Oz. Mag. With 7-1/2" Wt. \$8.95
 Super heavy duty 12" 12 1/2 oz. Alnico V magnet PM with 1 1/2" 8 ohm voice coil. This speaker is equal to 60 oz. of old type magnet. Will take 25 watt peak. Stock No. CH-13. Net \$17.00 two for \$34.00

MCGEE HAS THE SPEAKERS

Following speakers listed are latest production. No factory throwouts. All from the largest factory who furnish the original equipment to America's biggest Radio Factory. Every speaker guaranteed.

3" PM 1 Oz. Alnico 5 Magnet. \$0.90
 4" PM 1 Oz. Alnico 5 Magnet. \$1.20
 5" PM 1 1/2 Oz. Alnico 5 Magnet. \$1.20
 6" PM 1 Oz. Alnico 5 Magnet. \$0.90
 5" PM 1 1/2 Oz. Alnico 5 Magnet. \$1.10
 6" PM 1 1/2 Oz. Aln. 5 Mag. Square 1.98
 6" PM 3.16 Oz. Aln. 5 Mag. Square 2.45
 6" PM 1.5 Oz. Aln. 5 Mag. Square 1.40
 6" PM 1.5 Oz. Alnico 5 Magnet. \$1.40
 10" PM 4.04 Oz. Mag. \$3.95

Hot Buys in Mag's—With Trans.

4" PM 1 Oz. Aln. 5 2500 Ohm Trans. \$1.49
 4" PM 1 Oz. Aln. 5 2500 Ohm Trans. 1.49
 5" PM 1 Oz. Aln. 5 2500 Ohm Trans. 1.69
 5" PM 1 Oz. Aln. 5 1000 Ohm Trans. 1.69
 5 1/2" PM 1 Oz. Aln. 5 2500 Ohm Trans. 1.89
 6" PM 1.5 Oz. Aln. 5 7000 Ohm Trans. 1.99
 6" PM 1.5 Oz. Aln. 5 2500 Ohm Trans. 1.99
 6" PM 2.15 Oz. Aln. 5 7000 Ohm Trans. 2.49
 6" PM 3.16 Oz. Aln. 5 1000 Ohm Trans. 2.98

Hot Buys in Field Spkrs. With Trans.

5" 450 Ohm with 2500 Ohm Trans. \$1.98
 5" 450 Ohm with 7000 Ohm Trans. 1.98
 6" 1500 Ohm with 7000 Ohm Trans. 2.98
 6" 450 Ohm with 7000 Ohm Trans. 2.98
 8" 1000 Ohm. Less Trans. 2.49
 10" 1000 Ohm. Less Trans. 2.49
 12" 450 Ohm RCA. Less Trans. 4.98
 12" 1000 Ohm Magnavox. Less Trans. 4.98

Famous Magnavox Speakers

6" Auto Speaker—4 Ohm. \$2.49
 7" Auto Speaker—4 Ohm. \$2.49
 8" Auto Speaker—4 Ohm. \$2.98
 8" Auto Speaker—3 PM. \$1.79
 8" 12 Oz. Alnico 3 PM. \$2.49
 10" 21 Oz. Alnico 3 PM. \$4.98
 12" 21 Oz. Alnico 3 PM. \$5.98

Save Up To 50% On Cinaudagraph Field Coil Speakers

Regular Dealers Stock of new type Cinaudagraph Replacement speakers. Brand new, individually cartoned. Don't pass up this value.

3" 450 Ohm Field Cinaudagraph. \$1.79
 4" 4 Ohm Field (Auto) Cinaudagraph 1.79
 4" 450 Ohm Field Cinaudagraph. 1.79
 4" 4 Ohm Field (Auto) Cinaudagraph 1.79
 6" 450 Ohm Field Cinaudagraph. 1.99
 6" 1000 Ohm Field Cinaudagraph. 1.99
 8" 1000 Ohm Field Cinaudagraph. 2.49

HOT ITEM—AUTO SPEAKERS

MAGNAVOX UTAH
 6 1/2" Square 4 OHM \$1.49
 6 1/2" Round 4 OHM 1.49
 6x6" Auto Speaker 4 OHM 1.98
 8" Motola-Philco 2.49
 8" Motola-Philco 2.49

HEAVY DUTY AUTO P.M.s

Heavy duty PM speakers with 34 inch voice coils and 3.16 oz. Alnico V magnet. Made by a top flight manufacturer this year for radio radio replacement.


6 inch 3.16 oz. Alnico V.P.M. \$2.49
 6 inch 3.16 oz. Alnico V.P.M. 2.98
 8 inch 3.16 oz. Alnico V.P.M. 2.98
 8 inch 3.16 oz. Alnico V.P.M. 2.98

McGEE RADIO COMPANY NOW AT OUR NEW AND LARGER QUARTERS 1422 GRAND AVE., KANSAS CITY, MISSOURI

What's New in Radio

TWIN-TILT PICKUP CARTRIDGE

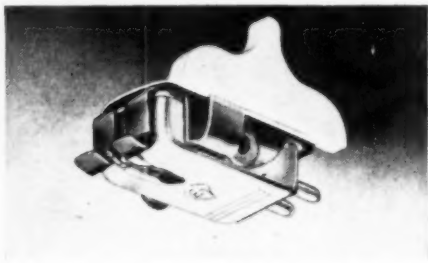The "Twilt"—a new phono pickup cartridge for all three speeds—is announced by *Electro-Voice, Inc.*, Buchanan, Michigan. This single cartridge, with a single "Twin-Tip" replaceable needle, plays 78, 45 and 33 1/3 r.p.m. records without weight change



and with a tracking pressure of only six grams on either needle-tip.


The twin-tilt cartridge mounts easily in any standard pickup arm—with no more adjustment required than reducing the needle pressure. Special silicone moistureproofing gives the crystal cartridge twenty times greater protection against humidity.

This cartridge is available in "Torque-Drive" crystal and variable "Magnetic" types, with replaceable twin-tip .001 sapphire and .003 osmium needles. The dimensions are 1 1/4" wide and 3/4" high, including tilt control lever. Length is 1 1/2".

MAGNETIC TAPE ERASER

The Accessories Division of the *Amplifier Corp. of America*, 398-2 Broadway, New York 13, New York, is producing a new design called the "Magnerasor," which provides complete and instantaneous erasure of recorded reels of magnetic tape, without running the tape past the erase head. It will also effectively demagnetize erase and record playback heads when held in close proximity.

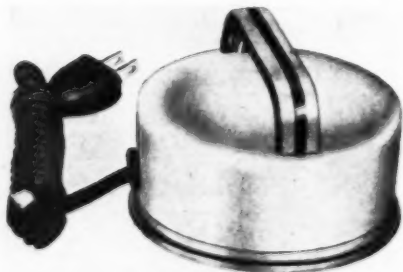Measuring 4 1/2 inches in diameter by 2 inches in height and weighing 2 pounds, the "Magnerasor" removes all normal and overloaded signal from all



types of recorded tape, with either plastic or paper base, and lowers the residual noise level as much as three to six db. below that of new, unused tape. The erase function is accom-

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page, and the issue number, delay will be avoided.

plished by placing it on the reel of magnetic tape and moving it around the circumference.


The housing, of turned aluminum, has a finger-fit handle, and the momentary control, push button "on-off" safety switch prevents the possibility of a.c. current being applied when the instrument is not in use. It operates on a line voltage of 100/130 volts and 25/60 cycles.

TEMPERATURE COMPENSATED RELAY

A relay recently developed by *Sigma Instruments, Inc.*, 45 Ceylon Street, Boston, Massachusetts, will give operation at constant voltage regardless of temperature, or at decreasing voltage with increasing temperature, according to the manufacturer.

Using a bimetal spring, this temperature compensated relay was developed for battery charge control where operating voltage must decrease with rising temperature. With 25 milliwatts operating power, voltage settings are stable to one percent, and windings are available for all common charging voltages.

This same construction also makes

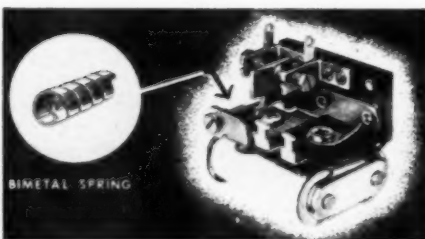

available a new relay type giving operation at essentially constant voltage from -50° centigrade to +85° centigrade. Adjustments are offered for voltages from .01 v. up, at sensitivities of 5 to 25 milliwatts.

TUBULAR TWIN LEAD

Under the catalogue number 14-271, *American Phenolic Corporation*, 1840 S. 54th Ave., Chicago 50, Ill., introduces a new twin lead for television and FM antenna lead-in applications.

The tubular shape of the 300-ohm *Amphenol* product provides security against deterioration caused in most cases of flat twin lead by collection of moisture or moisture and dirt on the polyethylene insulation. The tubular shape was designed to hold this moisture or dirt outside the concentrated field between the conductors. It also provides lower wind resistance than do some other types, and greater strength.

The conductors in the new twin lead

are seven strands of #28 copper wire; the outside diameter is approximately 5/16". Any conventional coaxial cable type insulator may be used to support



it. The weatherproof features should make it very desirable for transmission line in cities where smoke is heavy, or along the seacoast where salt-bearing fogs are a problem.


MINIATURE MICROPHONE

Altec Service Corporation, 161 Sixth Avenue, New York 13, N. Y., is the manufacturer of a new miniature microphone smaller than a stack of six dimes. The mike when in use is mounted on what resembles a conductor's baton.

This small, omnidirectional microphone, because of its inconspicuousness, was used exclusively in the annual presentation of awards by the Academy of Motion Picture Arts and Sciences last March 24. Throughout the ceremonies, the speakers were completely visible during the talks, and for newsreel sound and nationwide broadcasting.

VIBRATIONPROOF CONNECTORS

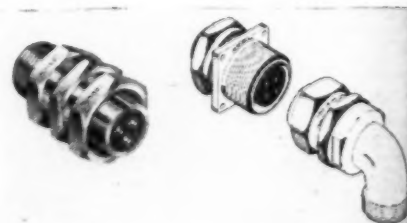Radio shielding, pressurizing, and moistureproofing are new features of the Vibrationproof series of AN-type connectors, which have been completely redesigned by the manufacturer,



Cannon Electric Development Co., 3209 Humboldt St., Los Angeles 31, Calif.

The shell material is aluminum alloy with Dural coupling nuts; low millivolt drop contacts are copper alloy, silver plated. The series has been tested in actual aircraft operation, and radio shielding is accomplished

RADIO & TELEVISION NEWS

MONEY BACK GUARANTEE — We believe units offered for sale by mail order should be sold only on a "Money-Back-If-Not-Satisfied" basis. We carefully check the design, calibration and value of all items advertised by us and unhesitatingly offer all merchandise subject to a return for credit or refund. You, the customer, are the sole judge as to value of the item or items you have purchased.

THE NEW MODEL 247

TUBE TESTER



Model 247 comes complete with new speed-read chart. Comes housed in handsome hand-rubbed oak cabinet sloped for bench use. A slip-on portable hinged cover is indicated for outside use. Size: 10 1/2" x 8 1/4" x 5 1/2". ONLY.....

\$29.90
NET


Check octals, loctals, banam jr. peanuts, television miniatures, magic eye, hearing aids, thyatrones, the new type H.F. miniatures, etc.

Features:

- A newly designed element selector switch reduces the possibility of obsolescence to an absolute minimum.
- When checking Diode, Triode and Pentode sections of multi-purpose tubes, sections can be tested individually. A special isolating circuit allows each section to be tested as if it were in a separate envelope.
- The Model 247 provides a super-sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals.
- One of the most important improvements, we believe, is the fact that the 4-position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

THE NEW MODEL 670

SUPER METER

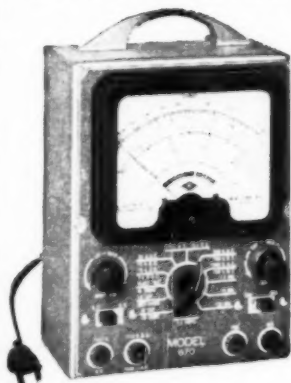

SUPER METER. A Combination VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE, INDUCTION and DECIBEL MEASUREMENTS.

D.C. VOLTS: 0 to 7.5/15/75/150/750/1500/7500. **A.C. VOLTS:** 0 to 15/30/150/300/1500/3000 V. Volts. **OUTPUT VOLTS:** 0 to 15/30/150/300/1500/3000. **D.C. CURRENT:** 0 to 1.5/15/150 ma.; 0 to 1.5 Amps. **RESISTANCE:** 0 to 500/100,000 ohms, 0 to 10 Megohms. **CAPACITY:** .001 to .2 Mfd., .1 to 4 Mfd. (Quality test for electrolytics.) **REACTANCE:** 700 to 27,000 Ohms; 15,000 Ohms to 3 Megohms.

INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries.

DECIBELS: -10 to +18, +10 to +38, +30 to +58.

The model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5 1/2" x 7 1/2" x 3".

\$28.40
NET

The Model S-35—a POWERFUL

REFLEX PROJECTOR

COMPLETE WITH WESTERN ELECTRIC BUILT-IN DRIVER UNIT

CONSERVATIVELY RATED AT 35 WATTS—WILL EASILY HANDLE UP TO 55 WATTS WITHOUT BLASTING

Heavy gauge aluminum in the main trumpet section completely eliminates blasting and blaring. New plastic diaphragm overcomes the resonant peaks of the old type; also it is absolutely impervious to atmospheric changes whereas the old type was subject to atmospheric corrosion. Complete unit unconditionally guaranteed for one year.



Specifications:

POWER (CONSERVATIVE) — 35 WATTS; AIR COLUMN—3 1/2 FT.; DISPERSION—60°; POWER (PEAK) —55 WATTS; BELL DIAMETER—15"; IMPEDANCE—8 ohms; FREQUENCY RANGE—130 to 5000 C.P.S.; PROJECTION—1/2 mile; FINISH—Attractive two-tone crystalline. The Model S-35 Comes Complete with Built-in Driver Unit. ONLY.....

\$28.50
NET

20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS

GENERAL ELECTRONIC DISTRIBUTING CO.

DEPT. RN-6, 98 PARK PLACE, NEW YORK 7, N. Y.

SEE and HEAR the Signal with the new CA-12

SIGNAL TRACER



Features:

- Comparative intensity of the signal is read directly on the meter—Quality of the signal is heard in the speaker.
- Simple to operate. Only one connecting cable—No tuning controls.
- Highly sensitive—Uses an improved vacuum-tube voltmeter circuit.
- Tube and resistor capacity network are built into the detector probe.
- Built-in high gain amplifier—Alnico V speaker.
- Completely portable—Weighs 8 pounds—measures 5 1/2" x 6 1/2" x 9".

This model also available in Kit Form. All parts assembled ready for wiring. Order Model CA-12 Kit. **\$21.95** Only.

Complete with self-contained batteries and instructions. **\$29.95**

The New Model 770—An Accurate Pocket-Size

VOLT-OHM MILLIAMMETER

(Sensitivity: 1000 ohms per volt)



Features:

Compact measures 3 1/4" x 5 1/2" x 2 1/4". Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. Housed in round-cornered, molded case. Beautiful black etched panel. Depressed letters filled with permanent white, insures long life even with constant use.

Specifications: 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 volts.

6 D.C. VOLTAGE RANGES: 0-7 1/2/15/75/150/750/1500 volts.

4 D.C. CURRENT RANGES: 0-1 1/2/15/150 Ma. 0-1 1/2 Amps.


2 RESISTANCE RANGES: 0-500 ohms, 0-1 Megohm.

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

\$13.90
NET

The Model 88—A COMBINATION

SIGNAL GENERATOR AND SIGNAL TRACER

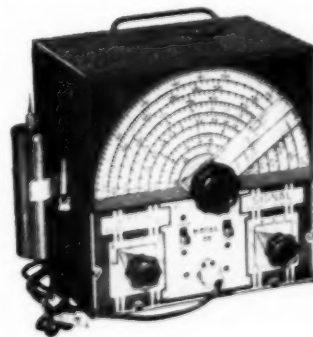

Signal Generator Specifications:

*Frequency Range: 150 Kilocycles to 50 Megacycles. *The R.F. Signal Frequency is kept completely constant at all output levels. *Modulation is accomplished by Grid-blocking action which is equally effective for alignment of amplitude and frequency modulation as well as for television receivers. *R.F. obtainable separately or modulated by the Audio Frequency.

Signal Tracer Specifications:

*Uses the new Sylvania 1N34 Germanium crystal Diode which combined with a resistance-capacity network provides a frequency range of 300 cycles to 50 Megacycles. The Model 88 comes complete with all test leads and operating instructions. ONLY.....

\$28.85
NET



THERE'S A CINAUDAGRAPH SPEAKER FOR EVERY PURPOSE

CHOOSE FROM 105 DIFFERENT MODELS

Whatever your speaker problem, you'll find the answer in a Cinaudagraph Speaker. From two-inch midgels to 15-inch giants, Cinaudagraph Speakers give better performance and longer life.

CINAUDAGRAPH'S newest series includes heavy duty 12-inch and 15-inch PM speakers, with two-inch voice coils and 25-ounce Alnico 5 magnets. They are top performers, the result of Cinaudagraph's precision engineering, manufacture and inspection. To be sure you get the best of quality speakers, always specify CINAUDAGRAPH.



**World's Finest, Most
Complete Line**

DIVISION OF AIREON MFG. CORP.

SALES OFFICE and FACTORY 1401 FAIRFAX TRAFFICWAY KANSAS CITY, KANSAS

CANADIAN OFFICE: Charles W. Pointon, Queen at Bay St., Toronto, Ont.
EXPORT OFFICE: 13 E. 40th St., New York, N. Y. CABLE ARLAB



FREE


Illustrated Cinaudagraph Catalog. WRITE TO: Dept. 150Q, CINAUDAGRAPH SPEAKERS, 1401 Fairfax Trafficway, Kansas City, Kansas

by sphere and cone joints made in accordance with Navy Bulletin RE49A-501A. For insulating material, a new synthetic resilient material with high dielectric has been adopted that will function satisfactorily at -70 degrees (F.) up to +390 degrees (F.).

For the time being, the new series will carry the prefix of an AN shell (such as 08 or 06) with the letters "AF" for a complete number, making the identification 08AF; when "AN Board" approval is granted, "AN" is expected to be added, as "AN08AF."

45 R.P.M. RECORD CHANGERS

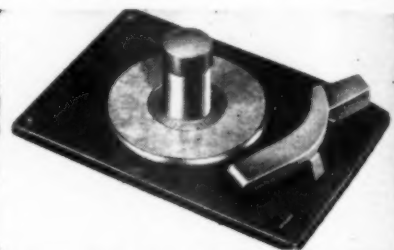One of the major producers of the new 45 r.p.m. record changers, *Crescent Industries, Inc.*, 4140 W. Belmont, Chicago, Illinois, is now turning out




the new 45 r.p.m. changers in quantity for manufacturers and soon hopes to make them available to distributors.

The company has stepped up its activity greatly in order to satisfy as much as possible of the demand for the new RCA development, and the record changers will be distributed through authorized *Crescent* distributors on a national basis.

SOLDERING PLIERS

The electric soldering pliers recently placed on the market by the *Durst Manufacturing Company*, 11110 Cumpston Street, North Hollywood, California, employ a current-resistance principle introducing a faster and more positive method of soldering.

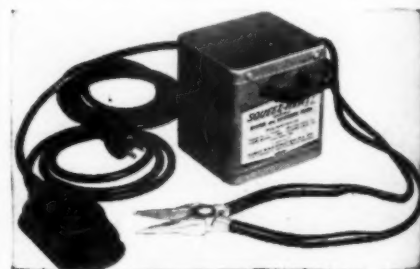They are designed for wiring and soldering and are especially adaptable to compact assemblies. The wires or parts to be soldered are held by the pliers, and the foot switch is depressed for an instant, heating the wires or part sufficiently to melt the solder. The current-resistance principle em-



ployed heats the work only at the point of contact, and the instantaneous heat requires no tinning, heat elements, or tips; the pliers are always cool.

These pliers do the combined work of standard pliers plus a soldering (Continued on page 125)

WITH PRACTICAL

BUILD YOUR CAREER

TECHNICAL TRAINING

You can become a Radio and Television Technician now!

A million new jobs—almost 4,000 a week—will be created in the television industry during the next five years according to estimates of industry leaders.

Now you can get complete practical, technical training in the MSOE laboratories.

This special course prepares you for any of the following careers:

Television Serviceman	Broadcast Radio-Operator
Radio Serviceman	Police, Taxi-Cab and Railroad Transmitter Operator
Radio and Television Retailer	Police, Taxi-Cab and Railroad Receiver Serviceman
Supervisor in Radio and Television Assembly	
Radio and Television Tester	

OTHER COURSES AVAILABLE

SERVICE 6 to 12 Months	Heating and Air Conditioning
• Electricity	PROFESSIONAL 3 Years
• Welding	• Electrical Engineering
• Refrigeration	Bachelor of Science Degree
TECHNICIAN 1 to 2 Years	Major in Electronics or Power
• Electrotechnics	
• Radio and Television	
• Electronics	
• Refrigeration	

MILWAUKEE SCHOOL of ENGINEERING
Founded in 1903 by Oscar Werwath

MILWAUKEE SCHOOL OF ENGINEERING, N. Broadway and E. State, Milwaukee, Wis. Dept. RN-643

Without obligation send me free booklet "Career Building" and more details on course in Radio and Television or.....course.

Name Age

Address

City State

SHOOTS TROUBLE FASTER!

MAKES MORE
MONEY FOR YOU
ON JOB OR AT
SERVICE BENCH!



PRICE
\$9.95

at distributor or postpaid, direct. Sorry, no C.O.D.'s. Ohioans add 3% State Sales Tax

Signalette

MULTI-FREQUENCY GENERATOR

In radio service work, time means money. Locate trouble faster, handle a much greater volume of work with the SIGNALETTE. As a trouble shooting tool, SIGNALETTE has no equal. Merely plug in any 110 V. AC-DC line, start at speaker end of circuit and trace back, stage by stage, listening in set's speaker. Generates RF, IF and AUDIO Frequencies, 2500 cycles to 20 Megacycles. Also used for Checks on Sensitivity, Gain, Peaking, Shielding, Tube testing. Wt. 13 oz. Fits pocket or tool kit. See at your dist. or order direct.

Clippard

Instrument Laboratory, Inc.

DEPT. N, 1125 BANK STREET
CINCINNATI 14, OHIO

QUALIFIED JOBBERS WRITE, WIRE
FOR DETAILS.

Surplus CLEARANCE Sale!

DYNAMOTOR D-2



D-2 Converts to 110 V AC in ten minutes, diagram included, contains integral gear box having four 1/2" drive shafts turning simultaneously at the following speeds:
4000 RPM—Grinders, buffers, flexible shaft tools, etc.
150 RPM—Wrapping fishing rods, slow speed tools.
25 RPM—Dev. tray rocker for photo darkroom.
5 RPM—Turning barbeque spits. Adv. Disp. Beams. A Thousand Other Uses Around the Work Shop.

\$7.95 ONLY

DYNAMOTOR D-1

D-1 Converts to 110 V AC in ten minutes, diagram included, has shaft with squirrel cage blower, also gear reducer with 2 shafts and pulleys at the other end. 1001 uses.

\$6.95 NEW

RM-29 PORTABLE FIELD TELEPHONE

An ideal portable field telephone. Complete in a rugged steel case for years of wear. Ringer circuit and TS-13 handset. No leather case to deteriorate. Compact 5"x6"x9"—also used as remote control on SCR-284. Simple two wire operation. 15 miles distance and upwards. Can be used for television installation, intercom system, construction companies outside and inside work, etc. Light weight, 13 lbs. Excellent condition.



SPECIAL LOW PRICE EACH... **\$9.95** 2 for **\$18.95**

BC-727 INDICATOR BOX
With two red jewel pilot light assemblies. It's a steal! Each **29c**

HEADSETS!
HS-23 High Impedance, HS-33 Low Impedance, Army Air Force Type, cord and plug.
HS-30 Low New **\$1.59** Used **98c**

MIKE ADAPTER
M-299 for SCR-522 permits use of carbon mike in place of magnetic. New Each **\$2.50**

BC-733 D
A 10-tube superhet receiver for lateral blind landing guidance (CAA type certificate) TC-1045. Excellent condition 108-110 MC. Tube complement: 1-12SR7; 2-12SR7; 1-12A6; 1-12AH7GT; 2-12SG7; 3-717A—tubes alone worth more than this low price.

SCHEMATIC FURNISHED Each **\$5.95**

AN/CRW-2 V.H.F. RECEIVER
6 tubes: 3-6SL7, 1-6SN7, 1-6SG7, 1-6J5. Dynamotor, plug-in coils and sensitive relays. This was one of the Army's "Secret" V.H.F. remote control receivers. Operating at about 110 MC. A thousand and one uses. Like new in a metal case. Each **\$5.95**

COMPLETE BEAM ROTATOR ASSEMBLY LP-21A AND 1-82A

A large 5" indicator 1-82A, and an LP-21 loop (removed from aircraft). A complete perfect beam rotator system with indicator. Loop in low impedance—contains selayn transmitter, etc. **\$7.95**

Loop alone... **\$5.95** Indicator alone... **\$4.25**

WAFER SWITCHES
10 assorted, rotary, gang. Removed from equipment. ALL 10 for **\$1.00**

LIP MIKE & CORD SET
MC-419 lip mike with cord CD-318 or CD-508, with PL-68, JK-48 and switch. New **\$1.59**

HOOK-UP WIRE
Approx. 400 ft. assorted gauges and colors—about 2 to 4 ft. length. **98c**

CORD CD-605 OR 604
A two foot cord with a PL-55 plug; with low to high impedance transformer for your headset. Will match HS-30 **39c**

CORD 307
A six foot head set extension cord with PL-55 plug on one end and a jack on the other. NEW. **59c**

ANTENNA LOADING UNIT
MC 432 contains 2 pole, 5 position rotary switch with silver ceramic variable condensers, and coils for matching VHF transmitter to AN 109 antenna with 50 ohm line. Useful parts. New Each **\$1.39**

TOGGLE SWITCH
S.P.D.T. luminous tip bat handle. NEW. 4 for **\$1.00**

SLIDE SWITCH
S.P.D.T. designed for portables, etc. 10 for **\$1.00**

AUTOMATIC RECORD CHANGER
Play 10" or 12" records. Special purchase Stewart-Warner Strobosonic. Each only **\$12.95**

6" PM SPEAKER
Beautiful new stock. Alnico magnet. Each **\$1.95**

MINIMUM ORDER \$2.00. ALL PRICES FOB CHICAGO. 20% Deposit required on all COD orders. Price subject to change without notice.

TRACEOMETER HICKOK
Ideal for the radio service man. Design for accurate general testing. Good condition.

Voltage measure, tracing, etc. Ea. **\$79.95**

RELAYS
24 V. { S.P.S.T. D.P.S.T. 160 ohms 4 for **\$1.00**

MODULATOR UNIT Each **\$2.95**

ANTENNA RELAY UNIT
BC 442 010 RF Amp. Meter, change-over unit for use with Command Set Transmitter. Brand New Each **\$1.95**

BC-433G
15-tube superhet radio compass receiver 200 to 1750 Kc; CW-tone-voice. Like new. Similar to R5/ARN7. Schematics furnished Only **\$24.95**

GIBSON GIRL
Emergency transmitter balloon, kit, generator, case, etc. New **\$12.95**

COMMAND SETS
BC-454—Receiver 3-6 M.C. Used. Good condition. **\$7.95**

BC 457 TRANSMITTER
4-5.3 MC. Can be converted to 80 meters with slight modification. Ea. **\$9.95**

BC 458 TRANSMITTER
5-7 MC. Command Set **\$9.95**

PULSE AND SWEEP GENERATOR. Each **\$72.95**

MALLORY SWITCH
6 Pole 3 position single deck wafer switch. Each **39c**

TU 10B
Tuning unit for BC-375... a terrific parts value with a metal case. Brand New. See page 24 Nov. Radio Craft for conversion to 10 meter final. Without case. **\$2.10** Only **\$2.95**

TUBES
1625... 3 for **\$1.10** 5BP1 Scope tubes @ **\$2.50**
6V6... @ .49 5BP4 Scope tubes @ **3.45**
3D6... @ .49 35Z5... @ **.59**

BC-1206
Beacon Receiver 200 to 400 K.C.'s 28V plate and filament. Easily converted to broadcast band by adjusting of slug and tuned coils. Each **\$7.45**

T-17 D MIKE
The desirable single button carbon mike. With press the button to talk switch, 4' cord and PL-68 plug, mike cover. Features non-echo effect. New **\$2.49**

FILAMENT TRANSFORMERS
Fully shielded Pri. 100 V. Sec. (#1 winding 10.2 V @ 5 A. C. T.; #2 winding 10.2 V @ 10 A. C. T.) Secondary winding can be connected in series to supply 25 V. with a line Voltage of 115 Volts—60 Cye. New Each **\$3.75**

30 FT. CABLE
CO-213 7 Conductor cable with outside shield. Length of 30 ft. **98c**

DM-53A DYNAMOTOR
24V. in., 220V—80 M.A. out. USED **98c**

MICRO SWITCH
Control box with long leaf type S.P.S.T. normally open switch. NEW **39c**

INVERTERS

PE 109

12V input for radio compass. 115V. 400 cye. output. Used. Good condition. **\$29.95**

PE 218

Input 25-28 VDC—92 amp. output 115 V. 350-500 cycles. 1500 Volt amp. Used, Good Condition. **\$19.95**

PE 206

Input 28 VDC—38 amps. Output 80 V. 800 cycles, 500 Volt amps. Used. **\$8.95**

MAST SECTION

MS-51 Mast section. New **50c**

PLUGS and CONNECTORS

YOUR CHOICE for only **49c** each

For the SCR-522... PLQ-167, PL-172
For the BC-348... PLQ-103
For the BC-733... PLQ-254
For 200-F Radio Compass Inverter, PL-3108-22-48
For the SCR-274-N

... PL-147, 148, 151, 152, 153, 154A, 156, 258
For the BC-375... PL-59—PL-61—PL-64
For the ART-13... U-8U, U-10U, U-16U
For the ARC-1... U-15U, U-16U
MC-203A coupling Coax Fittings—
... PL-259A (83-18P)—UG-21U—UG-22U
PL-164 M-359 U-11/U

AN-3108-28-19P
AN-3108-12S } Combination Male and
AN-3100-12S-33 } Female
PL-63 SO-44 PL-62
PL-56 SO-86

6 VOLT MOTOR

A real beauty, removed from aircraft. Type used for auto fan. Each **98c**

BC-1066-A

IDEAL V.H.F. RECEIVER FOR THE HAM!
This battery operated set is contained in a beautiful black telephone finished wooden cabinet 8"x8"x14": 1-1D8GT Tube; 2-UT-237 Acorn tubes; 2 large airplane knobs, switches, variable condensers. This set can be converted to an ideal 2-meter transceiver for portable use. NEW **\$10.95**

RADIO CONTROL BOX BC-450

Used for remote tuning and operation of command receivers. Has three independent units in one, each consisting of dial crank, volume control, C.W. Phone switch, female power connector and phone jack. Used—excellent condition. Each **\$2.95**

INTERPHONE CONTROL BOX BC-606
Contains volume control, mike and phone jacks, switch, metal case, valuable parts. NEW **59c**

CONTROL BOX

Useful parts—2 S.P.S.T. toggle switches, wafer switch and knob, Sockets, Jack. **59c**

BC-312 DIAL KNOB ASSEMBLY 25c each

NESCORP ELECTRONICS Division of NATIONAL EQUIPMENT & SUPPLY CO., INC.

2635 W. Grand Ave., Dept. R

Phone Everglade 4-5870

Chicago 12, Illinois

You
See



THESE DISPLAYS IN FOUR HUNDRED RADIO PARTS STORES

...from coast to coast, and also Honolulu and Anchorage, Alaska, making it easy for you to pick out the "XL" for your microphone and radio equipment.

The XL Series is growing in popularity wherever quality radio equipment is used. Prices are reasonable.

Among the four hundred radio parts firms where you may buy "XL" fittings are the following: Valley Radio, Appleton, Wisconsin; Morrison's Radio Supply, Ashtabula, Ohio; York Radio, York, Pennsylvania; Electra Dist. Co., Nashville, Tennessee; Montague Radio, Beaumont, Texas; Prestwood Electronics, Augusta, Georgia; Orem Distributing Company, Saginaw, Michigan.


NEW XL-4 INSERT

4
10-amp.
contacts



Face
View
Pin Side

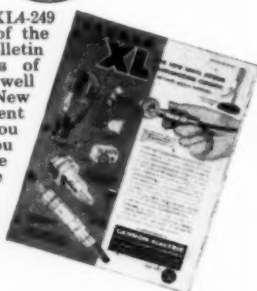Shown in the new XL4-249 — latest edition of the four-page XL Bulletin which lists prices of the XL-3 types as well as the XL-4. The New CEDR-9 will be sent with the XL, if you prefer, so that you may pick out the radio parts store nearest you carrying not only XL plugs but other Cannon Electric fittings.



Address
Department F-228.

CANNON ELECTRIC

Development Company

Division of Cannon Manufacturing Corp.
3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.

IN CANADA & BRITISH EMPIRE:
CANNON ELECTRIC CO., LTD., TORONTO 13, ONT.

WORLD EXPORT (Excepting British Empire):
FRAZAR & HANSEN, 301 CLAY ST., SAN FRANCISCO

AFCA



NEWS

This Association is a patriotic non-profit organization, with chapters in most of the larger cities, dedicated to developing and maintaining efficient personnel, commissioned, enlisted, civilian, for the supply (including design and development), installation, maintenance and operation of communications and electronic equipment for Army, Navy and Air Force and their supporting civilian activities. It publishes a magazine "SIGNALS" at its national headquarters in Washington. Every American interested in any way in communications is eligible and invited to join. Further details may be obtained by addressing the secretary at 1624 Eye St. N.W., Washington 6, D. C.

AFCA Third Annual Meeting

The third annual meeting of the Armed Forces Communications Association was held under Navy sponsorship at Washington, D. C., on March 28th and 29th.

The directors' meeting and chapter representatives' meeting were held in the morning of March 28th. The AFCA luncheon was addressed by Capt. A. A. Burke, U.S.N., and Mr. Wayne Coy, Chairman, Federal Communications Commission. At the general business meeting in the afternoon, the annual report of the association was presented, and honor awards were announced. The speakers were: Leighton H. Peebles, NSRB Assistant Director of Production; Major General Spencer B. Akin, Chief Signal Officer of the Army; Major General Francis L. Ankenbrandt, Director of Air Force Communications; Rear Admiral Earl E. Stone, Chief of Naval Communications; Fred R. Lack, President-elect of AFCA; and Capt. Robert J. Foley, Office of the Chief of Naval Communications, who briefed the members on the Navy demonstration scheduled for the following day. At the conclusion of the business meeting, the color film, "The Secret Land," was shown.

At the annual banquet, Dwight R. G. Palmer, President of *General Cable Corporation*, served as toastmaster. Addresses were made by Brig. General David Sarnoff, President of *RCA*, and Vice Admiral John D. Price, Deputy Chief of Naval Operations for Air.

The second day of the convention, March 29th, was devoted entirely to Navy exhibits. These included a visit to the *USS Requin*, the radar picket submarine which was moored at the Naval Gun Factory, to acquaint the Association with a type of submarine currently under the development and evaluation process, and a tour of the *USS Adirondack*, called an "Amphibious Force Flagship."

At the Naval Air Station, advanced models of experimental aircraft from the Naval Air Test Center at Patuxent River, Md., were flown past the spectators at low altitude, and there was a demonstration of Marine Corps piloted helicopters from Quantico, Virginia. In addition, exhibits were visited at the Naval Research Laboratory and the Naval Photographic Center.

The newly elected national officers of AFCA, who will take office on July 1, 1949, are as follows: President—Fred R. Lack of *Western Electric Company*, New York; Vice-Presidents—Theodore S. Gary of *Automatic Electric Company*, Chicago; Thomas J. Hargrave, *Eastman Kodak Company*, Rochester; Rear Admiral Earl E. Stone, USN; J. R. Cunningham, *United Air Lines*, Denver; and C. O. Bickelhaupt, *American Telephone & Telegraph Co.*, New York. New directors are: Walter Evans, *Westinghouse Electric Company*, Baltimore; Paul Goldsborough, *TWA*, Kansas City; and W. G. Eaton, civilian scientist at *Wright Field*, Dayton. W. C. Henry of the *Ohio Independent Telephone Co.* was elected Executive Committee member-at-large.

CHAPTER NOTES

Cleveland

The Cleveland Lifeboat station of the United States Coast Guard was the scene of the April 14th meeting of the Cleveland Chapter. The meeting was devoted to an inspection of communication facilities and electronic applications, including radio beacons and remote control facilities, as used in the varied services furnished by the Coast Guard.

Kentucky

The March meeting of the Kentucky Chapter was held at the Lexington Signal Depot Officers' Club on March 11th. After the business meeting, a "white elephant" auction was held to replenish the chapter treasury. The program concluded with the Signal Corps picture, "Attack, Battle for New Britain."

The April meeting was held in the lobby of the new Lexington Telephone Company Building. Chapter President Murray P. McQuown reported on the AFCA Third Annual Convention which he had attended in Washington, D. C. The feature of the evening was the *Lexington Telephone Company* demonstration of the new dial system.

Louisiana

The charter of the Louisiana Chapter, newest AFCA chapter, was presented by Rear Admiral Earl E. Stone, Chief of Naval Communications, at a

RADIO & TELEVISION NEWS



H. V. MICAS SEND FOR LISTS OF OTHERS

Fig.	Mfd.	Voltage	Mfg.	Price
D .01	1200VDC	Spr.	\$.50	2 For .95
D .00025	2500VDC	Spr.	.29	2 For .55
D .0004	2500VDC	Micamold.	.39	2 For .75
D .00047	2500VDC	Micamold.	.39	2 For .75
D .0001	2500VDC	Micamold.	.25	2 For .45
D .01	500VDC	C.D.	1.05	2 For 2.00
C .01	3000VDC	Sang.	.49	2 For .95
C .0003	2000VDC	Spr.	.75	2 For 1.45
C .0009	3000VDC	Sang.	1.00	2 For 1.95
C .00082	3000VDC	C.D.	1.00	2 For 1.95
C .002	3000VDC	C.D.	1.65	2 For 3.25
C .005	1500VDC	Sang.	1.65	2 For 2.95
C .004	6000VDC	Spr.	1.00	2 For 1.95
C .0006	3000VDC	Spr.	.95	2 For 1.85
C .0008	3000VDC	Sang.	.95	2 For 1.25
E .0016	3000VDC	Sang.	.40	2 For .75
E .00090	3000VDC	Sang.	10.00	2 For 19.00
B .08	1500VDC	Sang.	12.00	2 For 23.00
B .045	2000VDC	Sang.	24.00	2 For 47.00
B .0015	2000VDC	Sang.	24.00	2 For 47.00
B .001	2000VDC	Sang.	19.00	2 For 37.00
B .002	1500VDC	Sang.	1.45	2 For 2.85
C .006	2500VDC	Micamold.	.35	2 For .63
E .00027	2500VDC			

WRITE FOR LISTS OF OTHER VALUES



BAND PASS FILTER

#70473. Sharp band pass peaked at 700 cps. Bandwidth: 650 cps at 20 db. Down from peak. High-to-high impedance. Can be plugged into phone output of receiver for good results. Cuts out QRM New, with circuit diagram. \$1.50

NAVY LINE FILTER. G.E. 100 amp filter with 2x5 mfd 50V oil filled cond. Operates 110VAC DC. SPECIAL. Price \$1.98

CARBON PILE VOLTAGE REGULATORS

Type "A": Coil current .105 to .115 amp. 80 volts, Leland Electric. \$2.95
Type "M": Input: 22-30 v. coil, 30 amps. Output: 19 v. 5.7 amps. Spec. # V19000-2c. Leland Electric (see shown). \$2.95
#35X045H: 22v. 1 to 3 amps. for K-4B Gunsight. Webster. \$2.95



TRANSTAT (AMERTRAN)

INPUT: 0.115v. 50-60 cy. Max. OUTPUT: 115v. 100 Amp. All units NEW. Guaranteed. Price \$95



RELAYS

Type	Contacts	Rating	Res. Coil	Mfg.	Price
H . DPDT	24	28VDC	.170	GE	\$1.75
H . SPDT	24	28VDC	.175	GE	1.25
H . SPDT	24	28VDC	.1750	GE	1.75
H . SPST	24	28VDC	.180	GE	1.75
G . DPDT/SPST	(NO)	12VDC	.44	Leach	1.45
G . DPDT	22	28VDC	.160	Leach	1.25
D . SPST(NC)	24	28VDC	.250	Allied	1.39
I . DPST(NC)	14	VDC	.85	Price	1.50
D . SPDT	24	28VDC	.2800	Allied	2.50
H . SPST	24	28VDC	.2400	G.M.	2.00
D . DPDT	24	28VDC	.280	Allied	2.00
D . SPDT	24	28VDC	.280	Allied	1.10
D . DPDT	24	28VDC	.280	Allied	2.10
D . SPST(NC)	75	MA	.60	Allied	1.10
H . DPDT	20	30VDC		Dunce	2.00
H . DPDT	10	14VDC		Dunce	2.00
H . DPDT	24	28VDC		P.B.	1.75
H . SPDT	24	28VDC		GE	2.00
H . SPDT	24	28VDC		GE	1.75
A . DPDT	12	VDC		Dunce	2.40
A . SPDT	10	12V 60Cy 125		Dunce	2.40

Send for Lists of Other Types



FREQ MULT UNIT

ART-13 Xmfir Assy. 2 to 18 Mc. Doubling Package setup, for two 1625 Tubes. No coils. Complete Assy. 1.5 tubes w/ckt Diagram. Price \$8.95
UTC #60399-Audio Xfmtr 1.1 Ratio 50,000 ohm imp. 3 db. \pm 1db. 50-3000 cy. CUNCE. Price. .98c
ARC 9468-Mod. Xfmtr 807 to 807S Class "C". Price \$1.65
UNIVERSAL OUTPUT XFMR-Amer. Sillcor. Pri.: 20000, 10000, 5000, 4000/ohms. Sec.: 500, 15, 7.5, 3.75, 1.25/ohms. 3 db. F 14 to 17000 cy. \$4.75
MOD INPUT XFMR-T202, 6V6 PI to 811 Grids for ART 13 (M7472064). \$1.49

SEND FOR LISTS OF AUDIO EQUIPMENT

COMMUNICATIONS EQUIPMENT COMPANY

WRITE FOR BLUE FLYER

3" OSCILLOSCOPE KIT

BC 929 Indicator using 9 Tubes, 3BP1, 6SN7, 6H6, 6B6G, 6X5, 2X2 (now 400 cycles) easily conv. to 60CY. 115V. New-Complete w/Tubes and conv. instr. incl. Dia. \$22.50

5" OSCILLOSCOPE KIT

BC 704 (less pwr. supply) uses 8 Tubes-5BP1, 6AC7, 6H6, includes wooden Carry Case, Diag. and Tubes. Price. \$30.50
3BP1... \$2.25 5CP1... \$3.75
F5123... 2.50 15PPT... 3.50
5BP1... 1.95 2X2... .69
5BP4... 4.95 6L6GA... 1.00



TRANSFORMER SPECIALS!

115V60Cyc Input
Plate & Fil Xfmrs.
Equip. Conservatively Rated

FILAMENT TRANSFORMERS

Trans. 5Volts/6amp	\$2.25
F5083: 6.3VCT/6A, 5V/2A	1.85
F—: 2.5VCT/6.5A	3.25
F—: 6.3VCT/2A, 6.3VCT/2A	2.45
F5087: 6.3VCT/1A, 6.3VCT/7A	2.75
F5103: 6.3V/1A, 6.3V/1A	1.95
F5123: 6.3VCT/5A, 6.3V/1A	2.25
F5127: 6.3VCT/3.2A, 6.3VCT/1A	2.25
F0674: 8V/1.5A	2.75
F—: 2.5/1.75A, 6.5/8A, 5/3A, 6.5/6.	3.95
F7414: 2x2.5VCT/6.5A	3.25
F161: 6.3VCT/7A, 6.3VCT/5A, 5VCT/6A.	
2x6.3V/6A, 6.3V/3A	3.95
F829: 6V/2.5A, 6.3V/3A	1.75
F38A: 6.3V/2.5A, 2x2.5V/7A	3.25
F112: 2x2.5VCT/6.5A, 2.5V/6.5A	4.25
F14A: 6.3V/6A	1.95

PLATE TRANSFORMERS

P410: 800VCT/40MA, 760VCT/500MA	\$6.50
P415: 600V/450MA	4.95
P699: 2x300VCT/150MA	2.25
P403: 70V/1A	2.25
P413: 510VCT/150MA, 650VCT/15MA	3.00
P842: 600VCT/0166A, 250VCT/077A	2.95
P885: 1620VCT/400MA HV Ins.	11.95
P894: 2x200V/350MA, 2x20V/01A	1.95
P450: 2x150V/940MA	4.50
P371: 240VCT/830MA	3.95
P345: 1470VCT/1.2A 3500T	24.00

COMBINATION TRANSFORMERS

C965: 780/600MA, 6.3V/2	\$3.95
C111: 2x300V/42MA, 55V/125MA, 45V/3.5MA	3.95
C608: 880VCT/150MA, 5V/3A, 6.3V/6.25A	4.25
C931: 585VCT/86MA, 5V/3A, 6.3V/6A	3.95
C055: 525VCT/75MA, 5V/2A, 6.3V/1.8A, 10V/2A	4.45
T102: 1080VCT/55MA, 6.3V/1.2A, 6.3V/1.2A	5.95
C548: 600VCT/155MA, 6.3VCT/5A, 5VCT/3A.	
HV Ins.	3.95
C899: 2x110VCT/01A, 6.3V/1A, 2.5VCT/7A	4.50
C760: 6.3VCT/10A, 65V/1A, 100VCT/1A, 40V/1A, 18VCT/1A, 18V, 6V/1A, 6.3V/1A	5.25
C254: 825VCT/190MA, 5VCT/3A	3.95
C367: 5VCT/3A, 580VCT/040A	2.95
T160: 1120VCT/70MA, 590VCT/082A HV Ins.	12.50
C579: 24V/900MA, 770V/0025, 2.5V/3A HV Ins.	4.25
T378: 2500V/004A, 2.5V/2A HV Ins.	8.95
C375: 1120VDC/600MA, 2x5VCT/6-2A, 6.3VCT/3A, 6.3V/300MA	14.95
C364: 6.3VCT/3A, 5VCT/6A, 610VCT/330MA	4.50
C434: 40V/01A, 6.3V/1.25A	1.95
C383: 215VCT/300MA, 6.3V/6A	2.29
C360: 640VCT/080A, 5VCT/3A, 6.3VCT/3.2A	3.95
C821: 1500V/4MA, 6.3V/6A, 2.5V/1.75A, 3500	
Test	6.95

FILTER CHOKES

.03HY/2A, \$1.25; 8.5HY/125MA	\$1.50
25HY/65MA, \$1.00; 6HY/150MA	1.50
Dual 7HY/75MA, 11HY/65MA	1.65
7HY/140MA, \$1.60; Dual 2HY/100MA	.75
Dual 2.5HY/130MA, \$1.25; 11HY/150MA	4.25
.01HY/2.5A, \$1.45; 35HY/350MA	7.25
Dual .5HY/380MA, \$1.00; 5HY/40MA	.55
2HY/200MA, 75c; Dual 120HY/17MA	2.45
30HY/20MA, 85c; 5HY/200MA	1.45
2.1HY/200MA, \$1.20; 2x2.1HY/55A	9.95
25HY/75MA, \$1.40; 20HY/300MA	7.95
Dual 22HY/600MA, 44HY/400MA	1.75
.03HY/7A, \$9.50; Dual 10HY/150MA	3.50
Dual 1.52HY/167MA, \$2.49; Dual 2.2HY/550MA	5.95
5HY/200MA, \$1.49; 1.35HY/1A	4.95
12HY/100MA, \$1.75; 1HY/100MA	.60
2x2.5HY/700MA, \$6.95. Write for lists.	

FREE! FREE! FREE!
CEC FLYER: BARGAINS YOU NEED



BATHTUB CAPACITORS

Fig.	Mfd.	Voltage	Terminals	Price
D	3N.1	400VDC	3	33c 4 For \$1.29
E	3N.1	400VDC	3	33c 4 For \$1.29
C	2N.1	600VDC	2	20c 5 For 95c
E	2N.1	600VDC	3	29c 3 For 85c
A025	600VDC	2	18c 5 For 85c
E2	400VDC	2	40c 2 For 75c
C	2X.25	600VDC	2	25c 4 For 95c
A	2X.25	600VDC	3	29c 3 For 85c
D5	1000VDC	2	45c 3 For \$1.30
E1	600VDC	2	25c 4 For 95c
E	3N.1	600VDC	3	35c 3 For \$1.00
E5	200VDC	2	20c 5 For 95c
C05	600VDC	2	21c 5 For \$1.00
E5	600VDC	2	25c 4 For 95c
E5	120VDC	2	18c 5 For 85c
E1	600VDC	1	20c 5 For 95c
E	4	50VDC	2	25c 4 For 95c
E	1	400VDC	1	25c 4 For 95c
D	1	600VDC	2	30c 3 For 75c
C	3N.1	600VDC	3	27c 4 For \$1.05
D5	600VDC	2	25c 4 For 95c
D	2X.1	600VDC	3	29c 3 For 85c
D5	600VDC	1	20c 3 For 95c
E	2X.1	200VDC	2	20c 5 For 95c
E5	400VDC	1	20c 5 For 95c
A02	1500VDC	2	45c 2 For 85c
E5	600VDC	2	25c 4 For 95c
C5	200VDC	2	20c 5 For 95c
E	4	50VDC	2	30c 3 For 95c
E	20	50VDC	2	25c 4 For 95c

WRITE FOR LISTS OF OTHER VALUES


HEINEMAN CIRCUIT BREAKERS

Can be used for A.C. and D.C. operation. Amperes .010, .3, 7, 10, 50, 100, 150. SPECIAL. Each \$1.45
10 For \$13.25
100AMP, 3 Pole, 250V. 6.95




INTERPHONE CONTROL BOX

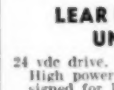Permits Transfer of H.S. from Receiver. 4" x 4" x 2" D. Contains JK-35A, JK-34A, Toggle Sw. Lum. Tip. Pot 50,000-ohms. Term Strip. A REAL BUY. PRICE. \$1.00



LEAR POWER UNITS

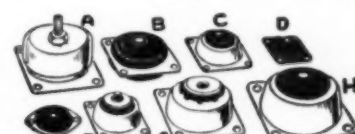24 vdc drive, 90:1 gear ratio. High power. Originally designed for landing gear retraction. Bicycle type sprocket for multi-purpose drive. Large quantity available \$6.95



SHOCK MOUNTS

Fig.	Type	Size	Price
D	L# 1	1 1/4 x 1 1/4 x 3/4" H.	10c
D	L# 2	1 1/4 x 1 1/4 x 3/4" H.	10c
D	L# 3	1 1/4 x 1 1/4 x 3/4" H.	10c
H	L# 15	1 1/4 x 1 1/4 x 3/4" H.	15c
H	L# 12	1 1/4 x 1 1/4 x 3/4" H.	15c
H	L# 35	2 1/4 x 2 1/4 x 1" H.	18c
H	L# 35	2 1/4 x 2 1/4 x 1" H.	18c
F	L# 4	1 1/2 x 1 1/2 x 1 1/2" H.	35c

Many Other Types. Send for List.

932 PHOTOTUBE

A gas photo tube having S1 response. Sensitive to red & near infrared radiation. Can be used with incandescent light sources. Anode Supply Volt. (DC or AC)90 Volts Cathode Current3 Amp. Ambient Temp.100° C. Sensitive at 8000 Angs.0065 μ Amp/ μ Watt Luminous Sens. at Oegs.65 μ Amp/Lumen Price, \$1.25; 2 For. \$2.25



PRECISION RESISTORS

1.01	125	1450	20000
3	128	1900	25000
5.05	150	12300	30000
10	200	4300	33000
18	250	5000	35000
30	300	7000	40000
43.5	430	7500	50000
50	468	8500	55000
75	800	12000	57000
82	920	12000	75000
120	1000	17000	We ship types
120	1100	17300	In stock
Above Sizes Each.	30c	Ten For.	\$2.50
100000.	150000.	200000.	250000
120000.	170000.	220000.	500000
Above Sizes Each.	40c	Ten For.	\$3.50


OTHER VALUES IN STOCK. SEND FOR LIST

COMMUNICATIONS EQUIPMENT COMPANY

CABLE ADDRESS: COMSUPO
PHONE DIGBY 9-4124
**131 LIBERTY ST. DEPT. N
NEW YORK 7, N.Y.**

C.E.C. MONEY BACK GUARANTEE, \$3 MIN. ORDER.
F.O.B. N.Y.C. SEND MONEY ORDER OR CHECK, ONLY SHIPPING CHARGES SENT C.O.D.

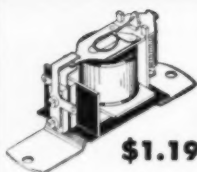You Can't Match these MID-AMERICA Values!




110-VOLT DC PLATE LOAD RELAY

6000-ohm coil, SPST normally open contacts. Extra sensitive and used for many applications. 1 1/2" high 1 1/4" wide, on 1 1/2" mtg. ctrs.
MA-1903

\$1.19 **\$1.19**

Silver Mica Button Condensers

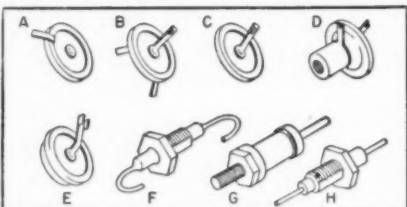

\$7.50 per 100 (all one type)


MA-3536 (G) 20 mmf	MA-3505 (C) 360 mmf
MA-3501 (D) 30 mmf	MA-3509 (A) 500 mmf
MA-3531 (F) 55 mmf	MA-3506 (B) 500 mmf
MA-3503 (A) 75 mmf	MA-3510 (C) 500 mmf
MA-3532 (H) 75 mmf	MA-3502 (D) 500 mmf
MA-3504 (A) 200 mmf	MA-3507 (E) 500 mmf
MA-3519 (F) 250 mmf	MA-3518 (A) 2000 mmf

No. 18 2-conductor Wire & Drum

Used for running 110-volt AC lines, extension speakers, etc. Full 175 feet of highest quality wire with tough, weather-resistant insulation. Complete with handy drum for spooling wire for storage. Limited quantity **\$2.39**

BRAND NEW METERS

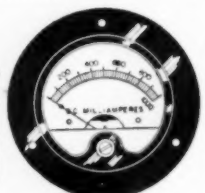Dejur Model 310 meter for all-around ham and test applications. 10 ma DC basic movement, 3 1/4" diameter flange; 2 1/2" body, 1 1/4" deep. Stock up on these while they last.
MA-2036 each **\$1.95**



Iron Core FM and AM IF TRANSFORMERS

Highly efficient for new construction and replacement. Hi-Q adjustable iron cores provide high selectivity and gain. Only 2 1/2"x1 1/2" square; spade lug mounting.

MA-2296 10.7 MC IF Transformer.....	each 49c
MA-2039 455 KC IF Transformer.....	each 35c

GRILLE CLOTH

Never before at our low price! Highest quality, golden-tone grille cloth, styled to harmonize with all cabinet designs. Generous 50" width. **\$1.79** per yard

Intercom Transformer Set

One transformer to match voice coil to grid, another for 50L6 and similar output tubes. Both of these fine units PLUS a momentary DPDT spring return push-button switch for less than value of one transformer alone! These are small, strap-mounting transformers.

Only 98c for All Three Units!

THIS MONTH'S SPECIALS!

T-17 Microphone and plug; used; good.....	79c
25 mh iron core RF choke; 100 MA DC.....	19c
25 mmf butterfly condenser.....	33c
50 mf butterfly condenser.....	33c
Mercury switch; flexible 18" leads.....	15c
Brand new BC-366 Jack Box.....	15c
SPDT Slide Switch; black bakelite knob.....	15c

ORDER FROM THIS AD!

Send 25% deposit with order. Pay balance plus postage on delivery. Get your name on Mid-America's select mailing list and get first crack at latest, greatest values in radio parts, electronic equipment, tubes, etc. Send orders to Desk E-69. Minimum order \$2.50.

MID-AMERICA CO. Inc.

2412 S. Michigan Avenue
Chicago 16, Ill.

luncheon meeting at the Jung Hotel, New Orleans, on March 15th. Admiral Stone said it was his personal opinion that the communications branches of the three services are leading all others in coordination under the unification of the armed forces. He described what is being done by the Joint Communications-Electronics Committee and declared that, as a result, the facilities of each service are being made more readily available to the other services. He cited the Berlin airlift as a good peacetime example of mutual support on the part of all three branches of the armed services. "It is truly an inspiring illustration of how two services—the Army and the Navy—can and are supporting the Air Force which is assigned the primary responsibility for accomplishing the task," he said.

The charter was presented to the interim president of the chapter, Harry B. Lackey, District Manager of the Southern Bell Telephone & Telegraph Co. Admiral Stone's speech was broadcast over a local radio station.

New York

The March meeting of the New York Chapter was held at the Officers' Club on Governors Island and commemorated the 86th anniversary of the Signal Corps. In honor of the occasion, the Chapter President, George P. Dixon, presented a pictorial history of the Signal Corps from its pre-Civil War days to and including World War II. The guest of honor was Maj. General Francis H. Lanahan, Commanding General at Fort Monmouth.

Philadelphia

The results of the annual election of officers for the Philadelphia Chapter have been announced as follows: W.

W. Watts of RCA Victor was re-elected President; William H. Knowles of International Resistance Co. was elected 1st Vice-President; Leslie J. Woods of Philco Corp., 2nd Vice-President; Joseph Bergman of the Signal Corps Stock Control Agency was re-elected Secretary; and W. F. Denkhaus of the Bell Telephone Company of Pennsylvania was re-elected Treasurer.

Pittsburgh

Chapter members attended a meeting of the Institute of Radio Engineers on March 14th at the Mellon Institute Auditorium. Mr. R. E. Stark, Vice-President of the Stupakoff Ceramic & Manufacturing Company (a group member of AFCA) spoke on "Ceramics That Talk."

Sacramento

The March meeting of the Sacramento Chapter featured a talk by Mr. Gordon A. Stevens of the Eastman Kodak Company. Mr. Stevens discussed the latest developments in high speed motion photography and the Di-transfer Process used in processing and printing color negatives. Prior to the meeting, chapter members and their guests from the Woodland Camera Forum of Woodland, California, and from the Sierra and Sacramento Signal Depot Clubs of Sacramento, reviewed an exhibit of aerial photographic equipment.

St. Louis


The St. Louis Chapter held a dinner meeting on March 21st in the Victoria Room of Garavelli's Restaurant. The Southwestern Bell Telephone Company furnished three sound movies for use at the meeting — "Trouble Underground," "The Telephone Hour," and "Stepping Along with Television."—30—

Bill Silverman, engineering student of Bronx, New York, alternates three months of study with three months of radio operating experience, scheduled over a two-year period. Aiming for a career as a radio-electronics engineer, Bill plans to specialize in marine equipment when he graduates and has chosen design as his field. As radio officer on the S.S. Marine Perch, he travels to Africa, England, and South America, while his classmates have to be content with less romantic jobs, and on top of all this experience and fun, he earns about \$300.00 for each trip.



HOW TO SOLVE TV RECEPTION PROBLEMS


IN LOCAL AREAS

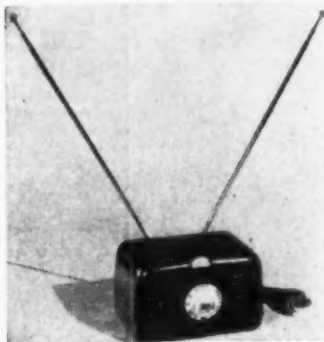

Jerrold In-Tenna is the only indoor TV antenna that will give you clear pictures on ALL TV stations in your area. It can be oriented easily to reduce noise and ghosts. The tuned pre-amplifier helps eliminate all kinds of interference from FM, TV and AM. It is easily and quickly installed in any home or apartment. The Jerrold In-Tenna will give your TV set the same performance that you could expect from a costly outdoor installation. List \$42.50

See the Jerrold In-Tenna at your radio wholesaler or parts jobber, or write to us for information.

IN FRINGE AREAS

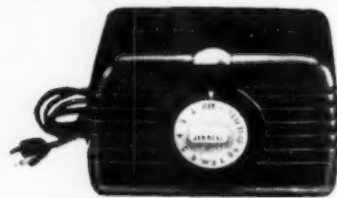

The Jerrold TV-FM Booster has a gain of 20 to 30 times over the entire 6 megacycle bandwidth of all TV channels—plus the FM band. Because of its high gain, Jerrold TV-FM Booster pulls weak stations out of the "mud" to give you the clearest possible pictures. Sight and sound tune together. There is no regeneration whatsoever. All kinds of interference, as well as ghosts, are either greatly reduced or completely eliminated.

See the Jerrold TV-FM Booster at your radio wholesaler or parts jobber. Or write to us for information. List, \$37.50.

JERROLD ELECTRONICS CORP.
CITY CENTRE BUILDING
121 N. BROAD ST. PHILA. 7, PA.

Television Receivers

(Continued from page 43)

voltage is obtained from a 4.5 mc. resonant circuit in the screen circuit of the tube and transferred to a 4.5 mc. amplifier, and from here to a ratio detector. Following this are two stages of audio amplification before the audio signal is fed to a loudspeaker.

Advantages of the Intercarrier System

Now that we have examined the underlying principles of the Intercarrier system and noted its application to commercial receivers, it might be well to evaluate its advantages and limitations. The greatest single advantage offered through the use of the Intercarrier system is its relative independence of many of the difficulties which beset the local oscillator and which affect the quality of the output in a conventional television receiver. Thus, consider what happens when the oscillator frequency drifts. In both systems, the resultant video and sound i.f. values will shift. Suppose that this shift is 200 kc. In a receiver employing the conventional television system, the video signal will be negligibly affected because 200 kc. is unimportant when compared to the total video spread of 4.0 mc. In the sound i.f. system, however, the discriminator linearity extends usually for ± 100 kc. on either side of the i.f. carrier frequency and a shift of 200 kc. will remove the signal from the linear portion of the characteristic, distorting or causing the complete loss of audio output.

Compare this with the same effect in a receiver employing the Intercarrier system. Since separation of the two signals does not occur in the i.f. system, the only effect this produces is to shift the position of the two signals along the i.f. response curve. This will alter somewhat the amplification ac-

corded these signals, but not to an appreciable extent since 200 kc. is negligible compared to the 4.5 mc. bandpass. When the two signals reach the video second detector, the resultant 4.5 mc. beat note will be obtained since the difference between the two carriers is fixed at the transmitter and nothing that occurs at the receiver can alter this relationship. The 4.5 mc. beat note will then pass through the video-frequency amplifiers and into the sound system unaltered by the local oscillator change in frequency.

Shifting of the local oscillator frequency due to hum or microphonics will likewise have negligible effect in the Intercarrier system because no matter how the oscillator frequency changes, the difference between the two carrier frequencies remains 4.5 mc. and it is from this difference that the sound output is obtained.

Fine-tuning controls are employed in conventional television receiver sets to counteract any drift of the oscillator frequency. Since oscillator drift—within nominal limits—does not appreciably affect the operation of a set using the Intercarrier system, this control may be dispensed with. However, several of the Intercarrier receivers on the market still include a fine-tuning control. With the control available, less precautions need be observed in designing the front-end tuning system, with resultant economy.

Another advantage offered by the Intercarrier system is a simplification of the design of the receiver. The number of stages in the sound i.f. system is reduced by two to three since the sound signal is first passed through all the video amplifiers before being transferred to the sound system. Furthermore, tolerances of the local oscillator are not critical, permitting the use of cheaper components, with less care required in the layout. In the i.f. system, the bandpass may be made symmetrical, as previously demonstrated, permitting the manufacturer

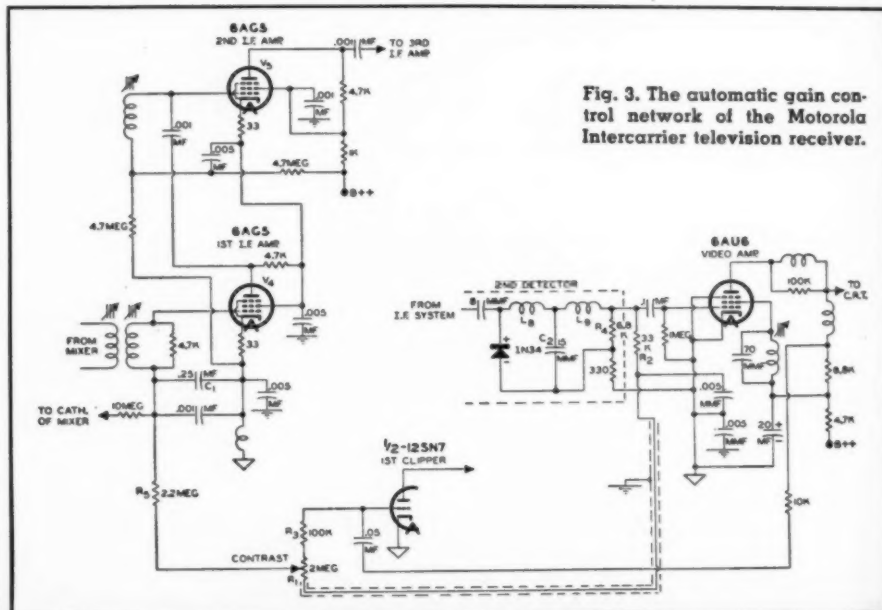


Fig. 3. The automatic gain control network of the Motorola Intercarrier television receiver.

**Crammed with
Bargains You'll
Never Again See!**

**Write Now or
Phone WO 2-7230**

**SCOPESCOPE
INFRARED**
Image - Converter
tube HiSensitivity
simplified design
2" dia., Wil-
nite screen—
resolution up to
60 lines/in.
\$22.00

Each... **\$8.98**
FORMER
 .5VCT/10A 10
 **\$5.95**
 KV§s&
 **\$12.95**

AMPLIFIER KITS—10 Watts HI FI

HIGH FIDELITY—Self-balancing cath. follower circuit with perfect linear response, phase inverter, 2-2A3, 6BG6 GP, 58TGT, 6SN7GT, incl. tubes..... \$14.95

HI KIT—with ALL-ELECTRONIC stage for picking up etc. magnetic & xtal pickup, 6X4, 6AR5, 6AV6, 6BE6, 6BD6, 6BE6, ECKT, Self-balancing cath. foll., phase inv. GP, 4 other stages plus all chassis, less output xfmr..... \$24.95

CHASSIS, less output xfmr..... \$14.95

WIRE & CORD sets 6 ft. UL..... \$1.30

Wire 100ft. assorted rolls..... 2.95

Intercom, Star-Wire..... 3.95

Meg long shaft 6 foot..... 2.95

TV COMPONENTS

A. Utah 9318 H-Bling	
Osc. Xfmr H'Sid.	\$0.98
U.T.C. 85002 Z-Bling	
Osc. Xfmr H'Sid.	.98
C. Yoke MagnDeflec aim	
RCA 20D1	4.23
D. Ion-Trap Magnet	
RCA 203D1	2.79
E. FocusCoil for MagnDefl	3.79
F. Hiv Flybak H'OutXfmrSimRCA	
211T1	4.98
H. V'Out Xfmr 500mmf/10KV	.40
I. Jfeff Hiv Cnder 500mmf/10KV	.40
J. Effers Hiv Cnder 500mmf/20KV	.75
K. TWIN 500ohmTV cable 100ft.	2.25
1000 ft.	\$17.50

DECALS T. Set of 8 10c
Write for Complete List RCA TV
Components—Big Discounts.

HELLER SPEED TACKER for
SPEEDY Two
cable installation

\$3.98

SPECIAL
STAPLES for above
HvyDty 5000 Boxed.
\$2.98





SNOOPERSCOPE INFRARED

Image - Converter Tube HiSensitivity simplified design 2" dia. Willemite screen Resolution up to 350 lines/in.

\$8.98

Write for qty. Prices, Each.

866A'S & XFORMER

115VAC 60cyc. Output 2.5VCT/10A 10 KV Insul.&Sckts.&Tubes	\$5.95
GE872A's&Xformer 12.5KV/sckts.&tubes	\$12.95


Remarkable Buy!
GE2J1G1 Selsyns
 With DATA 24V
 110V 60 cycle AC
 Used Test-
 ed. Two for **\$149**

RM29A CONTROL UNIT
 Self-Contained in 1
 Ringer Circuit.
 Locking-type selector;
 provides either Monitor
 or Direct Read Control,
 or uses as Telephone

BRAND NEW...\$8.95
 Pair (TW) for **\$15.95**

Hi Gain Dynamic Mike Xfmr
 UTC Super line 1000-6000 Hz
 4000 ohms tapped 25k &
 150 ohms 150V shield-
 50 Herm Sid

25k to	59¢
10 for	\$4.50



XTAL DIODES, THERMISTORS

IN34	\$1.19; 2 for \$2.20
10A	10 for \$10.00
IN21	21A, 22, IN23, 23A Ea.
\$1.00; 12 for\$10.00
IN21B	IN27
Ea.	\$3.75; 10 for \$14.99
D122B, IN26	\$3; 10\$27.50
D168391 Therm Compensator,	\$2.00;
3 for\$5.00
DI7036 HFW Meas.	\$60;
10-B Time Delay	\$60; 3 for \$2.50
VARIATOR CW20259 Type	38 C
USN\$2.95

[illegible]

pts. 98c



BASIC FOTOFLASH KIT
—Complete Pwr Supply incl
condrs, tubes, xfmrs, circ
diag, all instructions &
FOTO-FLASH Lamp & re-
flector. For 115 VAC. Only **\$29.95**

STUDIO KIT—Famed Air
Corps 1503 Set for 115V AC or bat-
tery w/ 2 lamps & refs. A **\$53.95**
terprise box of

FLASH—CONDENSERS—FILM	
7mfid 2500VDC/21.9 Watt Sec's.	\$2.75
51109-5 Watt-Sec's) for	12.50
USN perspective projector	3.98
15mf 330VAC 1800VDC	3.98
25mf 330VAC 1800VDC	6.49
16mf 600VAC 2800VDC	6.95
16mmPAN5061mGSAP	Camera.
54 rolls for	5.49

AMGLO Electronic Flash Lamps					
No.	Wattage.	Vd.			
5804X	100	15-25	\$13.95		
584RX	200	15-80		Each	
484RX	600	80-200		15.50	
68UM	200	13-60		13.50	
78PM	300	20-100		13.50	



BC456 Modulator Asst. Less Tubes & Dyn. 98c

BC457 " " " " " " " " " "

Tubes \$3.49

BC455 6-9.1 Mc. Used Less Dyn. 7.49

BC455 Less Tubes & Dyn Asst. 4.95

Collins Art-13 Speech Amplifier
Dynamic or Carbon Microphone, Audio Driver to P.P.C. Monitor tube. Less Tubes **\$4.50**
1-198 Sigen NEW
Test Coil 750-15 Mcs. Modulated attenuated w/10-100-200ohmpt & Pur supply 115VAC & 3 tubes 37, 41 & 62A NATL N Dial case to add. Range 100V Metal Case **\$14.95**

BC906 Monitor & FreqMtr **\$29.95**
RC1066 RCVR **\$29.95**
4-196 SigGen 150-225 Mcs. New 7.95
FreqMtr WaveMtr & Control Unit
 RC1162 p-RC1150
 150 to 2100Mc
 Ideal convert Citizen's
 Band Radio
 1150 Gcncy Pwr
 Supply, w/19 tubes
 New **\$25.95**
 SAME less **\$19.95**
 (D.T.)
FreqMtr & WaveMtr

Only (LT)	\$13.99
Pwr Supply Only	
(LT)	\$8.99
GIBSON Gal Xmtr	
.....	\$4.95
6' Gal Kite 17x17s	
38'	\$2.98
G' Gal Hov'sack W nrf	
.....	.98
G' Gal Sug Lamp Ant	
.....	.89
G' Gal Ballast 13W	
.....	4.98
G' Gal 13W Chptr	

DU BLES			
1A7	..\$0.49	5V5GT	..\$0.38
1A4T	1.26	5Z3	.81
1A7GT	.69	0-11 Ballast	.49
1B1 4016	..	0-127 155	.85
1B21/471	2.95	0AC7	.69
1B23	4.80	0AG5	.85
1B24	4.80	0AG7	.85
1B27	8.97	0AG7	1.27
1L4	..	0A5	.85
1L5GP	1.25	0AK5	.85
1GGGT	..	0AL5	.79
1N1	..	0B6	1.00
1N1.5	.75	0B87G	4.79
1N5GT	.69	0AT6	.49
1P1	..	0B87	.85
2A3	.86	0B8G	1.05
2B22-GL559	..	0H46	..
2C34	..	0C5	.85
2C34 RK34	.55	0C4	.27
2C40/446A	1.49	0C6	.71
2C42	2.44	0C7	1.09
2C44	1.69	0E8	.71
2C45	..	068X 1613	.71
2C43S	6.98	0F8G	1.04
2D21	1.20	0H0GT	.38
2E23	45.00	0RGT	.69
2E25 HY65	2.48	0J6	.85
2J21	11.98	0K5GT	.85
2J31	9.95	0K6	.69
2J33	14.50	0K7G	.64
2J34	18.95	0R8	.86
2J35	13.95	0R6	.86
2J42	29.85	0L7	.75
2J48	45.00	0N17 1615	.85
2J50	45.00	0N17	.85
2K20	6.95	0SA7GT	.60
2V3G	1.05	0SF5	.49
3B17/1291	..	0S8T	.75
3B25	1.95	0SH7	.72
3C23	2.45	0SH7GT	.94
3C25	2.45	0SN7GT	.69
3E29/820B	3.85	0U5 AG5	.81
4B27	2.49	0UGGT	1.49
4J47	45.00	0V6GT	.69
5J20	17.98	0V6GT	.69
5R4GY	1.25	0X3GT	.58
5U4G	.15	0Z7	.85
5U4G	.95	0Z7G	1.23

NEW STANDARD		
77R5	\$0.70	702A/702B\$1.49
702A/1203A	.38	702A/802B1.45
77S5/1201	.89	707B
77L7	.86	1011A/8011
77L7	.86	
70V7	1.04	722A/287A
30V Ballast	.47	723
10-4B Bal.	.47	723
30V	.47	723
12A6	.23	808
12AH7GT.	.87	810
12H6	.36	810
12K8	.85	813
12K8	.85	816
12SK7GT	.58	824
12SG7	.67	832
12SG7GT	.86	832
15-4 Ballast	.49	845
24C 3C24	.53	857A
24C 3C24	.53	860
28D7	.37	862A
30V	.78	875
30/44	.39	902
41	.58	930
43	.69	935
43 Special	.72	954
46A/24	1.90	954
46A/VT2	2.11	954
511A	.25	1297
515A	.25	1297/184
520H	19.49	1619
5207L	14.95	1625
5207L	14.95	1625
5047L	1.90	1629
527A	2.08	2020
527A	2.08	2020/Bukob
57B1B	.75	2193
5888A	.40	2193/2C22
597C7M	18.98	8012A
597C7M	18.98	8013A
531	1.80	8020
534	2.45	9001
534A/975	1.95	
534A/975	1.95	

TYPES		BLOWERS—ALL TYPES	
06	\$0.25	40 CFM/28vac Hvy	
	9.95	LR Type	\$3.40
	12.95	100 CFM/12	
	4.95	vacd	\$5.95
003		100 CFM/28	
072	1.85	vacd	\$4.95
7	2.98	Xfmr 12 or 28V	
8	9.80	to 115vac	\$1.98
005	11.95	250 CFM/28 vacd	8.95
06	49.00	250 CFM plus 28/115vac	\$10.95
08	3.90	Xfmr	
54/45	8.00	100 CFM/115vacd Hvy	\$7.98
4 Bal.	4.49	Dty	
		100 CFM/115vacd Hvy	\$10.98
		Dty	

ANTENNAS

Mobile minded? UHF
12" 30cm AT1 APN2,
ATSARR1 ATN com-
vertible, Citizen's
Band Threaded Coax
Term Insul Silb Pl
Cont w/waterproof gask,
Bango & hardware for
MOBILE mtrg.

49c

BRAND NEW...
3 for \$1.00; PL250

1	2.79	10' above	3.99
1	3.49	ANTENNA AN-30	
12	8.98	Telescopic Whip	
1	1.95	Collapses 12" to 9 ft	
1	SGP1	New O'Scan plug, ea.	\$1.49; 2 for \$2.49
1	3.95	ANTENNA AN-303	
1	2.98	Spring Swiveled Whip 33" lg.	\$1.25; 2 for \$1.98
1	12.95	ANTENNA MS49-54, 18 ft	
1	6.49	Whip	\$3.98
1	2.75	ANTENNA MS49-52, 12 1/2 ft	
1	4.95	Whip	\$1.69
1	6.49	MS49-55, 18 ft	
1	4.75	Whip	\$1.69
1		MS49-50, 25 1/2 ft	
1		Whip	\$1.98

3MP7 13.98
 7, \$2.69;
 for 4.98
 3.95
 MP7 G.E. Magn
 TV \$14.95
 for \$27.50; 10
 ... \$130.00

ii & Breakage

RECTIFIERS
 Selen FEDERAL
 100ma, 72c; 200
 ma 98c; 10/58.80
 Selen CT 18Vn/
 12out 1.5 A 1.49

Bridge Type	Price
1a	Out

XMFR
115V
PLATE
1400VCT
1.2A.5
Vina
1320VCT
2.7A.2
4A
1000VCT
tap,
8A.5V/6A
840VCT/110ma.530V/21ma
1A.6.3V/3A Cnd Hiv Hiv
700VCT/120ma.115V/100ma
5V/2A Cnd Hiv Inlet.5
650VCT/120ma.6.3V/2.1A.5
Hivins
500VCT/60ma.6.3V/4A Cnd
420VCT/85ma.6.3V/.9A Cnd

Speed	ViaR [®] Exp.	18V	14V	1.35	\$2.49
18	14	14	3.5	3.29	
18	14	14	5	4.25	
18	15	11		0.95	
18	15	13		14.95	
18	15	27		22.95	
36	28		3.9	1.49	
36	28	3.5		6.49	
36	28	5		7.25	
36	30	10		17.95	
36	30	18		26.95	
36	30	27		36.95	

00ma 90Vbias	87.2	90	75	0.15	1.49
V 550ma 6.3V		PRECISION RESISTORS			
x5V/3A	6.95	"TAB" — Specialists in precision resistors. Write quantity prices. NO MPFRS. CHOICE.			
x5V/3A	4.05	we ship types in stock:			
x6.3V/2A	32.95	116-950ohms @ 30c;			
SA Col		10/ \$2.50			
SA Col	3.29	100K-950ohms @ 40c;			
Vina	1.29	10/ 3.50			
Vina	2.39	MEGOHMS 2,855 4.5 9.95			

SOCKETS—All Types!

A.	RCA 5-pin GIANT for 803, RK28 USN	...	30c
B.	Johnson 4-pin bayonet for 86G, etc.	...	35c
C.	2-prong STEATITE Johnson, 807...	...	35c
D.	Johnson 7-pin Steatite 829B/829D...	...	35c
E.	Small Shell DUODECAL for 2BP1...	...	35c
F.	2-prong STEATITE Johnson, 807...	...	35c
G.	5-pin ACORN 9/16" dia.	25c
H.	Johnson 122-234 5/16" 721w/tube	...	35c
I.	2-prong STEATITE Johnson, 807...	...	35c
J.	5-prong STEATITE Johnson, 807...	...	35c
K.	7-prong STEATITE Johnson, 8025...	...	35c
L.	2-prong STEATITE Johnson, 807...	...	35c
M.	MIN 7-pin mica 347-913 & shield...	...	35c
N.	MIN 7-pin Amph 78-7FT, etc.	11c
O.	2-prong STEATITE Johnson, 807...	...	35c
P.	4-pinAmphenol 40RHS 44mtCeramic 2	...	35c
Q.	OCTAL SpindleplatesteatiteCin, etc.	...	35c
R.	4-pinAmphenol 40RHS 44mtCeramic 2	...	35c
S.	KLSTRON spindlelock plate CINCH	...	11c
T.	KLSTRON socket Cinch, etc.	35c
U.	KLSTRON spindlelock plate CINCH	...	11c
V.	OCTAL Amphenol 7888 micaKltteCeramic	...	35c
W.	11-pin 78811/931 Amphenol,	15c
X.	11-pin 78811/931 Amphenol,	15c
Y.	HiVols Safety 4pinAmph777A	...	35c
Z.	HiVols Safety 4pinAmph777A	...	35c
AA.	HiVols Safety 4pinAmph777A	...	35c
AB.	HiVols Safety 4pinAmph777A	...	35c
AC.	HiVols Safety 4pinAmph777A	...	35c
AD.	HiVols Safety 4pinAmph777A	...	35c
AE.	HiVols Safety 4pinAmph777A	...	35c
AF.	HiVols Safety 4pinAmph777A	...	35c
AG.	HiVols Safety 4pinAmph777A	...	35c
AH.	HiVols Safety 4pinAmph777A	...	35c
AI.	HiVols Safety 4pinAmph777A	...	35c
AJ.	HiVols Safety 4pinAmph777A	...	35c
AK.	HiVols Safety 4pinAmph777A	...	35c
AL.	HiVols Safety 4pinAmph777A	...	35c
AM.	HiVols Safety 4pinAmph777A	...	35c
AN.	HiVols Safety 4pinAmph777A	...	35c
AO.	HiVols Safety 4pinAmph777A	...	35c
AP.	HiVols Safety 4pinAmph777A	...	35c
AQ.	HiVols Safety 4pinAmph777A	...	35c
AR.	HiVols Safety 4pinAmph777A	...	35c
AS.	HiVols Safety 4pinAmph777A	...	35c
AT.	HiVols Safety 4pinAmph777A	...	35c
AU.	HiVols Safety 4pinAmph777A	...	35c
AV.	HiVols Safety 4pinAmph777A	...	35c
AW.	HiVols Safety 4pinAmph777A	...	35c
AX.	HiVols Safety 4pinAmph777A	...	35c
AY.	HiVols Safety 4pinAmph777A	...	35c
AZ.	HiVols Safety 4pinAmph777A	...	35c
BA.	HiVols Safety 4pinAmph777A	...	35c
BB.	HiVols Safety 4pinAmph777A	...	35c
BC.	HiVols Safety 4pinAmph777A	...	35c
BD.	HiVols Safety 4pinAmph777A	...	35c
BE.	HiVols Safety 4pinAmph777A	...	35c
BF.	HiVols Safety 4pinAmph777A	...	35c
BG.	HiVols Safety 4pinAmph777A	...	35c
BH.	HiVols Safety 4pinAmph777A	...	35c
BI.	HiVols Safety 4pinAmph777A	...	35c
BJ.	HiVols Safety 4pinAmph777A	...	35c
BK.	HiVols Safety 4pinAmph777A	...	35c
BL.	HiVols Safety 4pinAmph777A	...	35c
BM.	HiVols Safety 4pinAmph777A	...	35c
BN.	HiVols Safety 4pinAmph777A	...	35c
BO.	HiVols Safety 4pinAmph777A	...	35c
BP.	HiVols Safety 4pinAmph777A	...	35c
BQ.	HiVols Safety 4pinAmph777A	...	35c
BR.	HiVols Safety 4pinAmph777A	...	35c
BS.	HiVols Safety 4pinAmph777A	...	35c
BT.	HiVols Safety 4pinAmph777A	...	35c
BU.	HiVols Safety 4pinAmph777A	...	35c
BV.	HiVols Safety 4pinAmph777A	...	35c
BW.	HiVols Safety 4pinAmph777A	...	35c
BX.	HiVols Safety 4pinAmph777A	...	35c
BY.	HiVols Safety 4pinAmph777A	...	35c
BZ.	HiVols Safety 4pinAmph777A	...	35c
CA.	HiVols Safety 4pinAmph777A	...	35c
CB.	HiVols Safety 4pinAmph777A	...	35c
CC.	HiVols Safety 4pinAmph777A	...	35c
CD.	HiVols Safety 4pinAmph777A	...	35c
CE.	HiVols Safety 4pinAmph777A	...	35c
CF.	HiVols Safety 4pinAmph777A	...	35c
CG.	HiVols Safety 4pinAmph777A	...	

FILAMENT TRANSFO

6.3VCT/1A 16.6VCT/2.5A Csd
6.3VCT/2A 17.5VCT/3A Csd
2.5V/10A(866A Ximr)15KV1
2.5VCT/20A 6.75Vin or 6.75
200V/20 240V 15V 15V
6.6V/12A 6.6V/10.6A 3.5V
1.75A 1.75A
5V/15A KENYA KENYON
5V/115A KENYA KENYON
4.2V 5A HVIN 819440.
12.0V/6A Hmtchly CSD.51

PLATE TRANSFO

1200VCT/300MA Csd HVINs
2100V/10MA USN Csd HVINs
2100V/10MA USN Csd HVINs
3000V/10MA ChlTransWe D
3000V/10MA for Tube 2X21
10800VCT .095A Csd RATED
Csd RATED

13.5Hly/1
17KV Infr
15-20Hly/1
Caned 2.5
12HY/30
3HY/40V
30HY/40
15HY/130
BkltT/bd
50HY/12V




MERS	1.1	1.8	3.3	5.	10
HV.....	\$1.98	1.2	1.9	3.5	5.5
C S-60.....	3.49	1.25	2.2	3.673	6
KRYON™	4.49	1.3	2.25	3.75	6.5
T/20A.....	2.99	1.35	2.5	3.9	7
OKV test	4.49	1.4	2.7	4	7.5
.2.5V/		1.5	2.75	4.25	8
OFormer..	4.98	1.65	2.8	4.25	8.5
.....	4.98				
.....	12.95				
9.98; 100/\$49					
2 for 2.79					

Any Size Above 75c: 10 /\$6.50

Vac Precision HIV Resistors

SPECIAL \$1.00 10 to 37.50
1% .05 accuracy
1 MEG/MFCI .05/549
JAN-R29 .**\$1.98; 6/510**
30 MEG MVFR 20Watt
30 MEG MVFR 20Watt .**6/510**
50 MEG/IRC MVER/25W/
40KV/mtg.**\$1.98; 6/510**
30 MEG/20K 1% .**\$2.95**
1% accuracy
50 MEG/20KV 1% SPRAGUE
MTR w/o-
Mtr
IRC ATTENUATORS—100,000 ohms 20 pos \$14.98
250,000 ohms 20 pos 4.98

● THAT'S "T A B" THAT'S A BUY ●

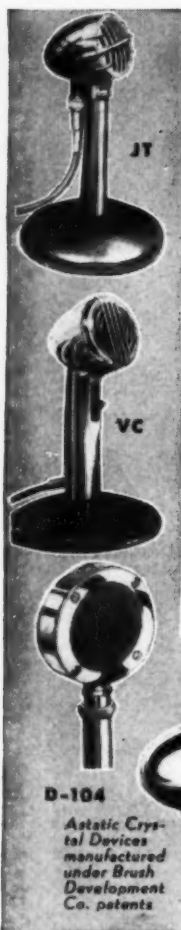


Here's Why **ASTATIC** MICROPHONES with CERAMIC ELEMENTS ARE GAINING WIDE, ENTHUSIASTIC PREFERENCE

OVERSHADOWING even the important technical advantages is one simple but undeniable fact—sound transmitted by Astatic Ceramic Microphones is the **MOST NATURAL** you've ever heard! Everyone has different words to describe the remarkable quality of voice reproduction . . . all agree that it is more **NATURAL** than anything they've heard. Try it. Judge for yourself. Of course you'll also be interested in the immunity of Astatic Ceramic Mikes to tropical heat or arctic cold, high humidity or dryness. Frequency response is unaffected through wide temperature range. They're amazingly rugged against accidental shocks and stresses, operational abuses which shorten or impair the service life of other types. Adaptable to existing hook-ups without requiring other changes in equipment.

Model	List Price	Cable Length	Output Level*	Range c.p.s.
D-104C	\$24.80	7'	-58 db.	30 to 7,500
IT-30C	18.15	7'	-62 db.	30 to 10,000
IT-40C	18.15	7'	-62 db.	30 to 10,000
T-3C	25.55	7'	-62 db.	30 to 10,000
VC	13.15	7'	-62 db.	30 to 10,000
VC-I	13.15	7'	-62 db.	30 to 10,000
CC	9.95	7'	-62 db.	30 to 10,000
CC-I	9.95	7'	-62 db.	30 to 10,000

*0 Reference Level = 1 volt per bar

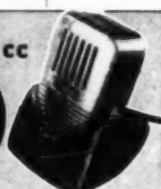

Low FACTORY-TO-YOU Prices New! **MIDWEST TELEVISION**

with **BIG 75 Square Inch SCREEN**

- 12½" PICTURE TUBE
- 12 TELEVISION CHANNELS
- PICTURE-HOLD CONTROL

EASY TERMS

Other Models Include:
SYMPHONY GRAND AM-FM RADIO-TELEVISION-
PHONOGRAPH with
DUAL-SPEED RECORD
PLAYER



30 DAYS TRIAL

Also
**Sensational NEW
MIDWEST RADIOS**
with DUAL-SPEED
Phonograph

MIDWEST RADIO & TELEVISION CORP.
Dept. T37A 909 Broadway, Cincinnati, Ohio

Name _____
Address _____
City _____ Zone _____ State _____

Send for TELEVISION Folder, Prices and NEW 1949 MIDWEST RADIO Catalog

new **Bogen H 623** 23 WATT UNIVERSAL MOBILE AMPLIFIER



- FOR 6 VOLT DC and 110 VOLT AC
- SIX POSITION MULTI-RANGE TONE CORRECTOR
- "CRISP" POSITION FOR IMPROVED OUTDOOR PERFORMANCE
- SPECIAL MOBILE PHONOGRAPH PICKUP
- REMOTE CONTROL OF PLATE SUPPLY
- CONSTANT VOLTAGE OUTPUT
- UNDERWRITERS' LABORATORIES APPROVED

LIST PRICE: \$177.50
(ZONE 2: \$182.00)

David Bogen
CO., INC.

663 BROADWAY, NEW YORK 12, N. Y.

Write for literature

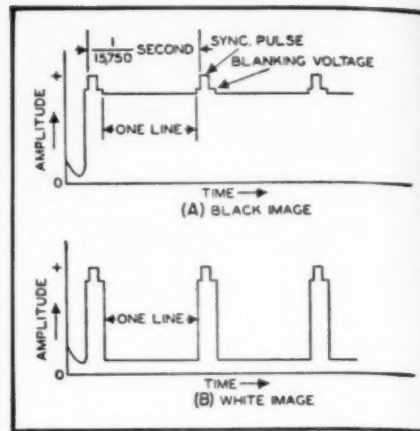


Fig. 4. The average voltage of a video signal varies with its modulation.

to design the oscillator so that it operates above the video and sound carriers on the lower television band and below these signals in the upper television band. Since it is cheaper to construct a stable low frequency oscillator than a stable high frequency oscillator, additional economy is possible. All these considerations point up the desirability of using the Intercarrier system.

Disadvantages of the Intercarrier System

The Intercarrier system is not without disadvantages, however. The appearance of the sound at the loud-speaker is dependent upon the mixing action that occurs in the video second detector. If something should happen to prevent the transmission of the video carrier—and this can and has happened—then no output at all is obtained at the receiver. Note that this is peculiar to Intercarrier systems and is not true in sets employing the conventional system. While it may be argued that the foregoing set of conditions seldom occur, yet there is another manifestation of this same effect that appears more frequently. Thus, when a white line or series of lines are being transmitted, the video level drops down to a very low value. See Fig. 4. If care is not observed at the transmitter, the level may easily drop to zero (corresponding to 100 per-cent modulation) resulting momentarily in no video signal. This causes the sound to disappear, also momentarily. This is usually repeated at line frequency (15,750 cycles) or field frequency (60 cycles) producing a 60 or 15,750 cycle buzz in the receiver. (The 60-cycle buzz is more evident because most people cannot detect a note as high as 15,750 cycles.) To prevent this, it is necessary to check carefully transmitter modulation. Current FCC regulations merely specify that the amplitude of the video carrier, when transmitting maximum white, may not be more than 15 per-cent of the maximum video carrier amplitude (which is attained when the sync pulses are sent). If this is amended to specify a definite minimum, say 10 per-cent,



GET THE

ALLOWANCE

SURPRISE TRADE-IN ***OF YOUR LIFE!***

On your USED TEST and COMMUNICATION EQUIPMENT

for **BIG SAVINGS** on

hallicrafters TELEVISION

Yes, now you can trade your used, factory-built Test & Communication Equipment . . . apply the generous "Surprise" allowance against the purchase of famed Hallicrafters TV—the television equipment that steals the show for its brightness, clarity and advanced engineering features.

So don't delay. Get YOUR trade-in deal working today. Simply tell us what you have to trade. We'll respond with an extra-liberal offer that's sure to surprise and delight you. Wire, write, phone or use the handy coupon below.



HALLICRAFTERS TV Model 509

The latest addition to the Hallicrafters TV line. Push button tuning on all 12 channels. **Dual Focus** for larger round pictures with 56 sq. in. rectangular picture or 64 sq. in. full circle picture for dramatic close ups—all at a flick of a front panel switch. Mahogany veneer cabinet. Transparent safety shield. 19 tubes plus 3 rectifiers.

ONLY

269⁵⁰

Complete with **ALL TUBES**. Shpg. Wt. 105 lbs.




HALLICRAFTERS TV Model T-506

Here's Television at a price, with all the big set features. 12 channel push button tuning. Static free FM sound reception and 23 sq. in. screen. 18 tubes plus 4 rectifiers. Shpg. Wt. 50 lbs. **Now ONLY**.....

149⁵⁰

Formerly sold for \$199.50

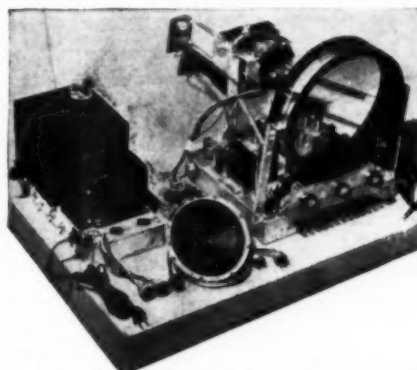

Model T-64

Chassis unit only, of Model T-509. Shpg. Wt. 60 lbs.

Plan your own TV installation and save money! 95 sq. in. picture with 12" tube; 64 sq. in. picture with 10" tube. Push button tuning on all 12 TV Channels. New **DUAL FOCUS** Switch for larger, round picture. Factory-wired and tested. Complete with 19 tubes plus 3 rectifiers, less picture tube. **Only**

\$169⁹⁵

Bracket for 12" tube installation.....\$ 8.50 extra
10" picture tube—type 10BP4.....\$34.00
12" picture tube—type 12LP4.....\$60.00

TIME PAYMENTS AVAILABLE

"Surprise" Trade-ins available on used, factory-built equipment toward purchase of any item in our complete Hallicrafters line. Latest Hallicrafters' catalog free on request.

**ALL PRICES F. O. B.
ST. LOUIS**

Phone: CHestnut 1125

FREE!

Big, new 1949 Catalog of Radio, Electronics and Television. The treasure chest of values. Order your copy today!

Walter Ashe Radio Co.
Bill Dubord, W@QDF, Mgr., Amateur Div.,
1125 Pine St., St. Louis 1, Missouri

R-49-6 a

☐ Rush bigger-than-ever "Surprise" trade-in allowance on my _____ for Hallicrafters TV.
(describe used equipment)

(show model of new equipment desired)

☐ Mail me my copy of latest Hallicrafters Catalog.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Walter Ashe **RADIO CO.**

**THE HOUSE OF "SURPRISE" TRADE-INS
1125 PINE ST. • ST. LOUIS 1, MO.**

STAND-BY STORAGE BATTERIES



GOULD Storage Battery—a completely covered black hard rubber case, with wing nut terminals on side. It's 6x10x10" high; non-spillable, 12 v., 34 amp. hours, 5 hour rate; weight 40 lbs. when fully charged. Brand New, shipped in original sealed carton.

Each..... **\$9.95**

ELECTRIC Storage Battery—same description as above. 24 v., 11 amp. hours. Size 8x8x7 1/2" high. Weight 34 lbs. In original sealed carton.




Each..... **\$12.95**

Battery Acid 1275 Sp. Grav.—Can be used in any storage battery—in hermetically sealed bottles. 36 oz. bottle... **79c.** 92 oz. bottle... **\$1.95**

TRANSMITTER-RECEIVER

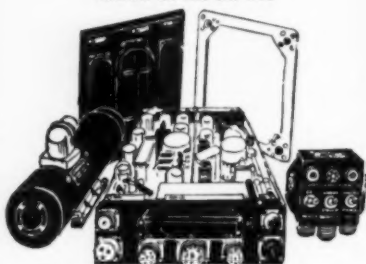Navy Model ABA-1 (CG-43AAG)
Army Model SCR-515A
Known as the BC-645



450 MC—15 TUBES, Brand New

Can be easily converted for phone or CW 2-way communication. Covering the following bands: 420-450MC ham band, 450-460MC for fixed or mobile, 460-470MC for citizens, 470-500MC television experimental. Size 10 1/2 x 13 1/2 x 4 1/2. Contains 15 tubes: 4-7FT, 4-7HT, 2-7E6, 2-6F6, 2-955, 1-WE-316A door knob.

Here is what you get:

BC-645 with 15 tubes
Dynamotor Keyer Unit,
CG-23AABJ
CWD-21AAX Instruction Book
Remote Control Unit. **COMPLETE \$12.95**

TRANSMITTER CONTROL

BOX Type C-30/ARC-5



Mfg. by W.E. Size 4 1/2 x 3 x 3". Equipped with slide fasteners, has 7 push button switches, 1 control switch and two multicontact jacks..... **\$1.49**

SELSYN MOTORS

50 V. 50/60 cycles. Can be used to turn small beam antenna or as indicators. 3 1/2" diameter x 5 1/2" high. Two can be used in series on 110V. A.C. Brand New. **\$4.95**
Per Pair.....



NAVY TBY TRANSCEIVER

28 to 80 Megacycles

Frequency equipment. Types of transmission MCW. Telegraphy and Telephony Power output, .5 watts. Complete with tubes, aerial. Head Set, crystal controlled. Microphone, 3 spare tubes **\$32.50**
and canvas carrying case.....

Watt-hour METERS

GE 1-16 single phase 60 cycle 115-120 volt 5 amp.—two wire—glass case.
WESTINGHOUSE—metal case—115-120 volt 60 cycle—5 amp. single phase.
SANGAMO—metal case—115-120 volt 60 cycle—5 amp. single phase. **\$6.95**
Sangamo 10 and 25 amp. **\$7.95**



Prompt Delivery—25% deposit required on C.O.D. order. Shipped F.O.B. New York—Write Dept. RN6

MICHAEL STAHL, INC.

39 VESEY ST.

New York 7, N. Y., WO 4-2882

then we would insure that the video carrier would never be lost.

Another factor that requires careful observance is the incidental phase or frequency modulation that sometimes develops in the video carrier when it is receiving the video intelligence. It has been found that under some circumstances the video carrier will receive a small amount of phase or frequency modulation while it is being amplitude modulated at the transmitter. In the subsequent mixing that occurs in the video second detector at the receiver, this phase or frequency modulation is passed on to the 4.5 mc. sound signal and is naturally not removed at the FM detector. The result again is a 60 cycle buzz or a 15,750 note.

Precautions are necessary in receivers, too. Here, the greatest single factor affecting proper operation is the relative magnitude of the video and sound carriers at the time they are mixed in the video detector. If the amplitude of the video carrier is very large compared to that of the sound carrier, then the amplitude of the beat note is very nearly independent of the amplitude of the video signal. This means that the FM 4.5 mc. beat note will not be affected by any modulation contained on the video carrier. Now, this stress on keeping the amplitude of the beat note as constant as

possible rises chiefly because the FM detector and the limiter which precedes it are not insensitive to amplitude modulation when it appears in a sizeable amount. Most servicemen believe that an FM detector and limiter will not respond at all to amplitude modulation and this is true if the amplitude modulation is small. However, if it becomes large, then it will affect the output of the FM detector and distort whatever audio signal is present.

The value of 26 db. as the difference between the amplification accorded the video and sound i.f. carriers will insure that the 4.5 mc. beat note receives little amplitude modulation.

Finally, there is the problem of attempting to maintain the sound limiter and detector tuned circuits at precisely 4.5 mc. Any deviation from this value, due to altered components, usage, humidity, etc., will cause the sound signal to be displaced to a non-linear portion of the detector characteristic, thereby producing a distorted output. Nothing short of a complete re-alignment of these stages will correct this condition. In sets using the conventional system, this condition can be corrected by re-tuning the local oscillator using the fine-tuning control.

(To be continued)

ADDITIONAL NOTES ON AMPLIFIER FOR SOUND ON FILM CONVERSION

By ROBERT L. MUHS

AFTER reading Mr. R. L. Newland's very short article on page 104 of the March Radio & Television News, entitled "Amplifier for Sound on Film Conversion," it occurred to me that a simplified circuit could be evolved.


If the amplifier used has a high impedance input and high gain (90 db. or more—such as for a velocity-type mike) a preamplifier stage is unnecessary, and the only requirements are that a photoelectric cell polarizing voltage be obtained from the amplifier "B plus" line and that the PEC signal be d.c. isolated from the amplifier input. The circuit (Fig. 1) covering these suggestions is somewhat simpler than Mr. Newland's.

Should a preamplifier be required, it can be mechanically independent of the projector mechanism. Connection

to the PEC can be made by a good mike cable, preferably 24 μ fd./ft. or better. To further reduce microphonics, a 1620 tube, a 6J7, or a 6SJ7 (in order of preference) should be used. If rubber suspension of the tube socket is necessary, grommets above and below the chassis will isolate the socket well.


To simplify further, an a.c. exciter lamp at 60 cycles can be used without objectionable hum, provided the lamp is rated two amps or above. A four- or five-amp lamp is preferred because of the stronger signal to the PEC, but probably a separate transformer would be required. The only time hum is noticeable is when there is no film in the sound gate, and this can be taken care of with the volume control during the threading time.

Fig. 1.

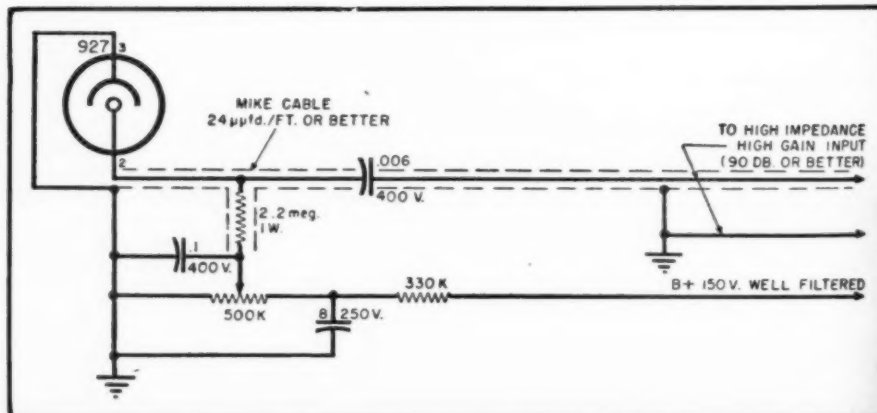

Announcing 3 GREAT COURSES IN RADIO

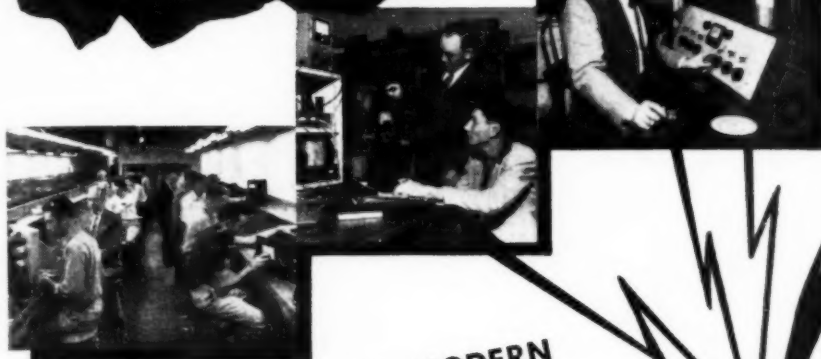1. MODERN RADIO SERVICING
2. COMPLETE GENERAL RADIO
3. ADVANCED BROADCAST TECHNICIAN




TRAIN NOW IN OUR MODERN
SCHOOL OF RADIO FOR THIS
FASCINATING AND PROFITABLE FIELD

Modern radio training requires a combination of facilities and a background of teaching experience that few institutions possess. The Tyler Commercial College Radio Department is proud of its well-equipped shops, classrooms and laboratories, operating under the supervision of skilled teaching personnel with years of radio experience behind them. The school of radio was established here more than thirty years ago, and has produced thousands of qualified graduates who have taken their places in the radio industry in this country and abroad.

Our courses are constantly revised and kept up-to-date in order to incorporate the latest developments in radio, including television, frequency modulation, and electronics. No effort is spared to produce the most effective courses for each job objective and to maintain a high standard of instruction in all branches of radio.

TYLER COMMERCIAL COLLEGE
115 South College Tyler, Texas

APPROVED BY
VETERANS ADMINISTRATION

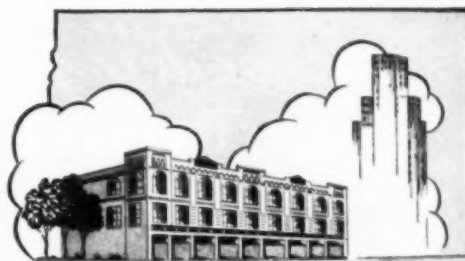

1. MODERN RADIO SERVICING

For the student interested in radio maintenance and repair work, we offer our course in MODERN RADIO SERVICING. In addition to a thorough foundation of essential electrical and radio theory, the course emphasizes maintenance and repair techniques, and includes much material on frequency modulation and television.

Average time to complete course ...
10 months

2. COMPLETE GENERAL RADIO COURSE

To qualify for employment in the commercial fields of radio, we have developed the COMPLETE GENERAL RADIO COURSE. This course provides all the necessary radio mathematics, radio law, radio and electrical theory and other material essential for successful preparation for both second and first class radiotelephone licenses. Special attention is given to television and frequency modulation problems now encountered on the newly revised FCC license examinations. International Morse Code work is also provided and is of special interest to students preparing for second class radiotelegraph or amateur examinations. For students whose particular interest is broadcast control room work, we have recently modernized our control room facilities to provide practical experience with late-type console equipment. Graduates of the complete general radio course are now employed in hundreds of broadcasting stations throughout the country. Other graduates are radio operators aboard ship, or working for airlines, in coastal radio stations, and in government radio positions.

Average time to complete course ...
12 months

3. ADVANCED BROADCAST TECHNICIAN COURSE

A higher level of specialized instruction is available for the licensed broadcast operator whose ambition is to qualify for a position of responsibility in his own field. This is the ADVANCED BROADCAST TECHNICIAN COURSE which requires at least a second class radiotelephone license as entrance qualification, and provides an intensified training in matters of particular interest to the future broadcast engineer. Subjects include basic engineering mathematics, fundamental design principles, details of various modulation systems, high efficiency linear amplifiers, directional antenna systems, broadcast speech input equipment, line equalizers, peak limiters and dynamic noise suppressors.

Average time to complete course ...
6 months

Send for Free Catalogue

For full details and catalogue regarding this unique school, write to the Tyler Commercial College, Room 202, T. C. C. Building, Tyler, Texas.

MAIL TODAY

A STATE APPROVED
INSTITUTION

Announcing 2 SENSATIONAL NEW INDOOR ANTENNAS By **WARD**

WARDS NEW TVI-49

Ward's portable TVI-49 will give excellent reception on all channels—orients easily in all directions. Chrome plated brass dipoles. The TVI-49 is sturdily constructed and weighted perfectly—it will not tip over—
List \$6.95



WARDS NEW TVI-43

The TVI-43 brings in all channels precisely and brilliantly. Most attractive—chrome plated brass telescopic dipoles, satin beige brown finish—blends perfectly with the most exacting interior.
List \$17.95

See any leading parts distributors or write for catalog today.



WARD PRODUCTS CORPORATION
1523 E. 45TH ST., CLEVELAND 3, OHIO
DIVISION OF THE GABRIEL CO.

80

MARS Station of the Month

W6USA Headquarters, Sixth Army, has grown into a key station. On the fifth of April, 1946, Major John Wilson, Jr., W4EUQ, operating fixed portable W6, worked W6WD on 75 phone. This was the first contact at W6USA. At that time, W6USA consisted of one BC-610 and one Super-Pro receiver. Today W6USA is housed in the penthouse on top of Building 35 in the Presidio of San Francisco and has four BC-610 transmitters, one SCR 640 transmitter, one Hallicrafter HT-18 (which allows use of NBFM), one VHF-152 and one SCR-639 receiver, and a SCR-211 frequency meter, oscilloscope, and PanaDaptor, and uses crystal or v.f.o. on all bands, c.w. or phone. Antennas at present are doublets for 80, 40 and 20 meters, and a three-element beam on 10 meters. The two-meter antenna is a five-element fixed beam.

If you think this is a "ham's" paradise, just listen to the new projects already started! Two twenty-four-foot towers are being erected, one for a three-element roto beam on twenty, and the other for a four-element roto beam on ten. Both are electrically rotated and have remote direction indicators. A five-element, two-meter rotary beam and a four element, six-meter rotary beam are also in the process of construction.

Five new consoles with sloping panels will house a complete receiving position consisting of receiver, pre-selector, modulation and carrier level indicator, speaker, necessary change-

over switches, key and mike jacks, and a phone patch, also separate jacks for remote line in case of emergency. Yes, Major Wilson would be surprised if he saw W6USA today, as would Colonel "Walt" Snyder and all the other officers and men whose cooperation made this possible.

W6USA has overseas schedules and is always ready to handle your traffic, maintaining operations from 0745 to 1630 PST and from 1700 to 2400 PST Monday through Friday. Every "ham" is welcome to "come up and see us some time." The visitors' book shows visits from every district as well as visitors from overseas and many SWL's.

W6USA is controlling station for MARS in the Sixth Army Area. The staff consists of SFC "Tony" Welzel (W2QC), Chief OP; M/Sgt "Robbie" Robinson (W6QIU); Sgt "Hank" Bowden (W6FHU); Cpl. "Whitey" Roen (license but no call); SFC "Randy" Arnold; SFC "Fred" Thourot, and Lt. Harold H. Haas, MARS Command Director, Sixth Army.


Call W6USA for traffic or just a rag chew.

-30-

Membership in the National Guard Military Amateur Radio Service is open to any Guardsman or recruit who possesses an amateur radio operator's license.

(See page 149 for details)

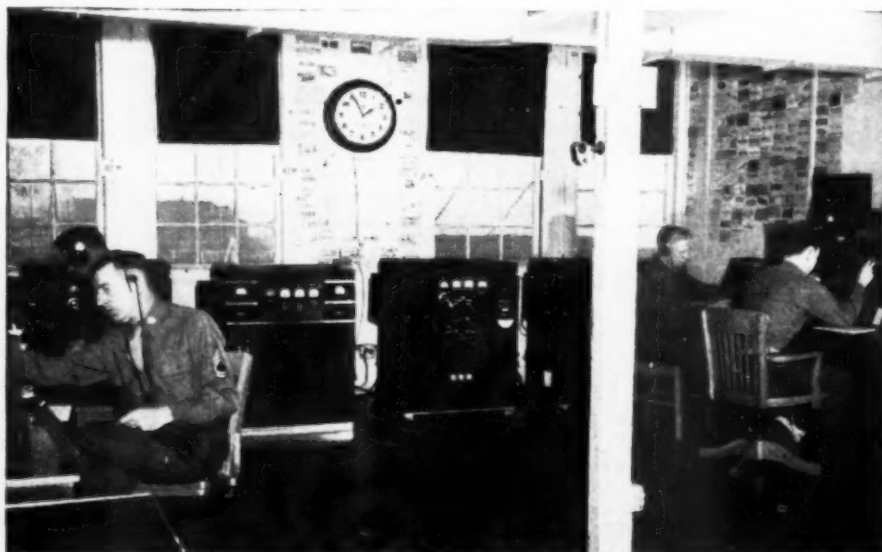Left to right: Tony (Sgt. Anthony E. Welzel, Richmond, Calif., W2QC), Hank (Sgt. H. R. Bowdon, Mayfield, Kentucky, W6FHU), Whitey (Cpl. Clarence A. Roen, McLaughlin, South Dakota, no call, although he is licensed), and Randy Arnold, performing the normal duties of W6USA, 6th Army, in the penthouse station in San Francisco, Calif.



RADIO & TELEVISION NEWS

ANNOUNCING!

Greater Values Than Ever Before in Our
New Larger Store at 189 Greenwich St.,
N. Y. 7. (Come in and Browse Around)
Formerly 63 Day St.

R-H-S LUCKY "7"

SPECIALS OF THE MONTH

TWO-SPEED PLANETARY DRIVE

Auxiliary Speed Reducer fits on
Condenser Shaft back of panel or
on dial knob shafts. Ratios 5 to 1
and 1 to 1. Fits any 1/4 inch round
shaft.

57c Each—Two for.....97c

PERMALLOY SHIELDS for CATHODE RAY TUBES

8" Shield.....\$1.47
5" Shield.....1.97

TRANSMITTING KEY

General purpose transmitting key on a heavy
die cast base, all mounted on a swinging bracket
thigh clamp. 3/4" pure silver contacts. Key can
be easily removed from clamp. Adjustable
bearings. Supplied with 5-foot cable and PL-55
phone plug.
Brand new—each.....57c

SELENIUM RECTIFIERS Full Wave Bridge Type

INPUT	OUTPUT	
up to 18v AC	up to 12v DC	1/2 Amp. \$1.47
up to 18v AC	up to 12v DC	1 Amp. 1.97
up to 18v AC	up to 12v DC	5 Amp. 5.27
up to 18v AC	up to 12v DC	10 Amp. 8.97
up to 18v AC	up to 12v DC	15 Amp. 11.57
up to 18v AC	up to 12v DC	30 Amp. 22.57
up to 36v AC	up to 28v DC	1 Amp. 3.47
up to 36v AC	up to 28v DC	5 Amp. 8.57
up to 36v AC	up to 28v DC	10 Amp. 14.57
up to 36v AC	up to 28v DC	15 Amp. 22.27
up to 115v AC	up to 100v DC	25 Amp. 2.57
up to 115v AC	up to 100v DC	6 Amp. 5.27
up to 115v AC	up to 100v DC	5 Amp. 22.57
up to 115v AC	up to 100v DC	3 Amp. 17.97

OIL CONDENSERS NATIONALLY ADVERTISED BRANDS All Ratings D. C.

2x.1mfd.	600v	\$0.37	1mfd.	2000v	\$0.97
.25mfd.	600v	.37	2mfd.	2000v	1.27
.5mfd.	600v	.37	4mfd.	2000v	3.47
1mfd.	600v	.37	8mfd.	2000v	3.47
2mfd.	600v	.37	15mfd.	2000v	4.97
4mfd.	600v	.57	4mfd.	2500v	3.97
8mfd.	600v	1.07	2mfd.	2500v	2.37
10mfd.	600v	1.17	1mfd.	2500v	1.27
1x.1mfd.	1000v	.47	.25mfd.	2500v	1.47
.25mfd.	1000v	.47	.5mfd.	2500v	1.77
1mfd.	1000v	.57	.05mfd.	3000v	1.97
2mfd.	1000v	.67	.25mfd.	3000v	2.67
4mfd.	1000v	.87	1mfd.	3000v	2.87
8mfd.	1000v	1.97	12mfd.	3000v	6.97
10mfd.	1000v	2.07	2mfd.	4000v	4.87
15mfd.	1000v	2.27	1mfd.	5000v	4.97
20mfd.	1000v	2.97	1mfd.	7000v	2.97
24mfd.	1500v	5.27	3mfd.	4000v	5.37
1mfd.	1750v	.87	2mfd.	3000v	3.47
1mfd.	2000v	.97	2x.1mfd.	7000v	3.27
.25mfd.	2000v	1.07	.02mfd.	12000v	9.97
.5mfd.	2000v	1.17			

HIGH CAPACITY CONDENSERS

10,000 mfd.—25 WVDC.....	\$4.97
23,500 mfd.—25 WVDC.....	3.47
2500 mfd.—3 VDC.....	.37
3000 mfd.—25 WVDC.....	2.47
2x1250 mfd.—10 VDC.....	1.27
1000 mfd.—15 WVDC.....	.97
200 mfd.—35 VDC.....	.57
100 mfd.—50 WVDC.....	.47
4x10 mfd.—400 VDC.....	.87
4000 mfd.—18 WVDC.....	1.97
4000 mfd.—25 WVDC.....	2.47
4000 mfd.—30 WVDC.....	2.97

PHONE DIGBY 9-0347

RADIO TUBES

NEW! STANDARD BRANDS!

1B24	\$4.87	802	\$2.97	OZ4	\$.67
1B26	3.97	803	4.87	1A5GT	.47
1B29	3.47	804	6.57	1A7GT	.47
1B32	1.97	805	3.87	1H5GT	.57
1N21	.47	807	1.07	1L4	.87
1N23	.77	808	1.57	1L6	.87
1N34	1.37	809	2.47	1LD5	.77
1P24	.87	810	5.97	1LE3	.97
2AP1	3.27	811	1.97	1LH4	.77
2C21	.27	812	2.47	1LN5	.67
2C22	.17	813	6.47	1NSGT	.57
2C26A	.27	814	2.67	1R5	.67
2C34	.27	815	1.87	1S4	.67
2C40	3.57	816	1.07	1S5	.57
2C44	.77	826	.47	1T4	.57
2C46	6.87	829B	5.97	2A3	.97
2D21	1.07	830B	3.57	3A5	1.37
2J21	9.87	832A	4.57	384	.67
2J22	9.87	833A	29.97	3Q4	.67
2J26	9.87	836A	.97	3Q5	.67
2J48	19.97	837	1.27	5T4	.97
2J548	39.97	838	2.87	5U4G	.47
2K25	23.97	841	.47	5V4	.87
2K28	11.57	843	.37	5W4	.67
2V3G	.97	845	4.17	5X4	.57
2X2	.37	851	24.97	5Y3	.37
3AP1	3.97	860	1.87	5Y4	.47
3B22	2.97	861	10.47	5Z3	.47
3B24	1.87	862A	497.47	5Z4	.77
3B26	1.47	864	.47	6A7	.67
3BP1	1.37	865	.97	6ASGT	.67
3CP1	2.67	866A	1.17	6AB7	.77
3C21	3.97	866B	1.17	6AC7	.77
3C23	2.47	869B	27.57	6AG5	.87
3C24/24G	.47	872A	1.47	6AG7	1.17
3C30	.37	874	.57	6AJ5	.87
3C31	1.47	876	.67	6AK5	.87
3D21A	1.47	878	1.27	6AK6	.67
3DP1	1.97	884	1.27	6AL5	.67
3E20	5.97	885	.67	6AQ5	.67
3GP1	4.97	902P1	4.97	6AQ6	.67
4AP10	2.97	905	1.87	6AT6	.47
4B24	2.27	923	.87	6AU6	.77
4E27	12.97	954	.27	6B4G	.97
5AP4	3.97	955	.37	6BG6G	1.97
5BP1	1.47	956	1.47	6B6	.67
5BP4	2.47	957	.27	6B8	.87
5CP1	1.97	958A	.27	6C4	.27
5CP1A	8.97	1613	.57	6C5	.47
5D21	34.97	1616	.87	6C6	.57
5F27	1.37	1619	.27	6D6	.47
5J22	11.97	1624	.67	6E6	.57
5LP1	13.97	1625	.37	6E7	.57
5NP1	8.97	1626	.37	6G6	.77
5R4GY	1.17	1629	.27	6H6	.47
6C21	24.97	1630	1.87	6J5	.47
6J4	5.87	1636	3.97	6J6	.87
9GP7	9.97	1638	1.47	6J7	.87
9JP1	3.57	1641	.57	6K6	.47
9LP7	3.57	1654	1.97	6K7	.57
10Y	.37	1851	.97	6L6	1.17
12DP7	12.97	1960	2.97	6L6G	.97
12G7P7	12.97	2050	.47	6L7	.87
15E	1.97	2051	.47	6N7	.77
15R	.77	8011	1.27	6Q7	.47
28D7	.37	8012A	1.47	68A7	.47
30 Spec.	.27	8013A	1.27	68C7	.67
45 Spec.	.47	8016	.97	68F5	.57
75T	2.97	8020	1.47	68G7	.67
100R	1.47	8025	3.57	68H7	.67
100TH	9.97	9001	.37	68J7	.47
100TS	2.37	9002	.37	68K7	.47
227A	2.97	9003	.37	68L7	.47
249C	2.57	9004	.37	68N7	.47
250R	9.97	9006	.27	68Q7	.47
250TH	19.47	CG3	3.97	6V6GT	.57
250TL	19.47	CK507A	1.47	6X5GT	.57
294A	4.97	CK1005	.27	6ZY5G	.87
304TH	3.47	CK1090	1.27	12A6	.17
304TL	.97	E1148	.67	12AT6	.57
305A	12.47	E150	.47	12AU6GT	.57
307A	3.97	F123A	9.97	12N5	.37
316A	.67	F127A	17.97	12S6GT	.37
327A	2.97	F128A	39.47	12SA7GT	.57
350R	1.47	F660	39.47	12SK7GT	.57
368AS	3.27	F862A	497.47	12SG7GT	.57
371B	.97	FG17	2.87	12SH7GT	.57
378A	1.97	FG81A	3.97	12SQ7GT	.57
434A	3.27	FG95	8.97	12SR7GT	.57
446A	.67	FG105	9.97	14A7	.87
450TH	18.47	GL697	29.47	14Q7	.57
451	1.47	HY69	3.97	24A	.67
530	22.57	HY615	.37	25L6GT	.57
531	2.97	ML100	19.97	25Z5	.47
632	2.87	ML101	29.47	27	.47
659	.87	ML502	39.47	35/51	.57
575A	12.97	RK59	1.97	35L6GT	.57
703A	3.27	RK60	.57	35Z5	.57
705A	1.97	RK72	1.37	35Z5	.47
706CV	18.97	RK73	1.67	45	.57
707B	8.47	RK75	3.97	50B5	.67
708A	1.97	RK705	1.97	50L6GT	.57
713A	1.27	RX21	3.27	56	.47
715B	7.57	RX120	9.97	76	.47
715C	34.97	8836	2.97	77	.47
717A	.67	VR75	.97	78	.47
721A	1.97	VR78	.37	80	.47
725AB	12.97	VR90	.67	83	.77
725A	12.87	VR105	.67	84/8Z4	.67
726A	7.57	VR130	.57	11Z73	.57
750TL	44.97	VT127A	2.37	11Z6GT	.57
800	.97	VU111	.37		
801A	.47				

NOW AVAILABLE

1000 KC Crystal.....\$2.97
Socket......07

RF VACUUM SWITCH GE-1521

9200 volts peak. 8 amps. Used as antenna switch in
Collins Art 13.
Brand New.....\$2.47

TRANSFORMER—115 V. 60 Cy. HI-VOLTAGE INSULATION

2500v @ 15 ma.....	\$4.97
2150v @ 15 ma.....	3.97
2100v @ 10 ma.....	4.87
1800v @ 10 ma; 6.3v @ 2A; 2.5v @ 2A..	4.97
1750v @ 4 ma; 6.3v @ 3A.....	4.27
1600v @ 4 ma; 700v CT @ 150 ma; 6.3v @ 9A.....	6.47
525-0-525v @ 60 ma; 925v @ 10 ma; 2x5v @ 3A; 6.3v @ 3.6A; 6.3v @ 2A; 6.3v @ 1A.....	6.97
500-0-500v @ 25 ma; 262-0-262v @ 55 ma; 6.3v @ 1A; 2x5v @ 2A.....	4.47
500-0-500v @ 100 ma; 5v CT @ 3A.....	3.97
450-0-450v @ 300 ma; 140-0-140v @ 100 ma; 36v @ 1A; 6.3v @ 5A; 5v @ 3A; 110/220 Dual, Pri.....	7.97
400-315-0-315v @ 315v @ 200 ma; 2.5v @ 2A; 5v @ 3A; 6.3v @ 9A.....	5.97
385-0-385-550v @ 200 ma; 2 1/2v @ 2A; 5v @ 3A; 3x6.3v @ 6A—PRI. 110/220....	6.27
340-0-340v @ 300 ma; 1540v @ 5 ma.....	4.97
300-0-300v @ 65 ma; 2x5v @ 2A; 6.3v @ 2 1/2A; 6.3v @ 1A.....	3.47
150-0-150v @ 80 ma; 150v @ 40 ma; 6.3v @ 3.5A; 6.3v @ 1A.....	1.97
120-0-120v @ 50 ma.....	.97
80-0-80v @ 225 ma; 5v @ 2A; 5v @ 4A....	3.97
24v @ 6A.....	1.17
13.5v CT @ 3.25A.....	2.97
3x10.3v @ 7A; CT.....	7.97
6.3v @ 12A; 6.3v @ 2A; 115v @ 1A.....	3.47
6.3v @ 10A; 6.3v @ .6.....	2.97
6.3v CT @ 3.5A; 2.5v CT @ 3A; 2.5v CT @ 3A.....	2.97
6.3v @ 1A; 2 1/2v @ 2A.....	2.47
6.3v @ 21 1/2A; 6.3v @ 2A; 2 1/2v @ 2A....	4.97
6.3v @ 1A.....\$0.97 8v CT 1A.....	.97
2.5v @ 20A.....	3.47
5v @ 3A; 2.5v @ 2A.....	2.97
5v @ 20A, Dual 110v Pri.....	3.47

FILTER CHOKES

HI-VOLTAGE INSULATION

10 hy @ 400 ma. \$5.97	1 hy @ 800 ma. \$14.97
25 hy @ 160 ma. 3.47	10 hy @ 250 ma. 2.47
12 hy @ 150 ma. 3.47	10 hy @ 200 ma. 1.98
25 hy @ 65 ma. 1.37	10/20 @ 85 ma. 1.57
.05 hy @ 15 ampe 7.97	15 hy @ 125 ma. 1.47
1 hy @ 5 ampe. 6.97	15 hy @ 100 ma. 1.37
4 hy @ 600 ma. 5.97	3 hy @ 50 ma. .27
200 hy @ 10 ma. 3.47	30 hy Dual @ 20 ma. 1.47
600 hy @ 3 ma. 3.47	8/30 hy @ 250 ma. 3.47
325 hy @ 3 ma. 3.47	

All Tubes guaranteed, except for open filaments, shorts and broken glass, for which we check before shipment.
Please specify how to ship.

All Prices Subject to Change Without Notice

All merchandise guaranteed. Mail orders promptly filled. All prices F.O.B. New York City. Send money order or check. Shipping charges sent C.O.D. Minimum order \$5.00. 20% Deposit required with all orders.

RADIO HAM SHACK inc.

189 GREENWICH STREET . NEW YORK, N. Y.

EVERY SERVICEMAN CAN afford SUPERIOR TEST EQUIPMENT



**THE NEW MODEL 770 —
AN ACCURATE POCKET-SIZE**

VOLT-OHM-MILLIAMMETER

(Sensitivity: 1000 ohms per volt)

Features: • Compact-measures $3\frac{1}{2} \times 5\frac{1}{2} \times 2\frac{1}{4}$ " • Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. • Housed in round-cornered, molded case. • Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

Specifications: 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 volts. 6 D.C. VOLTAGE RANGES: 0-7 $\frac{1}{2}$ /15/75/150/750/1500 volts. 4 D.C. CURRENT RANGES: 0-1 $\frac{1}{2}$ /15/150 Ma. 0-1 $\frac{1}{2}$ Amps. 2 RESISTANCE RANGES: 0-500 ohms. 0-1 Megohm.

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

We manufacture a complete line of radio test equipment.

**\$13.90
NET**

Write Dept. RN-6 for FREE catalog today!

MFD. BY



SUPERIOR INSTRUMENTS CO.

227 Fulton Street

New York 7, N. Y.

at your regular jobber

CREI Prepares Young Men for Professional Careers with Industry-Recognized training in a minimum of time **RADIO-ELECTRONICS- TELEVISION ENGINEERING**

GRADUATES of the Capitol Radio Engineering Institute residence school are preferred by industry because of their training and ability. This recognition is the reason that CREI men quickly find good jobs in radio-electronics-television engineering and technical fields.

With 22 years of practical teaching experience in these highly technical fields, CREI offers an outstanding faculty, modern and complete laboratories, shops and equipment.

New students are accepted twice monthly and each may advance as rapidly as he is capable. The basic course with one specialized course requires an average of 20 months to complete, depending on the ability of the individual student.

CREI is recognized as one of the country's leading technical institutes. Its work is of college level. It prepares the young man for a good job in industry in a minimum of time.



Approved for
Veterans'
Training

CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute Founded in 1927

MAIL COUPON FOR FREE CATALOG
Capitol Radio Engineering Institute, Dept. 136-A
16th and Park Rd., N.W., Washington 10, D.C.

Please send me your catalog and details.

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

☐ I am entitled to training under G.I. Bill.

HIWAY COMPANY

**Go Mobile on our
ANNIVERSARY SALE!
TUBE OF THE MONTH—304TL**

Brand new, boxed. Ea. **79c**
ORDER 4 for \$2.95 AND WE PREPAY SHIPPING!

**Going Mobile!
VIBRATOR POWER SUPPLY**

6VDC to 180VDC at 50 mills. "National." Complete with cord, battery clips, and case. Brand new!
Wt. 13 lbs. Ea. **\$7.49**

**Going Mobile!
NOISE FILTER**

Cut out that generator hash. Brand new! Wt. 3 lbs. Ea. **\$1.29**

**Going Mobile!
ARC-4 TRANSCEIVER**

See our ad May '49 RADIO NEWS, page 171. A few left. They're still the hottest 2-metersetup to date! Wt. 41 lbs. Ea. **\$17.49**
With MT-230 Mount. Ea. **\$20.49**

19-55 RECEIVER

85 Kes. I.F. Top "Q" 5'er. Good condition guaranteed. Less dynamotor. Wt. 12 lbs. Ea. **\$8.95**

7-9 MC ARC-5 TRANSMITTER

With tubes and crystals. Brand new but not packed in factory carton. Wt. 13 lbs. Ea. **\$9.95**

**Going Mobile!
FAMOUS T-17-B MIKE**

Brand new! A dream of a buy! Ea. **\$1.59**
Order 2 for only **\$2.75**

The Hiway Policy: 25% DEPOSIT WITH ORDER. Remit in full—SAVE C.O.D. CHARGES. SATISFACTION GUARANTEED OR YOUR MONEY BACK!

HIWAY COMPANY

Electronic Division

1304 S. HOOVER ST.

(Just S. of Pico) (Fitzroy 6343)

LOS ANGELES 6, CALIFORNIA

Send for our FREE catalogue!

Transient Distortion

(Continued from page 47)

difficulty in securing effective feedback without incurring oscillation or instability. Usually a poor output transformer is blamed for this condition, but in the author's experience, several other factors are often of importance. The circuit shown in Fig. 2 is designed to operate with inexpensive, commercial-grade transformers, as many of these have a frequency response extending to above fifteen thousand cycles and are usable in circuits incorporating fifteen to twenty decibels of conventional feedback. The use of the bridge circuit raises the effective feedback to a much higher level; however, in any feedback circuit it is important to reduce stray capacities, inductances, and couplings to a minimum. Since in good operation, the feedback will extend up into the ultrasonic range, the effect of self-inductance in some types of paper condensers should not be neglected. Likewise, the resistive elements in the feedback loop should not be wirewound, if possible, especially the variable element of the bridge. Furthermore, the resistance of electrolytic condensers and ground returns may vary greatly at ultrasonic frequencies, and as a result it is often desirable to shunt electrolytics with small noninductive paper condensers and make firm ground connections to a copper busbar.

The phase shifting condensers shown in the diagram are C_3 and C_7 . C_3 is placed across the primary of the output transformer and serves the secondary purpose of stabilizing the circuit to prevent ultrasonic oscillation. Condenser C_7 is incorporated in the variable feedback control which acts as a resistive portion of the phase shifting system and provides variable phase shift. As different speakers will have varying characteristics, various values of capacitance should be tried to best match the high-frequency characteristics of the speaker. Generally, this will mean a definite increase in high-frequency brilliance due to improved ability to handle complex waves and also an apparent actual increase in speaker efficiency due to a decrease in apparent speaker inertia. However, too much capacity should not be used in the phase-shifting network or excessive high-frequency boost will be obtained.

In adjusting the circuit, the feedback control should be advanced and the variable bridge element adjusted to the point where low-frequency oscillation takes place due to regeneration. The bridge is then adjusted to a point slightly beyond the place where the low-frequency oscillation ceases. This is the point where maximum feedback may be attained, and if the circuit is functioning properly, the feedback control may be advanced greatly before high-frequency oscillation oc-

SAME WEEK DELIVERY!
WHY WAIT? ORDER TODAY!

RADIO TUBES

34¹/₂¢
ea.

YOUR CHOICE

LARGEST TUBE STOCK IN THE COUNTRY AT ROCK BOTTOM PRICES. Cartoned and Guaranteed . . . 39c ea. in smaller quantities.

34¹/₂¢
ea.

In lots of 100 or more

In lots of 100 or more

FREE!

\$20.00 List Value Cornell-Dubilier, Mallory, Aerovox, Sprague, Solar, Filter Condensers—ten fast moving filters FREE with each 100 tubes.

Popular GT Miniature and Localt Tubes. All individually cartoned and guaranteed best quality. Available at this low price and may be assorted. **THE FIRST REAL SCOOP FOR THE SERVICE DEALER.**

1A4	2A3	6D6	6X4	20	44
1A6	2A5	6F5G	6X5GT	2050	46
1B5	2A7	6F6GT	6Y6G	2051	47
1C6	2B7	6F8G	10	24A	50
1C7G	3A4	6G6	12A8GT	25L6GT	50B5
1D5G	3Q4	6H6GT	12A6	25Z5	50L6GT
1D7	3S4	6J5GT	12A7	25Z6GT	56
1D8GT	5U4Q	6J7GT	12AT6	26	57
1F4	5V4	6K6GT	12AUE	27	58
1F5G	5X4G	6K7GT	12C8	30	70L7GT
1G6GT	5Y3GT	6P5GT	12BA6	31	71A
1H4G	5Y4G	6Q7	12BE6	32L7GT	75
1H6GT	5Z3	6Q6GT	12F5	35	76
1J6G	6A7	6R7	12H6	35/51	78
7B6	6AC5GT	6SA7GT	12J5GT	35B5	81
7E6	6A3	6SC7GT	12J7GT	35C5	83
7C4	6A8GT	6SD7GT	12K7GT	35L6GT	84/6Z4
14X7	6AJ5	6SF5GT	12K8G	35W4	75
1B4	6AQ6	6SF7	12Q7GT	35Z5GT	112A
1C4	6AT6	6SG7GT	12SA7GT	37	89
1L4	6B6	6SH7	12SH7GT	37A	117Z3
1P5	6B7	6SJ7GT	12SG7	38	182B
1R5	6BA6	6SK7GT	12SJ7GT	39	183
1S4	6BE6	6SL7GT	12SK7GT	39/44	482B
1S5	6C4	6SQ7GT	12SN7GT	40	483
1T4	6C5GT	6SR7GT	12SQ7GT	41	
1U4	6C6	6U7GT	12SR7	42	
1V	6C8G	6V6GT	12SR7GT	43	

FM and TELEVISION TUBES

SPECIAL 49c each in 100 lots assorted 54c ea. in smaller quantities.			
1B3	6AL5	6SSGT	12AT7
2C34	6AQ5	6SN7GT	12AX7
2E24	6AU6	6SS7	12BA7
4A6G	6BD6	6T8	12S8
6J6	6BG6G	6W7G	19T8
6AG5	6BH6	6ZG7	
6AK5	6BJ6	12AU7	

54c CRITICAL TUBES

Sensational Low Price each in 100 lots assorted. 59c ea. in smaller quantities.					
OZ4	1LA6	2V3G	7F7	7X7	
1AD5	1LC6	3LF4	7G7	117L7GT	
1A5GT	1LE3	3Q5	7H7	117P7GT	
1A7GT	1LH4	6L6G	7J7	117Z6GT	
1G4GT	1LN5	6U5	7N7	24A	
1H5GT	1N5GT	7A4	7Q7	35Z4GT	
1J6G	1Q5GT	7A7	7S7	807	
1LA4	2A3	7E5	7W7		

IMPORTANT—100 lot prices also apply to mixed assortments of 34¹/₂c and 49c and 54c tubes. IF YOU WISH, tear out this page and send it in. Just write in quantities desired. Please print name and address plainly.

OUTPUT TRANSFORMERS



For: 50L6, 50B5, 50A5, 50C6, 32L7, 70L7, 26A7, 6W6, 28D7, 70A7, 1276, 6A5, 6B4, 25C6, 7C5, 2A3, 6A3, 6Y6, 25B6, 25L6, 6L6. . . each **39c**

For: 6V6, 6F6, 3Q5, 42, 41, 43, 45, 50, 71A, 12A5, 25A6, 25A7, 6N7, 6A6, 25N6, 25B5, 117L7, 117M7, 117N7, 117P7, 35A5, 6AH5, 6AL6. . . ea. **49c**

UNIVERSAL OUTPUT TRANSFORMER SPECIAL: Up to 12 watts to almost any speaker. . . 99c ea.

IF TRANSFORMERS

Standard replacement each. . . 45c
Standard replacement Midget. . . 45c

VOLUME CONTROLS

500,000 ohms with switch and long shaft—best brands. . . 35c
2 Meg. with DPST switch—long shaft. . . 29c

PM SPEAKERS



Nationally advertised brands—**GUARANTEED—best quality**
5" Alnico 5 Magnet. . . Lots of 10, ea. 95c
4" . . . Lots of 10, ea. 95c
4" with output for 50L6. . . Lots of 10, ea. \$1.15
3" . . . Lots of 10, ea. 95c
2" . . . Lots of 10, ea. 95c
Individual price . . . ea. 99c
6" . . . Lots of 10, ea. 99c
Individual price . . . ea. 1.59
5" with output trans- . . . former. . . ea. 1.65
10" . . . ea. 4.25
12" . . . ea. 4.95

Warm Weather Buys!

VIBRATORS

Standard 4-prong universal replacement. Very best brands. Ea. **\$1.29**

AUTO ANTENNAS

Snyder TC-3—Top cowl antenna. . . **\$1.99** ea.
C-30 . . . **1.79** ea.
Side cowl. . . **1.79** ea.

BUFFER CONDENSERS

.005 mfd 1600 WV . . . 17c ea.
.008 mfd 1600 WV . . . **\$1.20**
.01 mfd 1600 WV 10 for

PICKUPS

Shure—Astatic—wide response
Finest pickups—standard replacement. . . **\$2.95**

600Volt BY-PASS CONDENSERS

BUY our assortment of all 400V and 600V types listed below.

7 c 100 condensers for **\$5.95**



.001 mfd, 600 V. . .	ea. 7c
.002 . . .	ea. 7c
.005 . . .	ea. 7c
.01 . . .	ea. 7c
.02 . . .	ea. 7c
.05 . . .	ea. 8c
.1 . . .	ea. 9c
400 VOLT BY-PASS CONDENSERS	
.2 mfd . . .	ea. 9c
.25 mfd . . .	ea. 10c
.5 mfd . . .	ea. 15c

MISCELLANEOUS BUYS AT LOWEST PRICES!

CRYSTAL CARTRIDGE

Standard replacement crystal cartridge. . . ea. \$1.49

6-FT. LINE CORDS

Good Rubber with plug 10 for. . . \$1.25
Underwriters Approved 10 for. . . \$1.69

PUSH-BACK WIRE

100 ft. rolls. . . 49c ea.

SELENIUM RECTIFIERS

Standard 100 mil. . . ea. 69c
75 mil. . . ea. 59c

GE VARIABLE RELUCTANCE CARTRIDGE

List Price \$9.95
Your Cost. . . \$3.68 ea.
Octal Sockets. . . 10 for 49c
VARIABLE CONDENSERS
Two gang for superhet standard 1/4" shaft. . . 69c

PILOT LIGHTS

10 boxes for \$4.90 (10 bulbs per box) . . . 54c
1 box . . . ea. 49c
No. 40 6-8 Volts . . . 15 Amps.
No. 41 2.5 Volts . . . 50 Amps.
No. 44 6-8 Volts . . . 25 Amps.
No. 46 6-8 Volts . . . 25 Amps.
No. 47 6-8 Volts . . . 15 Amps.
No. 51 6-8 Volts . . . 20 Amps.

FILTER CONDENSERS

Highest Quality Standard Brands, All Fresh Stock Electrolytic. 60-60 mfd, 150 V. ea. . . 47c
(Small size, low price, use in place of 60-40, 50-30, 50-50, 40-40, 30-30, etc.)

15-15 mfd, 150V . . .	ea. 39c
20-20 mfd, 150V . . .	ea. 39c
30-30 mfd, 150V . . .	ea. 47c
40-10 mfd, 150V . . .	ea. 39c

40-20 mfd, 150V . . .	ea. 49c
40-40 mfd, 150V . . .	ea. 49c
50-30 mfd, 150V . . .	ea. 57c
50-50 mfd, 150V . . .	ea. 49c
15 mfd, 150V . . .	ea. 19c
16 mfd, 150V . . .	ea. 23c
20 mfd, 150V . . .	ea. 25c
30 mfd, 150V . . .	ea. 29c
40 mfd, 150V . . .	ea. 29c
8-8 mfd, 450V . . .	ea. 43c
10-10 mfd, 450V . . .	ea. 43c
20-20 mfd, 450V . . .	ea. 49c

8 mfd, 450V . . .	ea. 24c
10 mfd, 450V . . .	ea. 29c
10 mfd, 450V with 20-20 mfd, 25V ea. 39c	
15 mfd, 450V . . .	ea. 29c
20 mfd, 450V . . .	ea. 39c
30 mfd, 450V . . .	ea. 49c
30 mfd, 450V with 20-20 mfd, 25V ea. 59c	
10 mfd, 25V . . .	ea. 17c
20 mfd, 25V . . .	ea. 17c
25 mfd, 25V . . .	ea. 17c
100 mfd, 25V . . .	ea. 17c
20-16-16 mfd, 350V Sprague . . .	ea. 39c

All Merchandise is Brand New and nationally advertised brands.—Minimum order \$5.00; all shipments F.O.B. Chicago.—25% Deposit with order, balance C.O.D. **ORDER TODAY!** 20% additional on small orders outside continental United States. **LOW PRICE CATALOG SENT WITH FIRST ORDER.**

CLEAR-VAC CO.

5036 RAVENSWOOD AVE., CHICAGO, ILLINOIS

"Clear Heads Order from CLEAR-VAC"

SURPLUS

BRAND NEW TUBES

304 TL	ea. \$.90
Four for	3.00
5 RP1	ea. 1.95
5 RP4	ea. 2.95

SMASH VALUES IN COMMAND EQUIPMENT

BC-453	EXC. \$12.95
BC-454	NEW 4.95
BC-455	EXC. 7.95
BC-456	NEW 2.95
BC-457	NEW 6.95
BC-458	NEW 7.95
BC-459	EXC. 9.95
BC-496	EXC. 14.95

CONDENSERS

2 MFD. 4000V. Pyranol.	\$2.95 ea
4 for	\$10.00
2 MFD. 5000V.	\$3.95 ea
6 for	\$20.00
.25 MFD. 15,000V.	\$5.95 ea

VHF TRANSCEIVER

Ideal substitute for SCR-522, freq. range 140-144 mc. crystal controlled, 10 watts. The receiver section has two individual RF sections, feeding a common 3 stage 10mc IF amplifier. Both RF sections may be operated simultaneously, or either one individually. The receiver unit has 13 tubes. The transmitter is of straight forward design. Transmitter unit has 7 tubes, one #832 as final modulated by a pair of 6L6 and push-pull. Complete unit in case with tubes, crystals and diagram less dynamotor. **\$14.95**

EXCELLENT CONDITION. New Phantom Antenna for above unit, 3 lamps in parallel with sockets, complete for. **95c**

ALTIMETER TRANSCEIVER RT-3/ARN-1

Frequency 418-462 mc. FM with 14 tubes including: 3-12SJ7, 4-12SH7, 2-12H6, 1-V8150, 2-955, 2-9004, 24r Dynamotor, used. **\$4.95**

R-89/ARN-5A

Slide path receiver. Crystal control of local oscillator, 332-335MC, complete with relays, 7-6AJ5, 1-12SR7, 2-12SN7, 1-28D7 and 3 xtals: 6497 KC 6522 KC, 6547 KC, 90 cye. band pass and 130 cye. band pass filters. Both RF sections may be operated simultaneously, or either one individually. Beautiful cabinet and chassis as foundation for many interesting experimental and construction projects. Broad news band on 20.7 MC. IF's ideal for television. Schematic furnished. Used, excellent, less covers. **\$12.95**

BC-733-D

New **\$9.95**

EE-8 ARMY FIELD TELEPHONE

Sturdy, highest quality telephone at less than price of a better-class toy. With ringer. Requires only two flashlight batteries for each phone and two wires between each phone. Excellent condition. Used, Each. **\$7.95**

BC-620 TRANSMITTER-RECEIVER UNIT

FM transmitter-receiver, crystal controlled, two channels, freq. range 20-27.9 mc. 13 tubes, dual meter for testing filament and plate circuits. Used, good. **\$9.95**

MOBILE INSTALLATION KIT for BC-659 or BC-620

Consists of TS-13, MP-48; 4 section whip antenna; insulators, 2 maintenance manuals. NEW. **\$12.95**

BC-604 20-28 FM TRANSMITTER

For 11 and 15 meters; can be operated on 10 meters by use of proper scale; 10 channel pushbutton control with all tubes, meter, schematic, case and covers; less crystals. **\$10.95**

Used, excellent, with dynamotor. **\$14.95**

BC-684 27.0-38.9 FM TRANSMITTER

Same as above except for freq. range. New. **\$24.95**

10 CM RECEIVER-AMPLIFIER

Contains the following circuits: Blocking oscillator, C.R.T. gate circuit, Azimuth and Vertical sweep circuit, 5 stage 30Mc. IF strip with AFC circuit. Tube complement: 6-6N7GT, 2-6V6GT, 6-6AG7, 2-6L6GT, 8-6AC7, 2-6H6, 1-2050, 1-884. Used, excellent condition. **\$14.95**

VERTICAL ANTENNA

1/4 wave vertical dipole antenna, complete with 36 inch whip, 36 inch skirt, 7 ft. aluminum pole, mounting brackets and 8 ft. of coaxial cable with PL-259 plug. **\$12.95**

APQ-2 RADAR TRANSMITTER

200 to 500 MC—Used, good condition. **\$7.95**

APQ-9 RADAR TRANSMITTER

500 to 600 MC—Used, good condition. **\$7.95**

SPECIAL!

WESTINGHOUSE TRANSMITTER BC-122
Freq. range 325 to 800 KC; in portable field case; 3 meters plus excellent parts (less tubes)—An Excellent Buy—**BRAND NEW \$7.95 ea.**

All shipments FOB Chicago or Los Angeles unless specified. 20% Deposit required on all orders. Minimum order accepted—\$5.00. California and Illinois residents, please add regular sales tax to your remittance.

ARROW SALES, INC., DEPT. N

Main Office: 1712-14 S. Michigan Ave.
Chicago 5, Illinois

North Side Branch: 1802 N. Humboldt Blvd.
Chicago 47, Illinois

West Coast Branch: 1260 S. Alvarado
Los Angeles, Calif.

curs. This oscillation usually occurs at one of the speaker's higher resonant points and is preceded by a "ringing" sensation on high pitched tones. By carefully adjusting the bridge circuit, excessive hangover may be achieved in the low frequencies, if desired, due to regeneration.

As mentioned before, results obtainable with this type of circuit are very good, but as with any other type of equipment will depend to a large degree on careful construction and the quality of the associated components. It should be realized, however, that musical tastes may differ widely, and an excellent amplifier speaker combination is not necessarily a guarantee of a high degree of listening pleasure. In many musical selections there is very little real bass and the elimination of "synthetic" bass produced by low-frequency resonance may appear to the listener as lack of lower register in the equipment. Of course, bass boost may be used, but this tends to distort the proper reproduction of harmonic structures. In addition, faults originating in the accessory equipment such as tuners, pickups, and recordings may be emphasized.

In judging the performance of a reproducing system, one of the simplest methods is to use a microphone of good quality and observe the ability of the system to reproduce different sounds naturally. This method tends to eliminate outside sources of distortion such as might occur in a recording or radio broadcast, and the constructor has the advantage of having the original sound for direct comparison. As moving coil, dynamic microphones may be subject to transient distortions similar to those found in loudspeakers, the author prefers to use a good-quality crystal for maximum clarity. The human voice is a good test of a system's capabilities, as it covers a wide frequency range and may have very pronounced tran-

sients. However, do not be misled by speech mannerisms into assuming there is good reproduction, as these mannerisms may give the effect of naturalness even though the reproduction is quite distorted. The author has found that by using systems with superior transient response, the effect of poor acoustics is greatly diminished, and good pickup may be achieved at a distance from the microphone.

It is becoming increasingly evident that conventional distortion measurements are, for the most part, inadequate in judging the actual performance of audio equipment, and many audio men are beginning to rely on the ear as the final arbiter in sound reproduction. In the author's experience, up to twenty per-cent harmonic distortion may be tolerated in musical reproduction, provided the transient distortions produced in the loudspeaker by the resultant steep wave fronts are held to a low value. Likewise, fairly large amounts of intermodulation distortion, when achieved by means other than overloading the amplifier, are tolerable and may add a definite quality to the reproduction. Both of these distortions have a definite relation to the sounds being reproduced; however, transient distortion often means excessive distortion at one or more frequencies, and the resulting discontinuity can be very objectionable, especially in the higher register. As a result, there is often a very good reason for the frequency attenuation found in many systems and the various listening practices condemned by the exponent of wide-range reproduction. In cases of really good, wide-range systems employing binaural reproduction, the reproduction may be superior to the original because of the apparent ideal position of the listener and through the enhancement of instrument quality by added amplification.

-50-

CURING MINIATURE TUBE CONTACT TROUBLES


By MATTHEW MANDL

The base prongs of the miniature tubes used in television receivers are made of tempered metal and are subject to oxidation. If the tube socket does not exert too strong a grip on the prongs of the tube, electrical contact may be intermittent or lost entirely. A common result of this condition is an intermittent picture on the television screen. Streaks across the picture, or complete loss of picture may also result.

An offending tube of this type can usually be found by placing the finger over the doubtful tube and moving it back and forth slightly in the socket. If this makes the condition either better or worse, the tube should be removed and the prongs scraped clean with a small knife blade. Fine sandpaper can also be used to remove the oxidized coating. After replacing the tube in the socket again check to see if the condition is still present. If the trouble persists, the tube socket may have to be replaced, inasmuch as it obviously is not gripping the tube sufficiently. Often however, the situation

can be remedied without socket replacement by giving a slight bend to the tube prongs with a thin-nose pliers. This will, in effect, increase the contacting surface area of the prongs and make them fit tighter into the socket holes.

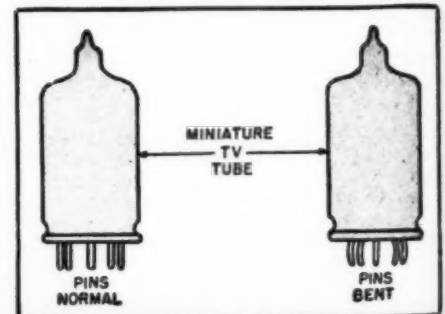(Left) Normal tube with straight prongs which due to oxidation may in time cause trouble. (Right) Bend prongs slightly so that they make better socket contact.



YOU'LL FIND BRANDS YOU KNOW AT *Almo* hallicrafters

RECEIVERS FOR THE RADIOMAN



MODEL 505 Your Cost, \$149.50


Hallicrafters Model 505 offers you television at a price you can afford. Twenty-three tubes assure you of steady, bright natural pictures. Famous Hallicrafters push button tuning permits easy operation—instantly locks each station in place.




MODEL 509 DUAL FOCUS. Your Cost \$269.50

You can choose the picture size you want with the Hallicrafters Model 509 Dual Focus. Choose either a 56 square inch rectangle or move up on the action with a huge round close-up of 64 square inches! Push button tuning locks each channel for best reception. A truly fine receiver for \$269.50, your cost.

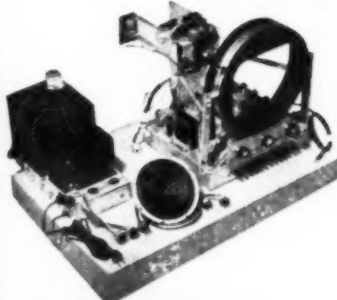MODEL T-64 CUSTOM CHASSIS. Your Cost \$169.50



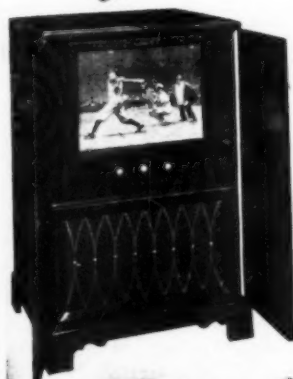
Here's the receiver chassis for your custom-made requirements. The T-64 comes complete with all parts assembled. It is the same unit as the 509 shown above with cabinet removed. T-64 has Dual Focus—your choice of a 56-inch rectangle or a 64-inch circular picture at a snap of a switch. Equipped with push button tuning. Chassis is completely assembled with all components, except CR tube.



NEW T-68 PROJECTION RECEIVER

This fine new projection receiver by Hallicrafters uses the Phillips Optical System to offer a clear bright picture that is 16 by 12 inches. Twenty tubes and five rectifiers, plus the projection tube, provide an unsurpassed projection unit. T-68 has push button tuning, and is housed in a Chippendale mahogany cabinet of unusual simplicity of design. Your Cost, \$695.00.

S-38 COMMUNICATIONS RECEIVER \$39.95

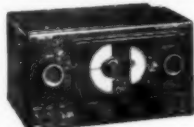


Famous Hallicrafters S-38 is the receiver that amazes the experts. This famous Hallicrafters communications receiver is the lowest priced unit on the market. Excellent reception on the Standard Broadcast band as well as three short wave bands. Continuous AM reception from 540 Kc to 32 Mc. Controls are: Speaker, Phones, AM/CW, and noise limiter switches, AF Gain, Receive/Standby, 4 Band Switches.

Send the Coupon for FREE Almo Broadcaster magazine.

Your Name

Street and Number

City.....State

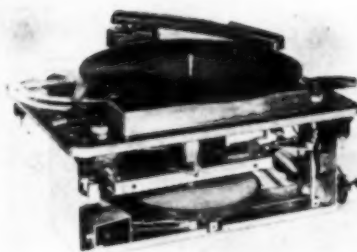

TWICE THE PLAYING TIME—HALF THE COST WITH TWIN-TRAX MAGNETIC TAPE CHASSIS. BY AMPLIFIER CORPORATION OF AMERICA


New Twin-Trax foundation type recorder chassis offers you one full hour of recording on a standard 7" reel of magnetic tape. This is accomplished by a revolutionary new method of recording on two sound tracks. This cuts tape costs in half—gives you twice the playing time on a standard reel.

A single connection to your radio picks off programs as you listen. Plug in a microphone and record voice and musical performance. Ideal for adapting existing amplification equipment for magnetic sound and reproduction. Or for use in permanent console installations.

You need only construct a preamplifier and bias oscillator. Circuits fully described in 32 page instruction book accompanying each set.

Attainable frequency response 50-9,000 cycles (plus-minus) 3 Db. Size: 6 1/2" H; 10" W; 13 1/2" D. Weight 16 pounds. Less tubes and accessories. Professional Net Price, \$89.50.

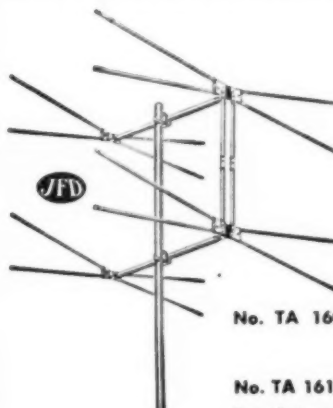Here's the Answer to FRINGE AND LOW SIGNAL Area Reception Problems



JFD STACKED ALL-BAND TV ARRAY

DOUBLE D-X-er

- Provides Minimum Noise, Less Fading and Reduced Multi-Path Reflections.
- Stacked Designed Offers High DB Gain on Both Bands.
- Maximum Sensitivity with Minimum Interference.

No. TA 160 (Single bay conical)
\$19.40 List

No. TA 161 (as illustrated with 1/4 wave-length jumper bars) **\$39.30 List**

Cut Installation Time and Costs!
With Unique JFD Mast Lead-In Stand-Offs
At amazingly Low Cost of 12c Each.



- Polyethylene Insert Assures Excellent High Frequency Transmission.
- Anchor Lead-ins Firmly in Place.
- Save Time . . . Save Labor . . . Save Money
- Available in All Lengths to Fit Every Mast Diameter.

Almo RADIO COMPANY
509 ARCH ST., PHILADELPHIA 6, PA.

Wilmington, Del. Branch
6th & ORANGE STS.

West Phila. Branch
6205 MARKET ST.

Nothing Finer!

CHICAGO FEATHERWEIGHT MULTI-TESTERS

Highest Quality—Chicago "Featherweight" Multi-testers are made with the precision of a fine watch. Strict tolerances provide accuracies far above commercial standards—readings are absolutely dependable.

Most Compact—Chicago "Featherweights" are the smallest multi-testers in the world. They are truly pocket-size instruments, weighing only a few ounces . . . a pleasure to use in or out of the shop.

Lowest Cost—Chicago "Featherweights" guarantee more real usefulness and dependability at considerably lower cost. There is nothing like a "Featherweight" for standing up under hard daily use. They are built to "take it."



Chicago "Featherweights"

Model 450A
Volt-Ohm Milliammeter for DC
Volts 0-5/10/50/500/1000 Mills 0-1
Ohms Full Scale 5000/50,000/500,000
Ohms Center Scale 30/300/3000
Net price \$10.90

Model 451A
Volt-Ohmmeter for AC and DC
Volts DC 0-10/50/100/500/1000
Volts AC & Output 0-10/50/100/500/1000
Ohms Full Scale 500,000
Ohms Center Scale 7200
Net price \$14.90


Model 452A
High Sensitivity DC Volt-Ohmmeter
Volts 0-10/50/100/500/1000 10,000 Ohms per Volt
Ohms Full Scale 2000/20,000/200,000/2,000,000
Ohms Center Scale 30/300/3000/30,000
Net price \$14.90

Chicago

There is a Chicago Multi-Tester for every purpose
Write for our complete catalog

CHICAGO INDUSTRIAL INSTRUMENT CO., 536 W. ELM ST. CHICAGO 10, ILL.

FREE

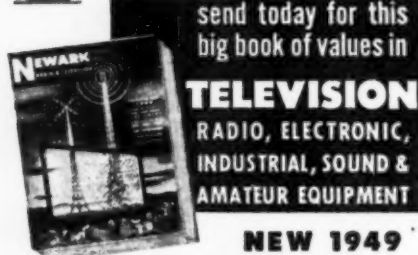

send today for this
big book of values in

**TELEVISION
RADIO, ELECTRONIC,
INDUSTRIAL, SOUND &
AMATEUR EQUIPMENT**

NEW 1949 NEWARK CATALOG

20,000 items including everything in STANDARD BRAND equipment! 148 pages packed with pictures, charts, and vital information!

KITS! SETS! PARTS! ACCESSORIES!

No matter how tiny the part, how tremendous the system . . . it's listed in this mammoth catalog . . . the one easy, satisfactory way to always get top-performing, top-value equipment! The most complete essential reference book for pros, hams, hobbyists, novices, oldtimers . . . anyone, everyone interested in TV, radio and sound equipment!

24-HR. MAIL SERVICE • ONE YEAR TO PAY

3 GREAT STORES! Uptown at 115 West 45th Street and Downtown at 212 Fulton Street in NEW YORK
323 West Madison Street in the heart of CHICAGO



MAIL COUPON TODAY

Newark Electric Co.
242 W. 55th St., NYC

Dept. F-2 Please send FREE Newark Catalog to:

NAME _____
ADDRESS _____
CITY _____ STATE _____

SAVE MONEY BRAND NEW GUARANTEED GENERAL ELECTRIC SELSYN

Type 2JIG1

Will operate from 110 volts, 60 cycle by using a resistor or a condenser in series. Size is 2 1/4" in diameter x 4 3/4" long. Ideal for beam antenna position indicator.

Price **\$2.75**
per pair — removed from new equipment




**HAYDEN TIMING
Type 45629R**

110 volts, 60 cycle, 2.2 watts, 1/240 R.P.M.

Price **\$3.00**
ea. net, new.

Type 36938-2

Price **\$3.00**
ea. net, new.

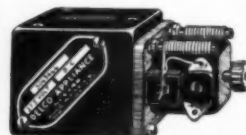

**DELCO ALNICO
Field Motor
Type 5069466**

27.5 volts D.C.
10,000 R.P.M.
1" x 1 3/8" x 2 1/4" long.
Price **\$3.00**
ea. net—new.

INSTRUMENT ASSOCIATES
147-57 41st Ave., Flushing, N. Y.
INdependence 3-1919

Super-modulated Rig

(Continued from page 52)

connected solidly to the chassis at each of their ends.

Jacks J_1 , J_2 , and J_3 and the eight insulated power supply binding posts are mounted along the rear lip of the chassis (Fig. 1, left). The a.c. power cord supplying the two filament transformers enters a grommet-lined hole just below jack J_1 . The 6.3 volt filament transformers (T_1 and T_2) are mounted under the chassis close together in the right-rear corner. The pilot light bracket is mounted near the center of the front lip of the chassis. Clearance holes (See Fig. 3) are drilled to pass the terminals of transformer T_2 . A similar transformer of different construction might be provided with wire leads. Fixed condensers, C_{11} and C_{12} , are mounted on top of the chassis near the final tank variable condenser and tank coil with which they are associated. All other condensers are below chassis.

The final tank coils posed something of a problem. The 100 μ fd. per-section tuning condenser (C_{12}) was chosen for high C and good flywheel action in this circuit. To work with this capacitance, the coils need to be somewhat small in inductance. We could find no small, manufactured plug-in coils (in the 75-watt category) having both center taps and end links. The problem was solved simply, however, by putting our own center taps on Barker & Williamson Type JEL end-lined coils. There is one unused contact on the ceramic five-pin plugs of these coils which conveniently accommodates the center tap lead. However, it becomes necessary to use the B. & W. 40-meter coil for 80-meter operation, the 10-meter coil for 20-meter operation, and a special coil which must be wound for 10 meters. The special coil is air-wound with No. 14 or 16 tinned copper wire and consists of 4 turns, 1 1/2" in diameter, spaced to a winding length of 2 inches. Tap the second turn. The link winding is 2 turns of the same wire airwound to the same diameter and supported not more than 1/4" from the "cold" end of the main coil. The final tank coils plug into a five-prong ceramic socket mounted on ceramic standoff insulators near tuning condenser C_{12} . (See Fig. 1.)

Tuning condenser C_{12} , being rotor-grounded to the chassis, is mounted on short metal pillars as close as possible to the coil socket.

Two uncased μ fd. condensers were used for C_{13} , C_{14} , and C_{15} mainly because of the small size of these large-capacitance units. (Note: electrolytic condensers cannot be employed in these positions.) These condensers, which are 3 1/4" x 1 1/8" x 7/8" in size, are mounted under the chassis by means of metal bracket straps under transformer T_2 . They are not shown in Fig. 3, since they hide much of the wiring.

RADIO & TELEVISION NEWS

An Excellent Book for the
Serviceman and Amateur!

RADIO TEST INSTRUMENTS

by Rufus P. Turner
Consulting Engineer, RADIO NEWS

TELLS HOW TO CONSTRUCT, CALIBRATE AND USE ELECTRONIC AND RADIO TEST EQUIPMENT

This well illustrated and practical manual will be an asset to any radio man's service library. It shows how to build, how to properly calibrate, how to use dozens of different types of radio and electronic testing devices. It covers briefly the theoretical explanation of radio, but only to make sure the reader first understands electrical and radio theory. The major portion of the book is devoted to technical data, which is presented in clear, understandable language. An ideal text for the practical radio man and a *must* for the radio serviceman.

Graphically Illustrated

Included are 182 informative illustrations—diagrams, charts, tables, and photographs—carefully chosen by the author to illustrate his sixteen chapters. RADIO TEST INSTRUMENTS is a unique presentation of a culmination of the author's own practices and applications. He has constructed and calibrated, tested and built, each piece of equipment described. And he shows how you can build and use these test instruments.

Covers Fully All These Test Instruments

- Multipliers
- Resistors
- Multi-Range Voltmeters
- Multi-Range Ammeters
- Ohmmeters
- Ultra-High-Resistance Meg-ohmmeters
- Volt-Ohm-Milliammeters
- Wattmeters
- Vacuum-Tube Voltmeters
- Decibel Meters
- Bridge-Type Impedance Meters
- Direct-Reading Impedance Meters
- Simple Capacitor Checkers
- Compact Capacitor Checkers
- Simple Coil Checkers
- Substitution-Type Capacitance Checkers
- Resonant Inductometers
- Precision Resistance Bridge
- High-Gain Null Detectors
- Oscilloscopes
- R.F. Test Oscillators
- and many others

Price \$4.50. Use convenient coupon
with full return privilege

ZIFF-DAVIS PUBLISHING COMPANY
185 North Wabash Avenue, Chicago 1, Ill.

June, 1949

A UNIQUE BOOK
IN THIS FIELD!

RADIO TEST INSTRUMENTS

ACCURATE . . . AUTHORITATIVE
PROFUSELY ILLUSTRATED
221 PAGES; 182 ILLUSTRATIONS
AN EXCEPTIONAL VALUE
FOR ONLY
\$4.50



MAIL THIS COUPON TODAY

Ziff-Davis Publishing Company, Dept. RN-6
185 North Wabash Ave., Chicago 1, Ill.

I am enclosing \$4.50 (check or money order) for which please send me one copy of RADIO TEST INSTRUMENTS. I understand that I may return book within five days for full refund if I am not entirely pleased.

Name

Address

City State

Keeping up
with radio



Good News

JUST THE BOOK FOR
HAMS TO RECOMMEND
TO BEGINNER FRIENDS



A New, Better
Fourth Edition of

THE RADIO AMATEUR NEWCOMER

the only comprehensive book for
the beginner!

You need no other book to get your license and get on the air. Written by the editors of RADIO HANDBOOK, especially for those just getting started, or getting interested in amateur radio.

- How-to-build simple equipment for a complete station on all newcomer bands.
- Operating instructions.
- Simple theory.
- Complete section of study questions, including those needed to pass the license exam.
- U.S.A. Amateur radio regulations.

MORE MATERIAL THAN EVER BEFORE!

Get it at your dealer, or look for its cheery red cover on your favorite newsstand.

\$1.00 PER COPY

On direct orders from us,
please add 10c for mailing.

Editors and Engineers

1302 KENWOOD ROAD, SANTA BARBARA, CALIFORNIA

ing and components which we wished to show in the photograph.

There is ample "breathing space" above and below the chassis, as will be seen from the photographs. This is essential to stable operation without feedback and interaction. The reader should avoid crowded construction as much as possible. The 807's, usually cantankerous as regards parasitics and feedback, were tamed completely by the baffle shield, tube shields, choke RFC, and parasitic suppressor resistor R_2 . Since providing each of these features, the tubes have shown no inclination to take off on their own.

Wiring of the circuit is entirely conventional. Keep all filament leads tightly twisted and close to the chassis. Hold these leads down to the chassis with soldering lugs bent to act as clamps. Keep all r.f. wiring as close as possible to associated coils and tubes. Use solid, insulated hookup wire to insure rigidity of leads. Make every connection tight mechanically before soldering.

We believe that best results will be obtained through the use of separate power supplies, as indicated by the labelled input terminals in Fig. 2. This would call for separate d.c. units as follows: (A) 350 v. at 125 ma., (B) 250 v. at 100 ma., (C) 90 to 150 v., (D) 45 to 67½ v., and (E) 400 to 750 v. at 200 ma. Batteries may be used for (C) and (D), and, considering their long life and simplicity, they seem to have the edge on a.c. operated grid bias supply units. A single power supply can be used satisfactorily for (A) and (B), provided such a unit will deliver about 250 milliamperes with good regulation and provided also that it supplies the 250 volts separately for the 6B4-G stage.

Initial Adjustment

After the tube heaters are placed into operation, connect the external exciter to jack J_1 . Place the 80-meter coils in positions L_1 - L_2 and L_3 . Feed in the external 80-meter signal and adjust C_1 to resonance as indicated by maximum brilliance of a pickup flash-lamp coupled loosely to coil L_2 . Now, neutralize the 6L6 stage, using either the pickup lamp or a crystal diode and milliammeter coupled to coil L_3 , adjusting C_2 until no lamp or pickup meter indication is obtained as condenser C_1 is tuned throughout its range.

(1) Connect a 0-150 d.c. milliammeter to jack J_4 .

(2) Connect a short piece of coaxial cable to jack J_2 and terminate this cable with a 50 to 72-ohm, 100-watt, non-inductive resistor or a 100-watt Mazda lamp. No plate voltage should be applied to any part of the transmitter at this time. Do not connect "B+" to the 6L6 stage until neutralizing has been completed.

(3) Ground jack J_1 temporarily.

(4) Plug in the 80-meter tank coil, L_1 - L_3 .

(5) Connect the other power sup-

plies, making sure that the C batteries are connected properly before switching on the plate and screen voltages to the 807's.

(6) Set condensers C_3 and C_4 to maximum capacitance.

(7) Switch on the external exciter (80-meter signal) and tune C_{12} for dip of the milliammeter. Examine the 807 circuits for parasitics.

(8) Transfer milliammeter to jack J_4 , noting lower plate current reading. Retune C_{12} for plate current dip. If any retuning is required, the position of the center tap must be changed on coil L_1 until dip occurs at the same setting of condenser C_{12} , whether the milliammeter is plugged into jack J_1 or J_4 .

(9) Repeat these operations on 20 and 10 meters. For 20-meter operation, feed a 40-meter signal into jack J_1 . Plug in the 40-meter r.f. driver coil at L_2 and the 20-meter coil at L_3 . (The r.f. stage does not need neutralization except on 80 meters.) For 10-meter operation, feed a 20-meter signal into jack J_1 , plug in the 20-meter r.f. driver coil at L_2 and the 10-meter coil at L_3 . Tune the 6L6 stage with the aid of a d.c. milliammeter plugged into jack J_4 . Adjust the center tap on L_1 , if required, according to instructions given in step (8).

(10) Remove ground jumper from jack J_1 and connect speech amplifier to J_1 . Connect r.f. ammeter (0-2 amperes) in series with the load resistor connected to jack J_3 .

(11) Note r.f. ammeter reading. Apply a continuous sine wave signal to the speech amplifier—or whistle a sustained single tone into the microphone. Note increase in ammeter reading on modulation. For 100 per-cent modulation, this increase will be 22½ per-cent of the initial reading. If a satisfactory increase is not obtained, it is very likely that the ratio of C_2 to C_1 is incorrect. Leaving C_2 at maximum capacitance setting, adjust C_1 until 100 per-cent modulation is obtained.

(12) Observe the output signal with an oscilloscope. This may be done by picking up a small amount of signal by means of a 2 or 3-turn coil of insulated hookup wire (about 2 inches in diameter) placed near coil L_1 , and applying it to the vertical plates of the 'scope directly. Set the internal sweep oscillator of the 'scope to about 1000 cycles. Set the sync control to its internal position. A broad band will be seen on the screen. Make a note of the height of this band. Whistle a steady note into the microphone, or apply a sine wave signal to the speech amplifier and note that the band pattern changes to a string of solid cycles. Measure the height of this new pattern from the peak of a positive half-cycle to the peak of a negative half-cycle. At 100 per-cent modulation, the peak-to-peak distance will be twice the original height of the band pattern. For best operation, it may be necessary to adjust the bias voltages of the 807's between the limits shown at the

terminals in Fig. 2. It seems reasonable, however, that best operation will be secured when the higher voltage values are used. An added advantage also will be some form of r.f. output control in the external exciter.

(12) Listen to the modulated signal with a crystal diode monitor or well-shielded non-oscillating receiver, to check audio quality, speech cleanliness, etc.

Performance

Any voltage between 400 and 750 normally may be applied to the 807 plates. The r.f. output will be close to the table c.w. values of 25 watts for 400 volts, 30 watts for 500 volts, 40 watts for 600 volts, and 50 watts for 750 volts. At 750 volts, it may be advisable to employ a wider plate spacing in tuning condenser C_{12} than is specified in Fig. 2.

With the milliammeter in jack J_1 , full 100 ma. should be read under loaded conditions with no modulation. The no-modulation plate current reading with the milliammeter at J_1 will be from 8 to 10 ma. Under full-loaded conditions with modulation, the plate current at J_1 will drop to approximately 65 ma., and the plate current at J_2 will rise to 35 ma.

In keeping with the features of the Taylor modulation system, the signal from this 807 rig will be found to have surprisingly narrow bandwidth and a loudness far exceeding expectations from either a 25, 30, 40, or 50-watt signal.

The author takes this opportunity to express his appreciation to Mr. R. E. Taylor of Los Angeles, originator and patent owner of the super-modulation circuit, for invaluable cooperation and guidance while the transmitter described here was under construction.

-30-

TV CLINICAL MEETINGS SCHEDULED

DURING the next six weeks, radio-television service dealers, repairmen, and engineers in eleven metropolitan areas from coast to coast will attend the remainder of a series of clinical meetings conducted by Henry M. Joseph, chief engineer of the Coastwise Electronics Co. in Los Angeles, manufacturers of Ferret equipment.

Technicians, dealers, and engineers attending these meetings will be instructed in the newest methods and procedures of servicing modern TV equipment. All phases of alignment, repair, and servicing are discussed and demonstrated.

The latter half of the twelve-week series is scheduled for the following cities: Buffalo, May 31; Syracuse, June 1; Albany, June 2; Boston, June 3; New York, June 7, 8, 9, 10, 13; Philadelphia, June 20, 22; Baltimore, June 24; Washington, June 27; Atlanta, June 30; New Orleans, July 5; and Dallas, July 7. Among the cities covered during the first half of the schedule in April and May were Chicago, Pittsburgh, Cleveland, and Cincinnati.

-30-

June, 1949

CONVERT DIRECT-VIEW TELEVISION TO LARGE SCREEN PROJECTION TELEVISION!

Any electro-magnetic deflection TV set can be converted! All you need are 3 basic components: lens, tube and power supply.

30 KV RF POWER SUPPLY

Dimensions—Length 14 1/2", Width 11 1/4", Height 12 1/4"

The above unit is complete including low voltage DC supply. The voltage is variable from 15KV to 30KV through a control on the front panel. The high voltage unit includes a focus control and voltage tap variable from 4KV to 6KV for use with 5TP4 Projection Kinescope Tube. The high voltage 30KV-6KV cables are 3 ft. 11 inches in length and are of the safety type. Utilizes 6 tubes. Net Price Complete.....\$99.50



SPELLMAN F1.9 PROJECTION TV LENS

Dimensions: Length 7", Diameter 4 1/4"

F1.9 EF.5 in. (127.0 mm.) This lens incorporates in barrel a corrective lens for use with a 5TP4 projection tube. It is easily removable for use with flat type tubes. Lens can be utilized to project picture sizes from several inches to 7 x 9 feet.

Complete with mounting ring. Machine slotted Mounting Ring available for hand focusing adjustment. Has 4 holes for easy mounting on plate. \$8.00 extra.



5TP4 PROJECTION KINESCOPE TUBE

Features a metal backed white fluorescent screen having high brightness and contrast. Net Price.....\$67.50

Only \$90



HIGH VOLTAGE METER 0 TO 30 KV

A precision-made instrument with range from 0 to 30 KV. Has 4" scale and only draws 20 microamps. Bakelite meter panel housed in solid oak cabinet. Meter has jack connector for convenient connection to oscilloscope in checking voltage wave forms. Net price.....\$67.50

Send for Free Complete Technical Details

HIGH VOLTAGE COILS

5 KV.....	\$ 3.25
10 KV.....	7.75
15 KV.....	7.75
25 KV.....	35.00
30 KV.....	35.00

FILAMENT TRANSFORMER FOR 1 B 3 Rectifier Tube.....90c

HIGH VOLTAGE TELEVISION CAPACITORS

Specifications: Joffers Type SKC Capacitors

Type	Capacity	Operating Voltage	Net Price
SKC 10-10	1000 mmfd	10,000	.45 ea.
10-20	500 "	20,000	.84 ea.
10-30	300 "	30,000	2.10 ea.
SKC 20-10	1600 mmfd	10,000	2.52 ea.
20-20	1200 "	20,000	3.36 ea.
20-30	600 "	30,000	4.17 ea.
SKC 30-10	3200 mmfd	10,000	4.17 ea.
30-20	2500 "	20,000	5.01 ea.
30-30	1200 "	30,000	5.85 ea.

NEW REAR PROJECTION PLASTIC TELEVISION SCREENS

The screen surface consists of a conglomerate arrangement of microscopic plastic crystals that "Pin Point" the projected image providing unexcelled angular viewing with a minimum loss of projected light. It is estimated that there is a loss of approximately 10% of light viewing the image at 45 degrees off center.

Light transmission percentages are controlled to obtain the maximum efficiency of the television optical projection system.

Net price of Rear Projection Screen, per sq. ft. . \$3.00

include 25% Deposit With Order, Balance C.O.D.

SPELLMAN TELEVISION CO., INC.
DEPT. A, 130 WEST 24th STREET, NEW YORK 11, N. Y. • AL 5-3680

Get Your Commercial License!

WITH THESE BRAND-NEW BOOKS

"RADIO-TELEVISION Questions and Answers"

A separate book for each element of the study-guide questions pertaining to the various classes of commercial U.S.A. radio operator licenses. You need buy only those elements required for the license you want.

The F.C.C. is expected henceforth to revise questions element by element. Now, to keep up to date, you need buy only a new element, not a complete new book!

NOW READY!

Element 2: Basic Theory and Practice

Element 3: Radiotelephony

Element 4: Advanced Radiotelephony

Please do not order elements not yet announced. They will be published and announced soon after the F.C.C. completes each revision.



85¢ EACH

BUY FROM YOUR FAVORITE RADIO PARTS DEALER. If he cannot supply you, we will ship postpaid at \$1 for one, or 90c each for two or more.

Editors and Engineers 1102 KENWOOD ROAD Santa Barbara CALIFORNIA

FEDERATED SPRING SPECIALS SAVE YOU MONEY!



RCA 12" PM SPEAKER

12 watt capacity. For replacement and PA use. 2.15 oz. Alnico 5 magnet. Special... **\$3.75**

Same, but with extra-heavy, 4.64 oz. Alnico 5 magnet..... **\$4.49**


200 MA PWR. XFORMER

800 V c.t. @ 200 ma; 6.3 V c.t. @ 4 amps; 5 V c.t. @ 3 amps. Flush mtg. Electrostatically shielded. Bargain..... **\$3.75**



RCA 2" x 3" SPEAKER

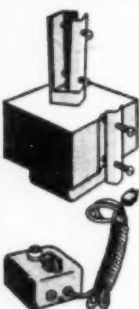Genuine RCA oval midget speaker for portables, intercoms, etc. Excellent sound quality. Your cost **79c**




NEW! KOENIG ANTENNA ROTATOR

At last—a quality antenna rotator at really low cost. The new Koenig Rotator will peak your TV, FM, or ham antenna for top reception. Powerful motor is weatherproof-encased. 360° rotation. Universal clamp easily attaches to any mast. Tiny control box permits "arm-chair" operation from any 110 V AC house current, and flashes limit of rotation. New, and only..... **\$17.95**

GE PYRANOL COND. 10 MFD., 600 V DC

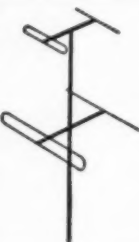4 1/2" mtg. cntrs. Measures 4 1/2" high, 1 1/4" wide. Unusual value..... **79c**



ALL-CHANNEL FOLDED-DIPOLE TELEVISION ANTENNA

The most popular antenna type in use today. Can be oriented separately for high frequencies. Antenna is matched to 300 ohm line. Durable aluminum construction. Comes complete with reflectors and mast. Less lead-in..... **\$7.95**

TELEVISION FOCUS COIL

Standard, top-quality coil for use on most magnetic focus TV sets. Similar to RCA #202D1. Only..... **\$2.51**



TV Horizontal Output Transformer



RCA #204T1 type, for use with CR tubes such as 10BP4, 5BP4, 12JP4, and similar tubes requiring 50% magnetic deflection. Your cost..... **\$4.95**

Please include 25% deposit with order. Balance C.O.D. Minimum order \$5.00. Dept. 28E

Federated Purchaser
INCORPORATED
NEW YORK CITY
80 PARK PLACE
Digi 9-3050

CABLE REORDER PURCHASER
ALLENTOWN, PA.
1115 HAMILTON ST.
Allentown 3-7441

Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO & TELEVISION NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

CONDENSED DEALER CATALOGUE

Designed to provide greater convenience for radio and appliance dealers and television installers, and to industrial purchasers of electronic materials, a condensed dealers' catalogue has been issued by the American Phenolic Corporation.

The new listing illustrates Amphenol radio frequency cable and r.f. connectors, the most popular sizes and dimensions of polystyrene sheets, rods and tubes, and microphone connectors used in audio applications, measuring instruments, photoelectric devices, etc.

Also contained in the catalogue are descriptions of Amphenol TV and FM antennas and accessories, such as extension masts, stand-off insulators, insulator clamps, and mounting bases.

Refer to the Dealers' Condensed Catalog on business letterhead, addressing American Phenolic Corporation, 1830 S. 54th Ave., Chicago 50, Ill.

REPLACEMENT LOUDSPEAKERS

The first complete listing of all Cletron speaker types and sizes has just been issued by Cleveland Electronics, Inc., 6611 Euclid Avenue, Cleveland 3, Ohio.

The catalogue includes radio speakers for use in the home and the automobile, FM and TV sets, and for sound work in laboratories and in public address systems. All of the Cletron speakers feature aluminum voice-coils and are built to RMA standards.

Copies of the catalogue may be obtained by radio service technicians and jobbers on request.

CLAROSTAT'S NEW NO. 49

Presenting an exceptionally complete line of resistors, controls, and resistance devices, a new No. 49 catalogue is available from Clarostat Mfg. Co., Inc., Dover, N. H.

All of the items recently added to the Clarostat line are included, as well as additional numbers in the various listings. For greater convenience in radio service work, the listings concentrate on universal numbers wherever feasible, so that a minimum inventory will take care of maximum replacement needs.

RADIO SHACK LISTING

A 1949 catalogue of all the electronics equipment, covering the fields of communications, television, sound, testing, and research, that is distributed by the Radio Shack Corporation has recently been published.

The all-inclusive listing covers everything from completed equipment

and kits down to the smallest components, as well as hardware, accessories, and literature. Another feature is a detailed index, showing the products by manufacturer.

Write the Radio Shack Corporation at 167-N Washington Street, Boston 10, Mass.

CATHODE-RAY TUBE BOOK

The booklet describing the modern cathode-ray tube, published by Allen B. Du Mont Laboratories, Inc., has come out in a new edition of 63 pages.

This edition includes material relative to the history, development, design and structure, and the uses of the cathode-ray tube. In addition to the full-page frontispiece reproduction of a wall chart depicting the modern cathode-ray tube, there are 68 illustrations provided to add to the general interest and attractiveness. Besides the information on the cathode-ray tube, as such, there are chapters on the cathode-ray oscillograph, television, and radar.

The booklet, "The Cathode-ray Tube and Typical Applications," is available generally to the trade through radio-parts jobbers for the sum of fifty cents.

RCA KINESCOPE COMPONENTS

The Tube Department of Radio Corporation of America is offering a 32-page booklet, "RCA Television Components for Kinescope RCA-16AP4," which provides technical data on characteristics and dimensional outlines for components used in designs employing the RCA-16AP4 picture tube.

The booklet, in addition, contains typical deflection circuits and an associated circuit of a pulse-operated, high-voltage supply for the 16AP4.

When writing ask for Form CTV-1004, addressing Commercial Engineering, RCA Tube Department, Harrison, N. J.

DYNAMOTOR CATALOG NO. 649

A companion piece to its No. 349 Converter Catalog is being offered by the Carter Motor Company, 2644 N. Maplewood Avenue, Chicago, Ill. This is the No. 649, consisting of 24 illustrated pages.

The booklet gives complete mechanical and electrical specifications on all Carter dynamotors, including the original genemotor and magmotor. Performance charts, oscillograph reproductions, and dimensional diagrams supplement the hundreds of specifications covering the various standard models.

Requests for this comprehensive literature should be made on company letterhead addressed to the manufacturer.

INDIVIDUALIZED TV INSTALLATIONS

The custom-made television units manufactured by *Sightmaster Corporation* are described in a recently published booklet, which gives diagrams and specifications for the installations.

These units are installed in a wall, and the television picture is seen in a decorative frame on the wall. A feature exclusive with *Sightmaster*, called "Sightmirror," transforms the television viewing area into a mirror when video is not being received, making it ideal for luxurious living rooms, but it is also suitable for classrooms, offices, or reception rooms.

The booklet may be obtained from the New York office of *Sightmaster Corporation*, at 20 East 35th Street, Zone 16.

CUSTOMER RELATIONS HELPS

A manual of public relations, prepared in handy, pocket-size form, fully illustrated for easy reading, is being offered by the *Radio Corporation of America*.

The booklet contains helpful hints on how to win and hold customer goodwill, ranging from such details as how the service technician should properly introduce and identify himself on his

first contact with the customer, to ascertaining customer preference in placement of the receiver and antenna.

Entitled "The Care of Television Customers," this handbook, originally compiled for use by *RCA TV service technicians*, is being made available to the radio and television trade. Single copies may be obtained from the *RCA Service Company, RCA Victor Division*, Camden, New Jersey.

STANCOR REPLACEMENT CATALOGUE

A four-page illustrated catalogue on the *Stancor* line of television replacement components, including two horizontal output transformers recently introduced, is now available from *Standard Transformer Corporation*, 3580 Elston Avenue, Chicago 18, Ill.

The two new units, A-8117 and A-8118, are designed for replacement of the parts used in leading brands of TV receivers. Other *Stancor* TV components, such as deflection yokes, focus coils, and filters chokes, are described with detailed specifications and prices. Ask for Bulletin DD337R.

LATEST HICKOK MODELS

A new four-page folder describing and illustrating the complete line of dynamic mutual conductance tube testers is offered by the *Hickok Electrical Instrument Company*, 10524 Dupont Avenue, Cleveland 8, Ohio.

The folder is attractive and shows complete specifications of counter, portable, and display models, with technical and exclusive features itemized.

TWO NEW VICKERS PUBLICATIONS

Two catalogues are being offered by the *Vickers Electric Division, Vickers, Inc.*, 1815 Locust Street, St. Louis 3, Missouri: the *Selenium Rectifier Catalogue—VC-3000*, and *Photoelectric Cell Catalogue—VC-4000*.

The first, VC-3000, is a 24-page booklet illustrating rectifier characteristics, applications, design factors, and list prices. The other, a 12-page affair, illustrates self-generating photoelectric cell applications and design specifications.

Both are supplied with graphs and illustrations and contain much information that should be helpful.

ELECTRONIC GUIDE

The *Potter Instrument Company, Inc.*, 136-56 Roosevelt Avenue, Flushing, New York, is offering a brief guide to its line of high speed electronic counters, scalars, counter chronographs and special electronic frequency measuring and computing equipment in a four-page condensed catalogue.

A discussion of the electronic counting principle, methods of count detection, and typical applications is included in this booklet in addition to

ADC TRANSFORMERS

for Exacting Audio Specifications

ADC QUALITY PLUS SERIES

For AM & FM Broadcasting and Highest Quality Music Reproduction

1. $\pm \frac{1}{2}$ db 30-15,000 CPS, all types.
2. Low transmission loss.
3. Excellent longitudinal balance.
4. Power ratings at 30 cycles.
5. Either top or bottom mounting.
6. Silver plated terminals.
7. High permeability mu metal shielding... extremely low hum pick-up.
8. Complete impregnation... to eliminate corrosion and leakage.
9. Highest grade insulation materials... withstand voltages far in excess of normal requirements.

ADC INDUSTRIAL SERIES

For High Fidelity Music Reproduction

1. Dependable at lower cost.
2. Response guaranteed $\pm 1\frac{1}{2}$ db from 50 to 10,000 CPS.
3. Minimum insertion loss.
4. Power ratings at 50 cycles.
5. Same construction, insulation and impregnation as Quality Plus series.

Tolerances of $\pm \frac{1}{2}$ db in transformer response from 30 to 15,000 CPS with low transmission loss and low harmonic distortion are guaranteed in the ADC "Quality Plus" series of transformers.

Over the range 50-10,000 CPS the Industrial series guarantees tolerances within $\pm 1\frac{1}{2}$ db. Thus a record of dependability uncommon in production transformers is provided for electronics engineers to serve for FM-AM Broadcasting, for high fidelity music reproduction, for video work and other electronics requirements.

TRANSFORMERS: Impedance Matching—Bridging—Filament—Input—Output—Filters—Plate Supply—Smoothing Chokes—Swinging Chokes.

COMPONENTS: Jacks—Jack Panels—Plugs—Patch Cords—Sound Effect Filters (Frequency cut-off adjustable from either end).

Write For Catalog today—complete details on available products. For Research laboratory, and product design, special specifications engineered and quoted. We invite your inquiry.



Audio DEVELOPMENT CO.

2845 13th Avenue South • Minneapolis 7, Minnesota

Cable Address: AUDEVCO

Audio Develops the Finest

Sun Radio's Annual Clearance!

CRYSTALS! All crystals have Army MC harmonic ratings but Sun encloses directions for deriving the correct fundamental frequency in kilocycles.

CRYSTALS WITH A MILLION USES

Fractions Omitted											
412	420	431	440	447	473	484	493	502	509	515	519
413	422	433	441	448	474	485	494	503	511	516	522
414	423	434	442	451	475	487	495	504	512	518	523
415	424	435	443	452	476	488	496	505			
416	425	436	444	453	477	489	497	506			
418	426	437	445	454	478	490	498	507			
419	429	438	446	455	479	491	500	508			

I.F. Frequency Standards			For Crystal Controlled Signal Generators		
450	459.250	464.815	526.388	531.944	536.111
451.388	461.111	465.277	527.777	533.333	537.500
452.77			529.166	534.722	538.888

Crystal Frequency Standards 98.356kc
Easily altered for 100 kc Standard Mounted in low loss 3 prong holder
\$3.89 each

ASSORTED MISCELLANEOUS CRYSTALS
Fractions Omitted
372kc 377kc 383kc 388kc
374 379 384
375 380 385
376 381 387
39c each
priced at a fraction of the cost of their holders alone.

CRYSTALS For SCR 522
5910kc 7450kc 2045 2300 2435 3215 3550
6370 7580 2105 2305 2442 3237 3570
6450 7810 2125 2320 2532 3250 3580
6610 7930 2145 2360 2545 3322 3645
7350 2155 2390 2567 3510 3955
\$1.29 each
● Payments must accompany order. Enclose 20c for postage and handling. Minimum order—\$2.00 plus postage.

CRYSTALS FOR HAM USE
FT 243 Holder 1/2" SPACING
3735 KC... 69c each 5030 KC... 39c each
4190 KC... 39c each 5485 KC... 39c each

BC720—2-6 MC PB RECEIVER
6 tubes—4 PB preset to any frequency. Conversion instructions BC band supplied. Speaker supplied. Used but A-1..... **\$9.95**

SPERRY AMPLIFIER—with 4 tubes and many parts, with diagram..... **\$ 3.95**
VHF—NAVY CW TRANSMITTER, 80-105 mc, battery operated, with 2-1G4 tubes and instruction manual, less battery..... **5.95**
BENDIX—100 watt transmitter, 4 BC07s, 4-12SK7s and 3-807s, with complete conversion instructions for operation on 10, 20, 40, 80 meters..... **39.95**
ANTENNAS: 420-450 mc ant. for BC 645... **.39**
4 section telescope, opens to 3 feet..... **.39**
22" tapered for 150-200 mc with coax connector less coax connector..... **1.95**
PORTABLE AMPLIFYING MEGAPHONE, complete with carrying case, tripod, extra mike..... **29.95**
TUNING UNITS—from BC 375—TU 9B, TU 10B..... **1.95**
TRANSMITTER—RADAR—BC-1C72A, 150-210 mc, was originally used with BC-1068A Rec. & BC-1073A Wavemeter, complete with tubes and 115v-60cy power supply **19.95**
BC-746 TUNING UNIT—contains antenna and tank coils, tuning cond. ideal foundation for miniature transmitter—with
2 xtals..... **.99**
with 2 xtals, 1 in 80 meter band..... **1.29**
less xtals..... **.39**
METERS:
WESTON 2 in. rd. 500 micro-amp, with scale for 0-15/600v..... **2.97**
J.B.T. REED FREQ. METER—56 to 64 cy..... **9.95**
TRIPLETT—2" sq. 0-40 v DC METER..... **2.97**
SUN 2" rd. 0-300 V DC..... **2.97**
WESTINGHOUSE 3" sq. 0-150 V AC..... **3.49**
SIMPSON—2" rd. 0-15 V DC..... **2.97**

●TERMS: All items F.O.B., Washington, D. C. All orders \$30.00 or less, cash with order. Above \$30.00, 25 per cent with order, balance C.O.D. Foreign orders cash with orders, plus exchange rate.

SUN RADIO
OF WASHINGTON, D. C.
938 F STREET, N. W. WASH 4 D C

the description of the available standard counters, and "special problem" equipment for use in special-application calculating and timing.

EXPANDED CONDENSER CATALOGUE

The new *Illinois Condenser* catalogue recently announced contains detailed information on an expanded line of condensers, developed to serve the entire electronic field, from radio to television. The items shown supersede all prior listings.

Address *The Illinois Condenser Company*, 1616 N. Throop Street, Chicago 22, Illinois.

MOT-O-TROL BOOKLET

Westinghouse Electric Corporation, P. O. Box 868, Pittsburgh, Pa., has issued a 23-page booklet on Mot-O-Trol, its packaged electronic, adjustable speed drive for precise control of d.c. motors operated from a.c. sources.

Divided into three sections, the booklet discusses what Mot-O-Trol is, its construction and maintenance, and its technical applications, including typical uses in many industries. In writing, specify booklet B-4112.

S.R.R.C. OUTING AT CAMP KI-SHAU-WAU

It will be the order of the day at the Starved Rock Radio Club hamfest June 5. The location will be the Boy Scout Camp Ki-Shau-Wau, near Starved Rock State Park, Illinois.

An important part of the program will be the distribution of door prizes to registrants holding numbers drawn from tickets given each person attending. Recognition will be given to all those contributing equipment or credit slips for door prizes by the publication of donors' names and addresses in the club's advertising.

The S.R.R.C., using call letters W9MKS, was organized in 1934, and is proud of the reputation of its sponsorship of radio ham meetings. Members believe about 500 or more hams will attend. To obtain advance registration, at \$1.00 (\$1.50 at the gate), call on S. N. Warrner, W9TLC, President, S.R.R.C., Box 22A, Utica, Illinois. Lunch will be provided on the grounds, and there will be plenty of shelter, rain or shine.



Building a New Scope??



Use a large 9-inch C.R.T.

9GP7 only \$3.95

Electromagnetic Deflection

Long Persistence - Bluish Fluorescence

CHARACTERISTICS

Heater 6.3 Volts 0.6 Amps
Anode #2 4000 Volts
Grid #1 Cutoff 110 Volts
Peak-to-Peak Signal Swing 25 Volts
Standard Octal Base

Tube is securely packed in a light plywood crate. Shipping weight 22 lb. Shipment by Express Collect only.

SREPCO

STANDARD RADIO & ELECTRONIC PRODUCTS
135 E. Second St. DAYTON 7, OHIO - Tel. FURter 2174

TERMS: Cash with order, or 25% deposit, balance C.O.D.

NEW PRECISION ELECTRONICS SIGNAL TRACERS



MODEL 201
\$34.50

MODEL 251
\$49.75

Write for literature and name of your nearest Jobber

PRECISION ELECTRONICS, Inc.
641-643 MILWAUKEE AVENUE
CHICAGO 22, ILLINOIS

SIGNAL TRACER SPECIALISTS

RADIO & TELEVISION NEWS

International Short-Wave

(Continued from page 40)

cotton, palm-nuts, coffee, cocoa, rubber, copal gum, sugar, and ivory. Mineral products consist of copper, diamonds, gold, tin, cobalt, tantalum, silver, and radium. The Belgian Congo ranks high among copper-producing countries. The diamond fields in the southwestern district produce more than 6,000,000 carats a year, mainly industrial diamonds, of which the Congo is the world's largest producer. The uranium ore from the Katanga district is high-grade and furnishes about 90 per-cent of the world's supply of radium. The Katanga copper belt is 250 miles long by 25 to 50 miles wide.

To "The International Goodwill Station," OTC, its staff, and its OTC Club go our best wishes for the future.

Radio Indonesia


At the time this was compiled, John J. Gaynor, California, had just received, via airmail, word from Charles Stuart, producer and program director of English Foreign Broadcasts Section, *Radio Indonesia*, Batavia, that the "100 kw. transmitter is almost ready for testing." Watch for this one which by now may be on the air!

Mr. Stuart sent along this current list of transmitters of *Radio Indonesia* (ones without call signs are Armed Forces Program Broadcasters):

By frequencies: 2.240, YDB, 300 watts—Batavia, Java; 2.350, YCN, 250 watts—Pontianak, Dutch Borneo; 2.415, YDA2, 150 watts—Bandoeng, Java; 2.500, YDH, 100 watts—Semarang, Java; 2.600, YDD, 300 watts—Batavia, Java; 2.820, 300 watts—Garoe, Java; 3.240, YDI, 300 watts—Surabaya, Java; 3.270, YDL, 350 watts—Padang, Sumatra; 3.332, 800 watts—Solo, Java; 3.380, YDR, 250 watts—Ambon, Moluccas; 3.390, YDA, 3 kw.—Bandoeng, Java; 4.370, YH12, 5 kw.—Surabaya, Java; 4.840, YD14, 1.2 kw.—Surabaya, Java; 4.855, YDK, 250 watts—Palembang, Sumatra; 4.965, YDD, 300 watts—Batavia, Java; 4.895, 40 watts—Biak, Dutch New Guinea; 4.910, YDB2, 300 watts—Batavia, Java; 4.930, YDP, 250 watts—Medan, Sumatra; 5.030, YDQ, 250 watts—Makassar, Celebes; 5.070, 800 watts—Jogjakarta, Java; 5.515, YDH2, 800 watts—Semarang, Java; 5.620, 800 watts—Jogjakarta, Java; 6.170, YDB3, 1 kw.—Batavia, Java; 7.210, YDF2, 350 watts—Medan, Sumatra; 7.270, YDB3, 300 watts—Batavia, Java; 7.295, YDI3, 500 watts—Surabaya, Java; 9.550, YDQ2, 8 kw.—Makassar, Celebes; 9.720, 400 watts—Menado, Celebes; 10.365, PLB4, 3 kw.—Batavia; 10.640, 500 watts—Fort de Kock, Sumatra; 11.000, PLB9, 250 watts—Batavia, Java; 11.084, YDQ3, 2.5 kw.—Makassar, Celebes; 11.770, YDE, 3 kw.—Batavia, Java; 15.150, YDC, 3 kw.—Ba-

CLEAR THE ROOFTOPS FOR...

Another Vertrod First!

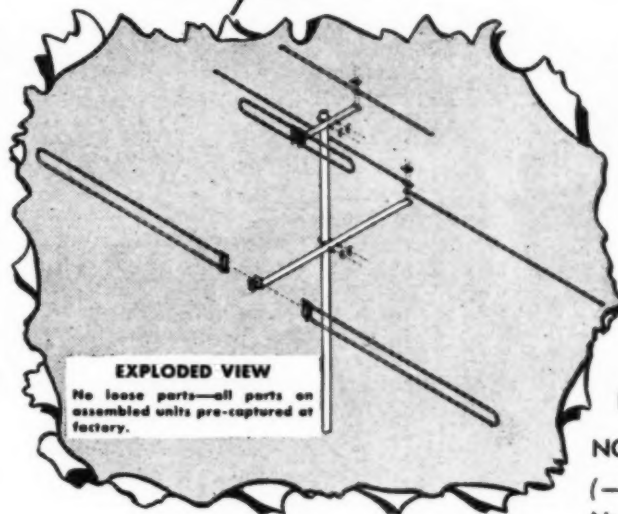

EXPLODED VIEW
No loose parts—all parts on assembled units pre-captured at factory.

SENSATIONAL "4'n1" TV ANTENNA

1. folded dipole
2. straight dipole
3. 72 ohm line
4. 300 ohm line

**ASSEMBLES
IN RECORD TIME—**

NO TOOLS REQUIRED!

(—that's right!

Not even a screwdriver!)


ALL IN ONE—SETS UP AS REQUIRED BY SIMPLE ADJUSTMENT OF JUMPER LINKS




HF straight dipole
LF folded dipole



HF and LF folded
dipole

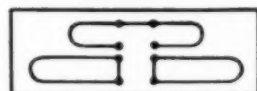


HF folded dipole
LF straight dipole

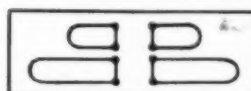

HF and LF straight
dipole

- Plated steel lock-seam 1" dia. tubing. Models available with 5 and 10 foot masts. (Furnished with two mounting clamps.)
- All tubular elements of hard tempered aluminum.
- Bakelite insulators which are non-hygroscopic.
- No loose parts— all parts on assembled units pre captured at the factory.

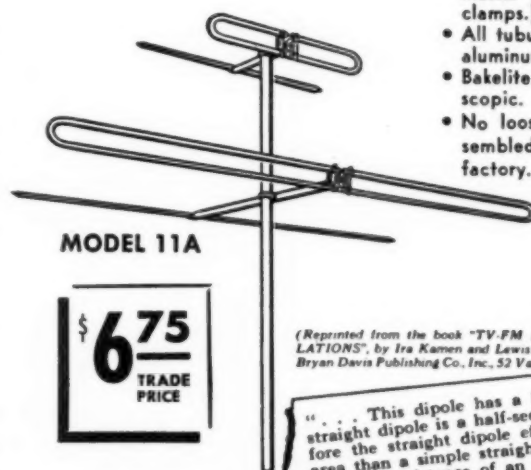

MODEL 11A

\$6⁷⁵
**TRADE
PRICE**

**FROM CARTON TO
ROOFTOP IT TAKES
LESS TIME TO INSTALL
A VERTROD "4'n1"**

(Reprinted from the book "TV-FM ANTENNA INSTALLATIONS", by Ira Kamen and Lewis Winner. Published by Bryan Davis Publishing Co., Inc., 52 Vanderbilt Ave., N. Y. C.)

"... This dipole has a broad-band characteristic since each straight dipole is a half-section of the folded dipole, and therefore the straight dipole effectively has a larger cross-sectional area than a simple straight tubular rod. It is a theoretical fact that the resistance of an antenna element increases more rapidly than its inductance as its cross-sectional area increases, and since Antenna Q = Inductance/Resistance it is apparent that a dipole made up of two half-sections of a folded dipole will have a relatively low Q characteristic and therefore a broad-band response.

MANUFACTURED BY



For information, contact your distributor or write direct.

DISTRIBUTORS: Exclusive franchises available in some territories. Write for details.


11 PARK PLACE • NEW YORK 7, NEW YORK

SEND BETTER - FASTER - EASIER WITH

JOHNSON

SPEED-X

KEYS!

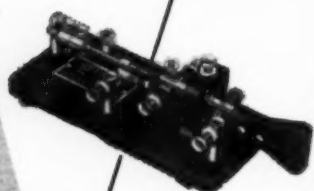

● Every cw man — beginner or expert — will readily appreciate the smooth, snappy action of Johnson Speed-X keys.

It's the kind of action that encourages faster, better sending with less conscious effort. It's the kind of key action that pleasantly surprises, no matter how much — or how often you send.

Popular member of the JOHNSON Speed-X line is the Amateur Model 114-513 illustrated above.

114-513 Features

Carefully tempered clock spring used for main and U-spring in Vibrator.

Heavy brass connector strips

Adjustable trunion screws

Heavy steel base, attractively finished with baked black wrinkled enamel

Adjustable weight and two adjustable black fibre paddles

Two sets of 1/8" pure silver contacts

Deadener wheel, post screws, springs and terminals are heavily chrome plated

Rubber feet to prevent slipping or tilting

HEAVY DUTY METAL HAND KEY

High quality at modest cost! That's a perfect description of the Standard Key 114-310. It has heavy die cast base finished in black wrinkled enamel. Bearings are extra smooth — adjustable. Contacts are 1/8" and of pure silver. There are provisions for plugging in JOHNSON Speed-X semi-automatic keys when desired. Net weight is 9 oz.



JOHNSON

E. F. JOHNSON CO. WASECA, MINN.

tavia, Java; 17.630, 2.5 kw.—Batavia, Java, and 19.345, PLF2, 2.5 kw.—Batavia, Java.

* * *

SBC

Here is some interesting information furnished by Starry, Pa., concerning the Swiss Broadcasting Corporation:

The chief of technical service writes Starry—"The Swiss Broadcasting Corporation maintains seven studios—in Basel, Berne, Zurich, Geneva, Lausanne, Lugano, and those of the short-wave service, also in Berne. All radio transmitters are being operated by the Federal Administration of Post, Telegraph and Telephone, exclusively. The center of Swiss short-wave transmitters is Schwarzenburg, a prosperous village in the Canton of Berne. They are used both for overseas telephone service and for broadcasting. Schwarzenburg has eight short-wave transmitters, with powers ranging from 10 to 100 kw. For overseas service, rhombic antennas are being used, and for the European Service, circular dipoles are employed. Schwarzenburg is located some twenty miles south of Berne, capital of Switzerland, and works together with the receiving stations of Chatonnaye, in the Canton of Fribourg. The transmitting station at Schwarzenburg was constructed by Hasler & Co. of Berne, licensed by Marconi Wireless Telegraph Co., Ltd., at Chelmsford, England."

Another official informed Worris, N. Y. that "the power of two of our transmitters is 25 kw. and we now have three at 100 kw. The bearings are on—for the various transmissions—New York, Winnipeg, Buenos Aires, Lima, Cape Town, Sydney, Melbourne, Tokyo, and Palestine."

* * *

Pakistan Verified

Via airmail from Government of Pakistan, Office of the Engineer-in-Charge, High Power Transmitters, Radio Pakistan, Headquarters, Karachi, Pakistan, on April 9, I received this message:

"In reply to your letter dated February 15 (forwarding the reception report of Radio Pakistan), I am sending you herewith a copy of our current Programme Journal (*Pakistan Calling*) and our verification card. Our present short-wave transmitter at Dacca is a 7.5 kw. set beamed towards the West by means of a single rhombic. We hope to operate two more 50 kw. short-wave transmitters from Karachi after a few months, and we shall be glad to get reception reports from you and from all such listeners from whom you might find possible to secure these for us." The signer was I. A. Ansari, Deputy Engineer-in-Charge.

The verification card is white with a green-and-black design (evidently the official insignia of Pakistan) in center; at the bottom in modern printing is the wording: "We have great pleasure in confirming your reception report of Radio Pakistan," followed by a list of

places where Radio Pakistan is now located—Karachi, Peshawar, Lahore, and Dacca (only Dacca was on short-wave when verification was made). Dacca was checked on the card, confirming my reports for February 13 and 15.

The *Pakistan Calling* was Vol. 2, No. 6 for March 16; it is issued fortnightly. Schedule for Dacca, 15.270 (this one now in use although *Pakistan Calling* listed both 15.27 and 11.89) was given: Transmission I—2030-2200; Transmission II—0030-0130; Transmission III—0600-1130; news in English at 2130, 0120, 0730, 1030.

* * *

Verification Data

Former KZRH and KZMB (now DZH-2 and DZH-4, respectively) do verify according to a letter sent to NZDXRA's bulletin "Tune In"; they say—"Both KZRH and KZMB do send out QSL cards. . . . We have had in the past few months a number of DX reports from N. Z., and as far as I have checked, these have been verified . . . but please assure your fellow DX-ers that we shall be glad to verify any reception reports received by us." Letter signed by general manager W. H. Wallace. (Gillett, Australia)

A letter from Radio-Lebanon, Beirut, Lebanon, recently came from Press Officer, Information Department, British Legation, Beirut, Lebanon; said English programs from Radio Lebanon are under the direction of "the information office of this legation," and asked for reports from time to time. (Pearce, England)

Radio Clube de Mocambique, "The Station for Happy Listening," sends new type of QSL card for CR7BU, power 7.5 kw., frequency 4.920 (but is nearer 4.930); other channels listed were 9.65, 4.82, 3.49, and 9.72. (Pearce, England) (Note that more recently the 9.72 outlet has been heard on approximately 9.76, instead.—KRB)

Reports to stations of ABC in the Inland Short-Wave Service should be sent to the Australian Broadcasting Commission in the capital city where transmitters are located (currently used ones include VLG6, VLR, VLH4, VLH5, VLH3, VLI2, VLI3, VLQ3, VLW3, VLW5, VLT5, VLT7).

QRA for Addis Ababa station is Imperial Ethiopian Government, Press and Information Department, Addis Ababa, Ethiopia. (Nattugglan, Sweden)

Address for CR6RG is Companhia de Diamantes de Angola, CR6RG, Radio Diamang, Dundo, Angola. (Nattugglan, Sweden)

Latest QRA for Tokyo s.w. stations seems to be R. H. Niino, Liaison Section, Nippon Hose Kyokai, Radio Tokyo Bldg., Tokyo Central Post Office Area, Tokyo, Japan. (Hardy, Calif.)


QRA of YSUA, 6.250, is "Radio Mil Cincuenta," la Avenida sur No. 50, San Salvador, Republica de El Salvador, C. A. (Hankins, Pa.)

IRC's are still not negotiable in French Indo-China, so do not send

RADIO & TELEVISION NEWS

OUTSTANDING VALUES NOW AVAILABLE

CLARK 15 WATT AMPLIFIER KIT

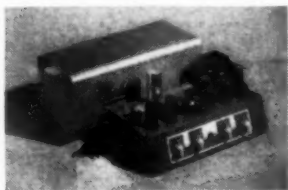

Another popular Clark kit. All first line parts to make an exceptionally fine unit.

- 6 tubes—2—6SQ7, 2—6V6, 1—6SN7, 1—5Y3GT.
- Mike and phone input.
- Separate treble and bass controls.
- Heavy steel chassis and cover.
- Frequency response 30-17000 CPS + 1DB.
- Output impedances 4-8-16-500.
- Hum level 65 DB below rated output.

Kit comes complete with all tubes and parts—ready for installation. Schematic, layout and instructions.

ONLY \$18.95 each

SNYDER AUTO ANTENNAS

Exceptional values—top quality.

Side Cowl—2 point mounting—fine chrome finish—66" extended—sturdy construction—with shielded lead.

\$1.79 each

Top Cowl—Universal mounting joint—sturdy construction—chrome finish—60" extended—with shielded lead.

\$1.99 each

ICA 100" Side Cowl antenna. High chrome finish. Shielded lead. Firm construction.

\$1.99 each

Five to a carton.....**\$9.50**

Heavy magnet 6" PM Oxford. Suitable for auto radio replacement speaker.

2.15 oz. alnico V magnet. **\$1.59** each



AUTOMATIC CAR RADIO

Fits any car. Easily installed. Will perform as well as the finest auto radios. Powerful 6 tube superhet. 3 gang tuning condenser for extra sensitivity. Full vision, slide rule dial. Beautifully finished case with decorative plastic tuning assembly. List \$39.95.

Your cost **\$27.97**

SUPER 25 WATT HI-FI AMPLIFIER KIT



Including all parts, schematic and layout diagrams, enabling you to easily build this fine, deluxe amplifier.

FEATURES:

- Ready punched chassis
- Multi-impedance output transformer 2-4-8-16-500 ohms for use with any PM speaker
- 2 mike inputs, 1 phone input
- Push pull phase inverter driver for low hum and distortion
- Hum level 65 DB below rated output.
- Separate bass and treble control
- 110-120 volt AC operation, on fuse UL approved line cord
- 6 tubes: 2—6SJ7, 6SC7, 2—6L6G, 5Y3
- Attractive, well-constructed steel chassis and cover. Baked hamerloid finish
- Indirect lighted panel
- Frequency Response 20-17000

Nowhere can an amplifier of comparable features be had for twice the price. This amplifier, designed from the famous Clark Amplifier, will fill 90% of all sound uses.

\$24.95 COMPLETE WITH TUBES

CROWE HEADS for AUTOMOBILE RADIOS

1940 thru 1949

- Under 1940 — Universal Underdash Mounting Dials. Dealers' Price.....**\$4.41**
- Tuning Units 706-T1 up thru 720-T1. Dealers' Price.....**2.03**
- Tuning Units with switch 706-T2 up thru 720-T2. Dealers' Price.....**2.80**
- Volume control units 700-V1. Dealers' Price.....**.88**
- Volume control units with switch 700-V2. Dealers' Price.....**2.12**
- Cable kits to fit Delco-Arvin-Philco. Dealers' Price.....**2.09**
- Motorola Cables. Dealers' Price.....**2.80**

When ordering, specify Make and Model of car and make and model of radio. Complete dial kit consists of "Head, Tuning Unit, and Volume Control Unit."

We carry a complete line of all auto radio equipment and accessories.

AUTOMATIC TOM THUMB "BUDDY" PORTABLE RADIO



Self-charging portable radio with patented battery rejuvenator. Increases normal battery life. Operates on AC, DC or battery. Very attractive case. 7 tube performance. Slide rule tuning dial. Batteries 67 1/2 VB—2-1 1/2 A.

\$29.95 Complete with batteries.

PREMIER VALUES

Standard replacement 4-prong vibrators.

New—guaranteed. **\$1.39** each

10 for **\$12.50**

Philco filter condensers. 40 x 10 mfd-200 V.

32c each

10 for **\$2.90**

Standard replacement type phono. cartridge.

Hi-gain—standard mounting. **\$1.39** each

10 for **\$12.90**

RMA guarantee 10 BP4CR tubes.....**\$25.00**
In factory sealed cartons.


6" 6 volt 4 ohm Motorola-type auto speakers. **\$1.59** each

10 for **\$14.90**

300 ohm transmission line. Heavy polyethylene insulation. 1000 ft. spools.

\$14.00 per 1000, Lots of 3000, **\$38.95**

RELUCTANCE CARTRIDGE

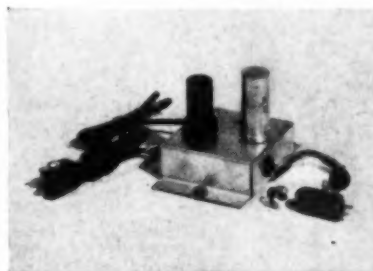

Well-known reluctance type phono cartridge. For best phono reproduction. With Farnsworth pre-amp. Will replace G-E reluctance cartridge and pre-amp. These two fine units for only.....**\$7.29**

individually.....Reluctance cartridge. **\$3.40**

Farnsworth pre-amp. **\$4.50**

WRITE FOR OUR LATEST CATALOG

Radio Parts Company, 614 RANDOLPH ST., CHICAGO 6, ILL.

NOW YOU CAN TAKE YOUR CHOICE OF Jensen SALESKITS!

Jensen Saleskits are designed especially to make the demonstration of fine needles easy for servicemen. What's more Jensen needles reduce surface scratch to an irreducible minimum, bring out the clear tone of the instruments you repair. Saleskits slip easily into your pocket; are colorful, impressive, money-makers. Boost your income by ordering your choice of Saleskits from your jobber today. Better than usual discounts. Full information by return mail.



AND THIS—
To increase your profit, an extra Bonus of a Concert or Classic Needle will be sent free with the Kit you order.

Radio Servicemen find their choice of these two Jensen Phonograph Needle Saleskits a real help in making extra-profit on service calls. You may select "Kit A" containing 3 Jensen Concert osmium-tipped long life needles priced at \$1 each and 3 Jensen Genuine Sapphire needles at \$2.50 each. Or "Kit B" with 3 Jensen Classic Needles at \$1.50 each and 3 Jensen Genuine Sapphire Needles at \$2.50 each.



JENSEN INDUSTRIES, Inc., 329 SOUTH WOOD ST. • CHICAGO 12, ILL.

Camco TV and FM ANTENNAS

(Swift-Rig)

Directional High Gain and Half-Wave arrays

Presto!... It's assembled

"Swift-Rig" antennas are completely assembled—Just Unfold and Lock In Place... A matter of only minutes.

PERMANENT LOW RESISTANCE... nickel plated brass screws and "SWIFT-RIG" LUGS at electrical contacts.

Write for catalog of complete line including Roto-Matic Window and Hy-Gain Indoor Antennas, Combination 300 ohm line and coaxial cable, Screw Eyes, Mast-Mounting Brackets (chimney, vent pipe, wall-mount), "Swift-Rig" Lugs, etc.

CAMBURN • INC.

32-40 57th St., Woodside, L. I., N. Y.

"America's Best Buy"

**RADIO TUBES—39c each
100 for \$35.00**

GT type. Cartoned and guaranteed.

01A	6A8	6K7	6X5	12SR7	40
1B5/258	6AQ5	6P5	6U6	12BE6	41
1G4	6AQ6	688	12A8	12BF6	42
1H6	6AT6	68A7	12AT6	12F5	38
1J6	6AU6	68D7	12AT7	12H6	46
1L4	6BA6	68F5	12AU6	12J5	47
1Q5	6BE6	68G7	12AU7	12J7	50B5
1R4	6BH6	68H7	12BA6	12K7	70L7
1R5	6BG6	68J7	12SF7	12K8	80
1R5	6AL5	68K7	12SH7	12Q7	117Z3
1T4	6C4	68L7	12SJ7	1288	12A
1U4	6C5	68N7	128N7	25Y5	6J7
3A4	6F5	68Q7	10	32L7	6K5
3Q4	6F6	68R7	20	37	7AF7
384	6H6	68U7	25L6	35W5	
3V4	6J5	6V6	25Z5	35Z5	
5Y3	6K6	6X4	25Z6	39.44	


49c each, 100 for \$45.00

1A5	6AC7	12AH7	35L6	58	83V
2A7	6B8	12SA7	32	71A	84/6Z4
5U4	6C6	12SK7	36	75	117L7
5Z3	6F8	12SQ7	50L6	77	117P7
6A3	6Y6	27	50	81	
6A6	6Y7	35/51	57	83	

COMBINATION SIGNAL TRACER AND SIGNAL GENERATOR \$29.95



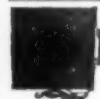The SIGNALYZER provides the following items of test equipment: Signal Generator, all frequencies. Audio, RF, IF. Signal Tracer. Audible output or meter. Test Amplifier. Test Speaker. Output Meter.



3 WATT AMPLIFIER \$14.95
Two tubes 12SJ7-117L7
2 inputs for microphone, instrument or phonograph pickup. 8" P.M. speaker. Mounted in a portable steel case.

Postage extra 20% deposit on C.O.D.
Write for latest bargain list featuring "America's Best Buys."

POTTER RADIO CO.

1314 McGee St., Kansas City 6, Mo.

them to Radio Saigon. QRA is Jean Pipon, English Department, Radio Saigon, Boite Postale 412, Saigon, French Indo-China. (URDXC)

Address for papeete is Radio Club Oceanien, Papeete, Tahiti. (DeMyer, Mich.)

Club Notes

England—ISWC, London, is now conducting an anniversary series of contests extending to July 31. Competitors are urged to (1) log as many amateur s.w. stations as possible and (2) to log as many international SWBC stations broadcasting the special ISWC programs as possible (these include Radio Australia, many stations in Europe, some in Africa, and in North and South America, and in October in all BBC overseas transmissions from London). Prizes include a silver trophy for the winner, several useful pieces of radio apparatus, also radio handbooks, and special radio manuals provided by leading radio dealers and manufacturers as well as by publishers interested in radio. Full details of the club's activities are available from Arthur Bear, 100, Adams Garden Estate, London, S. E. 16, England. (Rigby, ISWC, England)

Bachman, Pa., sends this data—"You may be interested in news of a new British club known as The Listeners' Association. Membership is open only to residents of the United Kingdom and to British citizens abroad. However, they will accept donations for their cause from anyone. Full information may be obtained from the secretary, Capt. C. H. Rolleston, 71, Victoria Road, Kensington, London W. 8, England. The Listeners' Association is a non-commercial body. It exists as a national organization to further the interests of the listener by acting as an intermediary between the listener and the BBC."

Sweden—Lars-Eric Hansson, Sweden, sends along this information—Goteborgs DX-Klubb (The Gothenburg DX Club) was founded in January 1947 by Anders Sandberg. At the beginning it had only five members. During the first year, the club grew very slowly, but then it began to expand more rapidly and now has about 50 members. Most of these are from Gothenburg, but there also are some members in other parts of Sweden, plus a British member and a German member. Mr. Sandberg is chairman; vice-chairman is Alf Hellstrom; secretary is Bertil Thorner; treasurer is Jean Hultbergh; other staff members include Helge Rydberg and Mr. Hansson; deputy of the staff is Nils Hildebrand. The members in Gothenburg get together each second Thursday at a cafe, where they spend a few hours discussing their hobby. The members also get an opportunity to read the short-wave magazines which the club gets on an exchange basis. The club's house organ, issued monthly, is called GDX-aren (The GDX-er) and was first

issued in December, 1947. Editor is Mr. Thorner; DX items are compiled by Mr. Hansson. Membership fee currently is four Swedish crowns and the QRA is Goteborgs DX-Klubb, % Bertil Thorner, Ockerogatan 3a, Goteborg W., Sweden.

USA—QRA of *The Dial Spinners' Club* is 75 Langdon Place, Lynbrook, New York; president is Bill Frothingham; vice-president is Tom Orr, 907 Fulton St., Rapid City, South Dakota. (Cornell, Ala.)

A new feature of the Short-Wave Listeners' Registry is the printing of a 1949 radio and hobby directory which will list all radio fans and hobbyists who have sent QRA's to the club. Purpose is to spread SWL friendship throughout the entire world, says Bill Camp, Club Editor, Short Wave Listeners Registry, 1042 Water St., Moosic 7, Pa.

This Month's Schedules

(NOTE: Between the time this was compiled and the time you read it, some stations will have gone on Summer Time—in such cases you will find current schedules to be one hour earlier than listed herein.—KRB)

Aden—ZNR, 6.765, heard well in England around 1415. (ISWC) Can anyone confirm this report?—KRB

Algiers—Radio Algiers, in verie, states "We broadcast very day from 1300 to 1500 in Arabic and from 1500 to 1800 in French"; frequency 9.570. (Gillett, Australia) Reported testing on 11.835 at 0500-0700. (Radio Australia)

Andorra—Radio Andorra, 5.978, heard recently from tuning 1745 to leaving it 1845, usual program of recordings and announcements. (Ferguson, N. C.)

Angola—via a verie card, *Radio Clube de Angola* advises that CR6RL, 9.470, and CR6RN, 8.090, operate 1330-1600, while CR6RA, 10.795, is on the air 0100-0300. (Gillett, Australia) CR6RH, 8.232, Hilla, has extended its schedule by a half-hour, now runs to 1500. (Swedish DX) *Radio Diamang*, CR6RG, 8.242, Dundo, heard 1400 to sign-off 1430 with Portuguese National Anthem; speech intelligibility low, with bad QRM from stations using both c.w. and (commercial) phone; another day heard from 1345 with orchestra music; has both man and woman announcer; no English noted. (Pearce, England)

Radio Clube de Angola, Luanda, sent QSL card for reception of CR6RN, 7.142; said this replaced the 8.090 channel, and asked for a check on CR6RL on 31.68 meters (approximately 9.470). (Pearce, England)

Argentina—LR4, *Radio Splendid*, Buenos Aires, appears to be on 11.880. (Stark, Texas) Bachman, Pa., lists this as LRS-2 and says is on 11.880, evidenced both by dial setting and by Spanish and English announcements; excellent 1815-1915. Leven, Brazil, also believes LRS-2 has moved from

SELENIUM RECTIFIERS AND SPECIALIZED ELECTRONIC COMPONENTS



VACUUM CAPACITORS

Standard Brands

12 Mmfd	20 Kv.	\$4.95
50 Mmfd	20 Kv.	4.95
50 Mmfd	32 Kv.	5.95

SILVER CERAMIC TRIMMERS

Type		
820-Z	5-20 Mmfd Zero Temp.	24c
822-N	5-20 Mmfd Neg. 300.	24c
822-AZ	4.5-25 Mmfd Zero Temp.	24c
823-AN	20-125 Mmfd Neg. 650.	33c

FENWAL THERMOSWITCH

Normally closed. Opens with temp. rise. Adjustable from -40° to +400° f each \$1.25

OIL CONDENSERS

2 Mfd 200VDC Bath	\$.20
5 Mfd 400VDC	.20
2 Mfd 400VDC Bath	.30
2X.1 Mfd 600VDC	.39
10 Mfd 440VAC/1500VDC	1.55
50 Mfd 330VAC/1000VDC	4.95
8 Mfd 600VAC/2000VDC	3.50
.15-.15 Mfd 8000VDC Voltage Doubler Type	3.95

ELECTROLYTIC CONDENSERS

Cap	WV DC	Each	Lots of 10	Lots of 100
100 Mfd	50	\$9.27	\$2.20	\$19.00
40 Mfd	150	.23	1.80	17.50
8-8-20 Mfd	350/150	.40	3.50	30.00
20-20 Mfd	400/250	.35	3.00	25.00
10 Mfd	450	.30	2.50	20.00
15 Mfd	450	.30	2.50	20.00
40 Mfd	450	.50	4.20	36.00

FULL WAVE BRIDGE TYPES

Input 0-15VAC	Output 0-13VDC
Type #	Current Price
B1-250	250 MA. 1.95
B1-500	500 MA. 1.95
B1-1	1 AMP. 2.49
B1-1X5	1.5 AMP. 2.95
B1-5X5	3.5 AMP. 3.95
B1-5	5 AMP. 5.95
B1-10	10 AMP. 9.95
B1-15	15 AMP. 13.95
B1-20	20 AMP. 15.95
B1-30	30 AMP. 24.95
B1-40	40 AMP. 27.95
B1-50	50 AMP. 32.95
B1-60	60 AMP. 36.95
B1-80	80 AMP. 44.95

FULL WAVE BRIDGE TYPES

Input 0-54VAC	Output 0-40VDC
Type #	Current Price
B3-150	150 MA. \$1.25
B3-250	250 MA. 1.95
B3-600	600 MA. 3.25
B3-5	5 AMP. 13.95
B3-10	10 AMP. 24.95
Input 0-72VAC	Output 0-54VDC
Type #	Current Price
B4-600	600 MA. \$3.95
B4-3	3 AMP. 14.95
B4-5	5 AMP. 17.95
B4-10	10 AMP. 32.95

FULL WAVE BRIDGE TYPES

Input 0-36VAC	Output 0-26VDC
Type #	Current Price
B2-150	150 MA. \$.98
B2-250	250 MA. 1.25
B2-300	300 MA. 1.50
B2-450	450 MA. 1.95
B2-1	1 AMP. 2.95
B2-2	2 AMP. 4.95
B2-3X5	3.5 AMP. 6.95
B2-5	5 AMP. 9.95
B2-10	10 AMP. 15.95
B2-15	15 AMP. 24.95
B2-20	20 AMP. 27.95
B2-30	30 AMP. 36.95
B2-40	40 AMP. 44.95

THREE PHASE BRIDGE TYPES

Input 0-126VAC	Output 0-130VDC
Type #	Current Price
3B7-4	4 AMP. \$2.95
3B7-6	6 AMP. 48.90
3B7-15	15 AMP. 70.00
Input 0-234VAC	Output 0-250VDC
Type #	Current Price
3B13-4	4 AMP. \$56.00
3B13-6	6 AMP. 81.50
3B13-15	15 AMP. 120.00

FULL WAVE BRIDGE TYPES

Input 0-115VAC	Output 0-110VDC
Type #	Current Price
B6-150	150 MA. \$1.95
B6-250	250 MA. 2.95
B6-1	1 AMP. 7.95
B6-3X5	3.5 AMP. 18.95
B6-5	5 AMP. 24.95
B6-10	10 AMP. 36.95
Input 0-234VAC	Output 0-180VDC
Type #	Current Price
B13-600	600 MA. \$12.95
B13-1	1 AMP. 16.95
B13-3	3 AMP. 35.95
B13-5	5 AMP. 54.95
B13-10	10 AMP. 69.95

CENTER TAPPED TYPES

Input 12-0-12VAC	Output 0-8VDC
Type #	Current Price
C1-10	10 AMP. \$6.95
C1-20	20 AMP. 10.95
C1-30	30 AMP. 14.95
C1-40	40 AMP. 17.95
C1-50	50 AMP. 20.95
C1-80	80 AMP. 26.95
C1-120	120 AMP. 34.95

*Select Proper Capacitor From List Shown Below, to Obtain Higher D.C. Voltages Than Indicated

RECTIFIER MOUNTING BRACKETS

For Types B1 through B6, and Type C1	\$.35 per set
For Types B13	.70 per set
For Types 3B	1.05 per set

RECTIFIER TRANSFORMERS

All Primaries 115VAC 50/60 Cycles		
Type #	Volts Amps.	Price
XF15-12	15 12	\$3.95
TXF36-2	36 2	3.95
TXF36-5	36 5	4.95
TXF36-10	36 10	7.95
TXF36-15	36 15	11.95
TXF36-20	36 20	17.95

All TXF Types are Tapped to Deliver 32, 34, 36 Volts.

RECTIFIER CHOKES

Type #	Amps.	Price
HY5 .02 Hy	5	\$3.25
Dimensions: 3 1/4" H x 3" D x 3 1/4" W		
Wt. 5 Lbs. Hermetically Sealed		
HY8X5 .02 Hy	8.5	\$7.95
HY10 .02 Hy	10	9.95
HY12 .02 Hy	12	12.95
HY15 .015 Hy	15	13.95

VARIABLE AIR TRIMMERS

Standard Brands—Screw Driver Adj.

	Lots of 10	Lots of 100
7.5 MMF	\$2.90	\$27.00
25 MMF	3.10	29.00
50 MMF	3.30	31.00
100 MMF	4.10	39.00
140 MMF	4.90	47.00

METERS

0-15 MA.D.C. Weston #56 2" Rd.	\$2.95
0-60 A.D.C. West. w./shunt, 2 1/4" Rd., aircraft type	3.25
0-120 A.D.C. West. w./shunt, 2 1/4" Rd., aircraft type	4.95
0-30 V.D.C. West. 2 1/4" Rd., aircraft type	2.95
0-300 V.D.C. 2 1/4" Rd. Bakelite Case Basic 0-1 MA.,	2.95

To avoid shipping errors, kindly order by type #. All prices subject to change without notice.

ATTENTION !!

INDUSTRIALS, EXPORTERS, SCHOOLS, GOV'T AGENCIES, LABORATORIES

Our engineering staff is at your service to facilitate the application of rectifiers to your specific requirements.

Write for quantity discounts on company letterhead.

Minimum order \$3.00. No C.O.D.'s under \$25.00. 25% deposit on C.O.D. Add 10% for Prepaid Parcel Post and Handling. Terms: Net 10 days to rated concerns only

Orders Promptly Filled from Our Stocks All Prices F.O.B. our NYC Warehouse

OPAD-GREEN COMPANY

71 Warren St. Phone: BEekman 3-7385 New York 7, N. Y.

**TELEVISION
SERVICING at a
PRICE YOU CAN PAY**

R. S. E. 3 inch TELEVISION SCOPE

Features:

**WIDE BAND VER-
TICAL RESPONSE**


FLAT TO 750kc

DOWN 3db

AT 1mc

VOLTAGE GAIN

OF 20 AT 5mc

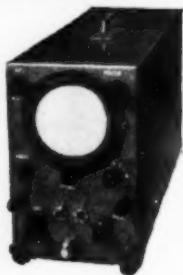

AR-3

The R.S.E., AR-3 Scope has been built by Armstrong to our rigid specifications. It's a complete unit that embodies standard horizontal amplifier and sweep circuits with normal sensitivity.

The case is 8" high x 5" wide x 14" long, attractively finished in "hammered" opalescent blue enamel. Operates on standard 110 volts—60 cycles—40 watts. Tubes, 3BP1—6AC7—6SJ7—6X5—5Y3—884. Instructions included. Complete specifications upon request. Satisfaction or your money back.

PRICE

\$49⁹⁵

**F. O. B.
DETROIT**

PUSHBACK WIRE



BELOW MILL PRICES!

2,000,000 feet—tinned copper—all 1st. class, double cotton serve, waxed finish. Available 1,000 foot rolls.

22 gauge (6 colors) \$3.98 roll

20 gauge (6 colors) 4.98 roll

18 gauge (brown only) 6.49 roll



OZ 4's (No Limit)

Fresh RK and RCA. Standard commercial grade, not JAN's.

**BUY 12 58¢
get 1 free EACH**

EGG CRATE OF 100 \$49⁰⁰



**Demand This
Seal of Quality**

ORDER INSTRUCTIONS

Minimum order—\$2.00. 25% deposit with order required for all C.O.D. shipments. Be sure to include sufficient postage—excess will be refunded. Orders received without postage will be shipped express collect. All prices F.O.B. Detroit.

**RADIO SUPPLY &
ENGINEERING CO., Inc.**
89 SELDEN AVE. DETROIT 1, MICH.

11.84 to 11.88, comments that formerly on 11.88 was LRR, *Radio Ovidio Lagos*, Rosario, which has not been heard for some time.

Buenos Aires, 15.290, noted a little before 1600, relaying LR1, *Radio El Mundo* and giving s.w. calls of LRX and LRX1; going at least to 1700 (now on winter time?). (Stark, Texas) Heard in New Zealand (an earlier report) to sign-off 1605. (N. Z. DX Times)

LRA1, 9.69, Buenos Aires, heard in Newfoundland 2030-2200 sign-off. (Peddle)

LYR1, 9.455, Buenos Aires, heard testing around 2320 to sign-off 0000; announced in Spanish and English, said testing to Europe; good signal in North Carolina; LRA1, 9.690, heard with announcement in Spanish of "Radio del Estado," and at 1830 announced official time as 2030, good signal. The 15.29 outlet heard with test transmission for Central and Western Europe from tuning 2128 to sign-off 2158; announcements were in Spanish and English, good level. (Ferguson)

Australia—VLR, 9.54, Melbourne, heard in England from around 0230 to closedown 0330. (Pearce)

AUSTRIA — *Sendergruppe West*, Dornbirn, good on 6.000, opening 0000 weekdays and 0100 Sundays. (N. Z. DX Times)

KZCA, 7.220, Salzburg, apparently has ended Saturday tests (which ran after 1800); heard in clear around 0400 and from around 0900 to 1000, other times jammed; QRA when testing was given as Station KZCA, A.P.O. No. 541, U.S. Army. (Pearce, England)

Azores—CS9MB, 11.090, Ponta Delgada, still 1500-1600, fair level, heard signing off 1600. (Ferguson, N. C.)

Bechuanaland — ZNB, 5.900, Mafeking, has been logged in England on a Sunday to 1430, weekdays to 1615, according to an item from a recent Swedish DX session.

Belgian Congo—OTH, 9.210, heard in Australia with native program and some announcements in French before signing off 1330 with anthem; reference made to *Radio Congo Belge*; good signal. (Gillett)

Leopoldville's OTC, 9.767, has announced it is now sending out report sheets to listeners. (Lyttle, Ontario)

Belgium—Brussels, 21.460, has been heard with tests, good strength, at 0600-0630, then going into scrambled speech. (N. Z. DX Times.) Is listed 21.450, where was heard recently by Arthur, West Virginia, calling Buenos Aires but could not make contact. *Radio Australia* reports the 21.450 channel testing 0400 with announcements in French and English.

Brazil—Ceara Radio Clube, 15.165, Fortaleza, heard to 1600; announced in Portuguese, Spanish, French, and English; believed to open 1500. (Stark, Texas.) Boice, Conn., got this letter from the station recently—"Your most welcome letter just reached us, and we surely were glad to hear from you.

We would very much appreciate your telling your friends there in Connecticut about our International Programme for we don't receive many letters from the States, which we sincerely regret. So give us a hand, will you? Your cooperation will be greatly appreciated by us. Let us hear from you again, won't you?" The International Programme is on the air Mondays and Fridays 1300-1500 over ZYN7, 15.165, with announcements in Portuguese, English, Spanish, and French, Boice advises.

Lyttle, Ontario, says he has heard PSH, 10.220, Rio de Janeiro, with good signal on many occasions around 1730-1800.

Weisberg, N. Y., says ZYK3, 9.565, has English daily ending 2045.

ZYB9, 15.155, Sao Paulo, heard with Portuguese and English language musical selections on Tuesday nights 1930-2000; no English announcements, but these musical numbers might help in building up a report for a QSL if the listener doesn't understand Portuguese; strong signal in Pennsylvania. (Bachman)

Radio Nacional, 18.050, Rio de Janeiro, heard with recordings when tuned 2005; at 2007 announced "Radio Nacional" and continued with music and announcements in Portuguese; at 2020 called Buenos Aires, Lima, and New York but did not seem to make contact; good signal. (Ferguson, N.C.)

Levens, Brazil, writes—"Radio Tamoi" is now on the air with two transmitters—ZYC8, 9.61, and ZYC9, 15.370; so far schedule is 0500-2200, transmission being parallel on both allocations. (Continued on page 131)

PARTS MEN TAKE TO THE WOODS

OUTDOOR Minnesota will be the scene of the Gopher Upper Midwest Radio Conference late this summer sponsored by the Gopher Chapter of the Representatives of the Radio Parts Manufacturers. The combined three-day business conference and outing will be held at Ruttger's Bay Lake resort at Deerwood, about 100 miles north of Minneapolis. Executives from factories represented by the Gopher members will meet distributors' key personnel from Minnesota, the Dakotas, Wisconsin, Iowa, and Nebraska.

Business sessions will be combined with fishing, boating, golf, tennis, swimming, and what-have-you, from Wednesday afternoon, August 31, through Saturday noon, September 3. Reservations may continue over the Labor Day weekend for those who wish to extend this trip into an added vacation. All arrangements and reservations are being handled by the Gopher Chapter, and attendance is expected to run close to 300.

This invigorating and attractive background for a business conference is a welcome departure from smoke-filled convention rooms, and the well-planned schedules are expected to accomplish much in factory-distributor relations.

—50—

RADIO & TELEVISION NEWS

NOT SINCE "BEFORE THE WAR" ...

SUCH TUBE VALUES AS THESE!

Brought to you by ART RADIO CO.—an old and trusted name

Don't rub your eyes—these amazing prices are really here. NOW, at Art Radio. An old and established name, Art Radio is famous for tremendous radio bargains. All tubes listed here are available im-

mediately from our huge stock. No waiting. Your order comes in—merchandise goes out—without delay. Stock up now at these terrific prices. All tubes individually boxed!

1L4	6AQ5	6X4	35B5
1R5	6AT6	12AT6	35C5
1S5	6AU6	12AT7	50B5
1T4	6BA6	12AU6	117Z3
1U4	6BA7	12AU7	9001
1U5	6BE6	12AX7	9002
3A4	6BF6	12BA6	9003
3Q4	6BH6	12BA7	954
3S4	6BJ6	12BE6	955
3V4	6C4	12BF6	956
6AG5	6T8	19T8	

ANY ABOVE
TUBE 33c each

\$2795 PER 100 Assorted

Please do not order types not shown on this list

70L7GT	44c each, \$39.00 per 100
1B3/8016	89c
6BG6G	44c
2051	44c
35Z5GT	39c

Specify SPECIAL OFFER
when ordering from this
ad.

SUMMER SPECIAL!
This Offering Expires August 15, 1949.
All types in stock as of June 1. Order
now, while they're still available. All
tubes backed by standard 90-day RMA
guarantee!

SPECIAL OFFERING! STANDARD BRAND "ALL-AMERICAN" TUBE KITS

BRAND	12SA7	\$0.59
NEW	12SK7	.59
	12SQ7	.59
	35Z5	.39
	50L6	.59
		INDIVIDUALLY BOXED

Actual bargain-
price value \$2.75 per kit

4 KITS FOR ONLY.....\$1000

All tubes standard brand, individually boxed in
white cartons. SENSATIONAL BUY!

Minimum order is \$10.00. Orders below \$10.00
cannot be accepted at these amazing prices.

6AK5	6SD7GT	6W4GT	12SN7GT
6AL5	6SJ7GT	6X5GT	12SQ7GT
6C5GT	6SK7GT	12A6 RCA	12S8GT
6C6	6SL7GT	12A8GT	25L6GT
6J6	6SN7GT	12J5GT RCA	25Z6GT
6P5GT	6SQ7GT	12SA7GT	32L7GT
6S8GT	6SU7GT	12SJ7GT	35W4
6SA7GT	6V6GT	12SK7GT	53

ANY ABOVE TYPE..... 37c each

\$3250 PER 100 Assorted

Please do not order types not shown on this list.

We also carry a complete line of other
famous-brand tubes and standard radio-
electronic components. Send for our cata-
log today.

ART RADIO COMPANY

115 LIBERTY ST., NEW YORK 6, N. Y.

PHONE: COrtlandt 7-2918

10% deposit with all COD
orders. All Prices F.O.B.,
N.Y.C.

For GREATER Earnings... LEARN RADIO-ELECTRONICS

This fast-growing science of RADIO, TELEVISION, RADAR and ELECTRONICS, offers tremendous opportunities, and in no industry is RADIO-ELECTRONICS more important than in aviation. A skilled technician who *knows* the modern application of electronic devices, as used in the aircraft industry, is always in demand... not only in aviation, but in many other industries. Many large organizations call on Spartan regularly for graduates. Often, students are hired months before graduation.

Don't confuse the RADIO-ELECTRONICS course offered by SPARTAN with other courses, offered anywhere! As a graduate from this famous school you will know the application to industrial control devices; to the search for petroleum; and the important uses of radar, television and other electronic equipment.

SPARTAN offers two complete and thorough courses. You will work on the most modern and complete equipment. You will build equipment. You may join the SPARTAN "Ham" Club. Either course prepares you for Federal Communication Commission license tests—first class radio telephone, second class radio telegraph, or class "B" radio amateur.



SPARTAN'S 21 years of teaching civilian and army personnel is your assurance of receiving the best possible training in the least possible time. You'll not need MORE than Spartan training—you cannot afford to take LESS.

BIG CATALOG—Free

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____

Dept. RN-69

G. I. APPROVED—Write TODAY for Complete Information

SPARTAN

SCHOOL OF RADIO AND ELECTRONICS

SCHOOL of AERONAUTICS
MAXWELL W. BALFOUR, DIRECTOR

COLLEGE of ENGINEERING
ADDRESS DEPT. RN-69

TULSA, OKLAHOMA

Simple TV Tuner

(Continued from page 49)

Make sure the oscillator frequency is on the high side of the fundamental frequency. If it is, the image frequency will appear on the high side of the fundamental frequency. If the image appears on the low side, the oscillator coil will require fewer turns for that channel. All of these tests can be made by modulating the signal generator and listening to the audio output of the receiver.

The alignment of the mixer grid coils is as follows: Tune the signal generator to the highest channel frequency. Rotate the channel switch to number one position and adjust L_1 for maximum audio output. L_2 is a short and requires no adjustment at this time. Next adjust L_3 then L_4 and then L_5 . All adjustments made at this stage are preliminary, but the oscillator coils will more likely than not require further adjustment.

It is possible to adjust L_1 , L_3 , and L_5 by spreading turns. The other coils are adjusted by removing turns. It is advisable to make several extra coils just in case too many turns are removed during adjustments.

Final adjustments are made while receiving a television signal. The oscillator coils can be adjusted so it is not necessary to adjust condenser C_4 for every station. Such adjustments will be critical. Condenser C_4 will give several megacycles change making the oscillator coils non critical.

The final adjustment of the mixer grid coils is made in favor of the picture. The coils should be adjusted to give maximum picture gain. This can be noted by the position of the contrast control.

The use of a small iron core simplifies this adjustment. Insert the core into the coil and note increase or decrease in gain. If the gain increases when the core is inserted in the coil, more inductance is required. On the other hand if the gain decreases, less inductance is required. By substituting a small hairpin of wire for the short circuit, L_2 can be adjusted. The adjustment of the coils is not difficult. If strong television signals are available, it is possible to adjust all coils on received signals.

The coils described are reasonably close to the desired frequencies. If the tuner is tuned within a few megacycles of a television signal, the buzz of the picture carrier can be heard. Rotate condenser C_4 for maximum buzz. Note the position of the condenser. If at full capacity, more inductance will be required in the oscillator coil. If at minimum capacity, less inductance is required. Make the necessary coil change and adjust condenser C_4 again for maximum buzz or actual television sound channel.


Of course, it is more desirable to make first adjustments with test equipment, but if such equipment is not

PLUG IT IN...AND IT WORKS!

Completely wired 29 TUBE CHASSIS FOR 12½" TV TUBE

Factory engineered, aligned and tested in accordance with most modern electronic methods

\$169⁵⁰

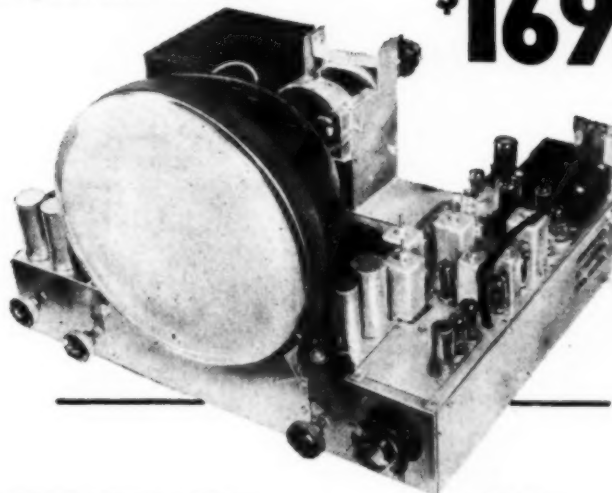

WIRED CHASSIS WITH 12½" CRT \$229.50

CHASSIS WIRED FOR 15" OPERATION (LESS CRT) \$179.50

NOTHING ELSE TO BUY OR BUILD!

This extraordinary direct view chassis, with licensed RCA circuits represents the utmost in TV value . . . The foundation of a \$900 retail value combination, it features large 84" picture screen, 29 tubes including 3 rectifiers, 13 channel tuning, long range reception, front focus control, high gain audio amplifier, automatic frequency control, and many other high-quality construction and operation advantages.

Comes with Schematics and full instructions.

EVEN A LAYMAN CAN INSTALL IT.

Standard RMA Guarantee on tube and chassis.

BUILD YOUR OWN Television Combination AT LOW FACTORY COST with LEHIGH ACCESSORIES:

High Fidelity AM & FM Tuners and Amplifiers, High Fidelity Speakers, Dual Speed Automatic Record Changers, and Custom Designed Decorator-Finish Genuine Walnut or Mahogany Combination Cabinets.

DESIRABLE TV CABINETS
ALSO AVAILABLE

Prices and Literature
on Request

BUY DIRECT FROM FACTORY AND SAVE!

Phone and Mail Orders filled on receipt of certified check or money order for \$25 as deposit . . . FOB N. Y., plus \$2.25 excise tax for each chassis.

Call in person at our factory showroom for
free demonstrations and instruction

LEHIGH TELEVISION COMPANY

601 West 26th Street, New York 1, N. Y. Dept. G

Telephone: ALgonquin 5-2046

Prices subject to change without notice.

SAVE \$ ON RADIO SURPLUS

CHOKES

1. C. A. 30 MH RF choke.....25c
40 amp .05 amp D.C.\$1.25
53 Henries, .015 App., 930 Ohms.....95c

SALE OF RADIO TUBES

68Q7, 6SA7, 12BE6, 50B5, 35B5, 35C5,
117Z3, 1B5, 1B5, 1T4, 1U4, 1U5, 3A4,
5Q4, 3V4. SPECIAL PRICE.....95c ea.
In lots of 25.....59c ea.

MAJESTIC HEAVY DUTY FULL WAVE SYN-
CHRONOUS VIBRATOR UNIT.....95c

00005 MFD, 2500 W. V. D.C. Trans. Mica.....35c
MIDGET CABINET-8 1/2" x 4 1/2" x 4 1/2" D.
Ass't. Colors, Holes for Vol. Control & Var.
Cond. Center Speaker.....69c

Signal Corps Phones-2 M. Ohms 8 M. Ohms
Imp.....\$1.25
2 Ft. Extension Cord (Female Plug).....40c

OIL FILLED FILTER CONDENSERS

1.-MFD-2000 volts.....95c ea.
1.-MFD-1000 working volts, 4 for.....\$1.00
2.-MFD-1000 volts tubular.....95c

FAMOUS BRAND RECORD CUTTING HEAD
Size 1 3/8x2 1/4 ready to fit your cutting arm or
bracket. SPECIAL.....\$2.95

TOBE TUBULAR ELECTROLYTICS

20-20 MFD, 150 V. 29c 40-40-20 MFD.....38c
40-40 MFD, 150 V. 37c 150 V.....38c
30-30 MFD, 150 V. 32c

2 1/2 M.H. R.P. CHOKE COIL-27c ea. 5 for \$1.00

3 BAND OVAL DIAL-7 1/2" L x 5 1/2" H.....79c

100 RESISTOR ASST. 1/4-1/2 WATT.....95c

Low-Loss Short Wave
Variable Condensers

1 1/2" Shaft Type

U Plate-30-40 MMFD.....25c

58 Plate-150-155 MMFD.....55c

53 Plate-210-215 MMFD.....60c

Lock Type Air Trimmer

Variable Condensers

2 Plate-12-15 MMFD.....10c

5 Plate-20 MMFD.....11c

8 Plate-30-35 MMFD.....13c

10 Plate-40 MMFD.....14c

14 Plate-56 MMFD.....20c

20 Plate-80-100 MMFD.....25c

27 Plate-100-110 MMFD.....25c

4 PR. WAFER SOCKETS-\$1.49 per C. each.....3c

PHILCO 4 MF-300 V-1 1/2 CAN CONDENSER-\$8.00
per C.....10c each

W.L.-10 W. 1,000 ohm Power Rheostat.....29c

100 ASST. SOCKETS-4-5-6-7.....\$3.50 per C

1,000 OHM WIRE WOUND POTENT.....15c

30 MY-FILTER CHOKE SHIELDED.....49c

UNSHIELDED.....39c

100 ERIC-1 WATT-2,000 OHM RES.....\$1.15

10 WIRE WOUND RES. KIT-8-50 W. ASST.....49c

2 METER RF CHOKES.....7c

2,000 ohm Wire Wound Rheostats.....\$1 per dos.

RCA-VICTOR NEEDLE CUPS-PIPING.....10c ea.

CARTER WIRE WOUND C.T. VARIABLE 20 OHM
RESISTORS.....\$1.00 per dos.

G. E. TAPPED VOLTAGE DIVIDER-200 WATT-
250 OHM-MOUNTED ON ASBESTOS BASE-TAPPED
AT 180-205 ohms.....25c

RCA 6 OHM POWER RHEOSTATS.....39c

RCA RUNNING BOARD AUTO AERIAL.....49c

PHILCO AUTO SUPPRESSOR-\$5.00 per C.....7c ea.

GEN. ELEC. WESTINGHOUSE, etc. 60 CYCLE WATT
HOUR METERS, slightly used, perfect condition,
same as used in your home.....\$1.125

5 Ampere.....\$3.50 10 Amps.....\$4.50

Philco relay tap tone control.....25c

Grind your own crystals-Pure Brazilian Quarts, all
sizes and thicknesses-1/2 lb. package.....\$1.00

340-degree dial with 10 push button attachment-
1/4" shaft-ideal for Xmitters-Sig. Gen. or Osc.....49c

RCA Band Switches-

3 Gang, 3 posit., 3 band.....30c

6 Gang, 5 posit., 4-5 band.....40c

Trimmer-Padder Asst.-all Isolantia-singles, dual-
triples-100 asst. pieces.....\$2.25

5"-450 ohm AC-DC dynamo.....\$1.35

ATTENTION: Prospectors

Explorers for Hidden Treasures!

Do you seek hidden treasures of rare metallic ores?

If so, construct a U.S. Army Type of Metallic Mine

Detector from these U.S. Army Mine Detector Amplifiers

that we are offering at a ridiculously low price.

Amplifier unit only (less tubes and batteries), with

cables, headphone cord and jack (no phones). Complete

Army wiring diagram. U.S. Army DETECTOR

SET Amplifier Type AN/FR-1.....\$1.95

No. C.O.D.'s. Eveready 45 volt batteries 2482.

\$1.75 ea., 6 volt A, 73c. 2-1N5 tubes.....95c ea.

TUBES-024-79c; 83-39c; 2A7-39c; 55-39c;

117L7-89c; 27-25c; 21B, same as 224-20c;

01A-25c; 31-20c; 85-5c.

DRY ELEC. FILTER COND. ASST. CONTAINS

10 PIECES ALL BRAND NEW 150-450V.....\$1.10

6 ASST. WET ELECTROLYTIC CONDENSERS.....59c

RADIO EXPERIMENTER'S SURPRISE PACKAGE-CON-

TAINS BYPASS & FILTER CONDENSERS, SHORT

WAVE TUNING UNITS, POWER AND AUDIO TRANS-

FORMERS, SOCKETS, RESISTORS, CHASSIS HARD-

WARE, OVER 20 LBS. OF VALUABLE PARTS.....\$4.95

DRILLED CHASSIS FOR 5-6 tubes 7"x10"x1 1/2"

-29c; 5"x10"x1 1/2".....25c

RCA ADJUSTABLE CODE INTERFERENCE WAVE

TRAP 450-475 K.C.....39c

PHONE JACKS-OPEN & CLOSED AUTOMATIC

TYPE.....18c

NATIONAL 2-15-100 VOLT ELECTRIC CON-

DENSER.....39c

PHY SPEAKER VOL. CONTROL-60 OHMS.....25c

SALE-PHONO RECORD ALBUMS-SALE

10"-3 comp.-15c; 4 comp.-20c; 12 comp.-49c

12"-3 comp.-15c; 4 comp.-20c; 12 comp.-69c

MINIMUM ORDER \$2.00-NO C.O.D.
SHIPMENTS-PLEASE INCLUDE POSTAGE

NEWARK
SURPLUS MATERIALS CO.

Dept. JE

324 Plane Street NEWARK 1, N. J.

available the above method will work provided adequate signal strength is available in your locality.

If a picture is received but no sound, the oscillator will be tuned to the low frequency side of the fundamental frequency.

Short leads are necessary if Channel 13 is to be covered. The total length of wire in this oscillator coil is approximately one and a half inches. Unnecessary lead length in wiring can increase the circuit inductance to a point where this frequency cannot be covered.

At the present time, only three low-frequency and three high-frequency television stations will be operating in most cities. In an effort to design a tuner around available parts a standard five-position switch was used.

This definitely covers the low channels, and three high channels can be covered due to the extreme range of condenser C_a . Either L_a or L_1 can be adjusted to cover more than one channel. The selectivity of L_1 and L_2 is sufficiently broad to allow such operation. A compromise adjustment of L_1 and L_2 would improve this type of operation.

The addition of an r.f. stage to the tuner would be an improvement but would complicate the construction to the point that special test equipment would be required to place the tuner in operation plus the necessary skill in actual construction.

-50-

Television Antenna

(Continued from page 37)

pickup signals. The reason for the high-gain antenna is that a stronger signal from the antenna will swamp the direct pickup on the chassis. The coaxial cable from the antenna should be connected directly to the internal antenna input terminals of the TV receiver through the matching transformer. The piece of balanced line between the external and internal antenna terminals should be removed. If there is still sufficient direct chassis pickup on any pattern so that it mars the picture, a metal bottom plate can be fitted to the base of the television receiver. Should direct chassis pickup still be present due to unshielded components, a wire mesh screen can be arranged about the inside of the TV receiver cabinet as a final corrective measure.

Many complex problems accompany even the average TV antenna installation, and they cannot be solved through application of haphazard techniques. It is usually less expensive to engineer an installation properly with the correct "asking price" for necessary components than to sell a low-cost installation which will subsequently have to be revised at a financial loss in order to maintain the customer's regard. A good installation completed at the very beginning will not imperil that good will.

-50-

A Compact Baffle

(Continued from page 57)

sions of the suspension elements (voice coil spider and cone rim annulus). Combining all these relations, we find that the maximum "undistorted" power output at any given low frequency is approximately proportional to the sixth power of the cone diameter! This means that at low frequencies a 12" speaker can deliver about 64 times as much useful power as a 6" speaker, and a 15" speaker can deliver about 4 times as much power as a 12" speaker. These relations do not tell the whole story, but they give an idea of the importance of using the largest possible speaker.

4. *Equalization.* In an absorbent walled conventional bass reflex or infinite baffle, the back radiation at higher frequencies is largely absorbed, while at lower frequencies it is largely reflected back to boost the bass response. In a labyrinth baffle, the back radiation comes into much more intimate contact with the lining, so a substantial portion of the back radiation at low frequencies is absorbed in spite of the relatively poor low-frequency absorption characteristics of the lining. Labyrinth baffles therefore give noticeably less bass boost than do other types. This is an advantage where a flat response is desired, and where all the audio components are of high quality. But where a strong over-all bass characteristic is desired, or where a strong bass boost is needed to offset deficiencies in some of the components, it is necessary to apply more bass boost in the tone control circuit than would be needed in the case of a conventional bass reflex or infinite baffle. It must be remembered, however, that tone compensation is effective only within the limits imposed by the moderate power capacity of our baffle. Undistorted power output cannot be increased by equalization.

5. *A Non-Absorbent Baffle.* Although the absorbent walled baffle gives a smoother response, a non-absorbent baffle can give surprisingly good results. A fairly satisfactory baffle can be made of corrugated paper or cardboard. The baffle consists of a corrugated paper box with baffle plates of the same material. The construction must, of course, be solid to avoid rattling. One way to accomplish this is to glue all joints.

To those who believe that a baffle should never be constructed of anything less substantial than three-quarter-inch plywood, this may sound like an absurdly flimsy construction. To be sure, it is inferior to a more rigid construction, as the walls and baffle plates vibrate noticeably at low frequencies, providing a partial short-circuit of back radiation tending to cancel the output from the front of the speaker. There would be little point, however, in making a non-ab-

sorbent baffle of wood, as it would be harder to make than the absorbent baffle, besides being inferior in performance.

6. *Testing the Baffle.* The ultimate test of a music reproducing system for the home is how it sounds in the home, playing music. No matter how flat its frequency response is in the laboratory, it will have resonant peaks in the home, caused by standing waves in the room. The home response thus depends as much on the location of the speaker and listeners as upon the laboratory characteristics of the reproducer. This does not mean that the laboratory values are useless. On the contrary, the more that is known about the reproducer's characteristics, the easier it will be to decide whether a defect in home response can be blamed on the reproducer or on the room, and the more readily the defect can be remedied.

If the reproducer's characteristics are to be tested by ear, using an audio oscillator, the test should preferably be run out-of-doors to minimize the production of standing waves. A less satisfactory alternative, where outdoor tests are not feasible, is to listen with the ear close to the speaker, in which case the standing waves are largely drowned out by the relatively high intensity sound reaching the ear direct from the speaker. Tests should be made not only of frequency response, but also of the power output at low frequencies. Actual music such as bass drum beats and organ pedal notes is better than pure oscillator tones for judging the adequacy of power output.


The closed acoustic labyrinth baffle which has been described above, has the following alleged advantages over other baffles:

(1) It has a smooth and extended bass response comparable with that of much larger conventional baffles, while providing more than enough output for most home purposes.

(2) It is small enough to be placed out of sight within most floor model radio-phonograph cabinets, or on a shelf behind a curtain, thus conserving space and eliminating the need for a fancy job of woodworking.

(3) It requires little skill or expense to make.

SEE LEO FIRST... for HALLICRAFTERS!

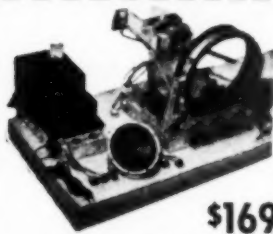

T-64 TV CHASSIS

For 10" or 12" tube

Big picture TV at a small-set price. Factory wired, aligned, and tested... backed by RMA 90-day warranty. With speaker and all tubes except CR tube. Hallicrafters new Dual-Focus switch picture on 10" tube.

\$169.95

DOWN PAYMENT \$33.95

gives instantaneous selection of either 56 or 64 square inch picture on 10" tube.

10" TUBE

\$34.50

12" TUBE

\$66.00

CONVERSION BRACKET

FOR 12" TUBE

\$8.50



LEO I. MEYERSON

W8GPK

CU ON 10-20 & 75 METERS


COMPLETE LINE OF HALLICRAFTERS

(DOWN PAYMENT 20%)

TV-509 (Television) \$269.50 SX-42 (Receiver) ...\$275.00
S-40A (Receiver) ... 99.50 S-53 (Receiver) 89.50
SX-43 (Receiver) ... 189.50 SX-62 (Receiver) .. 269.50
R-42 (Speaker) \$34.50

IT'S EASY TO BUY FROM WRL!

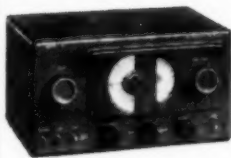Best E-Z Payment Plan in the country—We finance our own paper—no red tape! **ONLY 20% DOWN**—liberal trade-in on your present equipment. Deal with WRL—The World's Most Personalized Radio Supply House.



S-38 RECEIVER

Overall frequency range from 540 KC to 32 MC in four bands. Main tuning dial calibrated with precision accuracy. Separate electrical bandspread dial. CW pitch control adjustable from front panel, automatic noise limiter, self-contained PM dynamic speaker. 105-125 volt AC/DC.

For the first time
NEW LOW PRICE

\$39.95

Down Payment \$7.99

SPECIAL SALE—Brand new guaranteed 160 Meter Crystals in FT-243 Holders—**Each 98¢**
Frequency range 1800 to 2000
WRITE FOR OUR BIG LIST OF SPECIALS!

WRITE - WIRE
PHONE 7795

World Radio Laboratories
LABORATORIES INCORPORATED
COUNCIL BLUFFS, IOWA



GIANT RADIO REFERENCE MAP

Just right for your control room wall. Approximately 28"x42". Contains time zones, amateur zones, leading short-wave stations, monitoring stations. Mail Coupon Today and **25¢**

FREE

The most complete Ham Catalog ever assembled. Send for your copy today!



WORLD RADIO LABORATORIES
744 West Broadway
Council Bluffs, Iowa

Please send me:

☐ Radio Map
☐ New Catalog

Name

Address

City..... State.....

☐ List of Used Equipment
☐ Send Free Hallicrafters catalog

PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps • Write for information.

GENERAL TEST EQUIPMENT
38 Argyle Buffalo 9, N. Y.

SURPRISE PACKAGE

CONTAINS OVER \$2.50 WORTH OF Radio Parts such as superhet var. cond., Elect. cond., coils vol., controls, by-pass, Micron. Resistors, TRANS-11DW-etc.

All parts listed in our catalog. Please enclose postage 5 lbs.

RADIO MAIL ORDERS
Dept. RN, 2 West Broadway,
New York 7, N. Y.



"I think this is a mighty underhanded way for you to save money for a new television set!"



RADIO ENGINEERING TELEVISION ELECTRONICS

Thorough training in all phases of radio and electronics, open to high school and junior college graduates. Old established school specializing in Radio training exclusively. Modern laboratories and courses. Enrollments limited. Approved veteran training.

VALPARAISO TECHNICAL INSTITUTE
Dept. ED Valparaiso, Ind.

NATIONAL
TELEVISION



Model TV-7M

5

REASONS WHY IT'S A BETTER BUY

(1) Built, not assembled, by the leading maker of precision amateur and commercial radio receivers using quality NATIONAL components. (2) Exclusive Binaural Sound, using two speakers, does justice to FM. (3) Unique 37 mcs. IF minimizes interference. (4) Extra sensitivity brings in clear, bright pictures even in remote areas. (5) Records prove NATIONAL gives more trouble-free entertainment.

7-inch picture tube. Straight AC power supply (higher voltage). In handsome, durable metal cabinet at your National dealer's.

\$179⁵⁰



NEW TV RECEIVERS on the Market

EMERSON PHONORADIO

Emerson Radio & Phonograph Corporation, 111 Eighth Ave., New York N. Y., has announced that deliveries



are being made on the new "four-way" television Phonoradio console, Model 618.

This receiver has a 91-square-inch picture screen, using a 12½ inch television tube, in combination with FM and AM radio and including a phonograph with automatic record changer. The combination is encased in a console cabinet of matched crotch and striped mahogany veneers.

This model retails at \$529.50 and is believed to be one of the lowest priced, name "four-way" 12½-inch-tube TV radio-phonograph consoles now on the market.

DIRECT CURRENT TV SETS

Introduced into the New York market by Stewart-Warner Corporation, 1826 Diversey Parkway, Chicago 14, Ill., is a 10-inch television set operating on d.c. only, designed to eliminate the expense and other objections to the use of an a.c. converter. It is believed this innovation will give greater image stability.

The list price of the d.c. model is the same as that of the a.c. television receiver. It was intended particularly for apartment house areas, and utilizes the same cabinet as in the Stewart Warner consolette, model AVT-1.

Although this set is being distributed only in the Manhattan market, it will be available on special order for dealers in other areas where need for a straight d.c. set arises.

"PROTELGRAM" THROWS IMAGE

Intended primarily for TV viewing of large groups, a television picture four feet wide by three feet high has been demonstrated by North American Phillips Company, Inc., 100 East 42nd Street, New York 17, N. Y. The picture was projected from a small

cabinet containing a complete television receiver onto a conventional home movie screen, using a slightly modified "Protelgram" optical unit.

The "Protelgram" system can be used in conventional cabinets with built-in screens, featuring picture sizes ranging from 192 to 234 square inches. Studies by the company have shown that an image of approximately 200 square inches (20-inch diagonal) is ideal for most home applications.

The only necessary modification of the standard unit for the demonstration was a change in the positioning and optical characteristics of the corrector lens. No increase in power supply or chassis drive is required. The second anode voltage remains at 25 kv., and any chassis which will drive the "Protelgram" unit in its present form, producing the popular 200 square inch picture, will operate it satisfactorily with the new corrector lens leading to the three by four foot picture.

NEW ADMIRAL MODELS


With the addition of seven new models of 12½-inch picture tube direct-view television combination radio-phonographs, Admiral Corporation, 3800 West Cortland, Chicago, Ill., now offers a line of 23 video sets and combinations that feature picture tubes from 7 inches to 16 inches.

These seven sets are offered in three cabinet stylings; five of them, in two of the stylings, are housed in cabinets the size of an average radio-phonograph combination. The basic



difference in the two is that one has double full-length doors in the modern style, while the other has only top-half opening doors. The third styling is in Admiral's "Credenze" motif, with extra record storage space provided on each side of the combination.

RADIO & TELEVISION NEWS

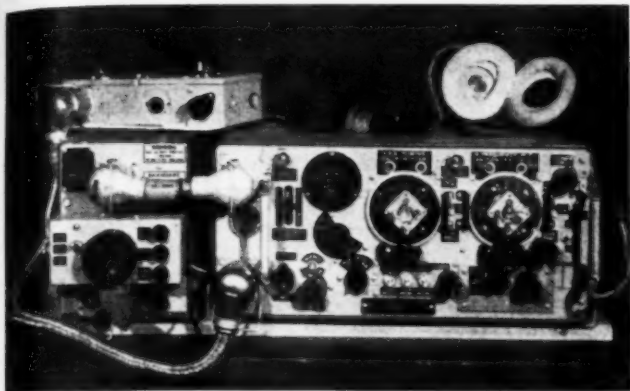

THE FAMOUS No. 19 ARMY RADIO

For communications on 2 to 8 Mcs and 230 to 240 Mcs.

SOLD COMPLETE. BRAND NEW with Supply Unit, Transmitter (807) Receiver, Aerial Variometer, Tubes, Antenna and base, Headset, Microphone, Key, Junction boxes, all interconnecting cables and complete Instruction Book. Also one complete set of spare tubes, spare headsets, brushes, fuses, etc. . . .

No. 19 MK II. For operation on 12 v. battery (Supply Unit No. 1—Dynamotor). In original Manufacturer's packing, 2 cases (Set Kit and Installation Kit). Net price. . . . **\$64.50**

No. 19 MK III. For operation on 12 and 24 v. battery (supply Unit No. II—Dynamotor and Vibrator). In original Factory packing, 2 cases (Set Kit and Standard Installation Kit). Net price. . . . **\$74.50**

TERMS. 25% deposit on C.O.D. orders. Prices net, F.O.B. Shipments will be made from warehouses Plattsburg, N. Y., or Montreal, Canada.

NORTH AMERICAN ELECTRONICS COMPANY

P.O. BOX 178, PLATTSBURG, N. Y.

**For The Best in Tape Recorders
Look For The TWIN-TRAX® Label**



TWIN-TRAX
4-HOUR PLAY



TWIN-TRAX STANDARD

TWIN-TRAX
PORTABLE

This label identifies the original and only TWIN-TRAX Recorder, manufactured exclusively by Amplifier Corp. of America. It is your assurance that the recorder bearing this label has the professional specifications that have made TWIN-TRAX the "choice of engineers everywhere."

TWIN-TRAX was the first commercially available two-channel tape recorder. Imitators have announced two-channel recorders with similar names and similar external appearances. But it's the performance that counts, not the appearance. And the performance of TWIN-TRAX recorders cannot be duplicated. Our leadership in the tape recording field has been undisputed since we designed the first magnetic recording amplifier in 1936.

Remember, imitative Twin-Track or Two-Track does not mean TWIN-TRAX, because TWIN-TRAX is the registered trade mark of the best in tape recorders, made exclusively by Amplifier Corp. of America. Send today for literature on the exclusive TWIN-TRAX line, and discover why TWIN-TRAX is the recorder engineers are buying.

*Registered Trade Mark.

AMPLIFIER CORP. OF AMERICA

398-2 Broadway

New York 13, N. Y.

JUNE SPECIALS

TEST EQUIPMENT

I-139A Test Set for SCR-522.	\$ 5.00
THERMISTOR BRIDGE—Made by Western Electric.	49.50
I-222A Signal Generator 150-230 M.C. 8-15 M.C.	69.50
IE-19A Test Set for SCR-522.	200.00
BC-306C Frequency Meter.	17.50
Model 105S Microwave Signal Generator 375-725 M.C.	49.50
Megger—500 V.—1000 Megohms. Mod. M-1000 B. Made by Interstate Mfg. Com. MI-48B. Used \$69.50.	99.50
Supreme Model 563—Audio Oscillator.	29.50
Test Set Type 89.	29.50
Calibrator I-200 115 V. 60 Cycles—345 and 621 cps Western Elec.	49.50
I-193A—Test Set for adjusting polarized relays—Western Elec.	150.00

MINE DETECTOR—SCR-625A Used for locating metal, underground pipes, gold, etc.	\$74.50
NEW with manuals.	45.00
USED—excellent condition	

FL-8 Range Filter, New.	\$1.50
Antenna Relay Unit—RE-2/ARC-5 Weston Antenna Current Indicator Meter, Relay, Vacuum Condenser, Excellent condition.	2.95
Handy-Talkie Crystal and coil sets—3885 K.C. to 5500 K.C.—Specify frequency—2 Crystals and 2 Coils per set. New.	2.25

I-82—Selsyn compass indicator, 5" 360 degree dial.	\$2.95
Plug will fit I-82, I-81.70
I-81—Selsyn compass indicator, NEW.	3.25

WESTON Electrical Tachometer meter Model 845 for use with Model 724 Magneto. Speed 0-2000 R.P.M. Ratio 2:1. NEW.	\$19.50
WESTON Tachometer Generator, Model 724, Type C. Good Used.	18.50
1st, 2nd or 3rd I.F. Transformer from SCR 522, 12,000 kc.—Iron Core Tuning, can be tuned to television I.F. freq. by removing padder cond. 35c ea.	1.00

APN-1 ALTIMETER INDICATOR—Basic Movement 0-1 ma., 5 ma. abunt. 270° scale. An excellent basic movement for constructing your own meters. NEW.	\$1.95
METER RECTIFIER, full wave midgeit Selenium, 10 volts, 30 ma. NEW.29

6" P.M. COMPARTMENT SPEAKER, 25 watts, 50-6,000 ohms. Waterproof. Used excellent	\$8.95
--	--------

SCR-522 EQUIPMENT

RADIO SET SCR-624C, SCR-522 Ground Station—includes SCR-522C, Chest CH-173A, Set of tools, Chest CH-172A, RA-62C 110VAC Rectifier power supply, Chest CH-170A, Antenna AN-94A, Antenna Mast, ETC. —Complete in 6 boxes. All cables, cords and lines NEW.	\$485.00
PLUGS—Set for SCR-522.	4.00
BC-631B—Jack Box.79
PE-94C—Dynamotor for SCR-522. NEW \$4.95. Used.	2.95
AN-104 Antenna STEEL. NEW \$1.95. COPPER.	2.95
BC-602—Control Box. NEW.	1.00

HS-23 Headset—Brand New with ear pads.	\$2.95
HS-30 Headset—Complete with matching transformer, 6 ft. cord, and PL 55 Plug. BRAND NEW.	1.95
HS-30 Headset. NEW.95
Extension Cord, CD-307A—New with PL 55 and JK 26.49
Headset Adapter MC-385D—High to low impedance.35
Dynamic Headset and Mike—P.O. Mark II. NEW.	1.95
T-17 HAND MIKE. NEW \$1.50. USED.75
T-32 DESK MIKE. NEW \$3.50. USED.	1.95

IDEAL MOBILE POWER SUPPLY

PE 237—Heavy duty vibrator power supply, 6, 12, or 24 v. input. 525 v., 95 ma.; 105 v., 42 ma.; 6.5 v., 2 amp; 6 v., 500 ma.; 1.3 v., 450 ma.; small supply 100 v., 17 ma.; 1.35-450 ma. with tubes, shock mounted. BRAND NEW.	\$29.50
--	---------

EE-8 TELEPHONE FIELD SETS with handset and ringer. Good used \$9.00 each. . . . pair **\$16.00**

Bassett Aircraft Radios and Accessories—Two-way radio. Communication—Transmitter freq. 3105 K.C.—All new equipment.	
MC6A—1½ watt trans.-recr., tubes, crystal, battery case, antenna.	\$31.50
MC6B—8 watt trans.-recr., tubes, crystal, vibrapack, antenna 6 or 12 volt.	49.50
MR3A Receiver—Range, weather and tower freq.	13.50
MCU1 Aircraft Microphone.	4.95
Headset and plug.	2.95
Model—TR15 Trailing antenna wire set.	6.95

400 Cycle Inverter—General Electric 5D21NH3A—Input 27 V., 35 amps, output 115 V.—485 V.A. single phase.	\$12.50
Sound powered head and chest set—Made by Automatic Electric Com. NEW.	5.95

PHOTOCON SALES

1060-2 North Allen Avenue Pasadena 7, Calif.
TERMS: I.o.b. Pasadena, unless postpaid.
25% on all C.O.D. orders.
Californians add 2½% sales tax.

GIBSON GIRL, SCR 578B Transmitter for sending distress signals from boats. Transmitter complete with balloon, hydrogen generator, kite and installation manuals. NEW. Export packed.	\$19.50
NEW. Domestic packed.	17.50
Transmitter only, tubes.	5.95

CD-501A CABLE for PE 103A-BC654A.	\$1.95
RM-29 REMOTE CONTROL UNIT, RINGER —NEW.	8.75

BC 357 J—BEACON RECEIVER, 75 mc., tubes. NEW.	\$ 3.45
MN 26C—RADIO COMPASS RECEIVER, tubes 150-1500 kc.	17.50
BC 464—TARGET RECEIVER, 5 channel remote control, battery case and ant. 68-73MC. NEW.	14.95
INTERPHONE AMPLIFIER—BC 709; Ideal for Aircraft, booster for telephones, etc. NEW.	4.50
INTERPHONE AMPLIFIER—CMX50128A, 12 v., 6 watts output P.O. TCS equipment with tubes and dynamotor. NEW.	8.50

TRANSFORMER: 5 v. at 190 amperes; 115 v., 60 cycle input. USED.	\$12.95
200-0-200 at 50 ma.; 6.3 v., 3 amps, output, 115 volt, 60 cycle input—NEW.	2.50
100 watt Class B modulation transformer P.O. BC 375. NEW.	2.95
PEERLESS HQ-20 line matching transformer, 50/125/200/500 ohms. NEW.	1.50

TUBE SPECIALS

1A5 \$0.55	VR150 . . . \$0.90	249C . . . \$ 1.75
5U4055	E114B50	304TL89
6A689	VT127A . . .2.95	7212.00
6BH61.05	232150	80185
6H660	232250	8033.95
6K7G60	232650	8071.25
6K8G60	232750	8371.50
6L6G60	232875	84939.50
6SH735	5HP41.95	891 Amperes
6SL7GT89	5BP42.50	NEW100.00
6SN755	5CP12.50	95435
6X5CT55	RKR731.25	9581.00
12A625	RKR731.75	16181.50
12H635	3079	162535
12K880	75TL2.50	162640
12SH735	21150	162945
12SK760	316A79	16302.95
12S760	725A9.95	900445
1E7G1.25	726A7.50	6 Amp. Tun-
3B2469	707B9.50	ESP2.95
WL53019.50		

CALIFORNIA KILOWATT SPECIALS

Transformer—Secondary 0200 V @ 325 ma. Easily C.T. for 3100-3109. 8 650 ma. Primary 105/110/115 VAC—American Transformer Com. Instructions included.	\$49.50
Transformer—2.5 V @ 10 amps. C.T.—15,000 volt insulation 115 V. AC. primary—Kenyon S-9883	5.95
CHOKE—Smoothing 20 henries 300 ma. 15,000 volt insulation—115 V.A.C. primary—Kenyon S-9881	12.95
.02 mfd—8,000 V.D.C. Oil Cond.—Aerovox M12.	\$1.39
.01 mfd—5,000 V.D.C. Oil Cond.—Aerovox M12.69
mid—3,000 V.D.C. Oil Cond.—Aerovox M12.79
.5 mfd—2,500 V.D.C. Oil Cond.—Aerovox M12.95

FACTORY TO YOU DIRECT!

THE NEW
Certified
TELEVISION KIT



10" KIT \$69.50*
*LESS TUBES

7" KIT \$59.50 \$94.50
Less tubes with all tubes

Money Back Guarantee—Buy it, inspect it, if you don't think it's the best buy on the market—return unused within five days and your money will be refunded.

All prices F.O.B. New York. 20% deposit with order
IMMEDIATE DELIVERY

Certified TELEVISION LABORATORIES
5507 — 13th AVE. BKLYN. 19, N. Y.

Walmar's June Bargains!!!

CONDENSERS—PYRANOL—OIL-FILLED
2 mfd 600v. DC W. .40 1 mfd 2000v. DC W. 1.65
4 mfd 600v. DC W. .55 8 mfd 2000v. DC W. 3.85
10 mfd 600v. DC W. 1.15 .25 mfd 3000v. DC W. 1.25
10 mfd 1000v. DC W. 1.50 .1 mfd 3000v. DC W. 1.25
.5 mfd 2000v. DC W. .50 .1 mfd 7500v. DC W. 1.75
.012 mfd 25,000v. DC W. .2.75 1 mfd 25,000v. DC W. 19.00
3.75 mfd 330v. AC. .35

CONDENSERS—BATHTUB—OIL-FILLED
.1 mfd 600v. DC W. .25 Mica .0008 mfd .95
2x.1 mfd 600v. DC W. .25 5000v. DC W. .95
3x.1 mfd 600v. DC W. .25 Mica .005 mfd 3000v. .85
.5 mfd 600v. DC W. .25 DC W. .85
.25 mfd 600v. DC W. .25

TRANSFORMERS—115V. AC 50-60 CYC.
Blas supply, secondary 90v. 1.1 A. .4.25
Filament 7v. 1.5 amp. (15,000v. Inaul.) .1.95
Hi-V. Fla. Sec. #1, 6.3v. 2A 4800v. DC Sec. .6.25
#2 2.5v. 1.75A 5700v. DC .6.25
Hi-V. Plate 4000v. @ .0022 amp. .6.25

TUBES — JAN — GUARANTEED !!!
6Y6069 2X250
6AC775 8362.50
6SN775 705A4.50
GL-446A90 5HP4 Scope3.95
GL-164190 12GP7 Scope15.00

\$ \$ MISC. BARGAINS \$ \$ \$ \$
Jones Terminal boards, barrier type, Cat. #8-142, 8 dual term. .35
Jones Terminal boards, barrier type, Cat. #10-142, 10 dual term. .45
G.E. 6 dual contacts terminal boards. .20
36 meg. 1F chassis, complete w/7 tubes, bandwidth .4 meg. .12.95
Rheostats ohmite model K, 3000 ohm 100W. 1500 ohm, 100 W., 200 ohm 100W. .95 Ea.
Relay rack, floating on rubber mounts—H 61" W 41", L 42" .25.00
Oscilloscope chassis, completely wired for 12GP7 tube, less power trans. .29.50
AC Syne. Transmitters, Bendix type 1-1, C69405, (Pair) .7.00 Ea.
GE meters 3" round—type Do-41, 0-1.0 RF amp. w/thermo. .3.65
GE meters 3" round—type Do-41, 0-20 KV., 1 mil. MVT. .3.75

Hundreds of Other Parts—Write for Flyers !!!
WALMAR DISTRIBUTING CO.
3002 Virginia Ave. Baltimore 15, Md.

CODE SENDING RECEIVING SPEED

Free Book

HIGH SPEED

WITHOUT NERVOUS TENSION

REVEALING BOOK shows how "crack" operators develop high speed and proficiency. Learn code for Amateur or Commercial Radiotelegraph License, or improve your sending and receiving with the Candler System which develops radiotelegraph experts and code champions.

CANDLER SYSTEM Box 528, Dept. 2-G Denver, Colorado

All of the sets are equipped with the new "Triple-Play" phonograph that automatically plays with one tone arm all sizes of all records, both microgroove and standard, at all the turntable speeds on the market: 33 $\frac{1}{3}$, 45, and 78 r.p.m.

In addition, all the sets have a specially designed, built-in turret tuner, originated by *Admiral*, that permits complete television channel coverage.


"THE BELMONT"

Television, radio, and phonograph, all forms of electronic home entertainment are provided in the Model 10AXF43, featured by *Raytheon Manufacturing Co.*, 60 East 42nd St., New York 17, N. Y. It is provided with *Raytheon's* Hi-Fidelity FM-AM radio, 20/20 super-circle television, and the new 45 r.p.m. microgroove automatic record player.

The entire surface of the 10-inch picture tube is utilized, and the circular screen thereby presents a 70 square-inch direct-view image. The Hi-Fidelity "ratio detector" FM and standard broadcast receiver with a voltage-doubler circuit provide extra power needed for true-to-life tonal response.

The 45 r.p.m. record changer incorporated in "The Belmont" automatically plays eight of the new seven-inch Vinylite non-breakable records.

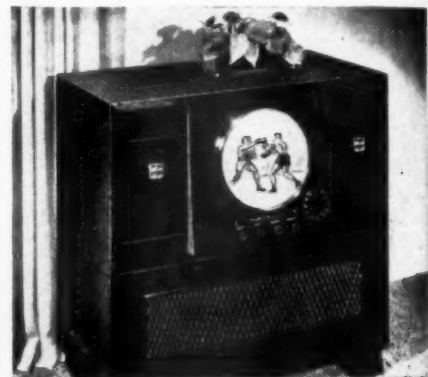Of contemporary design, the cabinet is finished in hand-rubbed mahogany veneers, and the television panel meets the eye at a level suitable for maximum comfort from a normal sitting



position. All TV and radio controls are on the front panel. The size of the cabinet is 33 $\frac{1}{2}$ by 34 by 39 $\frac{1}{2}$ inches.

DU MONT'S DE LUXE "MANCHU"

Newest addition to the *Du Mont* line is a de luxe television receiver model featuring a twenty-inch tube recently announced by the *Allen B. Du Mont Laboratories, Inc.*, 515 Madison Ave., New York 22, N. Y.


The "Manchu" is compact in design and offers a very large direct-view tube, with a screen of 213 square inches, AM and FM radio, automatic record changer for standard and LP records, and a high-fidelity audio system employing dual speakers for full-range reproduction.

Installation of the receiver equipment has been made in a cabinet

RADIO
TELEVISION NEWS

MAGAZINE LIBRARY

Now Available for Immediate Delivery

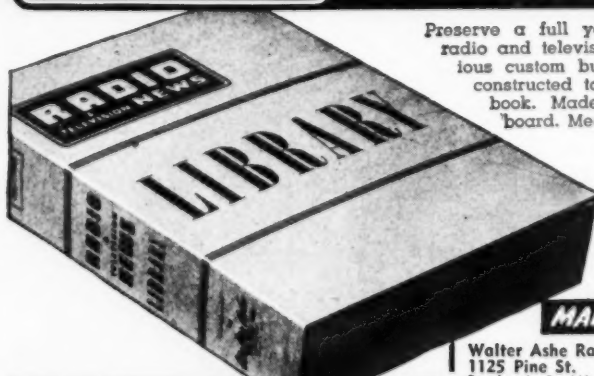

Preserve a full year's issues of your favorite radio and television publication in this ingenious custom built storage file. Printed and constructed to look like a Buckram bound book. Made of high quality Kraft fibre board. Measures 12" x 8 $\frac{1}{2}$ " x 2-3/16".

Only 50¢

Per set of 2. Plus 15¢ to cover pkg. & pstg. anywhere in U. S.
Holds 12 complete issues

MAIL THIS COUPON TODAY

Walter Ashe Radio Co.
1125 Pine St.
St. Louis 1, Missouri R-49-6b

☐ Rush my order for _____ sets Radio & Television News Library @ 50¢ per set of 2, plus 15¢ additional to cover pkg. & pstg.

☐ Remittance for \$_____ is enclosed.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Walter Ashe
RADIO CO.
1125 PINE ST. ST. LOUIS 1, MO.
PHONE Chestnut 1125

mounted on a teakwood table that rotates on a specially designed swivel mechanism, which permits the screen to be turned to any desired viewing position while the cabinet base remains flush against the wall.

One side and end of the cabinet is in beautifully grained mahogany, while the other side and end is finished in an antique Chinese jade lacquer. Heavy brass hardware is used on all four sides, and either the mahogany or jade surfaces may be employed as desired to complement the decorative motif of any room.

GAROD CONSOLETTA

Employing a 15-inch cathode-ray tube, a "Tele-Zoom" picture magnifier, and AM and FM radio reception, the new television consolette announced



by Garod Electronics Corporation, 70 Washington Street, Brooklyn 1, New York, comes in mahogany ("The Grand") or in a bleached mahogany version ("The Moderne").

According to the manufacturer, this is the lowest price 15-inch instrument in the de luxe consolette category, and when the normal 15-inch rectangular picture is enlarged to a circular close-up by pressing the "Tele-Zoom" control, the user has an image which is larger than the one reproduced on 20-inch tube receivers.

"The Moderne," Model 15TZ9, has a cabinet measuring 24 inches wide, 21½ inches deep, and 43 inches high.

MECK TEN-INCH TV RECEIVER

The John Meck Industries, Inc., Plymouth, Indiana, manufacturers of low-priced radio and television receivers, announces the production of a new



10-inch television set offering a 65 square inch picture.

June, 1949

**Just Off
the Press!**



The MOST COMPLETE Transformer Catalog in the Industry!

The big, new 1949 edition of the Stancor catalog has just come off the press. It's the catalog that every radio technician uses as his transformer "bible". . . and it's yours for the asking. Complete listings of over 400 stock items, handy reference charts, easy-to-use indexes and diagrams make this Stancor buying guide better than ever. Write for your free copy today!

● TRANSFORMERS AND CHOKES

Detailed electrical and physical specifications, including applications, ratings, dimensions and prices, give you all the information you need to select the right Stancor unit for your purpose.

● HIGH FIDELITY TRANSFORMERS

A complete listing of the new Stancor HF and WF series. Made for the discriminating audio engineer to meet applications where superior quality is a "must."

● AMATEUR TRANSMITTERS

Years of experience in meeting amateur and commercial communication needs are built into the high quality Stancor transmitting equipment listed in this catalog.

● HANDY CHARTS

A transmitting and rectifier tube chart, a driver-modulator chart, output transformer-tube chart, and a full page of dimensional drawings of all Stancor mounting types are "plus" features of this new catalog.

STANCOR TELEVISION CATALOG Be sure you also have the latest edition of the Stancor television replacement parts catalog. You can depend on Stancor television components . . . built with the same care that goes into Stancor original equipment for TV set manufacturers. Write for Catalog 337 or see your authorized Stancor distributor.



STANDARD TRANSFORMER CORPORATION
ELSTON, KEDZIE & ADDISON • CHICAGO 18, ILLINOIS

UNUSUAL PRICES PERFECT JAN. & STANDARD MAKE TUBES

Magnetrons	
2J21	\$14.00
2J26	18.00
2J27	18.00
2J31	18.00
2J40	54.00
2J49	36.00
2J50	45.00
2J61	45.00
2J62	45.00
2J32	14.95
714AY	4.00
725A	15.00
730A	12.00
Klystrons	
2K25	\$24.95
2K26	15.95
707A	9.95
707B	9.95
Pulse Modulators	
527	\$ 8.95
701A	6.00
715A	6.00
715B	6.00

Thyratrons	
C18	\$ 3.95
3C23	3.95
3C31	3.95
393A	3.95
394A	3.95
C6A	6.95
885	1.45

Rectifiers	
2X2	5.60
2X2A	7.95
3718	1.25
SR4GY	1.25
RK72	1.25
RK73	1.75
250R	9.00
705A	1.25
719A	14.95
866A	1.50
872A	2.50
8013A	4.95
1618	1.95
869B	24.95
8020	2.95

T.R. Tubes	
1823	\$ 9.95
1824	9.95
183A	12.95
721A	9.95
Power Tubes	
2C34	4.95
2E24	4.95
2E26	3.75
3C24	5.00
350B	2.40
368A	1.80
368B	1.80
446A	1.80
450TH	19.95
WL48B	8.95

801A	
801A	75
703A	1.80
802	4.25
803	5.25
807	1.35
808	2.95
813	6.95
814	2.95
832A	3.95
845	3.25
849	29.95
851	19.95
861	19.95
1624	.69
1625	.25
8012A	1.95
8025	3.95

Acorn	
1A3	29
954	45
955	45
956	45
957	35
958A	45
959	55
9001	55
9002	35
9003	45
9004	45
9006	35

C.R. Tubes	
5B1	\$ 2.25
5B1	2.75
5B4	4.75
5C1	2.95
5C1	4.95
5MP1	4.95
7D4	12.00
10B4	34.95
12J4	59.95
18A4	89.00
20B4	225.00



LIBERTY ELECTRONICS, INC.
135 LIBERTY STREET NEW YORK 6, N. Y.
WORTH 4-8242
ASK FOR FREE CATALOG

BEST BUYS

SUPERIOR ACCURATE POCKET SIZE V.O.M.



Sensitivity: 1000 ohms per v. Compact: only 3 1/2" x 5 1/2" x 2 1/4". 2% acc. 1 ma. meter. Zero adj. holds for BOTH resistance ranges. Handsome black bakelite case and etched panel. Measures the following: 6 AC ranges from 0-3,000 v. 6 DC ranges from 0-1,500 v. 4 DC current ranges 0-1.5 amps. 2 resistance ranges 0-500 ohms and 0-1 meg. Complete with test leads, batteries and operating inst., this is A BUY at only \$13.90.

NOW - IMMEDIATE DELIVERY. BIGGEST POWER TOOL VALUE EVER OFFERED!

The famous C.A.S.C.O. Deluxe Electromatic Power Tool Kit. 27,000 r.p.m. rotary AC-DC Power Tool Motor with 50 accessories provides a whole shop full of motor driven tools at your fingertips! Everything you need to make every job easier, faster, more professional looking! Motor is housed in sturdy Tenite case, formed to fit your hand. Easy to use—has 1001 uses. Drills, saws, grinds, sharpens, buffs, routs, etches, carves, sands, polishes, with the 50 accessories included and housed in Burgundy lined plastic tool chest. 36 page Project Book on THINGS TO MAKE included. ONLY \$19.95 ea.



HANDSET HANGER

Accommodates all makes and models (W. E. Kellogg, American, etc.) handsets such as TS-9, 11, 13, etc. Fastens to side of desk or on telephone or radio equipment. Felt facing protects handset. Black crackle finish only. \$1.95 ea.




LOOK! NO HANDS!

This mike leaves both hands free for mobile QSO's. Fastens to operator by simple snap strap. Western Electric button assures best quality obtainable from any carbon mike. Adjustable. Double action sw. operates push-to-talk or holds on. BRAND NEW only \$1.75 ea. POSTPAID in U.S.A. and CANADA.



RM-29A TELEPHONE

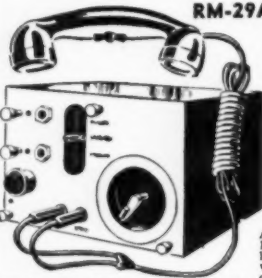


all BRAND NEW. PRICE \$12.95 ea.

REAL BARGAIN!

HS-16 Headphones with standard long cord (6 ft.) and adjustable headband. Unquestionably the best buy in surplus phones ever sold. Tested before shipping. Limited quantity. \$1.35 ea. POSTPAID in U.S.A. and Canada.



HARRIS SHOCK MOUNTS

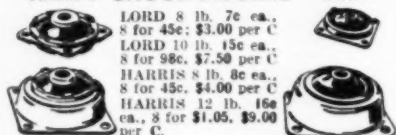

Send 25% deposit with order. Bal. C.O.D.

OFFENBACH & REIMUS CO.

372 Ellis St.

San Francisco 2, Calif.

Greater detail is provided by a new automatic frequency control system, and high-voltage power with improved regulation makes possible better contrast and increased brilliance.

The set, Model XL-750, has a cabinet of hand-rubbed mahogany measuring 15 inches high, 21 inches wide, and 19 inches deep.

FIVE-IN-ONE CONSOLE

A new television console (Model 9TW333), the first television receiver incorporating the new 45 r.p.m. music reproducing system, was announced by the Radio Corporation of America, RCA Victor Division, Camden, N. J.

The five-in-one combination offers 10-inch, direct-view television, standard and RCA Victor FM radio reception, and separate systems for the reproduction of 78 r.p.m. records, and the new 45 r.p.m. discs.

The console features RCA Victor's "Eye Witness Picture Synchronizer" and automatic multi-channel selector switch for television, five watts of push-pull power output, a standard "Silent Sapphire" permanent-point jewel pickup for the 78 r.p.m. record player and a miniature counterpart for the new 45 r.p.m. system, built-in antennas for the AM and FM radio bands, and thirty tubes and three rectifiers.

Although housing five entertainment units, Model 9TW333 measures only 40 inches high, 41 1/2 inches wide, and 23 inches deep.

PLASTIC TV CABINET

Molded in rich rosewood of G-E phenol formaldehyde plastics material, one of the largest plastics cabinets has been fabricated by the

General Electric Company, Plastic Division.

The housing was designed for a new low-priced table model television receiver produced at G-E's Electronics Park, Syracuse, N. Y., and is



molded in two parts, weighing eleven pounds. The largest section is 15 inches high, 11 1/2 inches wide, 17 inches deep, and has an average wall thickness of 3/16 inch.

The chassis of the set, with its 10-inch picture tube, is assembled to the plastics face panel and then locked through an opening in the back of the deep plastics case. The face of the cabinet has a generous picture opening framed with a projecting head. The receiver itself contains a simplified circuit which necessitates only 17 tubes and 3 rectifiers in addition to the ten-inch picture tube.

PORTIONS OF THE 160-METER BAND RE-OPENED

ALTHOUGH the case for restoration of 160-meter privileges looked hopeless for a long time, the FCC has finally opened portions of this band for limited operation effective April 7, 1949.

By Commission order FCC 49-188, dated February 17, 1949, Section 2 104 (a) of the Commission's rules was amended to show the frequency allocation of 1800-2000 kc. on a shared basis between Amateur Radio Service and Radio Navigation (Loran) Service subject to detailed conditions and limitations applicable to the Amateur Service, as follows:

(a) Mississippi River to East Coast U.S. (except Florida Gulf Coast states): 1800 to 1825 kc. and 1875 to 1900 kc., using type A-1 or A-3 emission. Power input to the plate circuit of the tube or tubes supplying power to the antenna shall not exceed 500 watts day, 200 watts night.

(b) Mississippi River to West Coast U.S. (except states bordering Gulf of Mexico): 1900 to 1925 kc. and 1975 to 2000 kc., using type A-1 or A-3 emission. Power input to the plate circuit of the tube or tubes supplying power to the antenna shall not exceed 500 watts day, 200 watts night, except in the State of Washington where daytime power is limited to 200 watts and nighttime power to 50 watts.

(c) Florida and states bordering Gulf of Mexico: 1800 to 1825 kc. and 1875 to 1900 kc., using type A-1 or A-3 emission. Power input to the plate circuit of the tube or tubes supplying power to the antenna shall not exceed 200 watts day, no operation at night.

(d) Puerto Rico and Virgin Islands 1900 to 1925 kc., and 1975 to 2000 kc., using type A-1 or A-3 emission. Power input to the plate circuit of the tube or tubes supplying power to the antenna shall not exceed 500 watts day, 50 watts night.

(e) Hawaiian Islands: 1900 to 1925 kc. and 1975 to 2000 kc., using type A-1 or A-3 emission. Power input to the plate circuit of the tube or tubes supplying power to the antenna shall not exceed 500 watts day, 200 watts night.

(f) The use of these frequencies by stations in the Amateur Service shall not cause harmful interference to the Loran system of radio navigation. If an amateur station causes such interference, the station licensee shall, as directed by the Commission, immediately cease operation on the frequencies involved.

A large part of the credit for the restoration of these operating privileges is due to the untiring efforts of NARC. Nice going, fellows.

-50-

Technical BOOKS

"POST WAR COMMUNICATIONS RECEIVER MANUAL" by Sams Staff. Published by Howard W. Sams & Co., Inc., Indianapolis. Price \$3.00.

This book has been designed for radio amateurs, professional operators, aircraft radio technicians, and short-wave listeners. Service data on most of the communications receivers produced in the period from the end of the war to mid-summer of 1948 have been included.

In addition to this service data, which appears in "Photofact" form, aligning and other adjustment information is given for the various receivers. One particularly valuable service rendered by the book is that of giving a list of standard replacement parts which may be used in the receiver being analyzed. Complete voltage and resistance charts are provided to facilitate servicing and adjustment of the receiver.

Thirty communications receivers, manufactured by Collins, Gon-Set, Hallicrafters, Hammarlund, National, and RME are covered in the text. In addition aircraft and marine radios from Airadio, Hallicrafters, Harvey Wells, Heath, Jefferson Travis, Leardo, Motorola, and Ranger are discussed and diagrammed.

Although such a brief description hardly does justice to such a text, those who will find it of the most value will be able to judge it best in the operating shack.

THE RADIO AMATEUR'S HANDBOOK (26th Edition, 1949). By headquarters staff of the American Radio Relay League, West Hartford, Connecticut. 736 pages. Price \$2.00.

This internationally recognized standard manual of amateur radio communications has been carefully revised and brought thoroughly up to date. Its twenty-five chapters cover the entire field from basic fundamentals to the latest techniques in single-sideband telephony.

In the time-tested Handbook pattern, the first four chapters are devoted to the history of amateur radio, electrical laws and circuits, vacuum-tube principles and data on high-frequency communication. Additional fundamentals are presented in conjunction with constructional chapters, and the student is given practical applications of the theory as he learns it.

A handy new section on practical filter design is included in the power-supply chapter which has been rearranged for maximum readability. Amateur very-high-frequency, ultra-high-frequency, and microwave techniques and equipment are covered in a five-chapter section.

Altogether, the Handbook is quite valuable for its well-organized information on assembling an amateur station, eliminating broadcast and televi-

• SPEEDY SERVICE
• GREATER VALUES
• BRAND NEW STOCK

ACORN

ELECTRONICS CORP.

OUR NEW QUARTERS
ARE BETTER EQUIPPED
TO SERVE YOUR NEEDS

☆ BARGAINS IN SPEAKERS



8" Magnavox PM 22 oz. Alnico III Magnet, 8 watts output. **\$2.99**
8 ohm V.C. Terrific Value.
10" PM Jensen, "Standard Series" P10T ST. 119. An excellent speaker for good quality radio sets or PA systems. Output undistorted 8 watts. Voice coil impedance 4-8 ohms. Wt. 7 lbs.
A great value at... **\$4.49**
12" high fidelity extended range 50-10,000 Cy. Jensen PM 12SH. Alnico V Magnet. 6-8 ohm voice coil. 9 watts output. Wt. **\$8.45**
12 lbs. List \$18.00.
12" coaxial JRP-40 Jensen high fidelity, tweeter woofer. Built-in network. Frequency range 50-12,000 C.P.S. Voice coil impedance 6-8 ohms. 12 watt undistorted output. Shipping wt. 15 lbs. **\$16.50**
List \$30.

☆ FILTER CHOKES

Hy	Mils	Ohms DC	Each
10	55	350	\$.69
15	70	420	.79
10	85	250	.57
10	150	70	1.49
2 1/2	235	60	1.59
10	250	100	2.95
10	300	55	2.79
5	400	300	3.25

VOLUME CONTROL WITH SWITCH, 1 meg. 29c each: **\$1.10**
4 for

TWIN LEAD TRANSMISSION LINE, 100' lengths. For TV Installation. **\$1.79**


ANTI-CAPACITY SWITCH, Federal. DPDT—neutral position. Perfect for TV Antenna Switch-Over. **\$1.29**

☆ HEAVY DUTY POWER TRANSFORMER

Pri. 110/220 v 60 cy. Sec. No. 1—410-0-410 @ 400 mils. No. 2—6.3 v @ 3 amps. No. 3—6.0 v @ 13.5 amps. No. 4—5 v @ 3 amps. No. 5—2.5 v @ 1.7 amps. Dimensions: H-6 1/2" W-6 1/2" D-5 1/2". Wt. 33 lbs. Made for U.S. Navy by G.E. Tremendous Value! **\$7.49**
3 for \$20

☆ COAXIAL CABLE

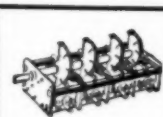Very Special RG-8U 50 ft. reels. Wt. 4 lbs. Per reel... **\$1.50**



☆ 4-GANG FM TUNING CONDENSER

Perfect condenser to cover FM band and similar applications. 3-30 mmfd per section. Statite insulated. Wt. 2 lbs.

Each **\$1.79**
3 for **4.75**

☆ POWER TRANSFORMERS



STANCOR POWER TRANSFORMER—Pri. 115 v 60 cy. Sec. 800 v ct @ 200 mils. 6.3 v @ 5 amps. 5 v @ 4 amps. upr. mt. Wt. 14 lbs. **\$4.89**

Pri. 115 v 25 cy. Sec. 680 v c.t. @ 225 mils. 10 v tapped @ 6.3 @ 5 amps. 5 v @ 4 amps. Wt. 16 lbs. **\$4.79**

Thordarson power transformer. Pri. 115 v 60 cy. Sec. 750 v c.t. @ 145 mils. 6.3 v @ 4.5 amps. 5 v @ 3 amps. upr. mt. Wt. 7 lbs. **\$3.29**

Pri. 115 v 60 cy. Sec. 720 v c.t. @ 150 mils. 6.3 v @ 4 amps. 5 v @ 3 amps. Half shell mt. Mounting centers 3 1/4" x 2 1/4". Wt. 6 lbs. A REAL VALUE! **\$2.99**

Pri. 115 v 60 cy. Sec. 600 v c.t. @ 100 mils. 6.3 v @ 3 amps. 5 v @ 2 amps. Half shell mtg. Mtg. centers 2 1/4" x 2 1/4". Dimensions H-3 1/4" W-3 3/4" D-2 3/4". Wt. 5 lbs. Made by Thordarson. BARGAIN. **\$2.69**

HIGH GAIN • WIDE BAND

☆ 5" SCOPE

Nationally Advertised
This scope is comparable to instruments selling at two to three times the price.

- Decade Attenuators (Frequency Compensated)
 - Push-Pull Deflection
 - Identical Vertical and Horizontal Amplifiers
 - Sensitivity .15 RMS Volts/inch
 - Bandwidth 2 cycles to 450 KC.
 - Z Axis Input • Calibration Test Signal
- List Our **\$99.50**
\$119.50 Price



☆ SILVER CERAMIC TRIMMERS

1.5- 7 mmfd Ideal for TV and UHF
3-12 " 29c each
5-20 " 4 for \$1
4 1/2-25 " 29c each
4-30 " 4 for \$1
7-45 " 29c each
35-55 " 4 for \$1



WARD LEONARD RELAY—DPDT—115 v 60 cy—coil 650 ohms. Each. **\$1.89**
LEACH RELAY—DPST—12 v DC. 67 ohm coil, heavy duty contacts. Each. **\$2.29**
ALLIED PLATE CIRCUIT RELAY—SPST, 7000 ohms, operates @ 2 1/2 mils. Each. **\$1.19**



☆ FP ELECTROLYTIC CONDENSERS

Upright mount
Unheard-of Prices!

Cy.	Volt	Price
10 @ 450v...		.34
20 @ 450v...		.39
30 @ 450v...		.49
20-20 @ 450v...		.67
30-30 @ 450v...		.70
40-40 @ 450v...		1.09
50-50 @ 450v...		1.10
20-20-20 @ 450v...		1.20
20-20-20 @ 475v...		1.34
20 @ 450v...		
50 @ 150v...		.30
40-40 @ 150v...		.70
20 @ 50v...		.70
20 @ 10v...		.70
40-40 @ 250v...		.70
90-90 @ 200v...		.90
20 @ 50v...		.90

ACORN ELECTRONICS CORP.

76 Vesey St., Dept. N-6, New York 7, N. Y.

PHONE WORTH 4-3270

TERMS: 20% cash with order. Balance C.O.D.
All prices F.O.B. our warehouse in New York City. No orders under \$2.50.



RADIO COURSES

Preparatory Mathematics, Broadcast, Marine Operating, Servicing, Aeronautical, Television, Frequency Modulation, Radar.

Classes forming for Summer term June 1.
Entrance examination May 16

Veteran Training. Literature
COMMERCIAL RADIO INSTITUTE

(Founded 1920)
38 W. Biddle St. Baltimore 1, Md.

TOP-QUALITY SURPLUS PARTS

—Removed from new equipment—
WESTON 1-708 5MA TUNING ("B") METER: Illuminated, shielded, Luminous Dial; mounts in 2 1/4" hole; 1 1/2" deep. With application diagrams, \$3.50. Extra 1M32 lamps, 25c each.
HIGH RESISTANCE RELAY: 5500 ohm 6ma coil, 3 pole single throw normally-open contacts; 2"x1 1/2"x1 1/4". \$1.00 each.
FL-5F AUDIO FILTER: 1020 cycles bandpass and rejection; straight-thru. High-impedance; 2 3/4"x2 3/4"x3". \$2.00 each.
FL-30 AUDIO FILTER: Same as FL-5F but Low-impedance. \$2.00 each.
MINIATURE STORAGE BATTERIES: 3-36v., 1-2v., dry-charged, rechargeable; each 3/8"x1 1/4"x3 3/8" (see RN Dec., p. 174). Set of 4, \$3.00.
B2166 JACK BOX, complete, 3 1/4"x4 3/8"x2 1/8". \$1.00 each.

Remit by Cash, Check or Money-Order and We Pay Postage
ENGINEERING ASSOCIATES
Far Hills Branch Box 28 Dayton 9, Ohio

NEW TELEKITS NOW \$59⁵⁰


Jobbers: Write for Information

**NEW
TELEKITS**
10-B \$82.99
7-B \$59.50




Sparkling new Telekit 10-B has 52-inch screen. Brand new compact lay-out has video tube mounted on chassis. Big illustrated easy-to-follow instruction book guides you step by step through easy assembly. No special knowledge of television is required. All you need is a soldering iron, pliers, and screw driver. Telekit 10-B, \$82.99. Tube kit, including 10BP4 and all other tubes, \$59.30. 10-B Telekit cabinet \$24.50. Telekit Guarantee includes free factory service.

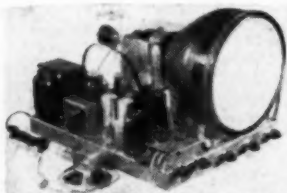Write for catalog listing 10-B and 7-B Telekits. New 7-B Telekit for 7-inch tube, \$59.50. Tube kit, including 7JP4, \$42.08. 7-B cabinet, \$24.50.



Note simple clean lay-out for easy assembly of new Telekit 10-B. Features 2 sound I. F. stages, a new pre-built, pre-aligned tuner that includes a stage of R. F. for distance reception. Easy-to-adjust horizontal lock circuits. Beautiful new model cabinets for 7-B and 10-B are heavily constructed of hand rubbed walnut.

**13
CHANNEL
TUNER
\$19.95**

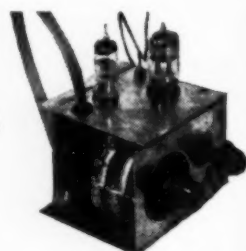

NEW 13 CHANNEL TUNER is a small compact unit with stage of R.F. Made to conform with Telekit or any other TV set having video I.F. of 25.75 Mc. Complete with tubes, pre-wired, pre-aligned; only three connections to make. See your jobber, or write to us for information. Your cost, \$19.95.

Write for catalog of Telekit antennas, boosters, television kits, tuners, television parts and tubes.

TELEKIT
ELECTRO-TECHNICAL INDUSTRIES
1432 NORTH BROAD STREET PHILADELPHIA 7, PA.

sion interference, recommended station operation practices, emergency operation and message handling, and fills current needs as a radio construction manual, reference work, and training text.

RADIO FUNDAMENTALS, by Arthur L. Albert. Published by McGraw Hill Book Co., Inc., New York. 595 pages. Price \$4.50.

Much of the material in this book was developed and expanded from lecture notes and problems which were being used in college and wartime radio courses. It is designed as a text for students who have not had electrical courses and thus is amply supplied with diagrams and illustrations. Summaries, review questions and problems follow each chapter.

Before entering into such subjects as oscillators, transmitters, vacuum tubes, and rectifiers, each of these being thoroughly covered in their respective chapters, the book discusses the fundamentals of acoustics and of electricity.

Upon mastering these very important chapters, with the aid of problems and review questions the student is led by progressive stages through the sections on circuits and power transfer and impedance matching, into the more complicated aspects of radio operation.

Television is but very briefly touched upon; the entire book is devoted to radio and is very well suited to the needs of those interested as a hobby, or those wishing thorough grounding in the subject as a prelude to repair and servicing.

THE AMPLIFICATION AND DISTRIBUTION OF SOUND, by A. E. Greenless, A.M.I.E.E. Published by the Sherwood Press, Pacoima, California. 302 pages. Price \$6.00.

This edition is intended to present a general survey of the principles of sound amplification and distribution for those engaged or interested in the planning, installation, or operation of sound-amplifying equipment. It can be recommended as an introduction for the beginner, or as a work of reference for the established public address engineer.

No advanced knowledge of mathematics is necessary to follow the text, and mathematical treatment of the subject has been introduced only where necessary. Proceeding from the study of fundamentals, this chapter having been included for the sake of completeness, the manual continues to the study of amplifiers, their special features, and their power supplies and performance. Radio receivers, microphones, record reproduction, and loudspeakers next come in for a share of attention, and the book concludes with discussions of installation planning, operation, and maintenance of equipment and testing devices.

This edition, being a revision and enlargement of the original, includes latest developments in the field of sound.

Bandswitching V.F.O.

(Continued from page 35)

Regardless of the theoretical stability of any oscillator, it still does not relieve the constructor of the necessity for using care in his work. Hams building any v.f.o. should see that all parts are mounted solidly. In the writer's unit, No. 14 solid wire was used for r.f. hookup. Supply wiring was cabled of No. 20 flexible, insulated wire. Tie points, cable clamps, lockwashers, and other constructional features which make for mechanical stability were used. When winding the coils, the largest wire was used which would fit the given form. One end was tied to a door knob and the required length unwound, stretched and wound on the form under tension. The final coils were given a light coat of Quartz Q coil dope and left to dry thoroughly before being used.

After construction and wiring was completed, the circuit was checked for correct continuity of wiring. This practice often saves grief and money on any job, as one error in wiring can cause plenty of trouble. Before turning on the power supply, the voltage regulator tap was set down on the voltage divider. Power was then applied and the slider moved up toward the high end until the VR tube ignited and remained ignited under key-up or down conditions.

From this point it was necessary to bring into use the receiver, wave-meter and a frequency meter. The popular surplus BC 221 frequency meter was used for calibration, and it does an excellent job. It is probably the most accurate frequency meter available to the average ham. A secondary frequency standard having output signals on 10, 100 and 1000 kc. would also be an excellent calibrator, but there are not many of them around that the average ham can borrow for one job. The BC 221 will indicate 1 kc. points in the 80-meter band, but this is a bit closer than necessary. Marks at each 10-kc. point on the 80-meter dial are entirely adequate. Starting with the 80-meter band, all oscillator padders were adjusted so that the desired bands of frequencies were centered on the National SCN dial. Then the doubler padders were adjusted for maximum output. These padders may require touching up when the v.f.o. is coupled to the rig. As was mentioned earlier in the article, some adjustments were necessary on the coils to allow perfect tracking.

Final tests with the author's unit showed that drift during warm-up was very small, amounting to only about 250 cycles on the 80-meter band. Changes in line voltage produced absolutely no change in oscillator frequency, even with the extreme downward surges caused by the starting of the refrigerator or oil burner. Loading appears to have negligible effect on the frequency. One remarkable

RADIO & TELEVISION NEWS

feature was that the stability on band 3 was just as good as it was on band 1. As for keying, it would be impossible, on any band, for a listener to distinguish the v.f.o. from the best crystal oscillator, as there is no chirp or drift whatsoever, even with the final in operation. As for power output, the drive is sufficient to excite a 6L6 or 807 as a buffer or multiplier. It is well known that the best stability in v.f.o.'s is coincident with low-power levels in the first stages.

To place the exciter in operation, it is necessary to connect 117 volts a.c. to terminals 5 and 6. Terminals 3 and 4 supply operating voltage to 117-volt a.c. relays when the send-standby switch is thrown to "send" position. At the same time, the circuit to terminals 1 and 2 is opened, disabling the receiver. To operate the v.f.o. without energizing the high-voltage relays or killing the receiver, it is only necessary to operate S₁. In this way, the unit may be tuned to any frequency within a band with the high power off. Ofttime cursed is the ham who tunes his v.f.o. across the band with his antenna radiating half a kilowatt or so. The best way to excite an 807 or 6L6 buffer stage operating straight-through is to remove the crystal or grid coil and connect the hot side of the v.f.o. output to the grid through a .0001 μ fd. condenser, while grounding the other side of the link. If operating the following stage as a multiplier, it will be necessary to couple the v.f.o. to the grid through a circuit tuned to the v.f.o. frequency, while tuning the plate circuit of the multiplier to the desired output frequency. The tuned-grid circuit is not desirable, however, when operating the 807 or 6L6 straight-through, as the stage is liable to "take off" as a tuned-plate-tuned-grid oscillator. Of course, the v.f.o. can be tuned a reasonable distance either side of the center frequency without retuning the following stages, but don't expect to be able to move from one end of the band to the other without retuning.

The author's transmitter, which, incidentally, was described in the July, 1946, and November, 1947, issues of RADIO NEWS, is presently being controlled by the v.f.o.

Our 26th Year

LEEDS
The Home of RADIO

QUALITY—PRICE
DEPENDABILITY

PLATE TRANSFORMERS
For Small Transmitters. DC Voltage Ratings are Approx. Values
Obtained at Output of a 2 section Choke input Filter. Using
Mercury Vapor Rectifier Tubes Pri. is for 115 V. 60 cy.

Type No.	Sec. Rms. Volts	Sec. DC Volts	MA.	H.	W.	D.	Price Each
P 57	660-660+	300	250	4 3/4	3 1/2	4 3/4	\$ 6.76
P 58	550-550	400	250	4 3/4	3 1/2	5	8.23
P 59	1080-1080	1000+	125	4 3/4	3 1/2	5 1/2	7.94
P 67	500-500	400	150	4 3/4	3 1/2	5 1/2	7.94
P 68	800-800	750	225	4 3/4	3 1/2	5 1/2	7.94
P 67	1450-1450	1200	300	5 3/4	6 1/2	4	19.84
P 68	1175-1175	1000	300	5 3/4	6 1/2	4	19.84
P 68	2100-2100	1750	300	5 3/4	6 1/2	4 1/4	24.99
P 68	1800-1800	1500	300	5 3/4	6 1/2	4 1/4	24.99

* For dual operation with simultaneous use of both sec ratings.
† Has 40-volt bias tap.

SCOPE & TELEVISION TRANSFORMERS & CHOKES

2500V. RMS @ 5 Ma D.C.—6.3V. @ 3 amps tapped at 2.5V. @ 3 amps; 2.5V. @ 2 amps	\$6.76
Type P-3171	
1700V. RMS @ 2 Ma D.C.—6.3V. @ 9 amps tapped at 2.5V. @ 2 amps; 2.5V. @ 2 amps	\$5.14
Type P-3170	
2 Hys @ 250 Ma D.C. 50 ohms	\$1.62
Type C-2991	
2 Hys @ 200 Ma D.C. 50 ohms	\$1.92
Type C-2974	
VERTICAL BLOCKING OSC. turns ratio pri. to sec. 1:4.2	
Unshielded type A-3000	\$1.18
Shielded type A-4000	1.62
HORIZONTAL BLOCKING OSC. turns ratio pri. to sec. 2:1	
Unshielded type A-3002	\$1.32
Shielded type A-4002	1.76
VERTICAL OUTPUT turns ratio pri. to sec. 10:1	
Unshielded type A-3035	\$3.09

SUPERIOR POWERSTATS
Smooth, efficient voltage control. 0 to 135V. output from 115V. AC line.

Type 20 (illustrated) 3 amps	\$12.50
116 for table mtg 7.5 amps	23.00
116U for panel mtg 7.5 amps	19.00
1126 15 amps	46.00
1156 45 amps	118.00

Also available for 230 volt input. Write for descriptive literature.

OIL FILLED CONDENSERS

1.78 Mfd @ 200VAC	29c
4 Mfd @ 500VDC	39c
1 Mfd @ 600VDC	29c
2 Mfd @ 600VDC	39c
7.5 Mfd @ 330VAC	98c
10 Mfd @ 330VAC	98c
2 Mfd @ 1000VDC	59c
.05 Mfd @ 2500VDC	95c
1 Mfd @ 5000VDC	\$2.95
2x.1 Mfd @ 7000VDC	\$2.00

GREENLEE PUNCHES
Cuts to 1/2" thick metal.
1" \$1.94
1 1/2" \$1.94
1 3/4" \$2.12
2" \$2.25
2 1/2" \$2.25
3" \$2.88
We carry a complete line of all sizes of punches up to 3 1/2" diameter.

FILAMENT TRANSFORMERS

Type 940 2.5VCT @ 10 Amps. 7500V Ins	\$2.79
Type 940 5 VCT @ 3 Amps. 2500V Ins	\$2.06
Type 941 5 VCT @ 6 Amps. 2500V Ins	\$3.38
Type 941 5 VCT @ 20 Amps. 2500V Ins	\$5.29
Type 943 5 VCT @ 3 Amps. 2500V Ins	\$1.91
Type 946 6.3VCT @ 6 Amps. 2500V Ins	\$2.79
Type 947 6.3VCT @ 10 Amps. 2500V Ins	\$3.67
Type 948 6.3VCT @ 4 Amps. 2500V Ins	\$2.35
Type 960 7.5VCT @ 8 Amps. 2500V Ins	\$4.12
Type 960 7.5VCT @ 10 Amps. 3000V Ins	\$4.99
Type 143 10 VCT @ 10 Amps. 3000V Ins	\$3.38
Type 961 Dual 6.3VCT @ 3 Amps. 2500V Ins	\$3.38
Type 941 5VCT @ 3 Amps. 2500V Ins	
Type 941 6.3VCT @ 3.6 Amps.	

GRID DIP METER
LYSCO
"DIPMASTER"
3Mc to 150Mc freq. range; calibrated dial, band switching (no coils to plug-in). Complete power supply and tubes. A really good buy.

\$33.50

TRANSFORMER SPECIAL
870 volt CT @ 250Ma with 80V bias tap
5 volts CT @ 3 amps
2 1/2 volts CT @ 10 amps
2 1/2 volts CT @ 3 amps
6.3 volts @ 1.5 amps
115V. 60 cycle primary

\$5.88

STEEL CHASSIS

Black Crackle	
5x10x3 18 Ga.	\$.97
11x17x3 16 Ga.	1.94
13x17x3 16 Ga.	2.35
19x17x4 16 Ga.	2.70

ALUMINUM CHASSIS
Heavy Duty

7 x 7 x 2	94c
7 x 9 x 2	\$1.06
5 x 10 x 3	\$1.00
7 x 11 x 2	\$1.15
7 x 13 x 2	\$1.23
10 x 17 x 3	\$1.88

CHOKES					
SMOOTHING		SWINGING		PRICE EACH	
TYPE	Hy	TYPE	Hy	MA	Price
C-80	10	C-87	4-16	150	\$3.09
C-81	10	C-88	4-16	200	\$3.82
C-82	10	C-89	4-16	250	\$5.29
C-83	8	C-90	3-14	300	\$5.39

All above 3000 Volts Insulation

RAYTHEON VOLTAGE STABILIZERS
Positive Stabilization $\pm 1/2\%$
Input 95-130 volts, 60 cycles single phase; output 115 volts stabilized to $\pm 1/2\%$. *Output 6.0 or 7.5 volts stabilized to $\pm 1/2\%$.

Catalog No.	Output	Cap. wgt.	Net Price
	Volts	lbs.	
VR-6110	15	4	\$15.00
VR-6101*	30	5	\$17.00
VR-6111	60	8	\$17.00
VR-6112	120	14	\$24.00
VR-6114	250	25	\$48.00
VR-6115	500	45	\$75.00
VR-6116	1000	92	\$125.00

OIL FILLED BATHTUBS
Special
19c Each \$10.00 per 100.
All 600VDC in following sizes: .05 Mfd., .1 Mfd., 2x.1 Mfd., 3x.1 Mfd., .01x.3 Mfd.

ISOLATION TRANSFORMERS
All 117 Volts to 117 Volts 60 Cy.
P-96, 40 watts \$3.60 P-98, 100 watts \$9.30
P-97, 80 watts \$5.10 P-99, 250 watts \$17.70

If not rated 25% with order, balance C.O.D. All prices F.O.B. our warehouse New York. No order under \$2.00. We ship to any part of the globe.

LEEDS RADIO CO.
75 Vesey Street Dept. RN 6
CORTlandt 7-2612 New York City 7



June, 1949

LEARN TELEVISION ELECTRONICS RADIO
Modern Completely Equipped Laboratories
DAY AND EVENING CLASSES
G.I. Approved—Veterans Receive Subsistence
ENROLL NOW!
ELECTRONICS INSTITUTE, INC.
21 Henry, Detroit 1, Mich.

AUTOMATIC M-80 AUTO RADIO

• Six Tube Superheterodyne • Three Gang Condenser • Powerful, Long-Distance Reception • Fits All Cars, Easy Installation
• Mounting Brackets Included
• 6 Tube model M80 \$29.97
• 5 Tube model X80 \$24.36

MAIL US YOUR ORDERS
All orders filled within 24 hours. Illustrated parts list on request. Sylvania and Cunningham tubes 50% off list.

Bill Sutton's Wholesale Electronics
Fifth at Commerce Fort Worth, Texas


LOOK at these BIG VALUES!

GENERAL ELECTRIC CAPACITANCE-RESISTANCE BRIDGE

Model YCW-1 \$29.95

Regular \$59.50 value. Accurate Wein-type bridge circuit. Measures .000005 to 200 mfd, 5 ohms to 20 megohms, and insulation resistance to 2500 megohms. A versatile test instrument that belongs on every service bench. Measures only 9 1/2"x12"x7". Operates from 110 volts AC. Brand new and at a scoop price! **\$29.95**

True Fidelity AM-FM Phono Amp

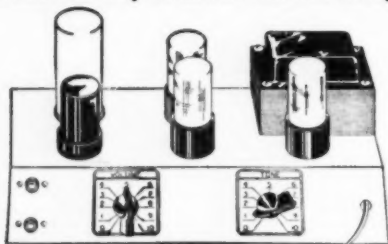

You'll enjoy every minute of listening pleasure with this high-quality low-cost amplifier. Plenty of big-set features at a price you can afford. Big room volume with hum-free output rated at 10 watts undistorted to any 6-8 ohm speaker. Input is dual purpose 68CT phase-inverter shock-mounted to reduce possible microphonics; push-pull 6V6 output; 5Y3GT rectifier. Input jacks for both high and medium impedances. Complete, compact unit measures only 9 1/2"x5 1/2"x5 1/2"; metal chassis finished in attractive brown wrinkle enamel. Wide-range tone and volume controls on front panel. Complete with tubes and line cord, ready for immediate operation on 115-volt, 60-cycle line. Greatest value ever offered at this low price. **\$17.95** complete

SEEBURG Model L Record Changer

Finest 2-post record changer on market. Will play 12" and 10" or 10" and 12" records. Base size 14" square. Automatic shut-off after last record. Best Astatic Cartridge and Permanent Needle. **\$17.95**

SPEAKER VALUES!
8" Magnavox, 21 oz., Alnico 3 magnet..... **\$3.95**
12" Magnavox, 21 oz., Alnico 3 magnet..... **\$5.95**
for use with above amplifier

Save \$26.30 on this SEEBURG RECORD CHANGER



Model DS-101 handles 10-inch or 12-inch records. Smooth, quiet action. Lightweight pickup arm with Astatic Q-type cartridge and permanent needle—the right combination for high-fidelity reproduction. Handsome formed walnut-finish wood base 12 1/2"x14 1/2". Complete with shielded cable and plug for connection to radio or amplifier, and line cord and plug for 110-V 60-cycle operation. Regular \$44.25 **\$17.95**

SAVE MONEY ON PARTS KITS!

- | | |
|--|---------------|
| (1) 100 asstd. mica condensers; pigtail and lug types. .000005 to .01 mfd.... | \$1.95 |
| (2) 40 asstd. push-on knobs for knurled shafts. Red, green, walnut, ivory.... | \$1.29 |
| (3) 25 asstd. 5, 10 and 20 watt vitreous enameled resistors. Values up to 25,000 ohms. No two alike..... | \$1.69 |
| (4) 100 asstd. 1/2-1-2 watt carbon resistors. All RMA color-coded. Most popular values..... | \$1.49 |

ORDER BY KIT NUMBER!

ORDER FROM THIS AD!

Select what you need from the big values listed here—and send your order now! Quantities are limited. Send 25% deposit with order. We ship C.O.D. for balance, all advertised items F.O.B. Chicago. When remitting in full, include sufficient postage—overages refunded. GET YOUR NAME ON OUR MAILING LIST. We carry complete stock PA equipment—BOGAN, MASCO Amplifiers—Shure, Turner Mike—University Speakers, etc./ Write for complete list.

NATION WIDE RADIO
(The Serviceman's Supply House)
572 W. Randolph Street
CHICAGO 6, ILLINOIS

LETTERS

from our readers

CONTESTANTS, HERE'S FOOD FOR THOUGHT

THE prizes to be awarded in the New Ham Contest are certainly generous and well worth working for. I would like to pass along a suggestion that may be of real value to those contestants who will take advantage of it.

"In nearly every city there is a large group of men in all age brackets who are excellent prospects. These men have all of the desirable qualifications for prospective hams. They have lots of spare time but little opportunity for human contact, a deficiency they are burning to remedy.

"I refer, of course, to chronic invalids. There are more of these than you might think, confined to home or hospital. Perhaps the most important thing that can be said about these people is that they are full of human nature. They think and react just as do physically fit persons and have the same range of tastes.

"This means that the men and boys among them are apt to be hobby-minded and technically inclined, just as most men are. It also means that in most cases they are easy to meet, to know, and to get along with. You have only to approach them as human beings and treat them as equals.

"Veterans' hospitals are the first place to look. Here you will find prospects in wholesale lots, with opportunities for group instruction as well as trained workers, the occupational therapists, who are eager to help you in your task. Civilian hospitals tend to have few permanent patients, but among them are those in iron lungs, an appalling number of whom will be there the rest of their lives. Looking at the ceiling gets kind of dull after a while, and it shouldn't be hard to get an iron lung occupant interested in radio. This assumes that he has good control of one hand or foot, which is actually all that is necessary to make a radio contact. By the way, c.w. is the most practical for these individuals. Phone would be awkward.

"Besides hospitals, there are other institutions, such as schools for the blind, where you can find likely prospects. Various social and civic agencies will put you in touch with persons confined to their homes. One of the beauties of this scheme is that support and cooperation will be available wherever you turn. Even the FCC will stretch a point here and there. Many local newspapers would be delighted to team up with radio clubs in organized drives to license invalids.

"It can be said, in all sincerity, that individuals and club members who follow the above suggestions will have

hit upon an excellent means for picking up extra contest-points. But they will have accomplished vastly more than that. Even if they fail to win RADIO & TELEVISION NEWS prizes, they will wind up the contest in firm possession of rewards of a different sort."

Warner Clements, ex 9FQX
Sherman Oaks, Calif.

Anyone who follows through on your very generous and intelligent idea, Warner, will indeed come out in possession of a mighty fine reward.

AN APPEAL

AS MEMBERS of the great amateur fraternity of radio operators in the United States, we are privileged to enjoy the opportunity of chatting with our fellow hobbyists via radio communications. The art as we hams practice it has enough scope to enable most of us to have a reasonably good time of it, whether our tastes run to c.w. or phone, or mostly experimentation and/or the frequent combination of these three.

"Due to the generous allocation of frequencies by the FCC, we have a wide choice of operating conditions in which to enjoy our hobby. Also, since we have the kilowatt as our power limit, most of us are able to strike a happy medium between our desires and our pocketbooks, assuming that for the majority the kw. is sufficient. Now, assuming that the above statements are sufficiently true to satisfy most of us, it would seem to be an obvious fact that American amateurs have more privileges and are better able to enjoy same than, perhaps, the amateurs of any other country. This is due principally to our economic status, which is still pretty good in spite of what some of the pessimistic observers would have us believe. Another contributing factor, of course, is the fact that there are many radio manufacturers who are amateur-minded and who cater to our desires with excellently fabricated components.

"With all of the foregoing concepts of our position clearly in mind, the writer has a proposition to make, a somewhat sporting proposition, since it is an appeal to the better sides of our natures, the side that favors the underdog. It will not necessarily benefit the individual operator, except perhaps indirectly. How about giving the small-time operator a break, the fellow who might not have much dough to sink into radio gear, the fellow who is just starting in as an amateur, as well as the fellow who likes a phone QSO but can't compete financially and technically with the 'half-gallon to a

RADIO & TELEVISION NEWS

kilowatt' boys on our low-frequency bands.

"We have just been allocated some frequencies in the 160 meter band. Not much. Just some bands that are 25 kilocycles wide. These we are to use on trial, so to speak, although they will probably be ours if we behave ourselves. Now my proposition is this: how about setting a voluntary limit of power input to the final of between 25 to 50 watts? From our viewpoint there would seem to be several reasons why this would be feasible and practicable to enable most hams to get the most out of the band. The frequency limitations are very small, and if just a very few high-power stations are on the air in a given area, it will effectively exclude all others. It is primarily a short-haul band, and even if power input is the maximum, there can be no real DX.

"If the average station will limit himself voluntarily to the above mentioned power maximum, it would appear that most stations would be able to work the guy across town and maybe outside somewhat. A good part of the possible QRM troubles will be eliminated as well as the BCI trouble. This band with power limitations could well be a good source of inspiration to the beginning amateur, and since there has been a real effort on the part of radio publications to build up the population of hams by their programs for newcomers, it would seem that this would provide a partial solution for the problem of where all the new hams will go.

"Before we sign off on this subject, we would like to give a specific instance of how power works on this band. From our location in Eastern Massachusetts, we have heard a station in New York near Albany coming through S 7 to 8 at 7:30 PM working a W3 in Pennsylvania. The W2 had 160 watts to an 813 in the final and was readable 100 per-cent of the time. He was occupying at least one-third of the 25 kc. sector (low frequency) and succeeded in taking two local stations within a 25-mile radius completely out of the picture. The local stations were coming in at the time, S4 and S5. They were both using very low power, needless to say. We could have worked the locals with 25 watts but not if the W2 was going to be on at the same time.

"So how about it fellows? How about giving the little fellow a break on this band. Since you can't work DX anyway—as more power just invites BCI troubles—since there are a lot of low-power boys who could get a lot of fun out of this band by your keeping the power down—why not 'live and let live' so that we all get some pleasure out of these new frequency allocations."

R. L. Parmenter, W1JXF
Roosevelt Ave., RFD 3
Middleboro, Mass.

If any of you luckier boys have been operating your powerful rigs at full

On the Warpath against capacitor troubles...

The SANGAMO
Pathfinder



TYPE 30
Molded Tubular

This molded capacitor is used extensively by television manufacturers. They find it easier to tie into their production lines because the especially designed, flexible leads are trouble-free... they resist breakage and they can't pull out! There is no wax to run when heat is applied. The thermo-setting plastic case is molded with less heat...less pressure...the element is not distorted in fabrication. This means greater dependability—no "hot spots." Try this stable, rugged, long-lived paper-tubular—you'll like it!

The SANGAMO
Chieftain



TYPE MT
Dry Electrolytic

The Chieftain is tiny, but durable! Meticulous care in manufacture protects against source contamination and assures corrosion-free elements. These capacitors have heavy insulating sleeves that are wax impregnated—not dipped. Positive electrodes are formed of rugged, etched-foil aluminum plate which insures longer life, greater dependability.

Small in size, with bare copper leads, the Chieftain is easy to mount—ideal for replacements—anywhere! Bulletin 825 gives complete information.

See your Jobber—if he can't supply you, write us direct.

Your Assurance of



Dependable Performance

SC494

SANGAMO ELECTRIC COMPANY

SPRINGFIELD, ILLINOIS

IN CANADA: SANGAMO COMPANY LIMITED, LEASIDE, ONTARIO

50th ANNIVERSARY
1899 - 1949

BARGAINS

KEY—Code Practice TAC J-38. New.....	.49
TRANSFORMER—Kenyon Trans. Co., Primary 110 v. 60 cy. Sec. 5v. @ 60 amp. C.T....	4.49
CATHODE RAY TUBE—5CP2.....	1.35
RADAR JAMMING TRANSMITTER—AN/APT2. Range 500-700 meg. 10 tubes. New.....	9.49
DYNAMOTORS—101-C. Input 13/26v. 12.6/6.3 amp. DC output 400v. @ 135 amp.; 800v. .020 amp. AC output 9v. 1.12 amp.	2.95
METERS—Western or Westinghouse 0-150v. AC. 2 inch panel mount.....	2.95
TUNING UNIT—(1st R.F.) 2F4C/2J1 T.3.....	.89
CONDENSER—3 gang Navy RBA L481, silver plated. No. 1, 251 mmf.; 2, 253; 3, 253; 4, 250 and 5, 252 mmf.....	3.49
TRANSMITTER—BC-947A (Mickey Mouse) 500 lbs.....	45.00
TRANSMITTER—BC-1072A w/tubes 110v. power supply, meter, variac, 110v. blower; 150-200 mc. Shpg. wt. 200 lbs.....	25.00

All C.O.D. orders to be accompanied by 25% deposit. Orders without postage will be shipped express collect. F.O.B. Berwyn, Md.

R. & T. ELECTRONICS COMPANY, INC.
9723 Baltimore Blvd.
Berwyn, Maryland Phone TOwer 5384

Make Your Career RADIO and TV

In no other industry does the future hold brighter financial promise and security than in AM and FM Radio, Television. These fields need and want men trained as announcers, script writers, disc jockeys, and radio technicians. It will pay you to investigate the Don Martin School of Radio Arts, established in 1937. Complete day and night classes... the latest equipment... and a staff of 30 nationally known instructors. Over 97% of the combination men graduates are placed on jobs immediately through the free placement service. Approved for veterans.

FREE—Write for Free Booklet "Your Future in Radio."

DON MARTIN SCHOOL OF RADIO ARTS
1655 No. Cherokee, Hollywood, Calif., HUDSON 23281

A
Stands for
Adjustable
and Always
Accurate



LECTROHM ADJUSTABLE RESISTORS

- Potentiometers & Voltage Dividers
- Temporary or Permanent Requirements in Different Line Voltages

LECTROHM ADJUSTABLE RESISTORS include a complete range of carefully rated styles from 1 to 100,000 ohms, 10 to 200 watts. You know they're right because they feature accurately spaced winding of low temperature coefficient resistance wire, low loss ceramic cores, silver soldered connections and rugged vitreous enamel coatings. Adjusting lug supplied with each resistor. Standard sizes and ratings available at your dealer NOW. Ask for LECTROHM!



5907 Archer Ave. Chicago 38, Illinois
Division of National Lock Washer Co., Newark, N. J.

TECHNICAL KO's

SPECIAL: 10% discount on orders of \$5 or more.

OIL FILLED CONDENSERS		TRANSMITTING MICAS	
.05 MFD 1000 V	\$0.35	.00005 2500 V	\$0.15
.1 2500 V	.75	.00005 3000 V	.35
.1 7500 V	1.65	.00005 5000 V	.85
2x.1 7000 V	4.10	.000067 2500 V	.20
.12 15000 V	7.95	.00025 2500 V	.25
.25 1000 V	.35	.00025 5000 V	.85
.25 4000 V	2.15	.0005 2500 V	.25
.25 6000 V	3.75	.00072 5000 V	.85
10x.25 600 V	1.05	.0008 5000 V	.85
.5 600 V	.28	.0001 2500 V	.25
.5 1000 V	.40	.002 1000 V	.20
.5 2000 V	.75	.002 3000 V	.65
.75 2000 V	.60	.003 2500 V	.30
.77 350 VAC	.30	.003 3000 V	.65
1.0 1000 V	.45	.004 2500 V	.35
2.0 200 V	.20	.005 1000 T.V.	.15
2.0 600 V	.40	.005 3000 V	.65
2.0 1000 V	.60	.006 2000 V	.35
4.0 600 V	.60	.008 1200 V	.15
4.0 1000 V	1.00	.01 1000 T.V.	.15
5.0 250 VAC	.35		
6.0 1000 V	1.45		
8.0 600 V	.85		
8.0 1000 V	1.75		
10.0 600 V	1.00		
30.0 50 VAC	1.40		
30.0 330 VAC	3.75		

25.0 Electrolytic 25 V	.40
100.0 Electrolytic 25 V	.50

RESISTOR KIT ASSORTED 1/2 & 1 W 100 for	\$1.49
BATHTUB KIT 3x1, .5, .05, etc.	.10 for .58
CONDENSER KIT .01—.00001	.100 for 2.99
MICAS .01, .002, .005, etc. ALL VALUES	.08
.01 150V PAPER (MIDGET)	.60 for 1.00
0.1 600V PAPER	.8 for 1.00

TELEVISION

BOOSTER—Your Troubles Are Over With Our High Gain Unit—Channels 1-13
Beautiful Mahogany Cabinet.....\$24.95
300 Ohm twin lead-100 Ft.....1.75
72 Ohm co-axial cable-100 Ft.....5.50
Standoff Ins. 3"-300 Ohm or co-ax......06
Expansion Bolts 1/4"x3"......09
Carboloy Drill 3/8"-5/16".....1.65
1/4" Friction Tape 1/2 lb. Roll......35

\$2.00 min. order F.O.B., N.Y.C. Add postage
50% deposit, balance C.O.D. with all orders.
Manufacturers' inquiries invited. Send for Flyer.
Prices are subject to change without notice.

TECHNICAL RADIO PARTS CO.


Moved to Larger Quarters
557 McDonald Ave. Brooklyn 18, N. Y.
Dept. RN13

\$139 PHONO AMPLIFIER

2 Tube AC-DC
3 at \$1.25 2 tubes—50L6—35Z5 \$1
PHONO OSC—2 TUBE \$2.75
Uses 35Z5, 12SA7, 2 tubes \$1.20
PHONO AMPLIFIER
3 Tube AC-DC
\$169



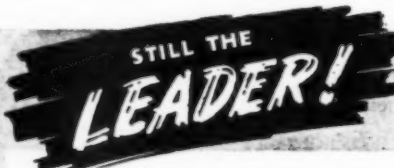3 at \$1.49
Volume and Tone Controls.
Uses 12SQ7, 35Z5, 50L6.
Set of 3 Tubes.....\$1.35
Output Trans......32
5" Alnico Speaker.....1.10
6" PM Speaker.....1.45
Alliance Phono Motors.....2.50
Pickup \$1.79—High Output Pickup.....1.99
All Above Wired & Tested
\$1 Deposit on all orders. Free Catalog RN
RADIO MAIL ORDERS
2 West Broadway, New York 7, N. Y.



The famous ACA-100 Amplifier — a self-balancing, drift-correcting, direct-coupled amplifier — the most satisfying musical amplifier ever designed. Based on early Loftin-White circuits, perfected by A. C. Shaney in 1936, and now brought to a standard of quality far above that of any corresponding amplifier. Exclusive features include:

- Push-Pull Triode Expander.
- Non frequency-discriminating noise suppressor.
- Push-pull hi and lo freq. variable equalizers.

If you are satisfied with nothing less than the best, write today for free technical literature.

Special models for all magnetic cartridges.



AMPLIFIER CORP. OF AMERICA

398-2 Broadway New York 13, N. Y.

blast, maybe you could take this little hint and just once in a while impose the power limit on your XMTRing.

UNDEMOCRATIC HAMS?

THE greatest single threat to amateur radio lies in the success or failure of the attempt to induce the FCC to raise the code speed requirements for amateur operators' licenses.

"Raise the code speed requirements or restrict the newcomer to code for one year, and amateur radio will be so exclusive that its extinction will become inevitable. Reduce the code speed requirements to 10 w.p.m., and amateur radio's position will be strengthened.

"The examination for an amateur radio operator's license should be designed to test the applicant's ability to operate amateur radio transmitting equipment. Requirements designed solely as a barricade have no place in the examinations and are unfair and undemocratic.

"It would seem that amateur radio is being misrepresented by some who claim to be its spokesmen. Speak up amateurs, what do you want? We who are striving to qualify for a license ask only the same chance you were given. Don't change the rules to exclude us, please."

C. D. Flynn
3118 N. Francisco Ave.
Chicago 18, Ill.

We hope the proponents of higher exam. requirements do not intend to be unfair, but it could look like that, so let's hear from the other side, too.

THAT POPULAR 10 w.p.m. AGAIN

IN REPLY to Marvin Gurlin's letter in the April issue, I think that he said a mouthful.

"I'm very much in favor of making the amateur exam. simpler instead of stiffer as some groups would have it. If the truth were known, it would be found that there was a higher percentage of c.w. operators under the 10 w.p.m. speed than there is now.

"Many of the 'old timers,' worried about the number of new hams crowding into our bands, would like to eliminate competition by making the exam. tougher. I have found that a newcomer must put out a fairly good signal or he just doesn't make contacts, and it doesn't take long to discourage the few poor risks this way.

"Don't put up barriers that scare new, and especially young, operators away from at least a fair start in this wonderful hobby.

"Yours for better hamming,"

Bob Fisher, W6EUF
Seal Beach, California

Maybe those young hams do need more encouragement. We'll do all we can, but there must be more fellowship in our ranks than these youngsters seem to think. Why don't some of you "old timers" show them and lend a helping hand?


What's New In Radio

(Continued from page 78)

iron, and thereby effect considerable labor savings; economy results from the use of less solder, and from its instant operation, with no waiting to warm up. It is effective from 14 to 30 gauge copper wire and can be used to silver braze small metal parts.

R-4A COAXIAL SWITCH

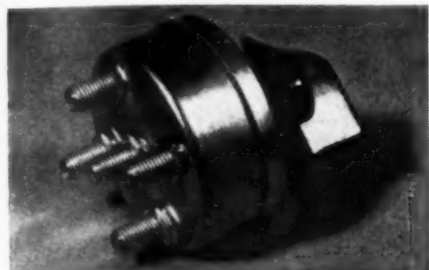A single-position, four-throw switch for use with coaxial cable has been produced by *The Workshop Associates*,



66 Needham St., Newton Highlands, Mass.

This switch was designed especially for use with television transmission lines but can also be used effectively in any r.f. application up to 350 mc. and in low-level audio systems.


The Model R-4A can be used with RG-11/U and RG-8/U as well as with RG-59/U coaxial cable, by using *Workshop* coaxial fittings and adaptors.

INTERPOLATING FREQUENCY STANDARD

Designed particularly for use with the Type 720-A Heterodyne Frequency Meter, the *General Radio Company's* Interpolating Frequency Standard will make accurate measurements at ultra-high-frequencies up to about 3000 megacycles.

The instrument provides a series of harmonics of a nominal one-megacycle signal whose fundamental is adjustable over a range of one per-cent. At the 100th harmonic and above, complete coverage from one harmonic to the next is obtained.

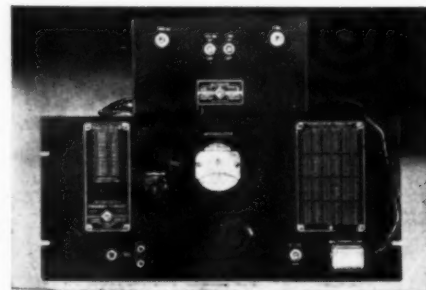General Radio Company, 275 Massachusetts Avenue, Cambridge 39, Massachusetts,



announces that an additional series of harmonics, based on a .1 megacycle fundamental, is also generated by the device for use with its Type 620-A Heterodyne Frequency Meter, on measurements in the range between 10 and 300 megacycles.

June, 1949

SENSATIONAL SUMMER SALE!

Here it is—just what you've been waiting for. Low, low prices on top quality merchandise! But you must act fast. Hurry, take advantage of this terrific saving now! Mail your order today.

SENCO DECLARES A DIVIDEND

When ordering 25 or more assorted tubes, deduct 5c from the price of each tube. (Does not apply to 12 tube sale.)

TUBES! ALL BRAND NEW! RCA GUARANTEE! IMMEDIATE DELIVERY! INDIVIDUALLY CARTONED!

19c EACH	39c EACH	45c EACH	50c EACH
(Cont'd)	(Cont'd)	(Cont'd)	(Cont'd)
6CSMG	12SA7GT	7F8	6K8
39/44	12S5	7A7	6L5
57A5	12SM7GT	7J7	6N6
1644	12SK7GT	7K7	6Q7G
V99	12SL7GT	7N7	6V7
X99	12SN7GT	12AT8	6T7G
	12SQ7GT	12AU7	7A7
	12S7	12A6	7B7
	14B8	12BE6	7B8
	14C7	12B7	7C5
	14F8	12BT7GT	7D7
	15	12C3	7Q7
6C8G	15	12C3	7Q7
6F7/VT70	19Y8	14B7	12BD8
6SN7GT	25Z6GT	25A6G	12C8
6SR7GT	25Z6GT	25B6G	14B8
6U7G	27	25B6G	19
7U7	30	25C6GT	19
12A6	31	25Y5	23
12A8GT	32	25D7	20S0
6AF5GT	35/51	32L7GT	20S1
12N6	35L6GT	33	30c EACH
12K8	35W4	34	02A
26	35Z4GT	34	1L4A
38	35Z3	43	1L4B
71A	35Z5	43Z5GT	1L4C
71	35Z6	49	1L4D
30c EACH	37	50L6GT	1L4E
1A3	38	50L6GT	1L4F
1A4	47	50L6GT	1L4G
1V	50B5	53	1L4H
2A6	50B5	53	1L4I
3A4	57	50c EACH	1L4J
5A2A	58	1A5GT	1L4K
5U4G	76	1A6	1L4L
5W4	78	1A7GT	6A85/6N5
5K4G	80	1A8	6AK5
5V3G	84/6Z4	1C5	6AL7
5V4GT	85	1C5G	6AQ7
5V4G	89	1C6	6AV8
6AD7G	45c EACH	1C7G	6B6G
6AF5	18S/25S	1D6	6B8
6A8H	11A	1D7G	6B8H
6A7B	1P5GT	1E5G	6D4
6A8B	1P5GT	1E7G	6D8 (with shield)
6A8GT	1R5	1F4	6E8
6A8B	155	1F7G	6G8
6C8	175GT	1G4	6H4/6G5
6C8GT	2A5	1G6G	6W4
6C8	2B6	1H4G	6W6
6H6GT	2A7	1H5GT	6V3
6J5GT	3Q4	1H6G	12A
6J7GT	3Q5GT	1J6G	12A7
6K6GT	6J7GT	1N5GT	12A7
6K7G	6B6	2A3	14A7
6K7GT	6D7	2A4	14Q7
6N4	6F5GT	2A4G	12B7
6SA7GT	6G6G	3A5	22
6SB7	6K8G	3D6	45Z3
6SD7GT	6P5GT	3L4	182B
6SF5GT	6R7GT	3V4	482B
6SG7GT	6SN7GT	5A3	483
6SJ7GT	6ST7GT	5Z4	60c EACH
6SK7GT	6V5	6A3	6AC7
6SG7GT	6V6G	6A4	1852
6Y8	6Z5	6A8	6L7G
6U6GT	7A4/KXL	6A87	117L7GT
6V6GT	7A5	6AC5GT	117N7GT
6X5GT	7A6	6A85	117N7GT
12AH7GT	7A8	6A85	117N7GT
12A7GT	7A7	6A87	117N7GT
12S7	7B6	6B8	117Z6GT
12J7GT	7C6	6C7	14A7
12Q7GT	7E5/1201	6F8G	80c EACH
12Q7GT	7E7	6F8G	6L6G

FAMOUS VOLUME CONTROLS
25,000 ohms V.C., 3" shaft; 50,000 ohms V.C., 3" shaft; 100,000 ohms V.C., 3" shaft; 250,000 ohms V.C., 3" shaft; 500,000 ohms V.C., 3" shaft; Tapped; 500,000 ohms V.C., 3" shaft; Tapped; 1 meg. ohms V.C., 3" shaft; Tapped.

IF TRANSFORMERS
Medium Size 456 KC-Input & Output.....32c
Medium Size 456 KC with AVC Tap.....39c

MINIMUM ORDER \$2.50

WHEN ORDERING—Send 25% deposit for all C.O.D. shipments. Include sufficient postage—excess will be refunded. Orders without postage will be shipped express collect. All prices F.O.B. New York City.

LOOK WHAT YOU GET FOR 1c AT SENCO!

TYPE	1 FOR	2 FOR	TYPE	1 FOR	2 FOR
955	\$.19	\$.20	EF 50	\$.39	\$.40
7193/2022	.19	.20	E1148	.39	.40
2C34/RK34	.19	.20	V55	.39	.40
VT32/45	.19	.20	SPECIAL	.39	.40
SPECIAL	.19	.20	8011	.49	.50
1626	.19	.20	VT90	.49	.50
1644	.19	.20	RKR 72	.49	.50
39/44	.19	.20	RKR 73	.49	.50
956	.39	.40	RK 72	.49	.50
957	.39	.40	HY 615	.49	.50
1629 MAGIC EYE	.39	.40	350B	.79	.80
			307A	1.49	1.50
			807	1.49	1.50

SPEAKER SAVING!

Here are the speakers you've been looking for! Quality so high, yet prices so very low. Why hesitate—take advantage of this *SENCO* saving now!

3" P.M.—.68 oz. Alnico V	\$.99
3" P.M.—1.47 oz. Alnico V	1.15
4" P.M.—1.47 oz. Alnico V	1.15
4" P.M.—Alnico V	1.69
5" P.M.—1 oz. Alnico V	.99
5" P.M.—1.47 oz. Alnico V	1.15
8" P.M.—2.15 oz. Alnico V	2.75
8" P.M.—4.84 oz. Alnico V Magnet	2.95
8" P.M.—.68 oz. Alnico V	3.75
10" P.M.—.68 oz. Alnico V	3.95
12" P.M.—.68 oz. Alnico V	4.95

Brand New WILLARD 27 Amp—Mod. 227-2

2 VOLT STORAGE BATTERY AND 2 VOLT VIBRATOR
Used in General Electric Model 2530 charge A.P.A.C. portables. Suitable for all farm radio sets. Individually boxed.

BOTH FOR	\$2.69	6 VOLT AUTO VIBRATORS
Battery alone	\$1.79	
Vibrator alone	\$.99	4 Prong.....99c each

POWER TRANSFORMERS

90 mil.—6.3V @ 3.3 amps—5V @ 3 amps	
100 mil.—6.3V @ 3.3 amps—5V @ 2 amps	\$2.65
120 mil.—6.3V @ 3.3 amps—5V @ 2 amps	2.78
150 mil.—6.3V @ 4.3 amps—5V @ 3 amps	3.95
200 mil.—6.3V @ 3.3 amps—5V @ 3 amps	3.19
15V C.T.	4.25

RCA INTERCOM for Home, Office, Store!

3-tube AC-DC amplifier circuit. Designed to operate with 2 remote stations connected in parallel. Remote stations not supplied. Two 500 ohm 1/2 watt and two single-pole double-throw switches are all that is required to make a remote unit for 2-way communication. Other Applications: Electronic Baby-Sitter, Phone-Amplifier, Code Practice Oscillator.

SPECIAL \$7.95 Complete with tubes and 100 ft. of cable.

CARTRIDGES

PNBB Shure Crystal Cartridge	\$1.69
Asatic Nylon Cartridge	2.79

AUTOMATIC RECORD CHANGER

110V, 60 cycle. Changes 12 10-inch and 10 12-inch records automatically. Has crystal cartridge arm. Complete.

\$11.95

OIL FILLED CONDENSERS

Standard Brand—Upright	
10 Mfd. 600 VDC	\$.69
10 Mfd. 600 VDC	.89
2 Mfd. 10000 VDC	1.90

MAGNAVOX SPEAKERS

12" P.M.—21 oz. magnet with 6V6 P.P. output, cord and plug	\$5.95
12" 1000 ohms field with 6V6 P.P. output, cord and plug	5.95
12" 680 ohms field with 6V6 P.P. output, cord and plug	5.95
8" 680 ohms field with 6V6 P.P. output, cord and plug	3.69

OUTPUT TRANSFORMERS—Sturdily Built

305	ea. 39c
50L5 PUSH-PULL	ea. 39c
6V6 PUSH-PULL	ea. 49c

SIGNAL CORPS DUAL HEADSETS

6 foot cord and tips. 2000 ohms. Individually Boxed—Brand New.

NOW ONLY.....ea. \$1.49

SEND FOR OUR FREE CIRCULAR!

SENCO RADIO INC.
DEPT J, 71 WEST BROADWAY, NEW YORK 7, N. Y.
TELEPHONE BEekman 3-6498

RADIO ENGINEERING!

COMPLETE Radio Engineering Course. Bachelor of Science Degree. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering, Business Administration, Accounting, Secretarial, Science. Graduates successful. 66th year. Enter June, Sept., Jan., March. Write for catalog.

TRI-STATE COLLEGE 1668 College Ave. Angola, Indiana

TINY RADIO!

Red plastic case. No tubes, batteries or electric plug-ins needed! Guaranteed to receive local stations. Only \$3.99 (ck. Mo. cash) postpaid or send only \$1.00 and pay \$2.99 C.O.D. Complete ready to play on any connection. With Personal phone. Get your tiny radio now!

MIDWAY SALES CO., DEPT. TRN-4, KEARNEY, NEBR.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS



TRANSMITTERS—ARC-5 & ATA

Lenny is shedding bitter tears at the ridiculously low price. But Buck says: "Let 'em have it!" So here it is:

4-5.3 Mes. **\$2.99 ea.** 5.3-7 Mes.

Complete with tubes and crystals in good condition. Get 'em while they last!

APN-4 RECEIVER & POWER SUPPLY

4 switch-selected channels. Freq. 1050—2,000 Kcs. With tubes. Used but in excellent condition. **\$9.95**

HS-23 HEADSET

High impedance. Fitted with rubber cushions. Brand new. A bargain hunter's buy! **\$2.49**

BC-456 MODULATOR

For 274-N. With tubes, less dynamotor. Brand new. Too hot to pass up! **\$2.95**

FAMOUS "ARB" RECEIVER

195 to 9,050 Kcs. Controlled by a 4-band selector switch. Features include 6 tubes, 3 micro-volt sensitivity MVC or AVC CW or MCW—sharp or broad tuning for extra sensitivity. 28V dynamotor. Used but in excellent condition. **Special! \$19.95**

APN-1 ALTIMETER 420 MC FM TRANSCEIVER

With tubes and dynamotor. Used but in good condition. **Ea. \$4.95**

TUBES—ALL NEW AND BOXED

211.....	29c
371A.....	99c
371B.....	99c
1616.....	69c
803.....	\$4.95
5CP1.....	1.50
5FP7.....	1.50
12DP7.....	13.95
Special: Brand new tube puller, boxed.....	19c

COLLAPSIBLE MOBILE ANTENNA

7 ft., telescopic, brass anodized. Boxed, brand new. **Ea. \$1.95**

SUPER-SPECIAL ! ! ! ! !

NEVER BEFORE SO MUCH FOR SO LITTLE!

Approx. 16 (sixteen!) lbs. of radio parts. EACH PACKAGE CONTAINS: transmitter, pots, condenser, crystal, knobs, switches, transformer, choke, insulators, PLUS brand new 10 ft. 3-eond. rubber covered cord. Absolutely no junk, no hardware. All good, useful parts. A \$14.50 value. All of them—yes, ALL for only..... **\$3.50**

Send for our **NEW FREE Catalogue!**

These prices are good for Month of **JUNE** only!

All prices F.O.B. Los Angeles. 25% deposit with order. Balance C.O.D.

Come in and see the **LARGEST** supply of surplus in the **BIGGEST** electronics warehouse on the West Coast!


COLUMBIA ELECTRONICS

522-524 South San Pedro Street
LOS ANGELES 13, CALIFORNIA

The adjustable frequency generated by the Interpolating Frequency Standard is determined primarily by a quartz-crystal oscillator. If increased accuracy is desired, the system can be standardized periodically in terms of standard-frequency radio transmissions from the National Bureau of Standards Station WWV.

RADIO FREQUENCY OHMMETER

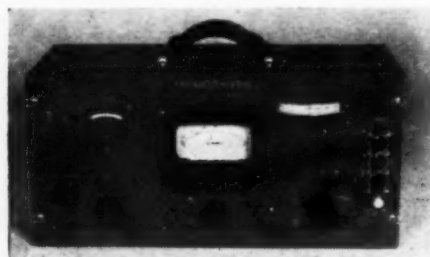The Type YKS-1 ohmmeter developed by the Specialty Division of the General Electric Company at Elec-




tronics Park, Syracuse, New York, is designed primarily to permit rapid and accurate measurement of r.f. resistance in coils, condensers, transmission lines, and antennas.

This direct-reading instrument has a range of from 50 kc. to 80 mc., and by means of a calibrated precision condenser provides a measurement of the series resonant reactance of the component under test. It will even measure the loss factor of fused quartz, and the more complex combinations of radio components.

HI-FIDELITY PHONO AMPLIFIER

Designed expressly for custom installations is the new Rauland 1825 high-fidelity phonograph amplifier having a detachable remote control preamplifier constructed to mount in any position to meet the mechanical requirements of any installation.

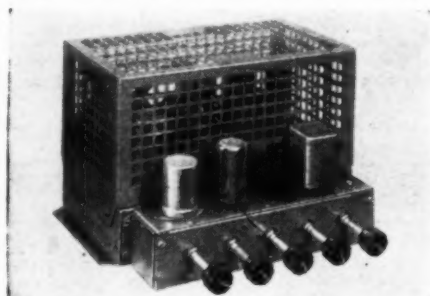Another feature of the Model 1825 is a five-position frequency cut-off for elimination of needle scratch and noise. A single control provides five steps of frequency cut-off and proper setting of the control restores the original clarity to favorite recordings.



In addition to the master volume control, an auxiliary volume control on the power amplifier prevents "cramping" of the main volume control and improves signal-to-noise ratio.

This amplifier, manufactured by Rauland-Borg Corporation, 3523 Addison St., Chicago, Illinois, delivers a power output of 25 watts, with not more than 5 per-cent total harmonic


distortion. Frequency response is plus or minus one db., 40 to 20,000 c.p.s.; output impedances are 4, 8, 16, 250, and 500 ohms.

"STABILINE" VOLTAGE REGULATOR

The Superior Electric Company of Bristol, Connecticut, announces the production of a new, small automatic voltage regulator rated at 2000 v.a. output, listed as the "Stabiline" Type EM 4102.

This regulator is electromechanical in operation and consists of a Superior electric "Powerstat" variable transformer controlled by an electronic detector. According to the manufacturer, it has a higher response speed than heretofore obtainable in automatic voltage regulators of comparable characteristics, and only three seconds are required to correct for the wide-line voltage excursion of 95-135 volts. The new design of the enclosure (the unit is offered as a cabinet contained or rack-mounting unit) is said to make all parts more accessible for maintenance and replacement.

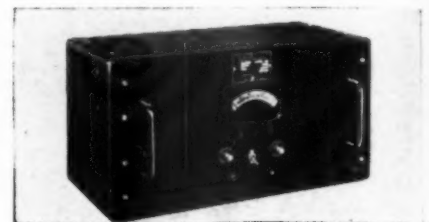The "Stabiline" is housed in a cabinet measuring 20 $\frac{1}{16}$ by 10 $\frac{1}{8}$ by 9 $\frac{1}{8}$ inches; on the front panel is a four-



inch voltmeter, an "on-off" switch, pilot light, and screwdriver adjustments for output voltage and sensitivity.

CATHODE-RAY OSCILLOGRAPH

A new high-sensitivity cathode-ray oscillograph, Series ES-500, has recently been introduced by Precision Apparatus Co., Inc., 92-27 Horace Harding Blvd., Elmhurst, L. I., New York. It is a 5" laboratory type with extended range and voltage regulated amplifiers for multi-purpose AM, FM, and TV applications.

Twenty millivolt vertical amplifier sensitivity permits direct alignment and/or adjustment of low-gain circuits and examination of minute signal levels. Among other features of the Series ES-500 are direct linear internal sweep coverage from 10 cycles to 30 kc., compensated multi-vibrator circuit, three position, "internal, external, line" sync selection, and a built-in phasing control.

The chassis panel is deep-etched anodized aluminum, and the over-all dimensions of the heavy gauge steel cabinet of fine dull black ripple finish are 8 $\frac{1}{4}$ by 14 $\frac{1}{2}$ by 18 inches.

KILOVOLTMETER

Manufactured by the Bradshaw Instruments Co., 348 Livingston St., Brooklyn 17, N. Y., the Model 4000, called the Kilovoltmeter, makes possible the measurement of television

RADIO & TELEVISION NEWS


and x-ray voltages up to 50,000 volts d.c. It has an input impedance of 1250 megohms, and the basic sensitivity is 50,000 ohms/volt.

Personnel handling the instrument are in no danger, as they are protected from high voltage by the shielded Polystyrene Probe, test leads are shielded, and the shields are connected together for greater safety.

NEW EQUALIZER AMPLIFIER

The Equalizer-Amplifier, Model EA-3, latest addition to the Astatic Corporation's units for use in connection with its Magneto-Induction Pickup Cartridge, makes a total of three such accessory items produced by this Conneaut, Ohio, firm.

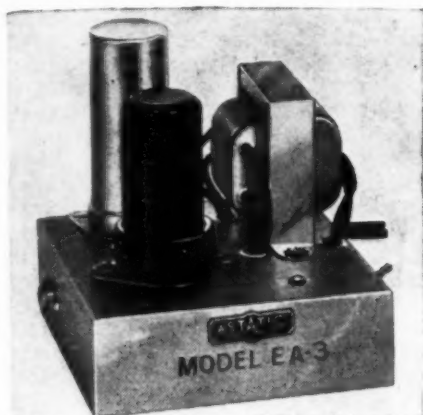With the advent of the new long-playing records, the Magneto-Induction Cartridge was developed by



Astatic to fit the new requirements. The Model EA-3 is a self-powered unit, providing "bass-boost" and equalization to adapt the Cartridge to standard phonograph input circuits.


NEW DISPLAY UNIT

Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey, has introduced a counter and window display unit, featuring an accompanying reference guide for the twelve assorted Quietone Filters being shown.


The reference guide lists the filters on display with their applications and slips into the back of the display unit to be used by the salesman whenever needed. The filters sell from 75 cents to \$2.25 each, and the total retail price of the kit is \$16.10.

GENERATOR KIT

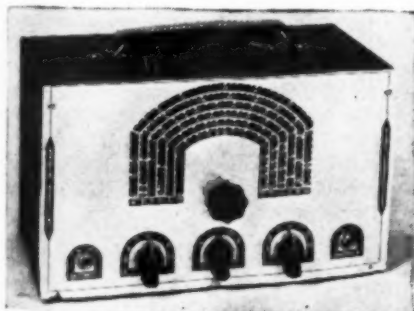Radio Kits, Incorporated, 120 Cedar Street, New York 6, N. Y., has re-



Modern Hams Junk Old-Style "Cans"!

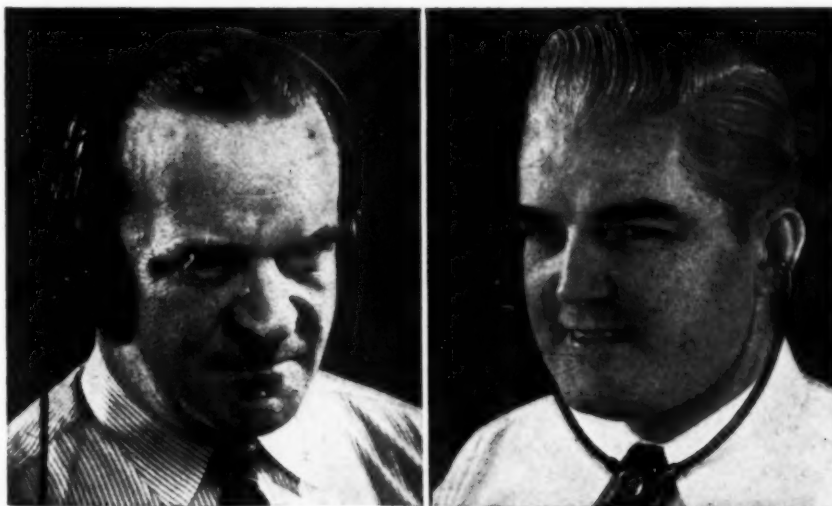

First basic improvement in headset design in 50 years

TELEX MONOSET

- Gives clear, crisp "near as here" reception
- Blocks outside noise
- Eliminates that "top-heavy" feeling
- Ends headachy ear pressure

Man, what relief to get rid of those pressure headaches from old-style earphones!

The TELEX MONOSET swings lightly under the chin like a stethoscope—never gets in your hair! The TELEX MONOSET delivers the signal into the ears, excludes all room noise automatically. The TELEX MONOSET gives undistorted output at maximum volume... plenty of "sock" easily adjusted with the built-in volume control.

Modernize your rig with a MONOSET

—successor to the earphone! Write Department H-6 for information.



Manufacturers of
TELEX Twinset, * TELEX Earset, * TELEX Pillow Speaker,
TELEX Precision Hearing Aids

Trademark*

TELEVISION RECEIVER—\$1.00

Complete instructions for building your own television receiver. 16 pages—11" x 17" of pictures, pictorial diagrams, clarified schematics, 17" x 22" complete schematic diagram and chassis layout. Also booklet of alignment instructions, voltage and resistance tables and trouble-shooting hints. —All for \$1.00.

CERTIFIED TELEVISION LABORATORIES
5507-13th Ave., Brooklyn 19, N. Y.

ELECTRICAL TRAINING

Intensive 32 weeks' residence course in fundamentals of industrial electrical engineering, including radio, electronics. Prepares for technicians, engineering aides. Approved for veteran training. 50th year. Next classes begin September 6, January 9. Catalog.

BLISS ELECTRICAL SCHOOL
7546 Takoma Avenue,
Washington 12, D. C.



GREYLOCK RADIO TUBE BARGAINS!

GT. Glass and Miniature Types

1RS	6AT6	12SA7	} 39¢ each
1S5	6BA6	12SJ7GT	
174	6BE6	12SK7	
1U4	6SA7GT	12SQ7	
3Q4	6SJ7GT	25Z6GT	
354	6SK7GT	25L6GT	

SPECIAL OFFER! All above types may be purchased in lots of 100 assorted, at \$34.50 per 100.

6AK5 } 49¢ ea. 6BQ6G } 89¢ ea.
6AG5 1B3-8018 }
6J6 6J6 2E34 } \$1.00

All tubes in individual cartons
TERMS: Net C.O.D., F.O.B. NYC. MINIMUM
ORDER \$5.00.

Write for Bargain Catalog N-6

Greylock Electronics Supply Co.
30 Church Street New York 7, N. Y.

AC CURRENT
Anywhere!

ATR

STANDARD AND HEAVY DUTY INVERTERS



For Inverting D. C. to A. C.

Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.



AUTO RADIO VIBRATORS

A Complete Line of Vibrators . . .

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

NEW MODELS NEW DESIGNS
NEW LITERATURE
"A" Battery Eliminator, DC-AC Inverters, Auto Radio Vibrators.

See your dealer or write factory

AMERICAN TELEVISION & RADIO CO.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA-U. S. A.

leased its Model SG2 signal generator which fulfills every servicing need from 150 kc to 32 mc.

With harmonics it covers the television and FM band up to approximately 100 mc. A 400-cycle audio is available for modulation or audio testing.

The kit has every part necessary, and it is provided with blueprints and step-by-step instructions to permit construction even by a beginner.

-50-

Spot Radio News

(Continued from page 16)

ice and serve as a source of essential propagation information required to set up a permanent allocation plan. Such a program would ease the economic problems involved in research and study, according to Goldsmith, with sponsored time supporting, in part, the expenses of ultra-high operation. The immediate allocation plan would be of invaluable assistance to the FCC, who have neither the staff nor the broadcasting facilities to engage in the vast studies required to prepare a complete ultra-high program now. Goldsmith believed that the immediate commercialism of ultra-high channels would cut years of confusion off the ultra-high allocation problem and bring the service into a cycle of quick public acceptance.

In a round-table session at the NAB, during which members of the engineering departments of FCC and broadcasters participated (John A. Willoughby, FCC acting chief engineer; Edward W. Allen, Jr., chief of the FCC technical information division; James E. Barr, chief of the FCC standard broadcast division; Cyril M. Braum, chief of the FCC FM broadcast division; Edward W. Chapin, chief of the FCC laboratory division; and A. James Ebel, WMBD; E. K. Jett, WMAR; K. W. Pyle, KFBI; O. W. Towner, WHAS; E. M. Johnson, Mutual Broadcasting System, and Frank Marx, American Broadcasting System, all of whom are members of the NAB engineering executive committee), it was disclosed that the audio tuning problem at the ultra-highs is more acute than the video, and perhaps the Inter-carrier system may thus be the more appropriate tuning method since it simplifies tuning. The synchronized carrier system also came up for a bit of discussion at the quiz session. Members of the FCC group indicated that this approach, sought as the answer to the very-high allocation problem, did not solve the interference difficulties encountered on adjacent channel operation or from radiating oscillators. The sync system was of material help on co-channel operation, FCC and the broadcasters indicated.

THE STRIKING GROWTH of TV was described effectively during the annual sales conference of the Edison Electric Institute in Chicago by Fred

A. Compton, general sales manager of the Detroit Edison Company, who declared that in Detroit . . . "We have been informed that television sales presently comprise from thirty per cent to as much as fifty per cent of the major appliance business."

Compton suggested that the utility men set up channels for the exchange of TV information within the industry and, in addition, maintain trained personnel who will be at all times familiar with TV set use and servicing problems. Stressing the acceptance of TV, Compton pointed out that even those anticipating TV reception have begun to buy, with 50,000 receivers sold in areas where stations are still under construction.

Commenting on the increased power income which has resulted from the use of television receivers, Compton said: "During the past year our television customers' bimonthly bills increased 18.3 per cent, of which 11.2 per cent was due to television."

IN ANOTHER PERTINENT report on TV and its impact on the economy of the nation, Dallas W. Smythe, University of Illinois economics professor and former assistant chief accountant in charge of economics and statistics for the FCC, said that by 1958, up to \$15,000,000,000 will have been invested in television. The economic implications of this new industry will affect many fields of business, Smythe declared. He pointed out that even collegiate football might be affected. In the case of the larger schools, through the sale of time, there would be some profit, but in the instance of the smaller universities and colleges, the results might not be so encouraging.

In the opinion of Professor Smythe, television will eventually replace most standard broadcast transmission.

IN CONTRAST TO Smythe's comments on the effect of TV on AM radio, Dr. Frank Stanton, CBS prexy, said at the 37th anniversary banquet of the IRE in New York City that TV will not replace AM.

Dr. Stanton declared: "It is a matter of record that no mass medium once developed has ever disappeared . . . Each has its own mass appeal, its own availabilities, its own use. And there are far too many millions of Americans, with too many different tastes and desires and moods at different times of the day, for any one medium to serve them all . . . When radio first flourished many people felt it would do away with, or seriously hurt, newspapers, movies, magazines and phonograph records. All have grown since the advent of radio, as the wealth and population and leisure time of the nation have grown. And I see no good reason for thinking the advent of television will fundamentally change this."

CAR TV has become the basis of many proposed bills in nearly half the states of the nation, which would limit or

RADIO & TELEVISION NEWS

NOW! BUILD 15 RADIOS \$14.75
COMPLETE KIT ONLY

ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
You Need No Additional Parts
The PROGRESSIVE RADIO KIT is the Only Complete Kit—Operates on 110-120 Volts AC/DC

Contains everything you need. Instruction book, metal chassis, tubes, condensers, resistors and all other necessary radio parts. The 36-page instruction Book, written by expert radio instructors and engineers, teaches you to build radios in a professional manner. The circuits are designed to provide excellent performance. Altogether, fifteen circuits are constructed, including 11 receivers, 1 audio amplifier and 3 transmitters.

SPECIAL OFFER
Electrical and Radio Tester sent absolutely FREE with each Progressive Radio Kit. Plus FREE Membership in the Progressive Radio Club. Entitles you to free expert advice and consultation service with licensed radio technicians. ORDER YOUR KIT NOW!

BUILD KITS !!
SAVE !! LEARN !!

VACUUM TUBE VOLTMETER KIT
A professional piece of test equipment you need for FM and TV. Attractive steel case. **\$23.95**
FREE: Book on Advanced Servicing Techniques.

5" Oscilloscope Kit
an absolute "must" for today's radio man **\$39.95**
FREE: Book on Cathode Ray Oscilloscope.

Volt-Ohm-Milliammeter Kit
simple to construct, inexpensive but accurate. FREE: Book on Elementary Radio Servicing. **\$14.95**

SIGNAL TRACER KIT
an invaluable aid in troubleshooting. FREE: Book on Radio Test Instruments. **\$21.95**

7" TELEVISION KIT
Factory-built and aligned 13 channel Tuner—18 Tube Kit—less tubes... **\$59.50**
Complete set of tubes, including Cathode Ray Tube... **\$39.95**
FREE: Television Servicing Notes.

10" TELEVISION KIT
Factory-built and aligned 13 channel Tuner—Complete kit, less tubes... **\$99.50**
Complete set of tubes, including Cathode Ray Tube... **\$57.30**
FREE: Television Servicing Notes.

PROGRESSIVE AMPLIFIER KIT
High Fidelity Humless Amplifier Kit, attractive aluminum chassis; complete with five tubes including selenium rectifiers. **\$16.00**
FREE: Book on Amplifiers.

Automatic Bike Radio
Can be mounted on a bicycle, or carried as a personal portable radio. Supplied with all bicycle mounting hardware and telescopic antenna. Anti-theft feature. Less batteries... **\$17.47**

Automatic Car Radio
6 tubes superhet. Three gang condenser, fits all cars... easy installation... mounting brackets included. List price **\$39.95**. NOW ONLY **\$27.97**

ECONOMY AMPLIFIER KIT... **\$5.95**
simple to build; complete with five tubes. FREE: Book on Amplifiers.

5 TUBE AC-DC SUPERHET KIT... **\$14.25**
complete with tubes and cabinet. FREE: Book on Building Receivers.

6 TUBE AC-DC 2-BAND SUPERHET KIT... **\$17.45**
complete with tubes and cabinet. FREE: Book on Amateur Radio Building.

7-TUBE AC-DC FM RECEIVER KIT... **\$29.95**
complete with tubes and cabinet. FREE: Television and FM Servicing Notes.

4 TUBE SUPERHET PORTABLE KIT... **\$12.95**
complete with tubes and cabinet; less batteries. FREE: Book on Unusual Radio Circuits.

All Merchandise Shipped F.O.B. New York
Deduct 2% if full payment accompanies order. 25% deposit required on C.O.D. orders. Write for further information concerning the above merchandise. Send for our Free catalog.

PROGRESSIVE ELECTRONICS CO.
Dept. RN-22, 497 Union Avenue
BROOKLYN 11, NEW YORK

Colpitts oscillator circuit, one of the two fundamental oscillator systems, which is used extensively in both transmitting and receiving equipment. Mr. Colpitts, who had retired in 1937 as vice president of Bell Telephone Labs, played an essential part in the achievement of transcontinental telephony in 1915 and in the radio transmission of speech across the Atlantic Ocean later in the same year.

His discoveries, recorded in twenty-four patents, won the plaudits of young and old in the classroom and lab, in industry and government. His brilliant concepts, which contributed so much to the welfare of our lives, will never be forgotten.

We mourn the loss of a servant of mankind.

AT LONG LAST, the Citizens' Radio Service has become a full-fledged communications service and has received its official rules and regulations for the

460-470 mc. band. Licenses will be issued generally, beginning June 1, to any citizen of this country 18 years of age or older. The licenses will have a life of five years and will be, in most instances, the only authorization required for operation of the station.

According to the rules, Citizens' Radio is intended for "fixed and mobile service . . . for use for private or personal radio communication, radio-signalling, control of objects or devices by radio," and will probably be employed, in the main, for communication on farms, between house and buildings or workers in remote locations; outlying camps and work crews; industrial plants; construction projects; and the control of devices such as gates and garage-door openers, model airplanes, display signs, etc.

Application forms for the licenses, which will be a simple card, will be available at the FCC field offices and in Washington. . . . L.W.

ADD A SPEAKER EXTENSION TO YOUR RECEIVER

LLEWELLYN JONES, JR.


THE conversion of an a.c.-d.c. receiver to accommodate an extension speaker does not pose too big a problem, as it merely entails the installation of a selenium rectifier in place of the vacuum tube rectifier already in place and an additional output stage. The accompanying diagram shows the wiring of the circuit before and after the conversion.

If the usual tube line-up is 35Z5, 35L6, or 25Z6, 25L6, and so on, remove the rectifier tube, and use the socket for an additional 35L6 (25L6) power amplifier stage. By using a PA tube with

the same filament voltage and current rating as the rectifier tube, no change will be necessary in the series filament circuit, and the new PA stage can be wired the same as the one already in the set.

The only other components needed will be a grid resistor and condenser, cathode resistor and condenser, and an extension speaker with an output transformer to match the tube installed. If desired, the added grid resistor can be a potentiometer, and this will serve as an auxiliary volume control.

An extension speaker and an additional output stage can be added to any five-tube a.c.-d.c. receiver without too much difficulty. The rectifier tube can be replaced with a selenium rectifier, and the filament voltage originally allotted to the rectifier tube can be used to heat the filament of an additional output tube. Wiring arrangement before conversion is shown to the left of the dotted line, while to the right is shown complete wiring details of the conversion.

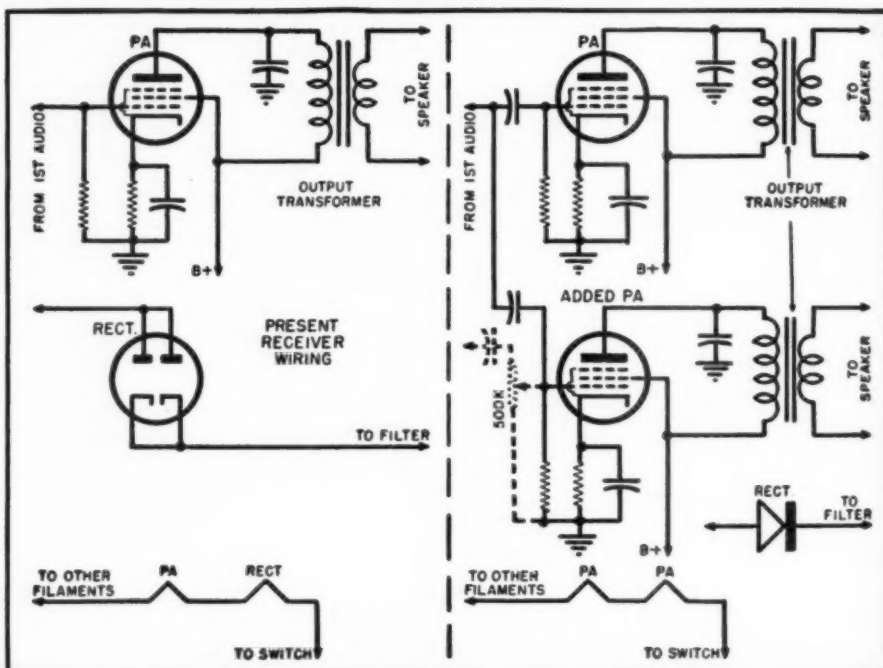

International Short-Wave

(Continued from page 108)

alternately with PRB7, 'Radio Tamoio' on 900 kcs. or PRG3, 'Radio Tupi' on 1,280 kcs., Rio de Janeiro; all these belong to the group, 'Emissoras Associadas.' He reports the new Brazilian ZYSS on 4.955, at Manaus, state of Amazonas (where time is 1 hour ahead of EST); logged first at 1900 with good level, signed off 1955; again heard later signing off 2130 when said was ending third period of transmission for the day and that would return 0500.

British Guiana—ZFY, 5.985, Georgetown, heard in Newfoundland 1830-1945. (Peddle)

Cameroons — Radio Douala, 9.160, heard in Australia with musical program 1330; signals fair. (Gillett.) Heard in Newfoundland Sundays 1430-1600. (Peddle)

Canada — According to announcement, former VONF and VONH calls have been changed to CBN and CBNX, respectively, following the confederation of Newfoundland with the Dominion of Canada. Now announce "This is the Trans-Canada Network of the Canadian Broadcasting Corporation, stations CBN and CBNX, at St. John's." New QRA is The Canadian Broadcasting Corporation, Newfoundland Division, P. O. Box E-5372, St. John's, Newfoundland, Canada. According to a letter received some months ago, by this time CKRO/X in Winnipeg, Manitoba, should be back on the air; watch for this one on 6.150. (Lyttle, Ontario.) Schedule for CBNX (former VONH) is believed to be 0600-2230 now. (Peddle, Newfoundland)

CBRX, 6.160, Vancouver, British Columbia, heard to sign-off 0302; news 0245-0300; QSL card gives power 150 watts. (Alfred, Ontario)

VE9AI, 9.540, Edmonton, Alberta, news 0000, 0100. (Alcock, Ky.)


Celebes — YDQ, 9.550, new call for this station at Makassar, power 10 kw.; also on YDQ-2, 5.030, 500 watts, and YDQ-3, 11.084, 3 kw.; schedules are YDQ, 1700-1800 (Indonesian), 1800-1900 (Dutch), 2200-0000 (Indonesian), 0000-0130 (Dutch), 0400-1000 (Indonesian); these transmissions are also on YDQ-2; YDQ-3 is used 0500-1000 (Dutch). Forces service is scheduled in Dutch, YDQ-3, 0500-0700; in Indonesian YDQ-2, 0700-0900; news in Dutch 1830 (YDQ), 0015 (YDQ, YDQ-2), 0115 (YDQ, YDQ-2), 0730 (YDQ-3); news in Indonesian 1730 (YDQ, YDQ-2), 1830 (YDQ-2), 2330 (YDQ, YDQ-2), 0900 (YDQ, YDQ-2); news in Makassar 0430 (YDQ, YDQ-2); in Buginese 0440 (YDQ, YDQ-2). (N. Z. DX Times)

Heard on approximately 11.086 (listed 11.084) in California, good level, to 1000 sign-off. (Dilg.)


Ceylon — Radio Ceylon, 15.12, has had improved signals here in East lately, mornings.

On April 1, the BBC became responsible for programming for 8½ hours a

ARE YOU A DIAL JOCKEY?

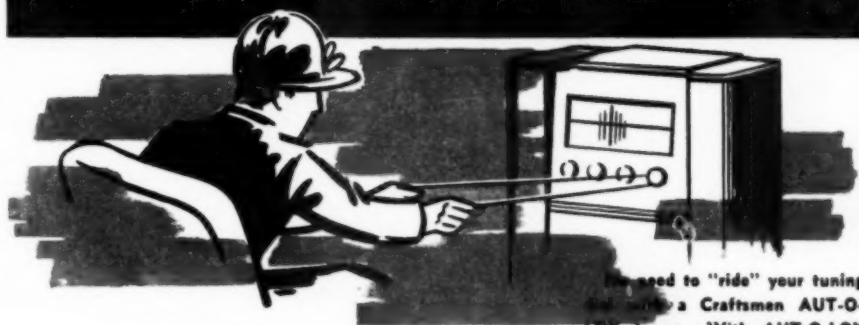

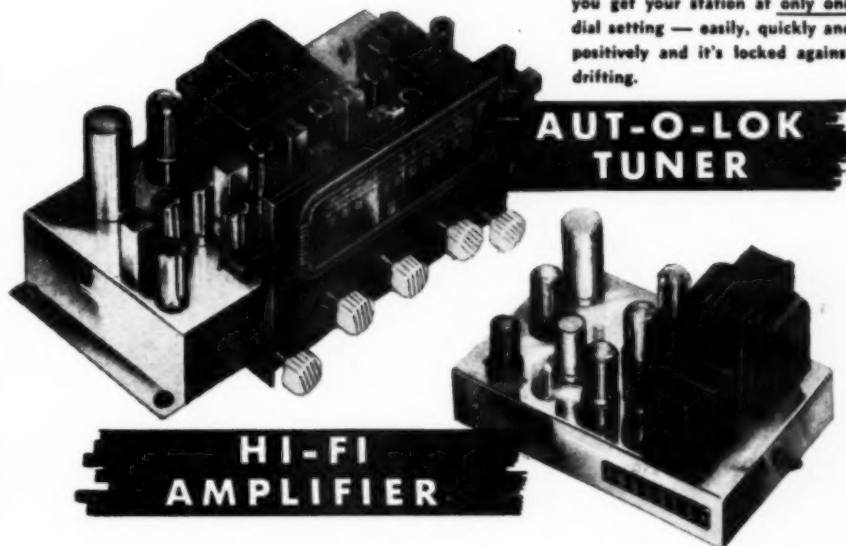Learned to "ride" your tuning with a Craftsman AUT-O-LOK tuner. With AUT-O-LOK you get your station at only one dial setting — easily, quickly and positively and it's locked against drifting.



FM-AM TUNER RC-8. Features automatic frequency control, most revolutionary development in FM design — entirely eliminates drift and multiple tuning responses. Nine shielded miniature tubes plus rectifier include double limiter and tuned RF stage in both FM and AM. Low-impedance loop, enabling flexibility in mounting, provides low-noise AM reception. Rear socket provides easy access to 6.3-volt AC and exceptionally well-filtered DC for supplying external pre-amplifiers, additional pilot lights, etc. Controls include separate bass, treble and switch positions for phonograph and

television audio inputs. Polished chrome chassis. Audio cable, escutcheon, decals, antennae, and detailed installation instructions furnished.

HI-FIDELITY AMPLIFIER RC-2. High-impedance input; 12 watts output at 1% distortion. Taps: 4, 6, 8, 15, 500 ohms. 65 db gain, including inverse feedback. Uniform frequency response from 20 to 20,000 cycles up to 8 watts output. Hum 65 db below rated output. Tubes: 6J5, 6SN7, (2) 6V6, 5Y3. Durable polished chrome chassis.

Sold by Better Distributors. Write for Circular "A"

The RADIO CRAFTSMEN, Inc.
1341 S. MICHIGAN AVENUE, CHICAGO 5, ILL.

RADIO & TELEVISION NEWS
Classified Columns Really Bring Results
Use Them Frequently

YOUR HOBBY DESERVES...




PRECISION JEWELERS SCREW DRIVERS

Tinkering with your television set, or building your own radio set? For precision work of every type, these eight Jewelers' Screw Drivers are perfect! Complete Set of Eight, from the smallest size 9 up to size 2... and they'll handle the most delicate job! Finest tempered steel blades... lowest price imaginable!

Only \$2.00 COMPLETE Money-Back Guarantee if Not Satisfied
PINE WATCH CO. C.O.D. \$2 plus postage, or send \$2 and we pay postage.
29 Eldridge St., New York 2, N.Y., Room 404

SURPLUS HIGH SPEED DRILLS MICROMETERS

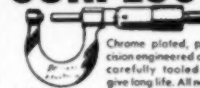

Chrome plated, precision engineered and carefully tapered to give long life. All new.
0-1" capacity . . . each \$2.25
1-2" capacity . . . each 3.50
2-3" capacity . . . each 5.50
3-4" capacity . . . each 8.50



All New Drills! Orig. value \$15.
30 assorted sizes and lengths \$3.50
SEND FOR FREE DESCRIPTIVE CATALOG

Send check, money order or cash. 25% deposit required on C.O.D. orders. All prices F.O.B. Culver City, Calif.
AIRBORNE SALES CO., INC. CULVER CITY, CALIF.

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

BC-375-E original schematic, tuning units, complete parts list, values, characteristics, circuit functions. Plate currents...\$2.00
BC-224-F, K, BC-348-H, K, L, R original schematic, parts list, AC conversion...\$2.00
BC-348-J, N, Q original schematic with parts values, plus AC conversion...\$1.00
BC-224-F, K, BC-348-J, N, Q, H, K, L, R (specify which) complete illustrated reprints of all pages from manuals on trouble-shooting and complete alignment, voltages, etc. \$2.00
ARC-4 schematic, parts, cabling...\$1.00
Another \$2.00 for 2-meter AC conversion with all specs, tune-up, color-coded wiring.
ARB (CRV-46151) complete and simplified schematics and alignment chart...\$1.00
Another \$1.00 for AC conversion with added AF, and broad-sharp, ave-mew, ew-mew, rf gain, af gain with on-off, phone jack, all on front panel.
ASB schematics, parts values, voltages; specify: Indicators CJP55AAZ, 55ABR; revr. CPR46ACJ; xmr CAY52ACU. Ea. \$1.00
BC-645 original and conversion...\$1.00
ARC-5 schematics, all units...\$2.00
ART-13 ham-band calibration charts...\$2.00
PE-117 conversion, mobile power for surplus revrs. 6v in. 12vac and B+ out...\$1.00
SCR-522-A, AM, and C schematics, parts lists with circuit functions, explanation of differences, chart for xtal selection...\$2.00
BC-659 & PE-117 schematics, voltages \$1.00
SCR-518 all schematics with circuit operation, values, reprint of manual...\$2.00
APT-5 schematic, AC power, complete set-up and tuning instructions...\$1.00
SCR-274N revrs. BC-453, etc., all schematics, AC conversion, local control adapter, alignment, parts locations, voltages \$2.00
BC-946B best AC home-rev. conversion \$2.00
PE-103 schematic, circuit explanation \$1.00

The following schematics are \$1.00 each:
APN-1; APN-9; APT-2; ARN-7; ART-13A; System hookup for BC-603, 604, 683, 684, 923, 924 (specify which); BC-1206-C; GO-9; GP-6, GP-7, TCE-2; MN-26; No. 19 Mark II; R-89/ARN-5A; RA-10; BC-733D; BC-433-G; SCR-625.

The following schematics are \$2.00 each:
BC-654; BC-603, 604, 683, 684; BC-923, 924; ID-6A, ID-6B, R-9A, R-9B/APN-4 (specify which); RU-16/GP-11; RU-17/GP-12; SCR-(-)183, 283; SCR-625.

Please remit with order. We pay postage. Send 25c and stamped addressed envelope for comprehensive list, cross-indexed for BC and SCR. Includes chart explaining code used in Army-Navy nomenclature.

R. E. GOODHEART 345 1/2 N. PALM DRIVE
BEVERLY HILLS, CALIF.

230 V.DC to 110 V.AC 60 Cycles, 7 1/2 KVA Output MOTOR GENERATORS at Sensationally LOW PRICE!

NEW, UNUSED, mfd. by Star Electric Motor Company of Bloomfield, N. J. Motor volts—230 DC. 7 1/2 HP. compound wound, 1800 RPM. equipped with 8" large flat contact field rheostat. Generator—7.5 KVA at 1800 RPM, 120 volts, single phase, 60 cycles, equipped with 13" large flat contact field rheostat. Ideal for ships, shipyards, industrials or wherever DC to AC conversion is desired. Domestic packed, FOB warehouse NYC. EACH...\$345.00
Substantial Discount on Quantity!

TELEMARINE COMMUNICATIONS CO.
280 NINTH AVE. NEW YORK 1, N. Y.
Telephone LOngacre 4-4490

Mass. Radio School

273 Huntington Ave., Boston 15, Mass.
Offers Training Courses for Radio Technician (Pre-Television) and Licensed Radio Operator (All Types) including maintenance and operation of General Electronic Equipment. Over 20,000 Alumni and 30 years radio training EXPERIENCE. Courses approved for G.I. Training for Veterans.

Send for Catalog
Licensed by Commonwealth of Mass.
Department of Education

SERVICE MEN'S RADIO PARTS KITS

100 Asst. Insul. Res. \$1.45	20 Asst. Knobs . . . \$.89
10 Asst. By Pass49	1 lb. Asst. Radio, HDW. .25
20 Asst. Trimmers . . .59	15 Asst. Sockets . . .69
25 Asst. Micas89	10 Asst. Elec. Cond. . .2.69
10 Asst. Vol. Cont. . .89	20 Asst. Term. Strips . .69
1 lb. Asst. Cut Wire . .69	20 9" Lengths Spag. . .15

BUY ALL ABOVE KITS FOR \$9.75
Please enclose postage
Radio Mail Orders, Dept. RN
2 WEST BROADWAY NEW YORK 7, N. Y.

day over the s.w. transmitters of *Radio Ceylon*, a station official informed Worris, N. Y. (I note that much of this material is the same as is relayed by the British Far Eastern Broadcasting Service in Singapore—KRB.) The official told Worris: "I am sorry to disappoint you but it is not planned to direct transmissions to North America. The programs will be beamed to China, Japan, Manchuria, Malaya, Burma, and the Far East generally, and to India and Pakistan." The Forces (SEAC) program on Sundays 1130-1330 has ended; this was beamed to the United Kingdom.

Chile—Rosenauer, Calif., has received a letter (in *English*) from Radio Sociedad Nacional de Minería (National Mining Society), Casilla 2626, Santiago, Chile; confirmed report on CE622; frequencies listed 11.730 and 6.220; no other information given. McPheeters, La., got similar information but lists 25-m. outlet as 11.750 and says has m.w. station on 1060 kcs., and another m.w. outlet (this one at La Serena), CA108, "Radio La Serena," on 1080 kcs., also parallels.

China—A Chinese station heard by Dilg, Calif., on about 9.685, carrying news 0900, may be Canton.

Hankow, approximately 11.495, heard around 1810 in New York State; signal poor with heavy CWQRM and QRN. (Geis.) Heard regularly in Hawaii around 0530-0800, good level. (Fellers)

Recently, the Communist-controlled North Shensi radio was heard giving five frequencies, probably all s.w.; 7.500 is one frequency (old XNCR); approximately 9.049 is another, and a possibility is 6.096; one of these outlets is heard with the 0840 news relay right on top of Cebu, 6.100, Philippines; XRR, 10.260, Peiping, also now relays North Shensi; all these have news 0840. (Dilg, Calif.) Peiping can be heard with fair signal early mornings here in West Virginia but by 0840 is buried in QRM. Dilg informs me that the Communist-controlled outlets no longer use call letters.

Gillett, Australia, reports a Chinese station heard faintly on approximately 5.018, just at the low side of Makassar which he puts at 5.020 (not 5.030 as generally reported); he hears the Chinese station around 0630 to after 0830, but it is too weak to get call.

BED9 is call of former XURA, Taipei, Formosa; BCB calls are BED2, 750 kcs., BED3, 1020 kcs., BED29, 1020 kcs., and BED22, 670 kcs. (N.Z. DX Times.) The 41-m. outlet is now on about 7.215, at least is lower than former listed 7.222, heard in California mornings. (Dilg.) Also heard by Stark, Texas.

A Chinese outlet is widely reported on approximately 11.685, mornings; Dorothy Sanderson, Australia, reports call as BCAF or PCAF (most likely the former), heard 0430 with well-known "March Militaire"; says this station has *English-Chinese* lesson daily at around 0600-0645. I heard this one regularly early mornings here in West Virginia, but it is badly CW-

LOWEST PRICES for HI-QUALITY TUBES

RADIO and TELEVISION

6AK5 6J6 6BG6G 10" Picture tubes 10BP4 12 1/2" Picture Tubes 12LP4
(The picture tubes carry a 12-month guarantee)

ALSO A COMPLETE LINE OF RADIO & TELEVISION TUBES

ALL
TUBES
CARRY
A
MONEY-
BACK
GUARANTEE

Up to 150,000 of some types of television tubes available.

Large discounts for wholesalers, manufacturers and exporters.

All tubes individually boxed or bulk whichever preferred.

All tubes branded N J R T.

WE DO
NOT
SUBSTITUTE
ON
SPECIFIED
TYPES

Orders shipped C. O. D. until credit established.

Direct all export inquiries to our export representatives:

CECO ELECTRONICS CO., 367-69 Broad St., Newark 2, N. J.

Territories still available for distributorships.

NEW JERSEY RADIO & TELEVISION TUBE CO.

715 ELIZABETH AVE.

ELIZABETH 4, N. J.

QRM'd usually. Stark, Texas, says call sounds BGAR or BUAR. Dilg, Calif., says this is definitely BCAF, Taiwan, Formosa, believed to be old XGAF moved from Nanking; XGAF was a Chinese Air Force Station. Signs off 1000, says Dilg. Fellers, Hawaii, airmails me that he hears this one around 0430 to around 0700 with excellent signals, all oriental.

Nanking, 9.732, usually is fair here in East around 0500 to around 0630 (depending when Dominican Republic puts its 9.735 carrier on the air); no English noted in this Nanking period.

At the time this was compiled I was hearing Chungking on 7.100 and 15.172 with news 0700; probably will be on Summer Time (one hour earlier) by the time you read this. The 11.913 channel recently has been running 0845-1140 or 1150, news 0900, 1100. This one has bad CWQRM in East, but some days is readable in 0900 news period. Direct from the station, I have this message—"We have changed our call signs to BEF6, BEF7, and BEF8 instead of XGOY and XGOX; in order to avoid confusion we always announce either 'The Voice of China in Chungking' or 'This is China Calling from Chungking' for our listeners' identification." I have heard both these given recently. Schedules just received (may now be one hour earlier if China is on Summer Time) are listed 15.17, 7.153, to Australia, New Zealand, East Asia, 0455-0635; 15.17, 7.153, 0635-0835, to East Asia, South Seas; 11.913, 7.153, 0845-1100 to North America, Europe; 11.913, 7.153, 1100-1150 to Europe, America, China, South Seas; news 0700, 0900, 1100; at the time this was compiled was being heard on this schedule in America but the listed 7.153 still remains actually on 7.100.

Cuba—COCH, 9.445, Havana, heard 2030-2130. (Peddle, Newfoundland)

Czechoslovakia—Prague, 9.55, still has news for North America 1900, in clear to 1910 when Paris carrier usually comes on and blankets Prague. (Boice, Conn.)

Denmark—OZH, 15.165, Copenhagen, is used Saturdays, Tuesdays, Thursdays 0500-0600 for Far East; news just before closedown. (Pearce, England)

Dominican Republic—HI1N, 6.050, Ciudad Trujillo, heard 1745-1900. (Peddle, Newfoundland)

Ecuador—HCJB, Quito, is now issuing schedules quarterly, free on request to HCJB, Casilla 691, Quito, Ecuador. English periods are scheduled now Tuesday through Sunday—0630-0730 on 12.455, 9.958; 1700-1800, 2100-2300 on 15.115, 12.455, 9.958; 2300-0030 on 15.115, 12.455, 9.958, 5.995; and to Europe at 1500-1600 on 17.890, 15.115. Incidentally, chief engineer Clayton Howard informs me: "We are getting a lot of good reports from Europe on our 16-meter transmissions, so are very much encouraged with this new frequency."

Finland—Here may be the answer to the question of some DX-ers as to whether Helsinki has left 9.500; I believe the newer QSL card lists 31-m.

June, 1949

A WIDE RANGE HIGH QUALITY ... INSTRUMENT



the new improved ESPEY 511 AM-FM RADIO

- Here is a fine radio, in chassis form, to please the most discriminating music lovers.
- Easy to install in any console cabinet old or new, the Espey 511 AM-FM radio chassis embodies the latest engineering refinements for lasting high quality and enjoyment at a price that defies competition.
- Features, 12 tubes plus rectifier and tuning indicator; drift compensated circuit for high frequency stability; tuned RF on AM and FM, high fidelity push-pull audio; 13 watts power output; wide range 12" PM speaker; smooth flywheel tuning; phono input provision; separate AM and FM antennas.

Other models available including 25 watt output.

Write Dept. KD for your free catalog.

Makers of fine radios since 1928.


ESPEY

MANUFACTURING COMPANY, INC.

528 EAST 72nd STREET, NEW YORK 21, N. Y.

TEL BUTTERFIELD 8-2300

Custom
Built

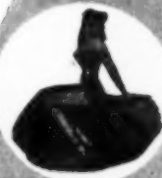

TELEMIKE

Picks up telephone conversation on both ends of the line for transmission to any type recorder or for group loud speaker listening. No electrical connection with telephone. Model "B" 1" round x 3/8" thick. Price \$15.00. Model "F" 1 1/2" x 4 1/2" x 1/4" thick. Price \$20.00.

MILES REPRODUCER CO., INC.
812 Broadway New York 3, Dept. RN6



CORRESPONDENCE COURSES IN RADIO and ELECTRICAL ENGINEERING

ELECTRICAL ENGINEERING Get good grasp of wide electrical field. Prepare yourself at Low Cost, for secure future. Modern course. So simplified anyone can understand quickly.

RADIO ENGINEERING Extra fine course in radio, public address, photo-electric work. Trains you to be super-service man, real vacuum-tube technician. Servicemen needed badly. Diploma on completion. Many graduates earning big pay.

WRITE Send postcard for Free Copies of \$25 Either school catalog, full details, all about Course deferred payment plan, experimental kits, etc. Electronic Kit given to students enrolling by June 1. LINCOLN ENGINEERING SCHOOL, BOX 931-R-6, LINCOLN 2, NEBR.

GOVERNMENT SURPLUS! WORLD'S LOWEST PRICE

PHOTO FLASH EQUIPMENT



COMES COMPLETE WITH
4 EDGERTON
FLASH TUBES
& REFLECTORS



EASY TO
CONVERT INTO
A 2-WAY PHOTO
FLASH UNIT


OPERATES ON 110V. AC & 12V. BATTERY

Brand new at a fraction of original cost. Contains finest component parts available. All necessary parts and complete instructions included. After conversion, works on 110V AC or 12V battery by a flick of a switch.

\$68.
COMPLETE

IMMEDIATE DELIVERY ON ALL MAIL ORDERS
CINEX, INC., 165 W. 46th St., N. Y. 19, N. Y., Dept. RN-6


Sensational New universal clamp

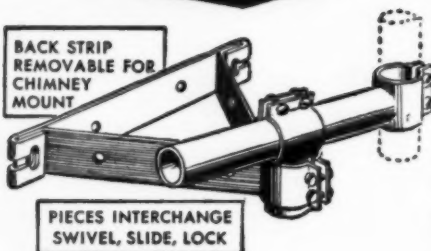


Licks EVERY antenna mounting problem! \$8.25 NET

LESS REGULAR DEALER DISCOUNTS

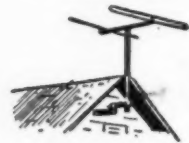UNIMAC is an installer's dream come true! This one unit completes your kit. UNIMAC mounts anywhere, in any position, handles all 1 to 1 1/4" masts, and swings them free and clear to perfect, upright position. NO GUY WIRES REQUIRED.



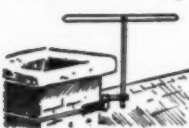Clears overhanging eaves on gables... masts need not be bent... mount fastens directly to house without extension blocks. NO GUY WIRES.



Clears lips on chimneys... choice of lag screw or strap mounting provided on part... NO GUY WIRES.



Base mounts easily on pitched surfaces... full adjustment for erecting mast and orienting antenna. NO GUY WIRES.



Mounts on horizontal or vertical window sash... swings antenna clear of obstructions. NO GUY WIRES.

UNIMAC is constructed of heavy steel throughout, with all joints welded, eliminating part failures. Sturdy, clean-cut appearance pleases customers, increases business. ONE-MAN CREWS NOW PRACTICAL.

There's no call back when you use Unimac



MARVIN RADIO-TELEVISION
Buckeye at East 89th St., Cleveland 4, Ohio

- ☐ Enclosed find \$5.10 (\$4.95 plus postage) for one sample.
- ☐ Enclosed \$..... for..... boxes of UNIMACS at \$29.70 per box of 6.

Name.....

Address.....

channel as 9.555. Pearce, England, reports he picked up Helsinki recently 0255 on approximately 9.560, says apparently has moved there from 9.500; heard another day 0345 and after 0400 was in parallel on 17.800.

France—Paris noted on 9.675 at 1415 with French news. (Norris, Lebanon)

At the time this was compiled, Paris had (temporarily?) suspended the second daily transmission to North America (beginning at 2100). (Worris, N. Y.)

French Equatorial Africa—Alfred, Ontario, reports Brazzaville on 15.160 (on Sundays at least) to sign-off 1055, program of French music.

The 6.024 channel heard with interval 1830 and at 1833 announced and continued in French, signal only fair. (Ferguson, N. C.)

French Indo-China—Radio Saigon in QSL card via airmail lists *English* sessions on 11.780 daily 1830-1845, 1930-2000, 0415-0530, 0830-0930. (Pearce, England.) A station believed to be Radio Saigon is again being heard on about 7.215, mornings; and a station believed to be in French Indo-China is heard mornings on about 6.087, relaying Paris. (Dilg, Calif.)

French Morocco—Radio Maroc, 6.005, heard 0130-0215 fade-out; seems to have French news 0145-0200, Arabic to fade-out. (Alfred, Ontario.) Location is Rabat.

Germany—RIAS, 6.080, Berlin, strong signal in England to 1100; also heard 1800 after "Voice of America" program, and with RIAS programs to 1900. Radio Stuttgart, 6.030, heard mornings and afternoons, blanketed in QRM after around 1230; news in German 0645, 1145. (Pearce, England)

Hamburg, 7.29, heard weekdays signing on 2300 with good signal; news in German 2345; fades out around 0200; same station logged 1720-1830 with good level, signed off 1900. (Leven, Brazil)

Greece—Mitchell, Perth, lists Athens on 9.607 at 0030-0235 and 0500-0800 daily; 15.345 heard 1000 with news in Greek at dictation speed; at 1040 news in *English*, followed by news in French; heard on 7.300 at 1100 with news in Turkish, followed by news in Russian, then in several Balkan tongues; music and commentaries followed to 1615 when news in Greek was repeated; at 1630 had preview of next day's program and left air 1635 with Greek National Anthem; said at sign-off 15.345 and 7.300 were parallel. (Radio Australia.) The 15.345 channel is still heard, with improved level, daily to U. S. at 1730-1830, news (by woman) at start. Schedules received by Hankins, Pa., are—Daily to Northwestern Europe and U. S. A. on 15.345, 7 1/2 kw., 1015-1045 news in Greek; 1045-1100 news in *English*; 1100-1115 news in French; 1730-1830 special program for U. S. A. (news in *English* and in Greek with a musical program in between). Daily on 9.607, 7 1/2 kw., 0030-0235, relay of Greek m.w. program; 0500-0800, also relay of Greek m.w. program. Daily on 7.300, 7 1/2 kw., 1200-1330 news

in Turkish, Russian, Rumanian, Serbian, Bulgarian, and Albanian (15 min. for each language). Interval signal is the first few bars of the Greek song, "Kato Ston Valto."

Radio Broadcasting Station of the National Greek Army, Larissa, 6.745, has news in *English* at 1430 then music to 1500; said *English* broadcast would be at same time on Tuesdays, Fridays, and Sundays; on Mondays and Thursdays at 1430-1500 has French; full schedule 0015-0200, 0500-0700, 1100-1500; power 500 watts; asks for reports to Radio Broadcasting Station of the Greek Army Corps, Larissa, Greece. (Pearce, England.) Bouras, Michigan, just returned from a stay in Greece, informs me that the head of Radio Athens told him Larissa is operating with less than 1 kw. power and is called The Armed Forces Radio Station, Troop 453, Class B, Army of Greece.

Honduras—HRN, 5.884, Tegucigalpa, heard 2145-2330. (Peddle, Newfoundland)

Hong Kong—ZBW-3, 9.525, heard on occasion in French to 0600 when BBC news was relayed; this apparently is not daily for more recently was heard at that time with recorded music compared in *English*. (Gillett, Australia)

India—Current (new) schedules of All India Radio, by channels, are—4.840, VUC2 0815-1230; 4.880, VUB2 0900-1230; 4.920, VUM2 0700-1200; 4.960, VUD2 0815-1230; 6.010, VUD8 0945-1315, 2215-2230; 7.210, VUC3 0200-0430, VUC2 0630-0800, VUC3 0815-1230, VUC2 2000-2200; 7.240, VUB3 0215-0400, VUB2 0630-0845, VUB3 0900-1230, VUB2 2100-2300; 7.260, VUM3 0200-0430, 0530-0630, 0700-1200, VUM2 2030-2230; 7.275, VUD10 0745-0815, VUD11 0915-1100; 7.290, VUD2 0630-0800, 2100-2300; 9.530, VUC2 0200-0430, VUC3 0630-0800, 2000-2200; 9.550, VUB2, 0215-0400, VUB3 0630-0845, 2100-2300; 9.590, VUM2 0200-0430, 0530-0630, VUD5 0815-1100, VUD3 1130-1230, VUM3 2030-2230; 9.620, VUD7 1400-1500; 9.660, VUD11 2215-2300; 9.670, VUD9 0340-0350, 0700-1315; 9.680, VUD2 0200-0400, VUD9 2215-2230; 11.760, VUD11 1400-1500; 11.790, VUD11 1130-1230, VUD5 1400-1500, 1845-1900, 2215-2300; 11.830, VUD8 2030-2115, 0215-0350, 0700-0915; 11.850, VUD4 0220-0400, 0730-1230, 2030-2230; 11.870, VUD11 2030-2200; 15.160, VUD7 1000-1045, 2030-2200; 15.170, VUD10 1110-1315, 1400-1500, 1845-1900; 15.190, VUD5 0030-0800, 2030-2200; 15.290, VUD10 0030-0730, VUD3 0830-1100, 2030-2230; 15.350, VUD9 0220-0250, 2030-2115; 17.760, VUD3 0220-0400, 0730-0750; 17.800, VUD7 1110-1315; 17.830, VUD7 0030-0900, VUD10 1000-1045, 2030-2200; 21.510, VUD11 0030-0800. (Legge, N. Y.)

English periods are now scheduled 2030, 17.83, 15.16, 11.87; 2130 (news), 17.83, 15.29, 15.19, 15.16, 11.87, 11.85; 0030, 21.51, 17.83, 15.29, 15.19; 0130, 21.51, 17.83, 15.29, 15.19; 0300 (news), 17.76, 15.29, 11.85, 11.83; 0630, 21.51, 15.19; 0730 (news), 17.76, 11.85, 11.83, 9.67; 1000, 17.83, 15.16; 1030 (news), 17.83, 15.29, 15.16, 11.85, 9.67, 9.59, 7.275.

RADIO & TELEVISION NEWS

6.010; 1215, 15.19, 11.79; 1400 (experimental), 15.17, 11.79, 11.76, 9.62.

Indonesia—Dilg, Calif., reports a Republican Indonesian outlet on about 7.620, schedule unknown and running until after 0930; later he heard this one signing off 0945 with "Good Night Melody."

Radio Solo, 3.300, Central Java, is on daily 0400-0900; Forces Broadcasting Station of the Dutch Strijdkrachten Radio Service, 5.020, Djogjakarta, is heard 0900, also on 5.620. (Cushen, N. Z., via URDXC)

Iran — Teheran, 15.100, normally runs to only 1410 but some days has been heard as late as 1430; news 1340. (Fargo, Ga.) EQC has moved from 9.680 to 9.660.

Iraq—HNA, 7.092, Baghdad, fair to 1400 with Arabic music; news in Arabic 1400 to 1410, then signs off with march. (N. Z. DX Times)

Israel—According to Bluman, formerly of Eritrea but now in Tel Aviv, Kol-Yisrael, Tel Aviv, 651 kcs. and 6.820, and Haifi, 8.170, are scheduled Mondays to Fridays inclusive 2345-0100; Saturdays 0030-0130; Sundays 2345-0130; daily 0430-0715; Sundays to Fridays inclusive 1000-1530; Saturdays 1000-1600; English daily 0700, 1000. (Radio Australia.) (Time of last English newscast may be in error, as formerly was at 1500; may have been converted incorrectly by Radio Australia.)

Italy—"Rome Calling" heard on 9.63, 6.085 with news 1615 during European session of 1545-1630. Schedules received from Rome list to Europe on 9.630, 6.085, 1545-1630, news 1615; for North America, 11.810, 9.630, English 2015-2055, news 2015; for Pacific, 15.120, 11.810, English 0520 during transmission of 0500-0530; for South Africa, 1340-1410, 11.810, 9.630, with English 1340-1355. (Pearce, England)

Japan—AFRS, 6.015, Tokyo, is usually a fair signal early mornings in East; best around 0600-0700. Occasionally, the station on 15.225 can be heard around 1820; at 1830 announces "N.H.K."

The 7.285 outlet has been good 0400 with English lesson. (Alcock, Ky.)

Kashmir—Radio Srinagar is broadcasting on approximately 4.866 in the 61-meter band. (Radio Australia)

Korea—HLKA, 7.935, Seoul, heard in England 1600. (Staples)

Lebanon—Printed schedules received airmail from Ned Norris, Beirut, list Radio-Liban on 8.036 at 0045-0100 (Sundays 0145-0200), 0630-0730, 1400-1515; news in French 0045 (Sundays 0145), 0630, 1400. I believe English is used between 1000 and 1100.

Libya—"This Is Your Forces Broadcasting Service," 4.790, Benghazi, heard from around 1430, often reaches R-7 between 1500-1600 when signs off with Ted Lewis' recording of "Good Night Melody"; at 1545-1600 has a sort of epilogue program—classical music and singing of hymns; speech intelligibility poor due to strong CWQRM. (Pearce, England)

Luxembourg — Radio Luxembourg, 15.350, signs on 0700; news in French

0700; the 6.090 channel heard on Sundays 1130-1300 with English program, then French; announced another English session for 1700. (Pearce, England)

Madagascar—Radio Tananarive, 12.127, heard 0745-0810, fair level. (Alfred, Ontario.) Fellers, Hawaii, reports the 9.695 outlet heard at 2230, signing on with "La Marseillaise"; then has musical program; news in French 2300; music 2320-0000 at which time station fades out; easily recognized by call "Ici Radio Tananarive."

Malaya—Dilg, Calif., says he hears Radio Malaya, Singapore, on 4.780 now mornings; no longer hears the (listed) 4.825 channel, probably has changed

frequencies; program is native. Says is good level on 7.200 mornings. Fellers, Hawaii, reports the 7.200 channel at 0630-0830 and later.

Rosenauer, Calif., received a QSL card from the Director of Engineering, Dept. of Broadcasting, Radio Malaya, Singapore, confirming his report; listed s.w. outlets at Singapore as 4.825, 6.135, 7.200; Kuala Lumpur as on 6.025.

British Far Eastern Service, Singapore, sent Kary, Pa., these schedules—0415-1130, 6.77, 11.88; 0600-1130, 9.69; 0415-0530, 1030-1130, 15.30.

Mauritius—Laubscher, South Africa, says: "Nothing here on reported Mauritius, although it should be on the air by now." World Radio Hand-

You Build 'em
in
ONE EVENING
but...

THEY LAST A LIFETIME!

EICO
INSTRUMENT
KITS

HIGH-PRECISION
VACUUM TUBE
VOLTMETER

Model 221-K
\$23.95

Tops in workbench versatility. 15 different ranges! AC and DC ranges: 0.5/10/100/500/1000 volts. Electronic ohmmeter ranges from .2 ohms to 1000 megohms in 5 steps. New features include Zero Center for TV discriminator alignment. DC input impedance is 26 megohms. Exceptionally accurate, big 4½" meter cannot burn out. Double triode balanced bridge circuit assures stable, guaranteed performance. Sturdy portable steel case with etched, rub-proof panel. 110-130 V. AC 50-60 cycle. Size 9 7/16" x 6" x 5".



FACTORY-WIRED VTVM
Model 221. Same, but completely wired, calibrated, and tested..... \$49.95



5" 'SCOPE

Model 400-K
\$39.95

Quality throughout! Laboratory precision scope, for FM, AM, & TV servicing. Deflection sensitivity: .30 volts per inch full gain. Linear sweep with 884 gas triode. Horizontal sweep circuit, 15 to 30,000 cycles. Frequency response of horizontal and vertical amps in from 50 to 50,000 cycles. Provision for external synchronization, test voltage, and intensity modulation. Complete with 2-6SJ7's, 2-5Y3's, 884, and 58P1 CR tube. Graph screen for measuring peak to peak voltages. Operates on 110 front of handsome 3-color etched, rub-proof panel. Size: 8½" x 17" x 13" high. Shpg. wt. 40 lbs. As with all EICO kits, easy-to-follow Pictorial and Schematic diagrams are included. FACTORY-BUILT OSCILLOSCOPE Model 400. The same high-quality, life-long instrument, but fully wired, assembled, and tested..... \$69.95

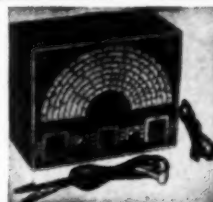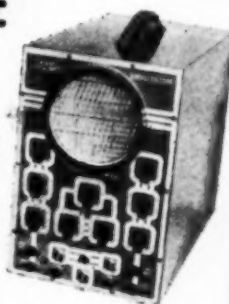

NEW

NEW! MODEL 320-K
SIGNAL GENERATOR \$19.95

A top-quality signal generator for every servicing need. Can be used for FM-AM alignment and to provide TV marker frequencies. Range: 150 kc to 100 mc in 7 bands, with fundamentals to 34 mc. Pure 400 cycle audio sine wave is available for audio testing and RF modulation. Many other high-priced features. Easily assembled and aligned with broadcast receiver. 8" x 10" x 5". Complete with tubes.

FACTORY WIRED AND ALIGNED
Model 320. Tested, ready-to-use. \$29.95

PENCIL-TYPE
HIGH FREQUENCY RF PROBE KITS

Germanium crystal probes for visual RF signal tracing and measurements to over 200 megacycles. ½" O.D., 6½" long.

Model P-75K. Can be used with EICO Models 221, 113A, or any VTVM! \$3.75
Model P-76K. For Model 400 scope.

Models P75 or P76. Same as above but factory wired and tested. Each... \$7.50

EASY-TO-FOLLOW SCHEMATIC
& PICTORIAL DIAGRAMS

come complete with every
EICO Instrument Kit.

Each kit fully guaranteed
to operate perfectly when
assembled according to
our instructions!



ELECTRONIC INSTRUMENT CO., INC.
276 Newport Street, Brooklyn 12, N. Y.

SCHOOLS: Special Discounts
To Quantity Users.

FOUND!

the "MISSING LINK" to
GOOD TV ANTENNA
INSTALLATIONS



MAST CLAMP LEAD-IN SUPPORTS

Made with POLYETHYLENE

(the ultra-low loss insulation material)

Now you can make any old or new TV installation last longer, look neater, perform better with the unique JFD Mast-Clamp Lead-In Supports. These new Screw Eye Insulators are JFD-engineered to anchor lead-ins firmly in place and assure better TV/FM reception.



Mast Clamps are made in all sizes for all applications, individually designed to fit masts from 1/2" to 2" O.D. Screw Eyes range from 3 1/2" to 12" in length.

JFD MANUFACTURING CO. Inc.

6711 16th Ave. Brooklyn 4, N. Y.

WRITE TODAY
for Valuable 4-page Bulletin #DBR

© Copyright 1949 by JFD Mfg. Co. Inc.

FIRST In Television Antennas and Accessories

All rights reserved. No part of above work may be reproduced in any form except by written permission of the manufacturer.

book lists Mauritius on 7.143 with 50 watts. Does anyone hear this one?

Monaco—Radio Monte Carlo heard 0100-0300, 1300-1715 on 6.035; 0600-0800 on 9.490; m.w. channel now appears 950 kcs. (Radio Australia.) Heard on 9.495 in French from 0600. (Pearce, England.) Is listed by station as on 6.035 and 9.490. Hakansson, Sweden, notified Peddle, Newfoundland, that is scheduled 0100-0300 on 6.035, 9.490; 0600-0800 on 9.490 and 11.810; 1230-1715 on 6.035, 9.490. The 25-m. outlet (around 11.810) was recently heard by Milne in N. Z. at 0300. I heard the 6.035 outlet recently, fair level, signing off in French 1715. According to GDX-aren, Sweden, that announces in French, Spanish, and English; all I've ever heard has been in French.

Mozambique—Lourenco Marques seems to have settled on approximately 9.750 (seems high as 9.760 at times here in West Virginia—KRB), for English periods at 0000-0100 and mornings to 1100 sign-off, excellent signal on West Coast in latter period; the 9.65 channel is heard 0000-0100 in Portuguese, musical program 0000-0015, news in Portuguese 0015-0030, and musical program 0030-0100. (Rose-nauer, Calif.)

Beira's CR71B, "Aero Clube da Beira," is back on the air again after some absence; good signal on approximately 7.200 (listed 7.155V); signs off 1500; supposed to have increased power (power listed 300 watts). (Laubscher, South Africa)

New Caledonia—Radio Noumea, 6.000, heard in Hawaii at 0300 and later. (Fellers)

New Zealand—ZL3, 11.78, ZL4, 15.28, now scheduled 1300-0130, 0200-0400, 0430-0620; the 0200-0400 period is beamed for "Australia and the Islands," while other periods are used for relay of Wellington (domestic) outlets. (Legge, N. Y.)

Nicaragua—YNEW, 6.963, Managua, heard 2100-2145. (Peddle, Newfoundland.) A letter from YNXW, Radio America, Managua, says it is now on 8.192 from 6.275.5 and using only 100 watts output; uses two 80 output tubes and four 6L6's for modulation; antenna is a "Y" type. (McPheeters, YNOW, 6.850, Managua, heard leaving air 2255.) (Hankins, Pa.)

Norway—Radio Norway heard on a Sunday over 17.825 at 0800-0830 (probably daily schedule); announced as operating in 13-, 16-, 19-, and 25-m. bands (presumably 21.730, 17.825, 15.170, 11.850); English announcements 0800, 0815, and 0830 closedown; program is for Norwegians abroad. On a Wednesday heard on 11.85 at 1430 when announced frequencies in use as in 13-, 16-, 19-, and 25-m. bands. (Pearce, England.) The 15.17 channel is excellent in W. Va., afternoons.

At the time this was compiled, the daily period for Norwegians abroad (some English) at 2000-2100 was being carried over 15.17, 11.735, 9.610.

Pakistan—Radio Pakistan, 15.27, Dacca, continues to be good level here

in East in 0730 news period; news scheduled 2130, 0730, 1030. Fellers, Hawaii, still hears the 2130 news at good level. Radio Pakistan at Karachi has ceased using 6.075 and broadcasts now only on m.w. 825 kcs. and 1,460 kcs. (Lampat, India)

Panama—HORT, 6.060, Panama City, heard 2130-2230. (Peddle, Newfoundland.) HOLA, 9.505, Colon, good volume 1830-2000; program and announcements in both Spanish and English; QRA is Apartado 44, Colon, Panama. (Bachman, Pa.)

Paraguay—ZPA1, Radio del Estado, Asuncion, transmits on 6.275 with 3 kw., daily in Spanish 1000-1200, 1800-2200. ZPA5, Radio Encarnacion, now has somewhat irregular schedule, seems to be 0930-1200, 1500-1705 (early sign-off announced due to electricity shortage); frequency is 11.945. (Leven, Brazil)

Philippines—DUH-5, 11.840, Manila, was heard by me recently for the first time in several months, at 0755 with news; time signal 0800 and man identified the outlet as "The People's Station, DZFM," which is the new m.w. call, I believe.

DZH-5, 9.690, Manila, heard 1630 in Australia, poor level. (Gillett) DZH-4, 6.000, Manila, heard 0335-0445 when is blocked out by QRM. (Alfred, Ontario.) Some mornings, Manila, 9.64, is fairly good level 0700-0730 when identifies as "DZRH, Voice of the Philippines." Ferguson, N. C., reports it announces at 0630 and continues with program of dance music, fair signal.

Portugal—Emissora Nacional, approximately 15.160, Lisbon, heard signing off with Portuguese National Anthem 1430; also heard often from 1600; one day heard at 1515. (Pearce, England.) Heard by Starry, Pa., signing off 1800 with Portuguese National Anthem; also by Ferguson, N. C., announcing "Emissora Nacional" at 1100.

Radio Clube Portuguesa, CS2WI, 12.875, Parede, logged 1700 with English vocal recordings; signed off 1740 with guitar music (vocal by man in Portuguese); man and woman announcers, plenty of chimes, no English noted; one day was still on after 1800. (Pearce, England.) Heard in Newfoundland 1900-2000. (Peddle)

Lisbon, 11.027, heard 0100 to 0245 fade-out; seems to be off Sundays. (Bellington, N. Y.)

Portuguese Guinea—CQM-7, 6.993, Bissau, heard in Newfoundland 1630-1800. (Peddle)

Portuguese India—Radio Goa is again operating on 7.230 at 0900-1030; 9.610 was used for only a short time. (Radio Australia)

Rumania—Under exceptional conditions, (through heavy CWQRM, Radio Bucharest, 9.252, can be heard 1600 with news; signs off 1630 with choral music.

The 6.210 outlet has English 1500-1530. (Short-Wave Review, London.) (This also may be at 1600 now.—KRB)

Siam—Bangkok announces as "49.7 and 30.62 meters"; has news 0615; some days at least takes program in

RADIO & TELEVISION NEWS

Indonesian-Malay after 0630; frequencies at the time this was compiled were 6.010, 9.798. (N. Z. DX Times.) Both these channels are heard on occasion in the U. S.; I note on 6.010 that some days the 0615 news is by a woman, other days by a man; the 9.798 channel has severe CWQRM. The transmission for overseas listeners begins 0500, runs to at least 0630 and some days seems to continue to almost 0700. The native program is heard by Balbi on West Coast around 0700-1007; uses 9.798 for this—and either 6.010 or 6.240.

The 9.798 outlet heard in Ontario at 0530-0630, good signal; CWQRM very heavy after 0600; news in native by woman 0545-0700; uses trumpet on half-hour. (Alfred.) Around 0630 when identifies I note (on 6.010 which is best outlet here in West Virginia) the station uses NBC-like chimes. Best day for East is Sunday when there is less QRM on this band early mornings. Balbi, Calif., says Bangkok's interval signal is 6 chimes.

South Africa—Weisberg, N. Y., has just received new schedules from SABC; in part, they are Johannesburg, 4.800, weekdays 2345-0130, 1120-1605; Sundays 2455-0130, 1100-1605; 9.870 weekdays 0315-0710, 0900-1110, Sundays 0315-1050; 4.373 carries all sessions. Cape Town, 5.880 or 9.610 at 1320-1500. These are for English periods and are not complete schedules.

Spain—Verie from Radio Mediterraneo Valencia gives schedule on 7.037 as 0700-1000, 1400-1800; station opens with march "Hacia Valencia," closes with "Marcha de la Ciudad." (Gillett, Australia)

Sumatra—According to verie, Radio Palembang is on the air daily 0430-1000 on 4.855 with programs in Dutch and Indonesian; QRA is Radio Palembang, Kantoerin Studio, Talang Djawa 7, Palembang, Sumatra. (Gillett, Australia)

Surinam—PZH5, 5.758, Paramaribo, heard 1745-2030. (Peddle, New foundland)

Switzerland—Berne is no longer using 11.815, 15.320, 21.520. New schedules are HER3, 6.165, to Europe 0020-0140, 0500-0830, 1030-1700 (Sunday 0245-1700.) HER4, 9.535, to Europe 0020-0140, 0500-0830, 1030-1700 (Sunday 0245-1700); to South America, 1830-2000; to North America, 2030-2300. HEU3, 9.665, to Great Britain and Ireland 1345-1530. HEI5, 11.715, to Australia and New Zealand 0215-0445. HER5, 11.865, to Australia and New Zealand 0215-0445; to India 0945-1130; to Near East 1145-1330; to Great Britain and Ireland 1345-1530; to Spain and Portugal 1545-1715; to North America 1730-1815; to South America 1830-2000; to North America 2030-2300. HED7, 15.120, to Far East 0745-0830; to Near East 1145-1330; to Spain and Portugal 1545-1715. HER6, 15.305, to Africa 0020-0140; to Far East 0215-0445, 0745-0930; to Africa 1030-1700; to North America 1730-1815; to South America 1830-2000; to North America 2030-2300. HER7, 17.784, to Africa 0500-0730; to Far East 0745-0930; to

SPECIAL FT-237 MOUNTING

For BC-604 and 603's and for BC-584 and 683's—NEW \$9.95

ANTENNAS FOR ALL USES



TELESCOPING ANTENNA WITH

Base Insulator: Four section, steel, extends 6" to 23 1/2". Diameter taper from 1 1/4" to 3/4". Each section fitted with adjustable locking clamp. Can be adjusted to length required for freq. Brown glazed base insulator and stand off. (Illustrated at left.) Price... \$12.95

WHIP STEEL—24 ft. two piece. Bottom section 4 ft. long. Taper 3/4" to 1/2". Bottom Sec. threaded 1/4". Price... \$2.50

TELESCOPING STEEL ANTENNA—3 Sections, 94" long. Telescoped 40". Size: 3/4" to 1 1/2". Price... \$1.50

ANTENNA ROTATOR—Ideal reversible motor for rotating all types of antennas at the top. Weighs only 4 1/2 lbs. Size: 7 1/4" L. less shaft. Gear box and Mtg.: 4 1/2" x 3 1/2". Motor size: 5" L. x 2 1/4" D. Shaft size: 3/8" x 1 1/4" threaded. Operates from 24 V. DC, 2 amps. 4.5 RPM or 36 V.A.C. Torque: 70 lbs. per inch. Price... \$8.95

TRANSFORMER for above item... 2.95

SELSYN TRANSMITTER AND INDICATOR SYSTEM

Ideal as radio beam position indicator for Ham, Television, or Commercial use. Complete with five inch 1-82 Indicator, Autosyn Trans., 12 Volt 60 cycle Transformer, and wiring instructions. Price... \$9.95

SELSYN 2161—Can be used as position indicator for antennas; 110 Volt 60 cycle. With instructions. Normally operates from 57.5 Volts 400 cycle. Price per Pair... \$3.00

SELSYN 2C-78248—115 Volt AC 60 cycle. Size V 3 1/2" x 5 1/4". Can be used to turn small antennas or for position indicator systems. Price per Pair... \$5.95

DYNAMOTORS

INPUT	OUTPUT	STOCK NO.	PRICE
12 V DC	220 V 100 MA	D 402	\$3.95
12/24 V DC	440 V 300 MA and 220 V 100 MA	D 104	\$9.95
12/24 V DC	F/No. 19 MARK I	F/S 23	\$9.50
12/24 V DC	F/BC-645	PE 101	\$2.95
12/24 V DC	220 V 50 MA	D 0518	\$2.95
24 V DC	F/Comm. Receivers	DM 32	\$1.95
14 V DC	230 V 100 MA	DM 20	\$3.95
9 V DC	450 V 60 MA. with Blower	D 9450	\$3.95

MISCELLANEOUS

BC-1206 C Rec. 200-400 KC. DET. 6 tube set.	\$6.95
TU-17 or 25 for BC-223—Price: NEW.	\$1.50
Coaxial Cable—125 OHM cotton covered—50 Ft.	\$1.00
Coaxial Cable—72 OHM Rubber covered—8 Ft.	\$1.50
Cable—4 conductor, Rubber covered, shielded—50 Ft.	\$2.00
Wire—Heavy duty 2 cond. Rubber covered #14 stranded—20 Ft.	\$1.00
Wire—2 Cond. Rubber covered Tirez #16—Per Ft.	.06
BC-645 A Transceiver.	\$4.95
Plugs for BC-375—PL-64 or PL-50.	\$5.55
Autosyn RPM Indicator 3500's.	\$4.95
Autosyn Fuel Pressure Indicator.	\$4.95
Autosyn Compass Indicator 1-82.	\$6.95
AC-Meter 150 Volt 400 Cycle 2".	\$3.95
Cable for BC-223 w/PL-150 each end.	\$1.75
Cable for BC-375 w/PL-61 each end.	\$1.75
Plugs for TCS EQ/587, 65F10, or 65F13.	\$2.95
Plug for 1-82 Indicator PL-118.	\$1.00
Plugs for LP-21 Loop, PL-112 or PL-108.	\$1.00
FL-8 Filter 1200 CPS.	\$1.75
BC-1023 Marker Beacon Rec. with tubes.	\$3.79
BC-301 Marker Beacon Rec. Less tube.	\$1.95
BB-54 2 Volt Dry Cell Battery.	\$1.50
BC-778 Gibson Girl Receiver—Only.	\$4.95
CD-365 Cord for LP-21 Loop.	\$1.50

ADDRESS DEPT. RN • ALL PRICES ARE F.O.B., LIMA, OHIO • 25% DEPOSIT ON C.O.D. ORDERS

FAIR RADIO SALES

132 SOUTH MAIN ST.
LIMA, OHIO

NEW TRANSFORMERS And CHOKES

ALL FOLLOWING TRANSFORMERS
115 V.A.C. 60 CYCLE INPUT

OUTPUT: 750-0-750 V.A.C. (600 V.D.C. after choke input filter at 250 MA.). Includes 6.3 V.A.C. winding at 5 amps and 5.0 V.A.C. winding at 4 amps. NH-106... \$7.95

OUTPUT: 600-0-600 V.A.C. at 250 MA., 12 V.A.C. at 3 amps; 12 V.A.C. at 3 amps and 5 V.A.C. at 3 amps. Designed for Army surplus transmitters. NH-108... \$6.90

OUTPUT: 250-0-250 V.A.C. at 60 MA., 24 V.A.C. at .6 amps; 6.3 V.A.C. at .6 amps. Designed for Army surplus Receivers. NH-109... \$3.00

OUTPUT: 6.3 V.A.C. at 6 amps. NH-110... \$2.25

OUTPUT: 24 V.A.C. at 2 amps. NH-111... \$2.25

CHOKES:

NH-115—8 Henries at 500 MA. filter choke, 5,000 volt insulation... \$8.67

NH-116—5-20 Henries 500 MA. swinging choke, 5,000 volt insulation... \$8.37

NH-117—8 Henries at 700 MA. filter choke, 7,500 volt insulation... \$12.90

NH-118—5-20 Henries at 700 MA. swinging choke, 7,500 volt insulation... \$12.45

ALL ABOVE ITEMS BRAND NEW—NOT SURPLUS!

WRITE FOR COMPLETE LIST OF HIGH VOLTAGE TRANSFORMERS AND CHOKES

INVERTER MG-149F

Input 24 Volt DC; Output 28 Volt DC, 250 VA 400 cycle, or 115 V. 400 cycle 500 VA. Appear to be unused; are re-refinished and tested. Price... \$14.95

TRANSFORMERS—110 Volt 60 Cycle Primaries:

Sec. 12 V. 1 amp.	\$1.50
Sec. 24 V. 1 amp.	1.95
Sec. 24 V. .5 amp.	1.50
Sec. 36 V.A.C. 2.5 amp.	2.95
Sec. 14-14 or 28 Volt—7 1/2 or 15 amp.	4.95

COMMAND RECEIVER & TRANSMITTER SETS AND ACCESSORIES

BC-454, 3 to 6 MC. USED... \$5.95

BC-455, 6 to 9.1 MC. USED... 6.95

DYN-6V, Can be used for Comm. Rec. # 0515... 2.95

TRANSFORMER NH-109 for Comm. Rec. 110 V... 3.00

TRIPLER REC. RACK—black... 1.50

TUNING CRANK or Knob... .65

CONTROL BOX BC-450... 1.95

CONTROL BOX BC-451... 1.50

Connector Pins—Male or Female—Per Doz... .60

BC-458, 5.3 to 7 MC. NEW: \$8.95... \$5.95

USED: T/20 ARC-5, 4 to 5.3 MC. NEW: \$9.95... \$9.95

BC-456 MODULATOR—Like New... 6.95

DUAL TRANSMITTER RACK—New... 2.50

TRANSFORMER NH-108 for Comm. Trans... 1.50

BC-442 Antenna Relay Box w/cond. New... 2.95

AC POWER SUPPLY AND SPEAKER

Completely wired power supply and speaker with volume control C.W. and on & off switch, housed in metal cabinet. For command receivers with connections to plus into receiver and 110 Volt 60 cycle line. Voltage output: 250 V. 60 MA., 6.3 V. and 24 V. Price: Completely wired... \$14.95

Kit of Parts... 9.95

MOTORS

6 or 12 Volt AC-DC Heavy Duty reversible motor with 3/8" x 1/2" shaft. Price: NEW... \$2.95

6 Volt AC-DC Motor—ideal for auto fans, models, etc. Shaft 3/8" x 3/4". Used—Tested... \$1.50

110 Volt 60 Cycle 1750 RPM Motor for fans or blower. Motor Size: 3" x 3". Shaft Size: 3/8" x 1". Price—NEW... \$4.95

NOW AVAILABLE AT ATTRACTIVE PRICES •

MARK II No. 19 RADIO SETS AND ACCESSORIES!

POLICE FM ALARM

FOR POLICE CALLS TAXI CABS AND OTHERS

Tunes 152-162 Megacycles

F. M. Superheterodyne, 115 Volts, A.C.-D.C. Tubes—12AT7, (2) 6B6, 19T8, 35B5, 35W4. 2 stages high gain 10.7 Megacycle I.F.'s. Ratio detector. Plastic cabinet 10 1/2 x 6 3/4 x 6 deep. Schematic and instructions. Shipping weight 7 lbs.

Sensitivity 10 Microvolts or better. Selectivity 250 K.C.'s or better.

Reception expectancy with attached antenna from 50 Watt transmitter 3 miles, much farther from transmitter of more power or outside antenna.

Ready to plug in and use; 28 Watts power consumption.

SEE YOUR DEALER FIRST OR WRITE

DELUXE CA-2 COAXIAL ANTENNA

FOR BEST RECEPTION—LIST

\$5

RADIO APPARATUS CORP.



303 FOUNTAIN SQ THEATER BLDG.

INDIANAPOLIS 3, INDIANA

20 to 28 MC FM RECEIVER BC-603 for 11 meters; can be tuned to 10 meters with slight modification; superhet, BFO, squelch; 10 push-buttons and manual tuning. Makes 10 meter converter or IF strip for 88-108 MC wide-band FM; with all tubes, speaker, case, diagram. **FREE CONVERSION INSTRUCTIONS.**

UNUSED.....\$19.95
USED, Excellent.....17.95
USED, Good.....14.95

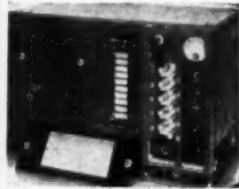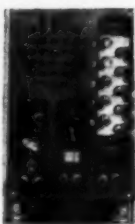DYNAMOTOR DM-34, 12 V input, when purchased with receiver.....\$3.00



20 to 28 MC FM TRANSMITTER BC-604 for 11 & 15 meters; can be operated on 10 meters by use of proper crystal; 10 channel; with all tubes, meter, diagram, case and covers; less xtals and drawer.

USED, Excellent w/dyn.....\$19.95
USED, Good, w/dyn.....15.95
USED, Good, w/o dyn.....12.95

BC-684 TRANSMITTER 27 to 38.9 MC; 30 watt 10 channel (as above); with covers, tubes, meter, diagram; less crystals and drawer.
U-1 with dynamotor \$34.95 Without dyn \$32.95
U-2 with dynamotor 29.95 Without dyn 27.95

PLUG. Cannon female fits into any of above FM sets. Does away with Mounting FT-237.....\$2.45

FM PORTABLE TRANSCEIVER BC-620, 20 to 27.9 Mc for 11 & 15 meters; can be extended to 10 meters by adjusting IF's; similar to BC-659, but has no built-in speaker.
UNUSED, original cartons.....\$19.95
LIKE NEW.....14.95

VIBRATOR POWER SUPPLY PE-120 for BC-650 & BC-620; operates from 6, 12 or 24 volts, depending on vibrator; with 12 or 24 v. vibrator, battery cable & plug. UNUSED.....\$12.95
Used, good.....\$9.95; Used, fair.....7.95



BELL, 24v AC or DC; 3" dia. with self-contained ringer coils & hammer; external flange for mounting. New, boxed, BLACK, 10 for \$8.50. \$1.00
CHROME PLATED, 10 for \$10. Each.....\$1.25

VIBRATOR, Rauland or Vokar JV-0014; "heart of PE-237" for SCR-604; input 6, 12 or 24v DC; 2 1/2"x2 1/4"x 5 1/2". NEW, boxed.....\$4.95



CABINET, 11 1/2"x6 1/2"x7 3/4"; slide-rule dial opening 7 3/4"x 1 1/2"; plastic, in 3 colors: ALL BROWN, 10 for \$8. Each.....\$0.89
BROWN, WHITE GRILLE.....1.05
ALL WHITE.....1.19



TROUBLE LIGHT for portable or permanent installation; has spring-operated pay-out reel & 6 ft. cord which can be maintained at desired length by window-shade action; ideal for mounting under hood of car, on workbench or in darkroom; lamp head has double-contact

bayonet socket for 6, 12 or 24v lamp & filters for clear, diffused or red light. A gadget with 100 uses. At this price you should have several. COMPLETE INSTRUCTIONS FOR INSTALLATION.
NEW.....2 for \$8. EACH.....\$3.50

M-1, new; U-1, used, excel; U-2, used, good

TERMS Postage extra. Please, minimum order \$2.00. Net Cash, 25% deposit on C.O.D.'s. FREE LIST.

ELECTRONIC SUPPLIES

219 East 1st St. Tulsa 3, Okla.

India 0945-1130; to North America 1730-1815. (Legge, N. Y.)

United Nations Radio, 6.672, Geneva, still has news daily except Sunday 1330. (ISWC)

Syria—Damascus has replaced 7.500 with 7.275. (Swedish DX.) The 12.000, 7.275, 6.000, and m.w. 592 kcs. and 752 kcs. are scheduled now daily 0730-0800 in English and 0800-0830 in French. (Radio Australia.) (This is probably not complete schedule.—KRB) The station informed Rugtvedt, Norway, it transmits 0000-0100 Arabic; 0645-0730 Arabic; 0730-0830 English and French; 1100-1545 Arabic. Milne, N. Z. reports the 6.000 outlet heard 0630 in Arabic.

Tangiers—Radio International, now on 6.110 from 6.115, heard from 1730 recently; call given in Spanish by man, in French by woman; still going 1915 with Spanish; during weekdays is heard at 1430 in Arabic. (Pearce, England)

Turkey—TAP, 9.465, Ankara, heard in England with English 1445.

Uruguay—CXA-19, 11.835, Montevideo, gives special news bulletin in Spanish for overseas listeners 1700-1730; announcements made in Spanish, French, and English. (Swedish DX)

U. S. A.—Latest AFRS schedules of East Coast transmitters include 1415-1745, WNRX, 11.89, to Europe, N. Germany, Norway, Sweden; 1400-1745, WRCA, 15.15, to C. Europe, France, Germany, Poland; 1400-1745, WBOS, 15.21, to Mediterranean, N. Africa, Turkey, Palestine, and 1400-1745, WGEX, 17.88, to S. Europe, Spain, Austria, Italy, Balkans. (Worris, N. Y.)

U. S. S. R.—Moscow begins a one-hour broadcast to India and other parts of Asia at 0700 on announced 15.340, 9.690, 6.180; latter can't be heard in Australia, other two heard well. (Gillett.) The 15.340 channel is good level here in West Virginia during this 0700-0800 (English) period.

Norris, Beirut, Lebanon, reports he recently logged Moscow on 15.212 (measured) with good signal at 1000-1030 in a Slavic tongue.

A Soviet station is being heard on approximately 10.50, strong, at 0515-0630, Chinese at 0600, parallel with 11.750. (Balbi, Calif.)

Radio Moscow presents a short Mailbag Program (no names mentioned) on Saturdays around 1908 on 15.23, 11.88, 11.72, 7.36, 7.29; 11.72 best. (Boice, Conn.)

Venezuela—Verie letter in Spanish from "La Voz de Carabobo," Valencia, gives new call on 4.780 as YVLA and on 1.350 kcs. as YVLB (formerly YV4RA and YV4RO, respectively). (McPheeters, La.)

Unidentified—A station has been heard on approximately 17.800 (just below 17.810 BBC), fading in 1115, sounds like AIR, still going 1210 but with BBC interfering. (Stark, Texas.) This is likely VUD7, 17.800, now scheduled 1110-1315.

Bellington, N. Y., reports a station on about 8.82 testing at 2135 tune-in,

fair signal but was right atop a Cuban station listed COCQ; played popular American recordings and other songs including some Spanish numbers; announced song titles in English; at 2140, with no announcement whatsoever, station disappeared. He also reports a station on about 9.54 testing 2330 sign-on; tremendous signal but had transmitter trouble and bad needle scratch from recordings; was in clear; signed off 0010; no announcements made. I wonder if this could have been ZL2, 9.54, Wellington, New Zealand, testing?

During the spring I have been hearing a very faint station mornings on 11.850 (not Delhi!) which I'm wondering if possibly might be former XORA, Shanghai. (Any data as to Shanghai's whereabouts on s.w. and current schedule would be welcomed.—KRB)

Last Minute Tips

Has the high-powered projected station at Fernando Po, off the West Coast of Africa, been heard testing yet? (I would appreciate any information on this one if it is heard.—KRB) The Radio Atlantico reported by NNRC some time ago as heard testing may have been Radio Atlantis, Tangiers, on 14.420.

A station heard by Dilg, Calif., on approximately 7.520, signing off 1000 with Dutch National Anthem may be Bandoeng or some other Indonesian; plays a lot of old American popular recordings, Dilg says.

SABC recently notified Laubscher, South Africa, that they still do not have call signs.

Pearce, England, observes that special broadcasts for overseas listeners at 1400-1500 from AIR, Delhi, are radiated on (announced) 15.17, 11.85, 11.76, 9.63; but says, however, that the 25-m. channels appear to be actually 11.76 and 11.79 (not 11.85).

Shortly before this was compiled, I received a flash from Anson Boice, Connecticut, that he was hearing a good signal daily from ZUD, Victoria, South Africa, testing on 17.748; said carrier comes on around 1300; occasional spot announcements to 1400, then may present SABC program or recordings; were calling BBC one day at 1425; said signs off daily 1430. A later flash on this from Boice says is still testing daily except Sunday on 17.748 at 1400-1430, R-9 signal.

For several months the Deccan Hyderabad station has been operating only on 730 kcs. m.w. (Radio Australia)

A new station reported by Indian correspondents to Radio Australia is at Jodhpur in Rajputana; announces as operating on 80 meters and is scheduled 0800-0930 except Sunday when is on the air 0800-1000; there are no regular English language programs but talks in that language are given on occasions; signs off with well-known Bengali National Anthem.

Gaynor, Calif., says he gets a strong station from Tiajuna, Baja California (Lower California, in Mexico) around

49 evenings; generally catches this one around 2000; says Spanish is too fast to get call letters.

All India Radio, 11.79, is putting in an average R8 signal in Connecticut 1845-1900. (Boice.) Also reported by Fuller, R. I., and Ferguson, N. C. Listed officially as in Indonesian, as experimental, and as on 15.17, 11.79.

DX-Radio, Sveriges Radioklubb, Sweden, reports Shanghai as on 11.870. (Can anyone confirm?—KRB)

A NNRC member has received a letter from Major Leslie Knight, Chief Broadcasting Officer, HQ Forces Broadcasting Service, MELF, Malta Garrison, which in part reads—"The latest news on the Forces Broadcasting Service, MELF, is that we are endeavoring to install three RCA ET-4750 transmitters in Malta, but owing to lack of technicians the progress is extremely slow. However, when the installation is complete, we shall endeavor to beam our transmissions so as to cover the whole of the Eastern Mediterranean. We anticipate to be transmitting by the end of March. We are now in the process of obtaining the necessary frequencies and as soon as these are finalized, I will give you full details." It was stated that Mombasa in East Africa is operating with a BC-610 transmitter, 250 watts, on 7.220; other stations in the network include m.w. outlets in Tripoli, Benghazi, Kabrit, and Cyprus. Benghazi was listed on 6.130 s.w. with 250 watts. Major Knight said: "These stations will continue to operate when the main transmitters at Malta are working but will relay transmissions of the main service."

Tips received at press time from Balbi, Calif., include—BEA8, 9.73, Nanking, now signs off around 1010 or 1015, excellent signal; JBD3, 15.225, Tokyo, has replaced JBD, 9.505, from 0300 on. Radio Ceylon, 15.12 and 17.73 now sign off 1200 instead of former 1130. Paris, 21.74, heard irregularly around 1030-1100 in French only. OIX4, 15.19, Helsinki, again heard with fine level 2200-2400, not on 17.78 any longer. DUZ5, 11.84, Manila, heard with good signal from 0400 on. XRR4, 10.26, Peiping, heard to 1030 irregularly.

ZRB, SAAF station, Pretoria, South Africa, at last is using 6.210 in parallel with 9.110. (Laubscher, South Africa)

XEQQ, 9.680, Mexico City, now seems to have an English-compered program on Saturdays 2230 or 2245 to 2315 or 2330; asks for reports to P.O. Box 940, Mexico City; program is called "South of the Border" and features hit tunes of the week from U.S.A. and Mexico. (Hankins, Pa.)

Late tips received airmail from Lampat, India, include—Radio Kashmir is transmitting on approximately 61.79 meters, leaves the air 1100; Radio Goa now operates on 7.230 at 0900-1030, closing with Portuguese National Anthem, broadcasts in Portuguese, Konkani, Urdu, Marathi, and Gujarati, is 500 watts. Deccan Radio in Hyderabad is not broadcasting on

s.w. 6.170 and 3.335 any longer; only on 411 meters with 5 kw.; in case this one returns to the air on s.w., it probably will be scheduled with the m.w. transmitter (which features English news 2210, 1000, and ends transmission at 1230).

Finally, these tips from Dorothy Sanderson, Australia, are offered—XGYA, 7.990, heard 0535 with Chinese news relay from XNCR; BCAF heard on 8.990 at 0545 with Western music, then in Chinese, and with English lesson on Wednesdays 0610-0645; DZH5, 9.69, Manila, heard 0515 with musical program and frequency details; DZRH, 9.64, heard 0530; DUH5, 11.84, heard 0515 with sponsored program of music

and news; DZH4, 6.000, heard 0545 with sponsored program; Saigon, 7.21, heard 0605 with news in French; Shiras, Fars, Iran, heard on 7.96 at 1545, bugle call and time pips, with Persian program (not on daily); SUX, 7.86, Cairo, heard 1530 with usual Arabic-type program of music and news; Johannesburg, 4.89, heard 1545, good signal; CR7BU, 4.91, Lourenco Marques, Mozambique, excellent in Australia 1530 in Portuguese.

Acknowledgement

Many thanks for all reports; keep them coming to 948 Stewartstown Road, Morgantown, West Virginia, U.S.A. K.R.B.

SURPLUS
GEAR

TV Builders! Hams! Servicemen!

NOW YOU CAN SAVE

← TWO WAYS →

AT R & M RADIO

STANDARD
EQUIPMENT
AND
PARTS

Save on equipment and replacement parts. Our stocks are as complete as they come: all ham gear, receivers, transmitters, all types of resistors, condensers, transformers and tubes; test equipment for the builder and experimenter. WRITE for monthly specials, bulletins, and price lists. Attention, Authorized Servicemen: Special bulletin and price list available!

All equipment F.O.B. 25% deposit or save C.O.D. charges by remitting in full.


T-17
CARBON
MIKE

Brand New
\$1.25
Each



HEAD
PHONES


69c
Used
\$3.50
Brand New

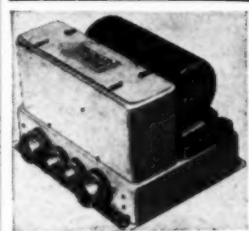

SPEECH AMPLIFIER

Modulator for Transmitter
High Volt. DC Power Supply
Model unit, BC-466-A or B
with dynamotor DM-33-A,
plugs and tubes. Approx. wt.
17 lbs. Tube line-up, 12J5GT,
1625, VR150, and many other
parts make this ideal purchase
for spare parts alone.
Diagram furnished. **\$3.75**

APN-4
RCVR
SCOPE
POWER
SUPPLY

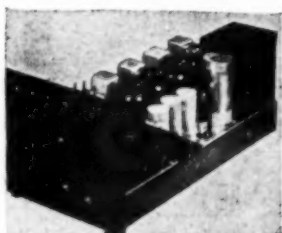

4 switch-selected screw-driver tuned RF channels; IF
freq. 1050 kc, band-width 45-60 kc; RF freq. 16 2000 kc.
Tubes: (2) 2Y2, (3) 6B4, (4) 6SK7, (1) ea. 5U4, 6SU7,
6SA7, 6H6, VR150. Makes fixed tuner for med. freq. police
calls or PA system. Has power supply for 5" scope, with
400 cycle trans. Electronic-controlled low v. supply; delivers
260 vdc. 150 ma. reg. to .01%. Power
supply alone worth more than price **\$8.95**

20% additional discount
on purchases of \$5 or more

TRANSFORMERS

For converting SCR-274-N to 115
Volts AC.

No. 1 Power Transformer. Primary
115v 60 cycle; sec—500 CT .06 Amp.
24v—1/2 amp.
Price only **\$3.90**

No. 2 Filament Transformer. Pri—
115v 60 cycle; Sec. 1—14v 7 1/2 amp.;
sec. 2 14v 7 1/2 amp. Series 28v 7 1/2
amp. Parallel 14v 15 amp.
Price only **\$4.50**

No. 3 Filament XMFR. Pri—115v
60 cycle; Sec. 24v 2 amps.
Price only **\$2.25**

• Speakers—Brand New

Permanent Magnet
4" **\$1.60**
5" **1.85**
12" Jensen in Metal Case **14.50**

• Heavy Duty Transmitting Chokes

8 HY—500 MA—5000 V INS.
Price each **\$8.95**

• Condensers—Fixed

.05 Mfd. 600 Volts	\$0.15
10 Mfd. 350 Volts	.69
15 Mfd. 150 Volts	.60
16 x 16 450 Volts	1.20
20 250 Volts	.69
40 150 Volts	.75
50 150 Volts	.69
150 25 Volts	.54
200 10 Volts	.45
8 x 8 Can. Electrolytic	1.50

Tubes (New, in Original Cartons).

12A6	69c	ODS-VF150	75c
12SR7	69c	12SA7	69c
12K8	69c	77	59c
12SK7	69c	78	59c
12SF7	69c	89	59c
1625	89c	38322	\$1.19
1626	79c	12J5-GT	69c
1629	89c		

R & M RADIO COMPANY

2701 WILSON BLVD. DEPT. RN-69 ARLINGTON, VIRGINIA

COMPARISON PROVES

AMERTRAN H.V. PLATE TRANSF. 1500-0-1500 volts 600 MA Pri. 110/220V 60 cycles. Continuous Duty. Fully Cased. 3 KV Insulation. Limited Quantity. **\$19.95**

PLATE AND FIL. Transf. Pri. 110V 60 Cy. Sec. 1120 V CT @ 600MA. 6.3 V @ 3A. 2x5V @ 6A. **\$9.95**

UTC type FA 5000 ohm plate to 500 ohm line and 6 ohm voice coil. 10 watts, 60 to 10,000 cps. 1 DB. GREAT VALUE. **\$2.75**

THORADSON PLATE TRANSF. 2370 volts CT at 250 MA tapped at 300-0-300 volts, plus 215 volt 55 MA bias winding. 110 volt 60 cy. pri. Fully shielded. **\$11.95**

AMERTRAN PLATE TRANSFORMER 1500-1250-0-1250-1500 Volts at 1.5 amps. Continuous Duty. Pri. 110/220 V. 60 cycles. Fully Cased. 5 KV Insulation. **\$39.95**

HIGH CURRENT TRANSF. 820 Volts CT at 775 Ma. Pri. 110/220 Volts 60 cycles. Fully Cased. Wt. 35 lbs. **\$6.95**

SELSYN MOTORS 115 volts 60 cycles, large size. 3 1/2" diameter by 5 1/2" high. Can rotate small beam antenna. Made by Bendix and Diehl. Transmitters only. Terrific value. **\$6.95**

STANDARD "METERS" BRAND NEW


2" 0-5 ma Basic. \$1.95	2" 0-200 microamp. \$4.50
2" 0-3 volts DC. 2.45	3" 0-50 amps AC. 4.95
2" 150-0-150 microamp. 3.49	3" 0-100 ma. 3.50
2" 0-30 amp DC. 2.45	3" 0-80 ma. 2.95
2" 0-1 ma Basic. 2.95	3" 0-75 amp AC. 3.95
2" 0-20 ma Basic. 1.75	3" 0-2 ma DC. 3.95
2" 0-500 ma. 1.95	3" 0-200 ma DC. 3.95
2" 0-10V AC. 2.50	3" 0-1 ma DC. 3.95
2" 0-30 V AC. 2.50	3" 0-20 ma DC. 3.95
2" 0-1 Amp R.F. 2.45	3" 0-15 ma DC. 3.95
	3" 0-150 V AC. 3.95

OIL CONDENSERS

20 mfd 330 vdc. \$1.95	15 mfd 1000 vdc. \$2.95
1 mfd 600 vdc. .25	2 mfd 1500 vdc. 1.25
2 mfd 600 vdc. .39	6 mfd 1500 vdc. 1.95
4 mfd 600 vdc. .59	1 mfd 2000 vdc. 1.45
6 mfd 600 vdc. .79	2 mfd 2000 vdc. 2.25
3/3 mfd 600 vdc. .79	4 mfd 2000 vdc. 3.65
10 mfd 600 vdc. .95	6 mfd 2000 vdc. 3.95
2 mfd 1000 vdc. .79	2 mfd 4000 vdc. 5.50
4 mfd 1000 vdc. .95	1 mfd 5000 vdc. 3.95

CHOKES BARGAINS

6 Henry 50 ma 300 ohms. 3 for \$0.99	
6 Henry 80 ma 230 ohms. 2 for .99	
8 Henry 160 ma 140 ohms. .99	
1.5 Henry 250 ma 72 ohms. .59	
6 Henry 300 ma 65 ohms. 3.75	
4.3 Henry 620 ma 42 ohms. 6.95	
Swing Choke 1.6/12 Henry 1 Amp/100 ma 15 ohm. 24.50	
.07 Henry 7 amps .5 ohm. 4.50	

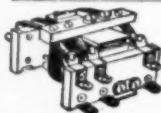

ADVANCE

D.P.D.T.

ANTENNA RELAY

110 V. 60 cycle coil Steatite insulation. Only **\$1.95** each.

As above but 3 P D T. **\$2.75**

FILAMENT TRANSFORMERS

110 Volt 60 cy Pri.—Fully Cased.	
6.3 V 10 Amps. \$1.89	
5 Volts 15 Amps. \$1.75	
2.5 Volts 10 Amps. 4.95	
2.5 Volts Ct 21 Amps. 4.95	

MULTI-SECONDARIES

5 1/2 V Ct 21 Amp. 7.5V 6A 7.5V 6A. \$5.95	
6.3V 21 Amp. 6.3V 2A. 2.5V 2A. 4.75	
5 Volts 4A. 6.3 volts 3A. 2.50	
2.5V Ct 20 Amps. 2.5VCT 20A. 7.95	
2.5V Ct 10A. 6.3V 1A. 5V 3A. 5V 3A. 4.50	

SOLA CONST. VOLTAGE TRANS. Pri. 95-125V. 60 Cy., Sec. 115V. reg., 120 V.A. **\$16.50** ea.

DUNCO RELAY DPDT 6Volt 60 cycle coil **\$1.39**

30 WATT WIRE WOUND RESISTORS

Ohms: 100-150-1500-2500-3k-4k-4500-5k-5300-10k-15k-18k-40k. **.15 ea. 8 for .99**

HERE'S VALUE

.004 1000 VDC Micas. 10 for \$8.99	
.01 600 VDC Micas. 10 for .99	
1000 mfd 25 VDC Electrolytics. 3 for .99	
2 Meg. 1/2 1% Meter Multip. IRC. 1.95	
25 Ma. Littlefuses. 15 for .99	
ERIE .0005 Ceramleons. 15 for .99	
C-D 1 Mfd 400 VDC oil Tubulars. 10 for .99	
.0015 5% Silver Micas. 10 for .99	
JAN 6C4 Tubes. New Boxed. 4 for .99	
Heinemann 5 Amp 110VAC CKT BRKR. .99	
Heinemann 25 Amp 110VAC CKT BRKR. 1.29	
2 Mfd 250 VAC Condensers. 6 for .99	
TRIM "Commercial" Head Phones. 3.75	
10 Meg 10 Watt Resistor. .99	
.02-400VDC Tubulars. 15 for .99	
Allied DPDT 24VDC Relays. .39	
MU Switch with Roller SPST 15A 110VAC. .39	
C-H Toggle DPST 20 Amp 260VAC. .85	

If not rated, 25% with order, balance C.O.D.—Minimum order \$3.00.

PEAK ELECTRONICS CO.

188 WASHINGTON STREET, DEPT. MR
NEW YORK 7, N. Y.

Mac's Service Shop

(Continued from page 60)

"Is there any good way to test or compare boosters?"

"One way is to run a signal from a signal generator into the booster with a 300-ohm resistor across its output. The r.f. probe of the VTVM can be used to measure the input and output voltages and so arrive at the gain. By shifting the frequency of the signal generator and plotting the consequent changes in output voltages, you can get a rough idea of the bandwidth. A better way to do this is to put in a signal from a TV sweep generator with about a ten-megacycle sweep and to pick off this amplified signal from across the 300-ohm load resistor with a crystal diode probe feeding into your 'scope. That way the response curve can actually be seen, and you can use marker pips to tell exactly at which frequency it peaks, dips, etc."

"Why is it that the same booster wants to oscillate on some receivers and not on others?"

"Very probably it is the antenna that makes the difference. The input circuit of the booster is designed to be loaded with the 300-ohm load of the lead-in. If the lead-in has standing waves on it, the impedance at the booster may be much higher and afford little or no loading, and the booster will want to oscillate. Incidentally, when a booster is on the edge of oscillation, its normal bandwidth is considerably narrowed, for

regeneration sharpens up the response."

"Hey, Boss," Barney said suddenly, "see if you can explain this one: The other night I was visiting a guy who owned a TV set, and the joker had three boosters lined up on the floor in front of the receiver. He had the dial reading and the position of each booster written down on a card for every live channel, and he followed this to the letter. For example, when he went from channel 5 to channel 4, he swung the booster nearest the set forty-five degrees out of line with the other two; and the picture was twice as good as it was when the booster was moved back into line."

"That sounds wacky," Mac chuckled, "but I think I understand it. Moving the booster changed the coupling, and hence the regeneration, between it and the other units. This change in regeneration increased the gain when the booster was in the critical position and so improved the picture."

"What do you think of cascaded boosters? Isn't one enough?"

"All I know is what I have seen, and I know cases where two or even three boosters got a picture when one could not do it. The effect is apparently the same as you get with stagger-tuning in the i.f. stages. The over-all gain is not much greater than that of a single sharply-tuned unit, but the response curve of the group is much better—hey!" Mac broke off, "aren't you listening?"

"Sure," Barney told him, "but I was just wondering if I couldn't borrow a balloon off of one of those bubble-dancers down at the Bijou!" —50—

CHECKING AUTO TYPE VIBRATORS FOR CONTACT BOUNCE

By ALLAN S. JOFFE, W3KBM

IT IS often interesting to check a vibrator when faulty operation is indicated to see if contact bounce is present. According to some, this condition can lead to low output, eventual sticking or welding of contacts due to excessive heat and wear, and a certain amount of hash due to excessive sparking.

When checking this condition with a cathode-ray oscilloscope, the suggested methods lead to confusing patterns not easy to interpret. With this in mind, the following method was developed.


The circuit shown represents a resistor of approximately .5 megohms and a condenser, plus a series battery of about 45 volts. This series combination is shunted across the pair of contacts under investigation. The alternate shunting and opening of the vibrating contacts results in a saw-tooth across the condenser. This voltage is then applied to the vertical input of an oscilloscope which will display the pattern in Fig. 1B if no bounce is present. If bounce is present, however, the pattern of Fig. 1C will be developed, the small saw-tooth being the result of the contact bounce. Its amplitude is smaller than that of the main saw-tooth because of the smaller charge time allowed the condenser.

The condenser may have a value of

from .1 to .5 μ fd. The relative amplitudes of the large and the small saw-tooth is an approximate measure of the degree of contact bounce present. This method also makes it very easy to determine if the particular vibrator will give proper operation when mounted off the vertical.

—50—

Fig. 1. Circuit arrangement for checking vibrator, along with oscilloscope pattern with and without bounce effect. The function of the series resistor is that of limiting the current from the battery when the contacts are closed.

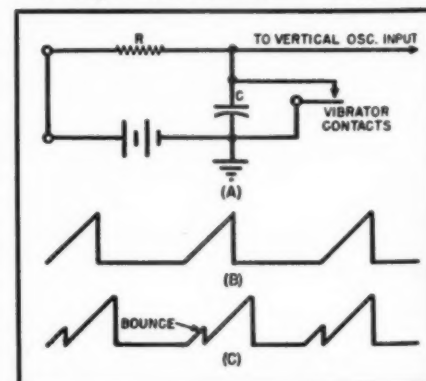

Signal Marker

(Continued from page 55)

visible to change the capacitance to some lower maximum value, such as 15 or 20 μfd . At considerably higher frequencies, when lower-capacitance tuning units are used, the frequency spread will be reduced, due to the lower ratio of minimum-to-maximum capacitance in the tuning condenser. At considerably lower frequencies, it will be necessary to change tuning condenser C_1 to a higher maximum capacitance unit, say 250 to 500 μfd . The values of inductance required to cover a specified frequency range with a given tuning condenser may be found from any of the *reactance charts* appearing in the various radio handbooks.

Additional Applications

Because they are interested in maximum utility, servicemen and experimenters, after reading the functions of an instrument, usually want to know what else the device will do. With this in mind, we list below several additional functions which will be performed by the signal marker.


1. *Wavetrap and interference eliminator.* Connected between antenna and receiver, the marker acts as a conventional wavetrap and as such may be used to remove or reduce an interfering signal, or to identify the frequency of such a signal.

2. *Frequency spotter.* Connected between an uncalibrated, modulated oscillator and a simple monitor (such as crystal detector and headphones), the marker serves as a rough frequency checker within its tuning range. To operate, tune the marker to eliminate (or reduce) the signal in the monitor, and read the unknown frequency from the marker dial.

3. *Filter.* The marker will serve as a simple narrow-band-elimination filter when connected in series with two stages or between two suitable circuit points. Its use in this manner is somewhat limited, however, since the marker circuit does not offer large attenuation to strong signals.

4. *Harmonic eliminator.* When connected between stages or between two suitable circuit points, the signal marker will serve to remove or reduce troublesome harmonics which lie within its tuning range.

-30-

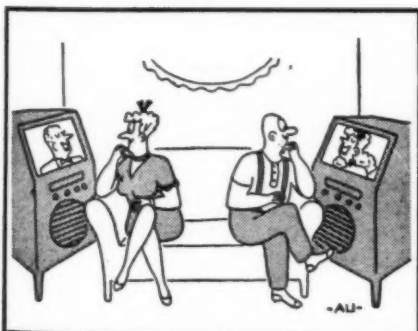

TUBES! NATIONALLY ADVERTISED BRANDS TUBES!

RCA — Kenrad — Sylvania — Tung-Sol — National Union — Raytheon — Philco — Hytron
All new tubes, 100% guaranteed, individually boxed.


REMEMBER—OUR TUBES ARE FULLY GUARANTEED. EVERY TUBE IS BRAND NEW. These Tubes Are NOT Manufacturer's Rejects or Seconds.

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
0A4G	\$.90	2X2	\$.18	6K6GT	\$.54	6Y7G	\$.15	12C8	\$.15
01A	\$.60	3A4	\$.75	6K7G	\$.50	6Z7G	1.40	12H6	\$.65
02A	\$.80	3B7/1291	\$.96	6K8	\$.55	6Z8G	1.40	12H6GT	\$.65
1A3	\$.80	3D6/1299	\$.96	6L5G	\$.96	7A4	\$.72	12J5GT	\$.54
1A4P	1.40	3Q4	\$.80	6L6	1.28	7A5	\$.72	12K7GT	\$.60
1A5GT	\$.65	3Q5GT	\$.85	6L6A	1.15	7A6	\$.65	12K8	\$.65
1A6	1.15	3S4	\$.75	6L7	1.15	7A7	\$.72	12Q7GT	\$.65
1A7GT	1.15	3R4GT	1.15	6N7	\$.85	7A8	\$.72	12SA7GT	\$.65
1B4P	1.40	3T4	1.40	6P5GT	\$.80	7B4	\$.72	12SC7	\$.80
1B5/25B	1.15	3U4G	\$.34	6Q7	\$.72	7B5	\$.72	12SF5	\$.65
1C5GT	\$.80	3V4G	\$.85	6R7	\$.96	7B6	\$.72	12SF7	\$.72
1C6	1.15	3W4	\$.96	6R7GT	\$.65	7B7	\$.72	12SG7	\$.72
1C7	1.15	3X4G	\$.85	6S7	\$.96	7B8	\$.72	12SH7	\$.80
1D5GP	1.40	3Y3GT	\$.45	6S8GT	\$.85	7C3	\$.72	12S17	\$.60
1D7G	1.15	3Y4G	\$.34	6SA7GT	\$.60	7C7	\$.72	12SK7GT	\$.60
1D8GP	1.40	3Z3	\$.85	6SB7-Y	\$.85	7C7	\$.72	12SL7GT	\$.85
1E5GP	1.40	3Z4	\$.96	6SC7	\$.72	7E6	\$.72	12SN7GT	\$.80
1E7GT	1.40	3A4	\$.96	6SD7GT	1.15	7E7	\$.80	12SQ7GT	1.40
1F4	\$.96	6A4/LA	\$.96	6SF5	\$.72	7F7	\$.80	12SR7	\$.80
1F5G	\$.96	6A6	\$.96	6SF7	\$.72	7F8	\$.80	12T3	\$.96
1G4	\$.96	6A7	\$.72	6SG7	\$.72	7G7	1.15	12T3(623)	1.15
1G6GT	\$.96	6A8GT	\$.72	6SH7	\$.80	7H7	\$.72	14A4	\$.96
1H4G	\$.80	6A87	1.15	6SJ7	\$.60	7J7	\$.96	14A7	\$.80
1H5GT	1.15	6A7G	\$.96	6SK7GT	\$.80	7L7	\$.80	14B6	\$.80
1H6G	1.15	6A7G	\$.96	6SL7GT	\$.85	7N7	\$.80	14C7	\$.80
1J6G	\$.96	6AF6G	\$.96	6SN7GT	\$.80	7Q7	\$.85	14F7	\$.80
1L4	\$.72	6AG5	1.25	6SQ7	\$.80	7V7	\$.96	14H7	\$.80
1L4A	\$.96	6AG7	1.15	6SR7	\$.85	7W7	\$.96	14I7	\$.96
1L4B	\$.96	6AK3	1.25	6S87	\$.85	7X7	\$.96	14J7	\$.96
1L4C	\$.96	6AL3	1.25	6S97	\$.85	(XXFM)	\$.96	14Q7	\$.96
1L4D	\$.96	6AL7	\$.96	6SV7	1.15	7Y4	\$.72	14R7	\$.80
1L4E	\$.96	6AQ7	\$.80	6T7G	1.15	7Z4	\$.72	14W7	\$.96
1L4F	\$.96	6AT6	\$.54	6U5	\$.72	10	1.40	19	1.15
1L4H	\$.96	6B40	\$.96	6U6	\$.65	12A	\$.65	22	1.15
1L4N	\$.96	6B7	1.15	6U7	\$.65	12A5	1.15	24A	\$.80
1L4S	\$.96	6B8G	1.15	6V6	1.15	12A6	\$.96	25L6GT	\$.60
1L4T	\$.96	6C4	\$.60	6V6GT	\$.72	12A7	1.15	25Z3	\$.54
1L4U	\$.96	6C5	\$.60	6V7G	\$.96	12A8	1.15	25Z6GT	\$.60
1L4V	\$.96	6C6	1.15	6W7G	\$.96	12AM7GT	1.15	28	\$.65
1L4W	\$.96	6C8	1.15	6X5GT	\$.54	12AT6	\$.80	27	\$.54
1L4X	\$.96	6D6	1.15	6Y6GT	\$.85	12BA6	\$.85	28D7	1.15
1L4Y	\$.96	6E5	\$.80	6Y8G	\$.85	12BE6	\$.65	30	\$.96
1L4Z	\$.96	6E5	\$.80					31	\$.96
1L4A	\$.96	6F5GT	\$.80					32	1.15
1L4B	\$.96	6F7	1.15					32L7GT	1.15
1L4C	\$.96	6F8	1.15					33	1.15
1L4D	1.15	6G6G	\$.96					34	1.15
1L4E	1.15	6H6GT	\$.60					35	1.15
1L4F	\$.80	6J5GT	\$.54					35A5	\$.72
1L4G	\$.96	6J6	1.25					35B5	\$.72
1L4H	\$.96	6J7	1.25					35L6GT	1.15

TERMS: 25% with Order
—Balance C.O.D.—F.O.B.
Chicago. Prices Subject
to Change Without Notice.
Minimum Order \$2.00.

FRANKLIN-ELLIS CO. 1313 West Randolph Street
Dept. RN-6 Chicago 7, Illinois

WEAKEST TV CHANNEL

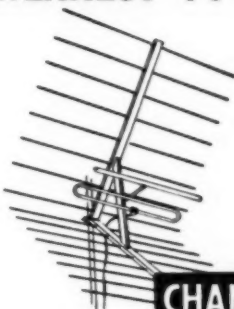

EQUALS
BEST!

with
SUPER GAIN

CHANNEL CHIEF

RADAR SENSITIVITY

Television owners—no "hard-to-get" channel with new radar type square corner antenna. You get a brilliant image on your weakest channel (7 to 13) by attaching "Channel-Chief" to your present antenna. Simple to install. "Channel-Chief" provides a power improvement of 1500% over conventional dipoles. 15° mirror-focus beam eliminates ghosts.

SERVICE MEN—Write for trade discount. Order now! Give channel number—25% dep.—bal. C.O.D.

CHANNEL-CHIEF CO.
37 Mall Dr., North Plainfield, N. J.

ONLY \$2495
Includes
60" Twin Lead



ANNIVERSARY!

We're celebrating with you by reducing our package rates up to 12%. Saving to you now up to 104% compared to Express. Various other reductions. Low cost plus service backed by half a century of courteous efficiency. Write today for our new rates.

Freight Forwarders... Est. 1889

LIFSCHULTZ
FAST FREIGHT
173 W. Madison • Chicago 2

DON'T CRY

FOR BEING OFF FREQUENCY!


Smile, for you know you're in the band with a BC-221 FREQUENCY METER. Completely checked and tested by experts—slightly used but guaranteed to be in GOOD WORKING CONDITION.

While they last, only \$79.50

TERMS: 20% deposit required with order, balance C.O.D. or 2% discount, check enclosed.

GUY WHITE RADIO

654 MULBERRY MACON, GEORGIA

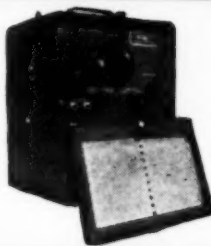

Announcing-

**THE THORDARSON
"24"
Replacement Line**



**Better Quality Transformers
At Standard Replacement Prices**

Everyone appreciates quality! It means satisfied customers—profitable repeat business. THORDARSON'S new "24" line of replacement power and output transformers meets—or exceeds—RMA standards. These high quality replacement transformers are exact replacements for all popular transformers used in the industry... yet they cost you no more than "run-of-the-mill" replacements!

**Enjoy the best — it costs no more!
"24" Output Replacements**

Specific duty transformers available in four models, 2,000 to 25,000 pri. imp. with 5 watts output.

Two models universal output replacements, four or eight watts output, pri. imp. 4,000 to 14,000, sec. imp. .1 to 29 ohms.

**New Universal Line to V. C.
With 70 v. Output Taps**

10 watts with secondary taps from 1/4 to 10 watts.

ATTENTION, SOUND SPECIALISTS:

Write for your Free Copy of the

"THORDARSON REPLACEMENT AND TRANSFORMER GUIDE FOR PRESENT-DAY AMPLIFIERS, TUNERS AND COMMUNICATIONS RECEIVERS."



Manufacturers of quality electrical equipment since 1895.
500 W. HURON ST. CHICAGO 10, ILL.

**Build Your Own
SPOT WELDER**
With This Brand New Transformer Unit **\$18.95**



Perfect as the basic unit for building your own low voltage, high amperage spot welder to operate on house current. Output, 190 amps at 5 volts. Momentary output, 1000 amps or more. For home workshops, industrial plants, garages. Hundreds of other uses. Original gov't cost \$160. Make a professional Spot Welder out of your drill press or any type of press without conversion. Plan and welding information furnished FREE! Shipping wt. 100 lbs.

COMPLETE PICTURE INSTRUCTIONS AND PLANS, alone (including information about new Supreme Spot Welder Kit), 10c

**PE-101-C
GENERATOR
POWER SUPPLY
or
DYNAMOTOR**

For operating your War S u p p l y equipment WITHOUT CONVERSION or your MOBILE RIG.

\$4.95 Brand New as Shown

**AS A GENERATOR
4 Outputs**

- 1) 12V at 12.6 amps or 24V at 6.3 amps
- 2) 400V at .135 amps
- 3) 800V at .020 amps
- 4) 9V at 1.12 amps—80 cycles

Requires small motor. NO CONVERSION NECESSARY. Full operating instructions supplied FREE.

**AS A DYNAMOTOR
3 Outputs**

- 1) 400V at .135 amps d.c.
- 2) 800V at .020 amps d.c.
- 3) 9V at 1.12 amps—80 cycles

Complete with gear box as built for use with BC-645 (not shown) **\$6.95**
Add \$1.35 ea. for mailing charge

SEND STAMPED SELF-ADDRESSED ENVELOPE FOR FREE BULLETIN

**Hermetically Sealed
POWER TRANSFORMER**
Primary: 117V—60 cycles **\$2.95**
Brand New!

Sec:
1) 1100V—C.T.—75 ma
2) 5V at 3 amps
3) 3V at 1.2 amps
Conservative Army rating. Good for high overload.
Add 25 cents each for mailing charge

RL-42-BANTENNA REEL
Brand New! **\$4.25**
With Bobbin. The Perfect Beam Reflector.
Add \$1.00 ea. for mailing charge

Synchronous (Self-Rectifying) VIBRATOR
Hermetically Sealed
Good for 1000 milliamperes. Does not require rectifier tube. Fits standard octal tube socket. Orig. Gov. price over \$5. 12 Volt Model... \$1.29
Add 85c ea. for mailing charge

**DY-9/ARC-1 (24V) or
DY-10/ARC-1 (12/24V)
DYNAMOTOR \$13.95**
Slightly Used
Add \$1.50 ea. mailing charge

**5BP4 Bk. & White
PICTURE TUBE**
Med. persistence—Perfect for television. **\$2.95**
Add 60c ea. mailing charge

**250 HI-POWER
TRANS. TUBE**
Brand New! Orig. Cartons **\$4.95**
Add 60c ea. mailing charge

TELEVISION & SCOPE TRANSFORMER
Brand New. Fully Guaranteed. Sec. tapped to supply either 2200 or 3300 V D.C. Also has 2.5 V insulated winding for 2x2 rectifier. Small size—3" x 2 1/4" x 2 1/4". NOT SURPLUS, BUT ESPECIALLY MANUFACTURED FOR U.S. Add 60c each for mailing charge **\$4.95**

ORDER DIRECT FROM THIS AD. No order less than \$2.50, please. Send check or M.O. Add mailing charges as shown. *Charges include postage, handling, insurance and tax. Heavy materials or large orders shipped fast freight collect. Satisfaction Guaranteed or Money Refunded.

ELECTRONIC SALES CO. Dept. RN-2
3923 VAN BUREN, CULVER CITY, CALIFORNIA

Beginning Amateur

(Continued from page 59)

straight forward in this c.w. transmitter, it worked fine on its fundamental frequency.

A factory-made unit is recommended for the plug-in tuning coil, L_1 . The one specified is neat and cheap, and of a type efficiently constructed that cannot be duplicated easily with ordinary home-shop facilities. In addition to the 40-meter coil listed, there are interchangeable coils for 10, 20 and 80-meter operation, making the transmitter very flexible.

A meter to measure the plate current of V_1 is very important, as this current indicates the condition of the tuning circuit. It costs a couple of dollars, but it is a very smart investment because it can be used with any transmitter you build, and you can be sure that you'll be rebuilding all the time! Flashlight lamps are often recommended as current indicators in "beginner" transmitters, but in my opinion they are not satisfactory. Mount the meter in a small box, fitting it with binding posts and a length of flexible lamp cord for leads, and connect it to the two right hand terminals on the back of the chassis. If it reads backwards the first time you turn on the transmitter, merely reverse the leads.

Generating radio-frequency power by means of modern vacuum tubes is a relatively easy process. The real trick in all short-wave transmitting work is to feed this power to an antenna and to make the latter squirt off some of it into space in the form of radio waves. Antenna theory is very complicated and, in some respects, not very clear, but the practical operation of certain forms of "sky wires" is pretty well understood. The folded dipole antenna makes a good start for the beginner because it is reliable. Use it to get on the air, and do your experimenting with the more complicated styles later on.

The antenna length bears a definite relationship to the operating frequency as determined by the crystal. Several factors for figuring the length of twin lead have been used with success. To get the length in feet, divide 459 by the frequency in megacycles. For our 7.15 megacycle crystal, this comes out to 64 feet, 3 inches. Add three inches for tying purposes, and buy a hunk of twin lead 64 1/2 feet over-all. You'll need another piece for the lead-in or transmission line, and its length will be determined by your location. The idea is to hang the antenna itself as high and as clear as possible, and to let the transmission line take care of itself. It can be as long as 100 feet.

You'll need a helper to stretch out the wire on the sidewalk. Measure off 64 feet, 3 inches carefully, using chalk marks, and spot the center position, also carefully. Trim the insula-

NEVER AGAIN

BRAND NEW—Genuine

WESTERN ELECTRIC

DRIVER UNIT with REFLEX PROJECTOR

\$19.95

Way Below Manufacturer's Cost

A Blast-Proof, Blare-Proof Reflex Speaker with a Projector especially designed for use with the famous WESTERN ELECTRIC DRIVER UNIT.

F.O.B. N.Y.C. 4 For \$75.00

WILL HANDLE UP TO 50 WATT WITH NO DISTORTION

25% DEPOSIT WITH ORDER, BALANCE C.O.D.

MANUEL KLEIN 74 CORTLANDT ST. NEW YORK 7, NEW YORK

tion $1\frac{1}{2}$ inches off of the two wires at one end only of the double wire; push these through one eye of an aerial insulator, twist them on each other, and solder well. Now, before you do the same at the other end, slip the latter through the two supporting holes of the dipole connector block. This is a $1\frac{1}{2}$ inch square of insulating material, designed to facilitate the connection of the transmission line to the flattop antenna section. Pull the antenna out to length, bare the second end, thread the wires through the second insulator, and check the antenna against the chalk marks before soldering.

Slide the connector block to the exact center of the antenna. Cut either wire of the pair, trim back the insulation about $\frac{1}{4}$ inch to each side, and bare the two ends thus formed. Bring one end of the transmission line (which is also the twin lead stuff) up through the bottom hole and the clamping strip of the block, bare its two ends, and join them to the antenna wires under the binding screws in the block. You are now ready to hang the antenna in the spot you have selected, using any strong wire in the other ends of the insulators to tie to trees, poles, chimneys, pipes, etc. Bring the free end of the transmission line into your radio "shack," fastening it where necessary with small stand-off insulators, to prevent swaying. The line connects directly to the two lugs on the L_1 coil socket marked C and D in the diagram. Don't solder it in place just yet.

Tuning up the transmitter itself is simple, since there's only one knob to turn. Plug in the lamp cord, seat the tubes, crystal, and coil firmly in their sockets, connect the key and the meter and turn on the switch, S_1 . Give the tubes 15 or 20 seconds to warm up. Regardless of the position of C_1 , close the key for a second and observe the meter. It will probably jump to a reading of 75 or 85 milliamperes. Close the key again, but this time, turn the knob of C_1 quickly. As you pass

through a certain position, the current will fall to a minimum of about 25 or 30 milliamps and then rise again. Find a setting of C_1 that gives a minimum of about this value as you key the circuit rapidly. Turn on your receiver, and you'll hear a thumping signal, due to direct radiation from the coil L_1 .

Warning: Don't touch anything on the transmitter except the C_1 knob. The coil L_1 carries the full plate voltage (about 350-400 volts) and is hot.

Turn off S_1 .


The coil L_1 , as manufactured, consists of two windings: a large one of 22 turns, connected to the plate circuit of the tube, and a small one of three turns, connected to the antenna through the transmission line. This antenna coil is a little too small to couple properly to lines of the 300-ohm type. Unsolder the inner end of the winding and add two more turns to it. Use common solid push back wire, and hold it down with little strips of Scotch tape.

Now solder the transmission line to points C and D on the L_1 socket, turn on S_1 , wait a few seconds, and press the key. The meter will show a higher reading, maybe up to 100 milliamps. Retune C_1 , a little, and you'll find that the meter dips again, but this time the "low" is about 80 milliamps. The new dip represents the load of the antenna, and means that the latter is accepting power from the transmitter. If you don't obtain a definite new dip of approximately this value, you may have to add or remove a turn from the antenna coil. Just remember to shut off the transmitter before grabbing it! With a little cutting and trying, you'll hit the right number of turns without too much trouble.

You're now on the air! Send a CQ, or call someone who has just sent one himself. When you hear your own call letters coming back at you, you'll know that you have made your first contact.

(To be continued)

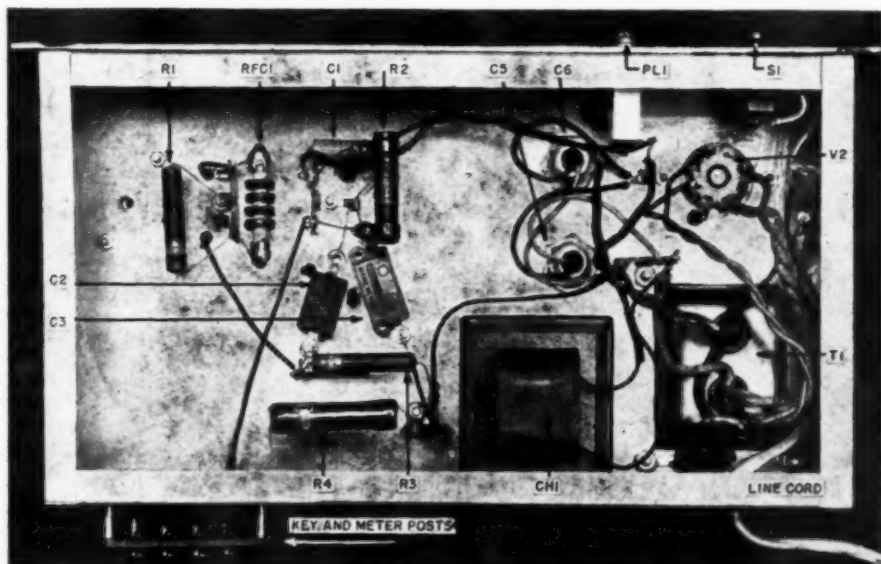Bottom view of the completed transmitter. The wiring is open and readily accessible.



QUESTION


Why do so many television sets use Sprague KOOLOHM Resistors for all 5- and 10-watt wire wound power resistor requirements?

ANSWER

Because Koolohms far surpass other wire wound resistor types in the essential characteristic of resistance stability. Also because, being doubly insulated, Koolohms can be mounted anywhere—even directly against a metal chassis. Koolohms are highly heat- and moisture-resistant. One type—the standard type handles any job. No need to worry about choosing special coatings. Moreover, Koolohms cost no more than ordinary resistors, and are actually cheaper in many cases.

SERVICE HINT

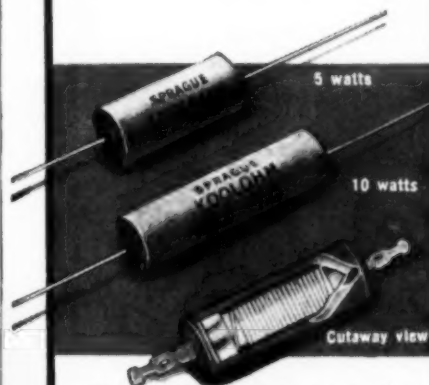Play safe by using Sprague Koolohms in all your work—not only in television, but wherever you want a really first class job. And remember: Koolohms can be used safely at their full wattage ratings, even in enclosed places. No need to buy a 10-watt resistor when the circuit only needs 5-watts. A 5-watt Koolohm dissipates a full 5 watts!



Wound with ceramic-insulated wire. More resistance in less space. Doubly protected, insulated and sealed by outer ceramic jacket. Highly resistant to moisture and heat.

SPRAGUE
KOOLOHM
Reg. U. S. Pat. Off.
WIRE WOUND RESISTORS

SPRAGUE PRODUCTS CO., North Adams, Mass.

(Jobbing distributing organization for products of Sprague Electric Co.)

QUANTITY BUYERS.... SUPER SAVINGS ON TUBES!

Receiving, Special Purpose, and Transmitting
JAN and Commercial, Bulk and Boxed

WRITE—WIRE—PHONE

For Quantity Prices

01A	7Q7	VT67	123A	807
0A2	7V7	VT127A	129R	808
02A	7Z4	VT158	203A	809
1A3	12A6	VU11	205B	810
1A3GT	12C8	VE532A	207	811
1A5GT	12H6	VL530	210	812
1L4	12J5GT	VL531	211	814
1L6	12K7	1826	217C	815
1L6S	12K8	1829	218	816
1LNS	12SC7	1832	224	826
1NSGT	12SF7	1842	227A	827R
1R4	12S67	1851	231D	828A
1R6	12SH7	1P23	250H	832A
1S5	12SJ7	2A46	250TH	836
1Y3	12SK7	1822	250TL	837
2A3	12SL7	2C22	251A	841
2A5	GT	2C26	264C	843
2A6	12SN7	2C26A	276A	851
2A7	GT	2C34	279A	852
3B7	12SR7	2C44	282	860
3Q4	12A7	1921	304TH	861
3Q5GT	1486	2E22	304TL	864
5V4	14Q7	2J21	305A	865
5V4GT	2	2J21A	305A	865A
5V3GT	30	2J22	316A	869
5Z3	33	2J26	327A	869R
5Z4	34	2J27	328A	869R
6A6	35Z5GT	2J31	350A	872A
6AF6	37	2J32	350B	876
6AR7	38	2J33	353A	876
6AC7	39/44	2J34	355A	878
6AJ5	45 SPEC	2J38	361A	885
6AK5	46A0	2J48	371A	889R
6AR6	50B5	2J48	371B	902-P1
6RE6	58	2J49	371	908
6B8	58	2J61	388A	918
6C4	59	2J62	388A	923
6CS	70L7	2J158	393A	924
6CSGT	72	2K29	417A	927
6C8	76	2V30	434A	930A
6CR6	78	3A4	446A	931
6D6G	80	3BP1	446B	931A
6E5	82	3C23	450TH	955
6F5	83	3C23	451	955
6F6	83V	3C24	510	956
6F7G	85	3C31	527	957
6FR6	117Z6	3D23	575A	958A
6H6	117Z7	3DP1	607	959
6HG6	AB150	3DP1	615	957
6J5GT	CB1	3HP7	631P1	991
6J5G	CE186	3J21	700B	CK1006
6J7	CE200	4A-11	700C	CK1007
6K7	CE1005	3C32	700D	1148
6N7GT	CE10	4E27	702A	1201
6O7	EF50	5AP1	703A	1203
6Q7G	ELC1A	5B91	704A	1613
6R7G	F123A	5BP4	707B	1614
6SA7	F129B	5CP1	708A	1616
6SC7	F921	5D1	708B	1619
6SC7GT	F681A	5FP7	710A	1624
6SD7GT	GL434	5GP1	713A	1625
6SF5	GL505	5J23	714AV	1626
6SF5GT	GL559	5J29	715A	1629
6SF7	HF100	6AJ5	715B	1630
6SG7	HF300	6H4	717A	1631
6SH7	HY615	6F4	720AV	1633
6SJ7	OB2	6J4	720CV	1635
6SJ7GT	Q1A	6GP7	720DV	1636
6SK7	RK34	9-3	720EV	1641
6SK7GT	RK60	10F67	721A	1642
6SL7GT	RK63	10T1	721B	1655
6SN7GT	RKR72	10V	722A	1682
6SQ7	RKR73	12GP7	723AB	1851
6V6GT	VC813B	12HP7	724B	7193
6V6G	VR65	15E	725A	8005
7A7	VR75	15R	726A	8011
7B4	VR90	24C1	726C	8012
7C4	VR105	28D7	731A	8016
7C5	VR124	357	750TL	8019
7C7	VR150	15TG	800	8020
7E6	VR314	60TL	801	8025
7F7	VTS	62A	801A	9005
7H7	VT59/	100TH	803	9006
7N7	39	105P	805	38111A

All Tubes subject to prior sale

ELECTRONIC EXPEDITORS, INC.
333 North Michigan Ave., Chicago 1, Ill.
State 2-5615



JOBS IN TELEVISION

YOUNG MEN 16 TO 60

There is a job opening for every qualified
trained Television Technician.

WE CAN TRAIN YOU
FREE EMPLOYMENT SERVICE

Visit Our Modern Laboratories and Class Rooms
Approved Under G.I. Bill of Rights

AMERICAN RADIO INSTITUTE

New York, N. Y. Syracuse, N. Y.
2010 Broadway 131 Shonnard St.
Mt. Vernon, N. Y. Buffalo, N. Y.
174 Gramatan Ave. 640 Main St.

"Teaching Radio Since 1935"

Phone-C.W. Transmitter

(Continued from page 64)

works very well without it, even under the regulation effects present in the PE 103 output circuit due to varying loads. The second item is the 6U5 tube shown at the top of the diagram (modulator) and which functions as a V. I. when talking into the microphone. While these tubes are normally used on circuits having relatively slowly changing voltage, such as a. v. c. circuits, it has been found that they respond rather accurately to voice frequencies and peaks hence one has been adapted for use with the present modulator. The tube requires between two and three signal volts for good operation and functions perfectly at the point in the circuit indicated in the drawing.

The half megohm potentiometer R_1 , Fig. 5, permits setting the eye so that it just closes, on a steady tone, for 100% modulation. Being an electron operated device the shadow has no lag and will be found of great value in keeping a fully modulated, non-spattering signal on the air.

Values of impedance used on the UTC S-20 modulation transformer T_1 are shown on the diagram. While the 4000 ohms primary impedance turns out to be right for the present (and probably other set-ups) the secondary impedance will, of course, vary with the plate voltage and plate milliamperes used by other constructors. The connection sheet accompanying the transformer will show how to obtain other wanted ratios.

In Fig. 1 the modulator controls are, (from left to right) top row; 6U5 volume indicator eye, and the 0-50 milliamperes Weston Model 506 milliammeter with pilot light immediately below it. The lower row (left to right), shows the high impedance or crystal microphone jack, low impedance or carbon microphone jack, "High-Low" impedance switch, (low impedance—second jack when in "down" position), modulation volume control, "Off-On" switch, output power (to transmitter) plug, and input plug (from PE 103 or a. c. power pack).

For rough usage the author prefers a rugged carbon microphone and has a surplus SW 109 unit as used by the Signal Corps. This has been modified by the installation of a surplus F1 unit. This is a single button carbon unit which is used in telephone work and equipment and which has, besides excellent quality, an output of approximately 1 volt when used in the "close talking" position. With this type carbon microphone in the second jack the rig is modulated 100% with the gain control at midpoint.

For different plate voltages it is advisable to experiment with various bias voltages applied to the grids of the final 815 in the modulator. For different plate voltages bias voltages of

from 12 to 22½ volts have been used. The criterion is the quality as determined by listening to a good monitor or receiver.

Power Supply

The power supply used for this rig is a PE 103 genemotor from the surplus market. These may be obtained for under ten dollars in the original overseas packing. They are exceptionally well built and sturdy and, although rated at 160 milliamperes at 500 volts, they are capable of much greater outputs—especially for intermittent service. Fig. 8 gives a set of performance curves for this type device. The curves are self-explanatory. The operating point on the author's set-up is indicated approximately by the 300 milliamperes point on the load curve. In addition these genemotors were designed for short-wave work and have an excellent set of built-in filters so that no external filtering is necessary to achieve a steady, hum-free output voltage.

Several minor changes were made by the author. They were, first, to put a jumper across the resistance labeled 3R2 in the dynamotor base. Immediately above the circuit breakers in the case of the genemotor will be found two flat, rectangular resistors lying one on top of the other. 3R2 is the bottom one and strapping it out takes some resistance out of the 6 volt line from the battery, through the genemotor, to the transmitter. Next, the circuit breaker 3E5 in the 6 volt circuit is strapped out which takes all the remaining resistance out of the 6 volt line. Then, the winding of the circuit breaker 3E3 is bridged with a 10 ohm, 10 watt resistor. Since the original winding resistance was 10 ohms this has the effect of making the breaker trip at between 325 and 350 milliamperes instead of just over 160 milliamperes as originally used. Finally, since the author uses the rig on 6 volts only while portable or mobile, the 12 volt brushes (in the longer end bell casing) were removed to get away from commutator drag. While the genemotor was out of the case the lead going to pin #7 on the output plug was unsoldered since the #7 lead in the connecting cable will be used to carry current from the small 7½ volt battery used in conjunction with an a. c. power pack (for keying) when on c. w.

Extra connecting cables for the PE 103, complete with 8 pin plugs, are available on the surplus market and four of them should be obtained. One will be used between the PE 103 and the modulator unit, another between the modulator and the transmitter. The female plug is removed from the third one and mounted on the front panel of the transmitter for power input. The other (male) plug is also removed and mounted on the front panel of the modulator for power input to that unit. The male plug from the fourth cable is mounted alongside this last plug for a connecting cable be-

tween modulator and transmitter units.

General

Since a rig of this type can be used in the shack, on the road, or at camp on hunting and fishing trips—and on all bands—power is one of the prime requisites for securing results from locations whose topography was not designed for radio transmission and reception. For this reason no circuit short-cuts or tricky construction were used. Rather, every advantage was taken of resonant circuit voltages and other features found in the largest transmitters, thus making for efficiency and for maximum possible output from the transmitter.

The rig has been used on all bands with uniformly good results, especially on 20 meters, since the home shack has a 20 meter beam. The Hawaiian Islands and similar distances are consistent DX while the last entry in the log shows a 5 and 9 signal on phone to KG6CQ on Guam in the Marianas Islands. In short the rig has lived up to every expectation and it is hoped that other builders may equal, if not exceed, these results.

-30-

RENEWING APPEARANCE OF WRINKLE FINISHED EQUIPMENT

ONE common fault of equipment housed in wrinkle finished cabinets is the dull appearance of such apparatus when dusty. Wiping with a dust rag does not remove all of the dust because of the nature of the wrinkle finish. Blowing with an air jet improves the appearance somewhat but does not remove the dullness.

A sure method of restoring the rich brilliant lustre of the original wrinkle finish is to go over it with a rag saturated with a mixture of carbon tetrachloride and light machine oil. Ten per-cent sewing machine oil and ninety per-cent carbon tetrachloride will prove excellent. The solvent quickly evaporates, leaving a thin film of oil on the finish. Periodic maintenance of this type will keep the appearance of the finish like new H.Z.

Clint De Soto Passes Away

Clinton B. De Soto, W1C8D, age 37, editor of "QST" for many years and more recently technical editor of "IRE," suffered a fatal heart attack on the night of April 27, 1949. Clinton De Soto was born in Ogilvie, Minnesota, and held an amateur license since 1926.

A leading figure in amateur radio, scholar, gentleman and capable administrator, "Clint" has left behind a host of grieving friends. He combined literary skill, unusual ability to bring out the best in his associates, and an unflinching devotion to his job. The IRE has lost one of its most capable representatives, and amateur radio, one of its most ardent supporters. The editors of "Radio & Television News" deeply regret the sudden passing of one of their most cherished friends.




What Receiver Would You Like to Have? What Do You Have to Trade-In? I Will Make You the Best Deal!

Nobody can beat Bob Henry on a trade-in! (I make the deals myself.)
Nobody can beat Bob Henry's world's lowest credit terms! (I finance the thing myself.)

Bob Henry gives you immediate delivery on practically anything in the amateur or communications receiver line. (I carry the world's biggest stock.) Bob Henry gives YOU FREE ten-day trial and FREE 90-day service! (I don't want you to buy anything you don't want.)

These are just some of the reasons why Bob Henry sells more receivers than anyone in the world! **EVERYTHING** has some trade-in value. Write me what you have and what you want. We can do business!

Bob Henry
W4ARA

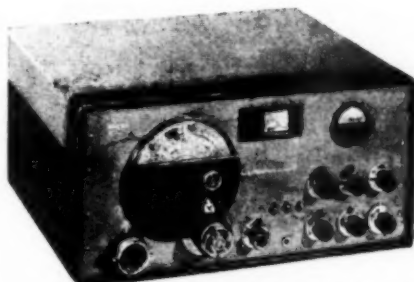

SX-42 Greatest continuous frequency coverage of any communications receiver—from 540 kc to 110 Mc. One superb unit with 6 bands; AM, FM, CW. Finest performance obtainable. **\$275.00**



SX-43 All essential ham frequencies from 540 kc to 108 Mc. In the band of 44 to 55 Mc, wide band FM or narrow band AM, just right for narrow band FM reception is provided. **\$189.50**

COMPLETE STOCK OF ALL HALICRAFTERS RECEIVERS AND TRANSMITTERS

Write for catalog, prices, time sale information

HENRY RADIO STORES

WORLD'S LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS

CUT HOLES FAST IN RADIO CHASSIS




WITH A GREENLEE
RADIO CHASSIS PUNCH

• GREENLEE Punches make this tough job easy. Merely turn with an ordinary wrench . . . make accurate, clean holes in a hurry. No reaming or tedious filing. There's a GREENLEE punch for each of these sizes: 1/8"; 3/16"; 1/4"; 5/16"; 3/8"; 1/2"; 5/8"; 3/4"; 1 1/8"; 1 1/4"; 1 1/2"; 1 3/4"; 2"; 2 1/4"—for cutting holes to take sockets, plugs, etc. Also GREENLEE makes Knockout Punches and Cutters for conduit and meter holes up to 3 1/2". Write for facts. Greenlee Tool Co. 1886 Columbia Avenue, Rockford, Illinois.



Here It Is! . . .

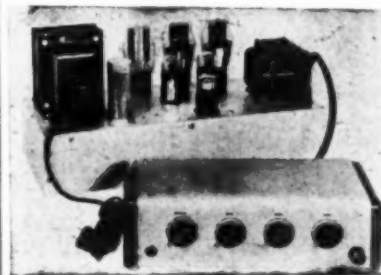

... THE NEW BROOK 10 WATT AMPLIFIER

Yes, this is it—a genuine Brook High Quality Amplifier in the moderate price field. An amplifier of incomparable performance . . . equalling Brook 30-watt models in all respects.

Use of triodes in all stages—together with Brook-designed transformers, permits cleanest amplification ever achieved. Distortion is reduced to the vanishing point.

No matter how discriminating you are, this new Brook All-Triode Amplifier will surpass your most exacting expectations. Hear this finest of amplifiers at your dealer's NOW!

Write TODAY For Free Copy of Technical Bulletin and Detailed Distortion Analysis

BROOK ELECTRONICS, Inc.

Dept. RF-9 34 DeHart Place
Elizabeth 2, New Jersey

SURPLUS BARGAINS

RECYR. & XMITTER

NEW BC-454 (3-6mc.) Recvr & your choice of either a 274N or ARC-5: 4-5.3mc. or 5.3-7mc. Xmr. (slightly used).

BOTH FOR

\$895



BC 450, 7 to 9.1 mc. (new).....	\$14.95
T20 ARC 5, 4 to 5.3 mc.	11.95
T22 ARC 5, 7 to 9.1 mc.	11.95
BC 450, 7-9.1 mc. (used).....	9.95
T22/ARC-5 7-9.1 mc. (new).....	12.95
(Used).....	9.95
T20/ARC-5 4-5.3 (used).....	4.95
274-N Type Trans. 2.1-3 mc. (used).....	7.95
BC 453 190-550 kc. (used).....	9.95
BC 454 3-6 mc. (new).....	9.95
(Used).....	5.95
BC 455 6-9.1 mc. (used).....	15.95
274-N Type Receiver 1.5-3 mc. (new).....	12.95
(Used).....	7.95
12 volt Dynamotor (can be used for above).....	10.95
ARB Recvr 190-9.05 continuous (new).....	1.49
ARB CONTROL BOX (Single or Double Type).....	14.95
BRAND NEW ARN-7/BC 433 Recvr 150-1750 kc. continuous (used).....	14.95
ASB-7 Indicator Unit with Tubes (exc. basic unit for 5" scope) (used).....	14.95

SELSYN XMITTER & INDICATOR



Ideal as Radio beam position Indicator for Ham, Television or commercial use. **\$595** Complete with I-82...

Spare set of Tubes for Command Recvr or Trans. Specify which set..... \$ 1.20
Dynamotor 6 volts DC-300 volts DC 85 ma. 4.95

SCR-522 TRANS. & REC.

With Case & all Tubes, Like New..... \$39.50
BC 375 Tuning Unit, New..... 2.40
FILAMENT TRANSFORMER-110 volt 60 cycle primary.....

12-24 volt at 2 amp..... \$ 2.95
3-24-30 volt at 20 amp..... 3.95
6.3 volt at 6 amp-5 volt at 3 amp-
33 volt at 150 ma..... 1.05

PLATE TRANSFORMER-115 volt 60 cycle primary.....
3200 volts NO CENTER TAP-NEW
Two (2) used SINGLE PHASE FULL WAVE
RECTIFIER CIRCUIT give 2900 volts
WITH 300 ma. LOAD..... 8.95
2 for..... 15.95

540 C.T. @ 150 ma. 5 volts @ 3 amp.;
6.3 volt @ 6 amp.; 5 volt @ 3 amp.;
880 C.T. @ 150 ma.; 6.3 volt @ 4.5
amp.; 1.7 volt @ 5 amp..... 4.95

HEINEMAN CIRCUIT BREAKERS.....
120 volts @ 10 amperes..... .80
120 volts @ 20 amperes..... 1.85
120 volts @ 30 amperes..... 2.40

FL-8 Audio Filter (new)..... \$1.70
Add 40c for postage.
DC Ammeter 60-0-60 (new)..... .97

FILTER CONDENSERS OIL FILLED

2 mfd. @ 600 volts, 3 for.....	\$ 1.39
10 mfd. @ 600 volts.....	.49
1 mfd. @ 1000 volts, 3 for.....	.49
8 mfd. @ 2000 volts.....	3.49
2 mfd. @ 2500 volts.....	2.39
1 mfd. @ 3600 volts.....	2.95
1 mfd. @ 4000 volts.....	3.49
2 mfd. @ 4000 volts.....	4.95
3 mfd. @ 4000 volts.....	5.45
2 mfd. @ 5000 volts.....	5.95

EE-8 FIELD PHONES

Headset, generator, ringer, etc. All in case. Fine for Garage extensions, Installation, work, etc. PHONES TESTED BEFORE SHIPMENT. Used in excellent condition. \$15.95 per pair, \$8.95 each. Remittance with Order. Minimum Order \$3.50. Orders F.O.B. Los Angeles, Calif. Prices Subject to Change without Notice.

ESEGE SALES CO. LTD.

Distributors of Surplus Radio and Electronic Parts
1306 Bond Street at Pico
Los Angeles 15, Calif.

RADIO ENGINEERING IN 27 MONTHS

Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced Radio Theory and Design, Modern laboratory. Low tuition. Self-help opportunities. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Gov't approved for G.I.'s. Enter June, Sept., Dec., March. Catalogue. **INDIANA TECHNICAL COLLEGE**
969 E. Washington Blvd., Fort Wayne 2, Indiana

SPEAKER RECONING

ALL WORK GUARANTEED

3"-\$1.40	7"-\$1.95	15"-\$4.00
4"-1.40	8"-2.20	4x6-1.90
5"-1.50	10"-2.70	5x7-2.20
6"-1.65	12"-3.00	6x9-2.50

OXFORD RECONING SERVICE

1030 Selby Ave. St. Paul, Minn.

TELEVISION PARTS & ACCESSORY CATALOG

Complete lines of the latest equipment
Send penny post card for your copy today

INTERSTATE SUPPLY CO.

24 S. 10th St. St. Louis 2, Mo

Reproducer System

(Continued from page 45)


expander are shown in Fig. 1. The principal elements determining the time constants of the circuit are the load resistor and bypass condenser of the 6H6. Increasing the size of these components will increase the delay and decreasing the values will decrease the delay. A two-megohm potentiometer might be substituted for the fixed load resistor to make a convenient means of adjusting the time delay to various types of music. It will be noticed that the cathodes of the 6SK7 and the 6SN7 are fed from "B+" through a voltage divider. This is necessary to provide good grid bias regulation. The optimum grid bias for the 6SK7 appears to be about 15 volts, while the screen grid voltage will vary from twenty to two hundred volts depending on the degree of expansion or compression.


In operation of the expander, the expander voltage control is turned down and the bias of the 6SK7 adjusted until no signal is heard. The expander voltage control is then advanced until only the loud passages come through the amplifier. The compressor operation is quite similar. With the compression control off, adjust the bias on the 6SN7 until the volume decreases slightly, then ad-

vance the compression control until the loud passages are reduced to inaudibility. A certain amount of delay in either system may be introduced by increasing the bias voltage. In both the compressor and expander, care should be taken that the input signal to the grid of the 6SK7 does not exceed one volt, or disagreeable distortion may result.

Fig. 2 shows the circuit for an interesting form of frequency discrimination when used in connection with an expander or compressor. The circuit allows the expander or compressor to operate when one range of frequencies alone is predominate. High and low frequencies are fed through suitable filter networks to the two halves of a 6H6. As the output polarities of the two diode sections are reversed, when both highs and lows are present, the net output voltage is zero. When the desired frequency range is present alone, an appropriate voltage is developed which operates the expander or compressor. It should be pointed out that the high frequencies, though having high audibility, may have considerably lower actual acoustic power. In averaging orchestral music it has been found that the average power in the three-hundred-cycle region is about ten decibels above that in the two-thousand-cycle region, and for this reason it is desirable in many cases to deliberately attenuate the low frequencies fed to

Fig. 3. Schematic diagram of the 40-watt, dual channel amplifier and volume expander.

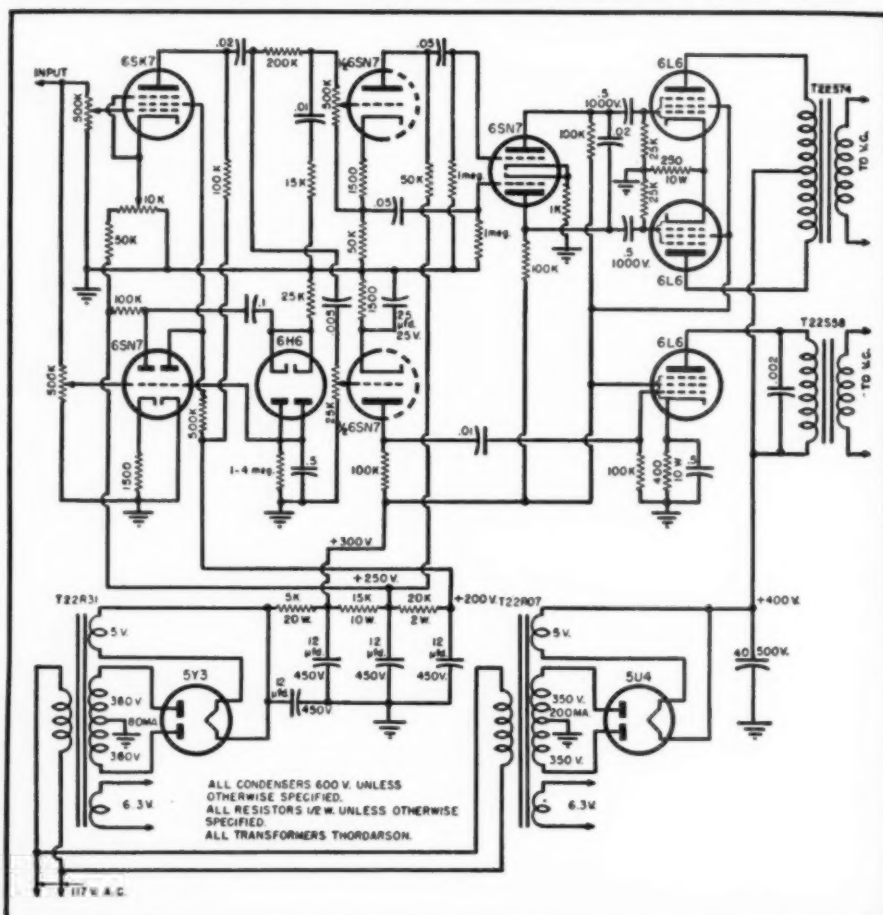

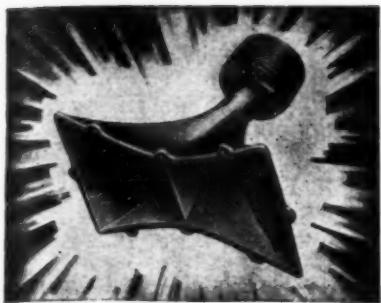

YOURS FOR THE FIRST TIME!

A Moderate priced Cellular Horn that reproduces at HIGH FIDELITY

IF YOU'VE been looking for a high fidelity cellular horn, at a moderate cost, just listen to the clear true-to-life tones reproduced by the new Racon two-cell high frequency horn and you'll agree your search is ended.

Product of Racon advanced engineering, this all cast aluminum high frequency horn is logarithmically expanded as two horns to give the widest distribution angle. Power capacity of unit permits choice of cross-over point which makes best possible use of available cone speakers. Designed for flush mounting in any cabinet. Mounting template supplied without charge.

Tweeter—Model #CHU2 Aluminum casting.
List price\$37.50
Tweeter—Model #CHU1 Standard Acoustic Cloth. List price.....\$30.00

Write today for our catalog

RACON ELECTRIC CO., INC.
52 E. 19th St. New York, N. Y.

SURPLUS CLEARANCE!

The following items were procured from a nationally known laboratory—quantities are limited and subject to prior sale—order today!

Echo Box—Type G.....\$ 8.95
25MFD/13,000 Volts D.C. Solar Capacitor.....\$ 4.95
Automatic Computing Sight Type 57—Sperry.....\$ 4.95
Variable D.C. Supply 0-6KV at 3MA. Dim. 20 1/2 x 17 x 12.....\$39.50
Luminous Tube Transformer—Jefferson 110V—60 Cy.—5000 V., 360MA.....\$ 9.95
Sola Constant Voltage Transformer Inp 95-125 V. 60 Cy. outp—115 Volts 17.4 Amps. 2KW.....\$85.50
Rectifier RA 57A—Western Electric less tubes.....\$45.00
Power Unit 24 Volt 10 Amp output; Input 105-125V. 60 Cycle. Housed in rack 17 1/2 x 13 x 20 1/2. Type PEC 105.....\$49.50
BC 957A Indicator Unit—less tubes.....\$24.95
Aircraft Modulator Unit M.I.T.—E.E. Radiation Lab with Blower and Magnetron Mounting.....\$18.95
Mark 1 Automatic Radio Direction Finder Radio Receiver Pt. 650777.....\$24.50
D.C. Motor 1/10 H.P., 24 Volts 4.6 amp 6000 RPM Holtzer Cabot.....\$ 2.45
Gyroscope Assemblies.....\$ 2.45
Fire Control Amplifier (Sperry).....\$ 2.95
Radio Transmitter 947-A Western Elec.....\$24.50
Range Unit BS-941-A Western Elec.....\$24.50
Control Amplifier Stabilized Turrets—(Sperry) Servo Complete with 4-6V6, 2-V8105 and 2-6SN7 tubes.....\$ 4.95
AM-14/AFT High Frequency Transmitter 80/110 V., 400-2600 Cy. & 24V. D.C.....\$16.95
7 ft. Relay Rack-Enclosed type taken standard 19" Panels; used but perfect.....\$32.50

RADIOSONDE (Weather)

Transmitter AN/AMQ-1D

Includes following: 1—Miniature Battery Transmitter complete with 3A5 tube—operates on 72 mc approx.; 1—Miniature sensitive relay SPDT with 100 ohm coil; 1—Temperature-sensitive resistance element; 1—Humidity sensitive strip; 1—Pressure, temperature, humidity chart, the entire unit is encased in the original packing and is brand new.
Price.....\$4.95



Model NFRD—Radio Noise Filter

If it doesn't work, send it back!

We absolutely guarantee that our Model NFRD will eliminate all line noises when properly connected to radios, television sets, short wave sets, motors, electric shavers, refrigerators, vibrators, oil burners, transmitters, and all other sources of interference. This unit will carry up to 12 amperes or 1 1/2 KW of power and may be used right at the source of interference or at the radio.
Small size only 3"x1 1/2"x7 1/2".
Very low price only.....each \$1.95

Write for Latest Catalog R-6 Listing Thousands of Relays, Resistors, Condensers, Switches, etc.

EDLIE ELECTRONICS, INC.

Telephone Digby 9-3143

154 Greenwich Street New York 6, N. Y.

the expander or compressor voltage control to make the electrical balance better over a wide frequency range. Use of a limiter is also possible.

Using combinations of the above elements, systems employing five or more channels may be constructed, with speakers placed on all four walls and the ceiling if so desired, and with changes in tone color and direction limited only by the ingenuity of the builder.

Fig. 3 is the schematic for an excellent basic system including two power amplifiers with a total power output of forty watts and a wide range volume expander. With slight modifications, this makes a very flexible unit as it may be used in the frequency division system described at the first of the article, with volume expansion applied to one or both of the channels, or in connection with an ordinary radio or phonograph to provide both volume and frequency range expansion. Though volume expanders have never seemed too popular in conventional systems, in multiple channel operation the effect is greatly intensified and more realistic, with best operation seeming to be achieved by placing the speaker fed by a conventional amplifier in the center of the room and the speakers from the high and low frequency amplifiers on opposite sides of the room. Between the quiet passages coming from a single source and the expanded passages coming from all over the room, the contrast is tremendous.

Aside from the expander, the amplifier itself features several novel aspects. A separate power supply is used for the screen grids of the power tubes as well as the driver stages and provides exceptionally good voltage regulation which results in lowered distortion and higher output. A special driver system is used in the push-pull amplifier as it was discovered speaker load impedance variations apparently produced distortion voltages on the grids of the 6L6's. For this reason, extremely low-value grid resistors are used, and the phase inverter is isolated from the output tubes. In listening tests, 6B4's were interchanged with the 6L6's, the difference being almost unnoticeable even though no inverse feedback is used.

In conclusion, the audio enthusiast will undoubtedly find that conventional single channel reproduction sounds dull and drab compared to a multiple channel system.

—50—


SAVE THOSE PARTS

DEFECTIVE selenium a. c.-d. c. rectifiers can be utilized as separate parts, and it is not necessary to dispose of them because they are not perfect.

Using a pair of lineman's pliers, take them apart, and you will find you have seven small, handy metal washers and one fiber washer. If the rectifier has round fins, you will have six large metal washers besides. G.R.J.

HARVEY HAS THE TOPS

AIRCHARGER Model 616

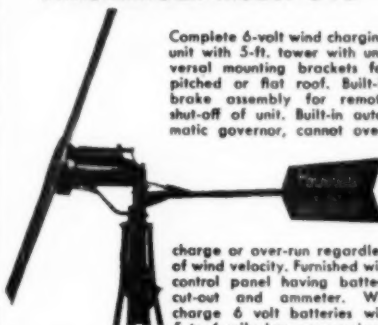

Complete 6-volt wind charging unit with 5-ft. tower with universal mounting brackets for pitched or flat roof. Built-in brake assembly for remote shut-off of unit. Built-in automatic governor, cannot over-

charge or over-run regardless of wind velocity. Furnished with control panel having battery cut-out and ammeter. Will charge 6 volt batteries with 5 to 6 mile breeze; maximum

charging rate 15 amps at 1100 RPM. These units are Brand New in original crates, with full installation and maintenance instructions.

Very specially priced at.....\$34.95

NEW 1949 TECHMASTER TV KIT



Exactly the same as the RCA 630TS chassis, complete kit of parts, including pre-wired and aligned RCA front end, punched chassis, with all major components and sockets mounted, as shown, all RCA tubes including kine, complete manual with service notes, all RCA. New, simplified point-to-point instructions. (Free circuit and parts list on request.)

Shpg. Wt. 85 lbs.....\$198.50

Kit as above but less 10BP4 tube.....\$168.50

Shipping Weight 55 lbs.


12-inch kine tube.....\$49.50

15-inch kine tube.....\$9.50

Available from stock.

FM TRANSLATOR

General Electric Model XFM-1

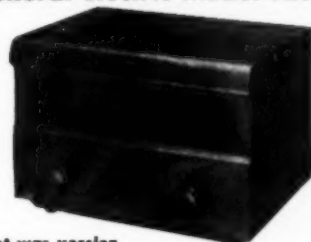

Post-war version of the old G.E. J.F.M.-90 Translator which was used and enjoyed by tens of thousands of discriminating radio listeners.

Covers 88-108 mc range, dial 12 inches long, uses guillotine tuning for highest efficiency, high stability. Designed for export, has power inputs for 110 to 250 volts, 50/60 cy. In attractive natural walnut cabinet—10 3/4" high x 15 3/4" wide x 11 3/4" deep, complete with 8 tubes. Tropic-proof construction. Quantity limited.

Special Price.....\$49.50

NOTE: All prices are Net, F.O.B. N.Y.C.

and are subject to change without notice.

Telephone: LUxemburg 2-1500

HARVEY
RADIO COMPANY INC.

103 West 43rd St., New York 18, N. Y.

RADAR, COMMUNICATIONS AND SONAR TECHNICIANS W-A-N-T-E-D For Overseas Assignments

Technical Qualifications:

1. At least 3 years practical experience in installation and maintenance.
2. Navy veterans ETM 1/c or higher.
3. Army veterans TECH/SGT or higher.

Personal Qualifications:

1. Age, over 22—must pass physical examination.
2. Ability to assume responsibility.
3. Must stand thorough character investigation.
4. Willing to go overseas for year.

Base pay, Bonus, Living Allowance, Vacation add-up to \$7,000.00 per year. Permanent connection with company possible.

Apply by Writing to
**D-4, P.O. Box 3575,
Philadelphia 22, Pa.**

Men qualified in RADAR, COMMUNICATIONS or SONAR give complete history. Interview will be arranged for successful applicants.

LEARN Electricity OR Radio-Television IN THE GREAT SHOPS OF COYNE



TRAIN QUICKLY!
OLDEST, BEST EQUIPPED
SCHOOL of ITS KIND in U.S.
2 Opportunity Fields

Come to the Great Shops of COYNE in Chicago during our 50th Anniversary Year! Get quick, practical training in RADIO-TELEVISION or ELECTRICITY. G. I. Approved. Finance plan for non-veterans. Mail Coupon Today for complete details.

NOT "HOME-STUDY" COURSES!
You learn on real, full-size equipment, not by mail. Finest staff of trained instructors to help you get ready quickly for a better job, a fine future.

FREE BOOKS Clip coupon for big illustrated Coyne book on either ELECTRICITY or RADIO-TELEVISION. Both books sent FREE if you wish. No obligation; no salesman will call. Act NOW!

B. W. COOKE, Pres.
COYNE Electrical & Radio School, Dept. A9-85H
500 S. Paulina Street, Chicago 12, Illinois

Send FREE BOOK and full details on:

☐ ELECTRICITY ☐ RADIO-TELEVISION

NAME.....

ADDRESS.....

CITY..... STATE.....

Within the Industry (Continued from page 24)

sales representative for the Radio Division *Sylvania Electric Products, Inc.*, and in his new post, he will work closely with *Sylvania* radio dealers and distributors in Michigan, Ohio, Indiana, Illinois, Wisconsin, and Minnesota, making his headquarters at 20 N. Wacker Drive, Chicago 6, Ill. The **L. S. TAUFENBACH** organization will serve as sales representative for the Pacific Coast on behalf of the *Radion Manufacturing Corporation* of Chicago. **JAMES L. FOUCH** will direct the sales policy for distributor, industrial, and custom-built items in his new capacity as sales manager for the *Cinema Engineering Co.*, Burbank, Calif., in the fields of TV, broadcasting, and motion pictures. **MID-STATE TELEVISION DISTRIBUTORS CORP.** will distribute the *United States Television* video sets in the Dayton, Ohio, area, from its office at 1808 E. Third Street. In his capacity as sales manager of the Magnetic Recorder Division of *Air King Products Co., Inc.*, **AB WAXMAN** will expand his department's activities to further its program in the rapidly growing industry. **JOHN E. KANE**, with many years' experience in both retail and wholesale distribution of radios and appliances, will serve as district salesman for the eastern portion of the *R. W. Fordyce Company* of Ardmore, Pa. The *Fordyce Company* is the district merchandiser of *Bendix* radio and television for eastern Pennsylvania. **RAYMOND S. PERRY** has been appointed general sales manager of the *Federal Telephone and Radio Corporation*, Clifton, N. J. He will direct all commercial activities of *Federal*, the American manufacturing associate of the *International Telephone and Telegraph Corporation*.

GENERAL ELECTRIC COMPANY, under its education fund, has awarded research fellowships amounting to \$18,460 to fifteen graduate students for advanced study.

Seven of the students received the Charles A. Coffin Fellowship for advanced study in electricity, physics, and the physical sciences. Eight other students were awarded the Gerard Swope Fellowship for advanced study in industrial management, engineering, the physical sciences, and various scientific and industrial fields.

The fellowships are awarded annually on a competitive basis to graduates of universities, colleges, and technical schools who have shown through previous work that they could undertake or continue advanced study either in this country or abroad. Funds for both the Coffin and Swope Fellowships come from the income derived from the \$1,000,000 *G-E* education fund.

Members of the committee selecting the winners represented six leading engineering and scientific organiza-

tions in the country, and these were assisted by four representatives of the *General Electric Company*, among them Dr. W. D. Coolidge, director emeritus of the *G-E* Research Laboratory, and A. D. Marshall, secretary of the fund.

RAY RICE, former publicity director for *Raytheon Manufacturing Company*, has resigned to open his own office at 60 East 42nd Street, New York, N. Y.

Mr. Rice, who has served as publicity director for *Raytheon* for the past four years, retains his staff and has taken over the space previously occupied by the company's publicity department. He will continue, however, to handle the *Raytheon* publicity on an account basis, adding one or two other accounts at a later time.

VINCENT DE PAUL GOUBEAU was recently elected vice-president in charge of the materials department of the *RCA Victor Division, Radio Corporation of America*.

Prior to his joining *RCA* in 1945, Mr. Goubeau served for three years in the Navy Department, as Chief of the Contract Clearance Division, which he organized and administered until elevated to the post of Deputy Chief of Procurement, and later, Chief of Procurement.

Mr. Goubeau is past president of the New England Purchasing Agent's Association and a former director of the National Association of Purchasing Agents. He was born in New York City and attended the De La Salle Institute.

THE NATIONAL VIDEO CORPORATION, a new manufacturer of cathode-ray tubes, located at 3019 West 47th St., Chicago, Ill., is now in full operation. Straight-line production, covering over 518 continuous feet is accomplished in the 40,000 square-foot plant.

President of the company is Mr. A. Cole, who has been in the cathode-ray tube industry for twenty years. New, streamlined machinery and equipment was installed in the plant so that each tube may be produced with a maximum of efficiency. Rigid inspection is given each finished product to help insure perfect tube construction.

A. H. NICOLL, president of *Graybar Electric Company*, was recently elected president of the New York Rotary Club. A member of the Club since 1939, he stepped up from the office of first vice-president to succeed Harry D. Schmedes.

A member of the Rotary Club's Board of Directors for the past four years, he is also a member of the Executive Committee of the National Electrical Wholesalers Association, a Trustee of the Union Dime Savings Bank, a member of the Board of Gov-

RADIO & TELEVISION NEWS

ernors of the Union League Club of New York, and a member of the Advisory Committee of the Chase National Bank's Grand Central Branch.

-30-

"MARS" PROGRAM OPEN TO AMATEURS

MEMBERSHIP in the National Guard Military Amateur Radio System is open to any Guardsman or recruit who possesses an amateur radio operator's license, it was recently announced by Major General Kenneth F. Cramer, Chief, National Guard Bureau. MARS activities would be in addition to the regular weekly armory training of the National Guard and purely on a voluntary basis.

Under the plan, "radio hams" may now gain experience and training as members of the recently-authorized service-wide system which will establish amateur radio networks in the armed forces. It provides an opportunity for amateurs to become a part of the communications system that would play a vital part in the defense of the United States in case of emergency.

The National Guard network would fit into the nationwide service MARS network in this way: The amateur operators would work their own sets at home and report to their local MARS Station Director at the armory or air base, and he in turn would check into a state net by reporting in to the state MARS Director or net control station—there will be one each for the Army and Air Guard in each state. These in turn will be netted into the numbered Army or Air Force MARS Directors and then, in a final check, would net in with Headquarters at Washington, D. C.

Amateur radio operators interested in participating in the MARS program and who can qualify for membership in the National Guard should contact the Adjutant General of their respective states or the nearest Guard armory or air base.

-30-

ERRATA

In the article, "Audio Transient Distortion," page 39, April 1949 issue, the oscilloscope patterns shown at top of page were arranged incorrectly. The individual pictures should be from left to right, top to bottom, F, A, C, B, D, and E.

...

The screen and suppressor terminals on tubes V₁ and V₂, page 60, April 1949 issue, are shown in the wrong sequence. To correct the error, interchange these two terminals.

...

PHOTO CREDITS

Page	Credit
29, 30, 31, 32.....	Keesler Air Force Base
33.....	U. S. Signal Corp.
36, 37.....	Workshop Associates, Inc.
38.....	Julian Krupa
41, 43.....	Motorola
53.....	Milwaukee Journal
82.....	Wide World
90.....	U. S. Army

SURPLUS BARGAINS

FM REC. BC 603

For 10 and 11 meters. 20 to 30 mc. superhet. BFO, squeeze; 10 push-buttons and manual tuning. Makes fine wide-band IF strip for 88-108 mc. FM with converter. Includes 10 tubes, speaker, case, and diagram. 12 volt. Used, good\$12.95

Radio Transmitter & Receiver APS 13. 410-420 mc. light weight, fully enclosed; 30 mc. I.F. Complete with 17 tubes, including 5/6J6, 9/6AG5, 2/2D21, 1/XR105. Brand new with manual.....\$17.95
APS 13 Racks. New.....1.00
Handy Talkie Batteries. Good condition BA-37 1.50
BA-38 1.00

COMMAND REC.

Used, Good.
BC453—10-550 kc.\$12.95
BC454—3-6 mc.5.95
BC455—6.9-1 mc.6.95
6 1/2" CONTROL CABLE
for above command
sets1.00



CONDENSERS

Variable 3-gang; 5.5-24mmf/sect.
New.....\$1.29
(5 for \$5.00)



CHOKES

2 1/2 Milli-Henry (Miller).
New.....25c ea. (4 for \$1.00)



INSULATORS

Porcelain Feed Through Type.
New.....1 doz. \$1.00



CLIMBING EQUIPMENT

Safety belt, leather, used, Good.\$2.95 ea.
Pole climbers and straps, used,
Good1.95 pr.



R-5/ARN-7 COMPASS RECEIVER

Includes broad-
cast band. Freq.
100-1750 kc. in 4
bands. 5-gang
tuning capacitor.
15 tubes: 4/6K7,
1/6L7, 1/6J5, 2/
6B8, 2/6F6, 1/
6N7, 1/6SC7, 2/
2051, 1/5Z4. Like
new.\$14.95 ea.
BC-433G Com-
pass Receiver,
Like new. \$14.95



Send 25% with Order. Balance C.O.D.
All Equipment F.O.B.

C & H SALES CO.

1850-C East Colorado St., Pasadena 8, Calif.

THE "ALL PURPOSE" TELEVISION KIT

10" 12 1/2" 15"

\$89.50

LESS TUBES



FEATURING

- Latest Type of Circuits
- AGC—Automatic Gain Control
- Picture and Sound Automatically Locked
- Sound Cannot Drift
- Non-Microphonic
- Stagger Tuned I.F. for Max. Gain and Ease of Alignment
- 12 Channel Tuner
- Electromagnetic Focus and Deflection
- Automatic Stabilized Synchro—Lock Circuit Holds Picture Steady
- Voltage Regulated Circuit for Stability

Large clarified stage by stage pictures and schematics to insure ease of construction. Guaranteed to work.

Money Back Guarantee—Buy it, inspect it, if you don't think it's the best buy on the market—return unused within 5 days and your money will be refunded.

All prices F.O.B. New York. 20% deposit with order.

IMMEDIATE DELIVERY


SOVEREIGN TELEVISION CO.

5508 New Utrecht Ave.

Bklyn 19, N. Y.

LICK low signal strength with a HIGH GAIN QUALITY Dielectric Duoband Antenna

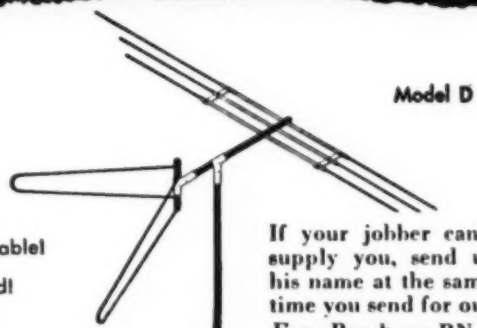The DIELECTRIC DUO-BAND, Model D (illustrated) — just one of the complete line of DIELECTRIC antennas— is designed to give excellent results on all channels, in low signal strength areas.



- Durable!
- Easily installed!
- No interfering high frequency unit needed. One DUOBAND — one lead . . . that's all you need!

If your jobber can't supply you, send us his name at the same time you send for our Free Brochure RN-1, which illustrates field patterns!

Dielectric PRODUCTS CO., Inc.

125 Virginia Ave. Jersey City 5, N. J.



SEND FOR FREE BROCHURE RN-1

SURPLUS BARGAINS

BC 375 GE-100 Watt Transmitter with tubes and one Tuning unit.....\$12.95

Retary Beam Drive Mechanism: Here is the well known PROP PITCH OR FEATHERING Motor used by hundreds of Amateurs for rotating directional beam antennas. Has 3 ton thrust bearing and 1/6 HP 24 Volt AC or DC motor. Will handle dual 3 element 10 and 20 meter beams. No back-lash and has gear reduction ratio of 9576:1. Good clean condition. Tested before shipment.....Price \$17.95
Converted and modified ready for unlimited rotation in either direction for AC or DC operation.....Price \$21.45

Transformer: 110 Volt 60 Cycle primary, 10 or 20 volt secondary for use with above motor.....Price \$2.95

Sound Powered Telephone Handset—No Batteries needed......Only \$3.95

1/4 inch Electric Drill 110 Volts AC or DC with Jacobs Hex Key Chuck.....\$18.95
With Jacobs Geared Chuck.....\$20.95

Table Microphone T32—with switch, 6 ft. cord & plug. One of the Army's Best. Ideal for Factory call system. Public address, amateur use.....Only \$2.45

6 Volt Pioneer Dynamo—600 Volt output @ MA DC. 5.6 Volt @ 28 Amp input. Size 6 x 5 inches. Ideal for mobile rig in car or boat. New. Only \$19.95

BC 325 Transmitter.....\$450

Government Manuals on BC 101, 221, 311, 342, 603, 604, 610, 659, 683, 684, SCR 284 or 508. \$1.75 each
BC 603.....\$16.50 BC 604.....\$22.95

Send for our new Electronic Bulletin.

ABELL DISTRIBUTING CO., Dept. N-7
5 E. Biddle Street Baltimore 2, Maryland

LEARN RADIO!

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
COMMERCIAL OPERATOR (CODE)
RADIO SERVICEMAN

Television Servicing

(Approved for Veterans)
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALT. 17, MD.



HOW TO GET THE MOST FROM YOUR RADIO "KNOW-HOW"

Learn all about a new, simplified way of fixing radios. Nothing complex to learn, no calculating. Used by beginners and experts. Send for FREE manual, "THE INSIDE STORY," today. 28 pages—illustrated—easy to read! Shows how obsolete methods prevent full use of your real ability. Explains use of NEW techniques. You owe it to yourself and your future to "get out in front" in your work.



SEND COUPON OR PENNY POSTCARD FOR FREE MANUAL TODAY!

FEILER ENGINEERING CO., Dept. 6H5
945 George St., Chicago 14, Illinois
Please RUSH my FREE copy of "The Inside Story"

Name

Address

City.....Zone.....State.....

Classified

Rate 20c per word. Minimum 10 words

RADIO ENGINEERING

SPECIAL Instrument panels made for Custom Constructors, Designers. Complete Service. Gilpin, Box 638, Rte. 4, Mt. Clemens, Mich.

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N., Valparaiso, Ind.

SALE

SELL Philco tube tester, Model 7050. Like new condition, \$35.00. Raleigh R. Mitchell, 821 Sewanee St., Harriman, Tenn.

SPECIAL parts made to your specs. Very reasonable. Leo J. Vince, W8FYA, 2805 E. 117th St., Cleveland 20, Ohio.

NC-100ASD RECEIVER, 1,300 to 30,000 Kilocycles. Best offer or trade for RME-84. Gabriel Cassetta, 352 S. Duquesne Ave., Duquesne, Pa.

SURPLUS: BC221 Frequency Meters, clean and in perfect condition \$49.50 each. Send orders to Monarch Electric Company, 411 Wood Street, Pittsburgh 22, Pa.

ALUMINUM Tubing, angles, sheets, fittings for complete beam. Write for list. Willard Radcliff, Fosterla, Ohio.

BROWNING AM-FM tuner RJ-12 with Browning installed drift compensating network and PF-12 power supply, \$80.00. Garrard Intermix record changer with G.E. variable reluctance cartridge, \$30.00. Roy Johnson, 1590 Unionport Road, New York 62, N. Y.

CODE tapes—Radiotelegraph practice tapes, designed for FCC preparation, Advanced, Beginners. Fits most phototube keyers. \$2.50 postpaid. Write Ultradyne Electronics, Oswego, Oregon.

POWELL Model B portable wire recorders. New. Professional quality. Records full hour. Seven available. List price \$225.00. Take one or all at \$75.00 each. G. A. Terpay, 7005 Wells Parkway, College Heights Estates, Maryland.

RECORD Changer Parts for leading makes of changers. We ship everywhere. Mail orders invited. Friend's Wholesale Distributors, 106 North Sixth St., Philadelphia 6, Pa.

RADIO Service Shop quitting business. Write for bargain list on test equipment and parts. John Hays, 162 W. Union St., Virginia, Ill.

HICKOK 156 Tracometer 3 months old, \$140. G. Bellis, 874 Lincoln Ave., Maywood, N. J.

TEST Equipment, Signal Generators, TV Sets and kits, Sewing Machine Motors, rebuilt Vacuum Sweepers. Bargains. Bendix, 727 N. Euclid Ave., Pittsburgh 6, Pa.

FILTER Choke Assembly: New 2 section 250 ohm D.C. resistance per section, breakdown voltage 1500 R.M.S. metal case. Order Today: \$6.75 each. General Mdse. & Equipment Co., Dept. 2A, Box 18, Sharon, Pa.

NEW 663-A RCP electronic voltmeter \$30.00, cost \$49.50. Hickock OS-10 signal generator with 0-10,000 cycle B.F.O. built in db meter, excellent, \$33.50. Solar condenser checker with AC-DC V.T.V.M., \$22.50. Supreme 561 new \$90.00. W-5MMK. H. E. Wirth, Bay City, Texas.

12B8 & 25B8 TUBES, Adapter Unit using 2 miniature tubes (6AT6 & 6BA6 for 12B8, and 12AT6 & 12BA6 for 25B8). Takes less space than original tube—nothing else to buy—just plug in & it works. Money-back guarantee. 12B8 or 25B8 unit complete: \$2.49 each. 10 units for \$22.50. Send 25% deposit, balance C.O.D. Write for free parts catalog. Commercial Radio, 36 Brattle St., Boston, Mass.

POWER & Lighting Plant: Portable, compact 110 volt A.C. 60 cycle 800 watts. (Same as house service) direct driven by 2 1/2 H.P. to 3 H.P. Latest designed engine. This Month Special direct from builder \$235.00. F.O.B. Sharon, Pa. Order Today. General Mdse. & Equipment Co., Dept. 2 B, Box 18, Sharon, Pa.

VACUUM tube voltmeter plans. Special feature give appearance (and performance) equal to factory built. Use parts you have. Plans, 10c. Hawkins Radio Co., 621 E. 31 St., Kansas City 3, Mo.

COAXIAL Cable. Identical characteristics as RG-58/U. Send dime for 3-foot sample. Harry H. Van Dick, Box 236, Little Falls, N. J.

RADIOS, record players, tubes, parts; send for free list. Mr. Morillo, Mike's Radio Service, 173 E. 101st St., New York 29, N. Y.

TOGGLE Switches, new H & H arrow 3 amp DPDT, ball handle, stem length 1/4", 4 for \$1.00, 9 for \$2.00. Rectifier capacitors, surplus Aerovox, 2000 mfd 35 VDC \$2.50 each. All items postpaid in U.S. Kissel Electric Products, 431-N. Sherman, Gallon, Ohio.

RADIO Diagrams under seven tubes 30c, over six tubes 60c. Television Diagrams \$1.00, with service data, \$2.00. State manufacturer and model number. Kramer's Radio Service, 36 Columbus Ave., New York 23, N. Y.

BC-348, LIKE new 110VAC, \$78. BC-314, like new, \$40. E. J. Czerwinski, 2835 Elm, Toledo, Ohio.

GRILL Cloth, Celanese, light and dark pieces, 1000 square inches for \$1 bill. Write for list of lowest priced national brand parts in nation. Burma Radio, Route 5, Grand Rapids, Mich.

TELEVISION, radio, tubes, parts. Send for free bargain list. Hallmark, 592 Communipaw, Jersey City, N. J.

BARGAINS: New and reconditioned Hallicrafters, National, Collins, Hammarlund, RME, Meissner, other receivers, tuner, television receivers, transmitters, amplifiers, speakers, etc. Lowest wholesale prices. Terms. Shipped on trial. Liberal trade-in allowances. Write. Henry Radio, Butler, Mo., and 11240 W. Olympic, Los Angeles, Calif.

BARGAIN Hunting? Radio Servicemen write. Sensational catalog. Henshaw Radio Supply, 3619 Troost, Kansas City 3, Mo.

HEARING Aids, Zeniths, others. All used but working. Make miniature transmitters or receivers. Complete with cords, ear piece, \$20 ea. Shelby Instrument, 321 W. 7th, Long Beach, Calif.

LOWEST Prices Radio Tubes, parts. Bargain lists, 3c. Potter, 1314 McGee, Kansas City 6, Mo.

WRITE Dept. RN18 for our free wholesale list of Radio parts & accessories. R. C. Radio Parts & Distributing Co., 731 Central Ave., Kansas City 6, Kan.

HOTTEST surplus list in the country. Electronics-Hydraulics, Aircraft-Gadgets. Dick Rose, Everett, Wash.

TWIN-LEAD: 300 ohm; \$1.65 per 100 feet. Send stamp for sample. Harry H. Van Dick, Box 236, Little Falls, N. J.

WANTED

AN/ART-13, BC-348, RTA-1B, AN/APN-9, R5A/ARN-7, AN/ARC-1, AN/ARC-3, BC-788-C, I-152, MN-26. Test sets with TS- or I-prefix, Dynamotors, Control Boxes, Transmitters, Receivers, Power Supplies, etc. State quantity, condition and best price first letter. HI-MU Electronics, Box 105, New Haven, Conn.

WANT To Buy a few BC-654 Transmitter-receiver sets or complete SCR-284A sets. Must be New or Good Clean-used condition. Write giving condition of set or sets available with listing of components and price asked. W. H. Gilman, 2144 S. Kedzie Ave., Chicago 23, Ill. Phone Bishop 7-6340.

WESTERN Electric CF-1, CF-2, CF-3, CF-4, CF-5, CF-6, H, H-1 Carrier, EE100, EE101A ringing equipments. All models teletype. All models RCA Marine transmitters. Box 485, % Radio & Television News, 185 N. Wabash Ave., Chicago 1, Ill.

SITUATIONS WANTED

SELECTED group of men, graduates of well-known trade school, desire employment in Radio Field. Will travel anywhere. Qualified in radio servicing, installation, test instruments, circuit operation, etc. Contact Placement Dept., Eastern Technical School, 88 Purchase Street, New Bedford, Mass.

COMMERCIAL Operator. First Phone and Telegraph desires assignment overseas. Box 19, North Buena Vista, Iowa.

HELP WANTED

EXPERIENCED men to take charge of radio maintenance department for small scheduled airline. Write to Box 483, % Radio & Television News, 185 N. Wabash Ave., Chicago 1, Ill.

INSTRUCTORS in Electronics and Radio. Prefer former Navy Radio Technician instructors willing to locate in the Detroit, Mich., area. Write to Box 452, % Radio & Television News, 185 N. Wabash Ave., Chicago 1, Ill.

SALESMEN to sell Nationally Advertised Brand Radio Tubes to Dealers and Servicemen at liberal discounts. Good commissions paid. Box 480, % Radio & Television News, 185 N. Wabash Ave., Chicago 1, Ill.

PATENT ATTORNEYS

LANCASTER, Allwine & Rommel, Registered Patent Attorneys. Patent practice before U.S. Patent office. Validity and Infringement investigations and opinions. Booklet and form "Evidence of Conception" forwarded upon request. Suite 414, 815 15th St., N.W. Washington 5, D.C.

HERMAN Lewis Gordon, Registered Patent Attorney. Patent Investigations and Opinions. Warner Building, Washington, D. C.

CORRESPONDENCE COURSE

HAM License! Got yours yet? If you find Morse Code difficult write for Free Code Memorizing lesson. Complete course \$1.00. Dept. R, Otto Luther, New Preston, Conn.

AMATEUR radio licenses. Complete code and theory preparation for passing amateur radio examinations. Home study courses. American Radio Institute, 101 West 63rd St., New York 23, N. Y.

USED Correspondence courses and books bought, sold, rented and exchanged. Catalog free. Lee Mountain, Pisgah, Alabama.

USED Correspondence Courses and Educational Books, bought, sold, rented. Catalog free. Educational Exchange, Summerville, Ga.

MISCELLANEOUS

HERE'S a natural for you electrically inclined people. Active coin machine business in Indian Head Resort Country in immediate area of over 15 million dollars public works projects. Virtually all post war equipment. Complete stocks of records and repair parts. Thriving year around business. Write John Kalasardo, Ladysmith, Wis.

F. M. CONVERTER, old to new band, with instructions. Paine, Cornelia St., Boonton, N. J.

VITAL radio information for beginners to engineers published in 13 radio magazines instantly located with monthly cumulative index. 200 listings add each issue. One year of index service \$1.50; two years \$2.25. Indexes for 1946 through 1948 available. Postcard brings full details free. Radiofile, 255 W. 84th St., New York 24, N. Y.

TECHNICAL Report No. 101. Practical Transformer design, construction and repairing. \$2.00 Postpaid. Conrad Roeschke, Buckhorn, New Mexico.

27 YEARS of experience Radio Repairing. Simplified system. No calculations. No formulas. Total price \$2.00 postpaid or C.O.D. Moneyback guarantee. Ross Radio, 14615 Grandriver, Detroit 27, Mich.

BRITISH Company prepared to accept from an American financial group or Radio and Accessory Manufacturers proposition for manufacturing under British patent license in America, the highly successful invention of Radio Intercommunication now being sold in great numbers in many parts of the world. Write to: Messrs. Cominphone Ltd., 8/10 North Audley St., London, W.1.

QSL-SWLS Postpaid! Samples free. W1HJ1, Box 32, Manchester, N. H.

RADIOMEN, Servicemen, Beginners. Make more money, easily, quickly. \$250 weekly possible. We show you how. Information free. Merit Products, 216-32R 132 Ave., Springfield Gardens 13, N. Y.

ELEMENT One revision complete, Elements Five and Six newly released questions only with answers for Radio-telegraph exams; one dollar. A. A. McKenzie, 245 Poplar Ave., Fairmont, Hackensack, N. J.

RADIO
and **TELEVISION NEWS**
Classified Columns
Really Bring Results
Use Them Frequently

TALK ANYWHERE INSTANTLY TO ANYONE!

JUST PUSH BUTTONS AND WITH INTERTALKIE


TALK TO OR FROM 1 to 7
DIFFERENT PLACES! Not a phone-volume—NO ELECTRIC "PLUG-INS" OR TUBES NEEDED! Sit or hang it! SIMPLE AND QUICK TO HOOK UP. For HOMES, OFFICES, STORES, FARMS, etc. Guaranteed satisfaction. Write for FREE details today!
SALES AGENTS as low as \$9.97 each
WANTED.



MIDWAY CO., RN-6, Kearney, Nebr.

June, 1949

The Meissner 9-1091-C AM-FM Tuner

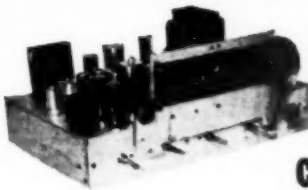

**THE IDEAL COMPONENT
FOR CUSTOM INSTALLATIONS**

COMBINES FIDELITY WITH STABILITY

Servicemen and others interested in custom installations will be quick to appreciate the many top features of the MEISSNER 9-1091-C AM-FM Tuner.

Here is real quality—precision workmanship—outstanding design, all combined to give you the very highest fidelity reception and at remarkably low price. Frequency response—sensitivity both are phenomenal! Compare the specifications below and your choice will be the MEISSNER 9-1091-C Tuner.

MEISSNER is designing a high fidelity amplifier for this tuner. Watch for the release announcement.

See The 9-1091-C Tuner At Your Jobber
Or Write For New Meissner Catalog

Features

- Frequency Response flat with plus or minus 2 db 30 to 15,000 cycles
- Bass Control provides 10 db boost at 40 cycles
- Treble suppression of 12 db at 8,000 cycles
- Input Jack for Crystal or high level magnetic type phono pickup
- Sensitivity less than 10 microvolts
- "Broad" or "sharp" selectivity for AM
- Hum level 60 db below full output
- Output 11 volts high imp. terminals, 2 volts on 500 ohm terminals
- 300 ohm FM antenna input. FM antenna and line act as efficient AM antenna

MEISSNER

MEISSNER MANUFACTURING DIVISION
Maguire Industries, Inc., Mt. Carmel, Illinois



*The Book that takes
Drudgery out of
Mathematics*

Only
\$1
postpaid

**SOLVES EVERYDAY
PROBLEMS
HELPS YOU GET
AHEAD IN LIFE**

How many times have you lost money because of a mistake in figuring? Do you know how to figure quickly and correctly? Can you figure discounts, interest rates, taxes and all the other calculations you meet up with in your daily life?

Are you having trouble qualifying for Civil Service Exams or Armed Services Promotions, because you're not up on mathematics?

Here is the book that gives you a good background in mathematics; that takes all the irritation and drudgery out of it. You don't need to be scared of mathematics, because here's the subject explained without tricks, without useless computations. Here's the book for men in Radio jobs; for business men; technicians and craftsmen, explaining and answering everyday mathematic problems in easy-to-understand words and illustrations.

Yes, it's the key to a simple understanding of mathematics. It's a real home-study course in mathematics for the man who's alert to its importance in the world today.

ELEMENTARY MATHEMATICS

● EASY — SIMPLIFIED — PRACTICAL ●

CONTENTS OF BOOK

- CHAPTER I. Arithmetic—Addition—Subtraction—Multiplication—Division.
- CHAPTER II. Factoring and Cancellation—Fractions—Decimals—Percentage—Ratio and Proportion.
- CHAPTER III. The Metric System.
- CHAPTER IV. How to Measure Surfaces and Capacity (Geometry).
- CHAPTER V. Powers and Involvement—Roots and Evolution.
- CHAPTER VI. Mathematics for the Manual and Technical Craftsman—Thermometer conversions—Graphs or Curve Plotting—Logarithms—Use of the Slide Rule.
- CHAPTER VII. Special Mathematics for the Radio Technician.
- CHAPTER VIII. Commercial Calculations—Interests—Discounts—Short Cut Arithmetic.
- CHAPTER IX. Weights and Measures—Useful Tables.

Send Stamps, Cash or Money Order.
Send Today for Your Copy of This Indispensable Book. It Can Be Carried Readily in Your Pocket.
(Size 6 1/2 x 9 in.)

ONLY

\$1

POSTPAID

TECHNIFAX

110 N. Franklin St., Chicago 6, Ill.



**HERE'S A
"REAL" SPECIAL!
RADIO-AMPLIFIER
STEEL CABINETS**

Handsome multi-use cabinets, made for RCA. Will beautifully any RADIO or ELECTRONIC EQPT., AMPLIFIER, POWER SUPPLY, TEST, INDUSTRIAL, or MEDICAL APPARATUS. Sloping dial (6 1/2" x 1 1/2"); GLISTENING CHROMIUM GRILLE & SIDE TRIM. Marine grey wrinkle finish. Overall: 16 1/2" x 23 1/2" x 10 1/2". Shpg. wt. 10 lbs. BRAND NEW! WHILE THEY LAST

→ **VARIABLE CONDENSERS:** 2-gang Super-het (2 1/4" x 1 1/2" x 1 1/2"), closes left; or TRF (2 1/4" x 2 1/4" x 1 1/2"), closes right. Ball-bearing shafts. Shpg. wt. 1 lb.

EXPERIMENTAL TUBES: Assortment of 20 receiving types for Testing, Research, etc. All filament tested.

→ **ALNICO MAGNETS:** NEW "EXPERIMENTAL" KIT of 10 asstd. powerful Bar, Block, "U," Circular, etc., types. Shpg. wt. 2 lbs. Kit of 10 for ONLY

SAVE TIME! SAVE MONEY!

REPAIR YOUR OWN SPEAKERS with these professional kits!

SPEAKER REPAIR KIT: The "BIG" kit—worth many times its price in convenience. Contains 25 asstd. mtg. rings, 10 spiders, 25 voice coil forms, 3 yds. felt strip, 20 chamois leather segments, kit of 16 shims in leather case, tube speaker cement, WITH INSTRUCTIONS. Shpg. wt. 5 lbs.

ONLY

SPEAKER CONE KIT: A LEOTONE SPECIALTY SINCE 1927! Handy assortment of 4" to 12" top quality moulded & free edge (magnetic incl.). Less voice coils. Kit of 12 asstd.

SPECIAL BARGAIN OFFER! BOTH "REPAIR & CONE KITS" FOR ONLY

SURPLUS ARMY FIELD WIRE (W-110B): twisted pair, all-purpose wire for indoor or outdoor use: Radio, telephone, or bell wiring. 7-strand steel & copper. Available only in coils 200 to 450 ft. Specify min./max. length desired. Shpg. wt. 4 1/2 lbs. per 100 ft. NOW AT THE RIDIC. 1/2¢ PER FT.!

Min. order \$2.00—20¢ deposit on all C.O.D.'s. Please add sufficient postage—extra refunded.

LEOTONE RADIO CO.
68 Day Street
New York 7, N. Y.

HOW TO CRACK the IRON CURTAIN OF LANDLORD RESISTANCE TO ROOF TOP ANTENNA CHAOS

KILL
THIS



USE
THESE



SOUNDCRAFT Multivideo Connectors

Any good antenna and 300 ohm feedline will operate many TV receivers with the same performance as if using separate antennas. Non-cumulative insertion loss of only 4 db. No cutting or boring of feedlines.

List Price \$12.85

REEVES *Soundcraft* CORP.
10 EAST 52nd STREET - NEW YORK 22, N. Y.

To REEVES SOUNDCRAFT CORP.
10 EAST 52nd ST., NEW YORK, N. Y.

PLEASE SEND STORY AND DISCOUNTS . . .

NAME _____

ADDRESS _____

INDIVIDUAL ☐

DEALER ☐

SAVE

at **RADIONIC** the
House of Radio and Television Buys

► **TV RECEIVER** The famous RCA 630TS design 91 sq. in. picture. 30 tubes. Beautiful cabinet. **\$295**

► **TV ANTENNA** H1-Lo freq. 2 dipoles with reflectors. 8 ft. steel mast. Hardware, brackets, insulators, complete. **\$7.25**

► **TRANSFORMER** RCA model. 400V @ 200 ma. 6.3V @ 4A., 5V @ 3A. Shell type, universal mounting. Shpg Wt: 9 lbs. **\$3.95**

► **SPEAKER** Genuine RCA, 10 watt, 12" speaker. Powerful Alnico V magnet. 3.2 ohm voice coil. New. Beautiful design. **\$3.95**

TUBES Standard brands up to 80% off. Send for list

RADIONIC EQUIPMENT COMPANY

Tribune Theater Entrance
170M Nassau Street :: New York 7, N. Y.
WO 2-0421 :: Open daily 9 to 6--Saturday 9-5

FREE! MAIL TODAY!

GET YOUR COPY AT ONCE!
of RADIONIC'S Bargain Catalogs, Radio & Television Sets--Parts--Accessories. Unbelievable Values!

RADIONIC EQUIPMENT CO., Dept 56
170M Nassau Street, New York 7, N. Y.

Please rush Free Copy of your latest Bargain Catalog of Radio and Television Sets, Parts, Tubes and Accessories.

NAME _____

ADDRESS _____

STATE _____

CITY _____

INDEX OF

Advertisers

JUNE
1949

[While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.]

ADVERTISER	PAGE	ADVERTISER	PAGE
Abell Distributing Co.	150	Leotone Radio Co.	151
Acorn Electronics Corp.	119	Liberty Electronics, Inc.	117
Airborne Sales Co., Inc.	131	Lifschultz Fast Freight	141
Alliance Manufacturing Company	16	Lincoln Engineering School	133
Allied Radio Corp.	9	Mallory & Co., Inc., P. R.	2nd Cover
Almo Radio Company	95	Martin School of Radio Arts, Don.	123
American Radio Institute	144	Marvin Radio-Television	134
American Television & Radio Co.	128	Mass. Radio School	132
Amplifier Corp. of America	115, 124	Melssner Manufacturing, Division	
Arrow Sales, Inc.	94	Maguire Industries, Inc.	151
Art Radio Company	109	Mid-America Co., Inc.	82
Ashe Radio Co., Walter	87, 116	Midway Sales Co.	125, 151
Atastatic Corporation, The	86	Midwest Radio & Television Corp.	86
Audio Development Co.	101	Miles Reproducer Co., Inc.	133
Baltimore Technical Institute	150	Milwaukee School of Engineering	78
Bell Telephone Laboratories	18	Mosley Electronic Specialties	153
Billiey Electric Company	14	Murray Hill Books, Inc.	86
Bilas Electrical School	127	McGee Radio Company	73, 71, 75
Bogen Co., Inc., David	86	Nation Wide Radio	122
Brook Electronics, Inc.	145	National Company, Inc.	114
Burlington Instrument Co.	24	National Radio Institute	3
C. & H. Sales Co.	149	National Schools	17
Camburn, Inc.	106	Nescorp Electronics, Division of National	
Candler System	116	Equipment & Supply Co., Inc.	79
Cannon Electric Development Company	80	New Jersey Radio & Television Tube Co.	132
Capitol Radio Engineering Institute	25, 92	Newark Electric Co.	96
Centralab, Division of Globe-Union, Inc.	20, 21	Newark Surplus Materials Co.	112
Certified Television Laboratories	116, 127	Niagara Radio Supply Corp.	83
Channell-Chief Co.	141	North American Electronics Company	115
Chicago Industrial Instrument Co.	96	Offenbach & Reimus Co.	118
Cinaudagraph Speakers, Division of		Olin Industries, Inc.	13
Airon Mfg. Corp.	78	Opad-Green Company	107
Cinex, Inc.	133	Oxford Reconing Service	146
Clear-Vac Co.	93	Peak Electronics Co.	140
Cleveland Institute of Radio Electronics	5	Photocon Sales	115
Clippard Instrument Laboratory, Inc.	78	Pine Watch Co.	131
Columbia Electronics	126	Potter Radio Co.	106
Comet Electronic Sales Co.	129	Precision Electronics Inc.	102
Commercial Radio Institute	119	Progressive Electronics Co.	130
Communications Equipment Company	81	Pyramid Electric Company	22
Cosmic Counters	129	RCA Institutes, Inc.	129
Coyne Electrical & Radio School	118	R & M Radio Company	139
DeForest's Training, Inc.	7	R & T Electronics Company, Inc.	123
Dielectric Products Co., Inc.	149	Racon Electric Co., Inc.	147
Editors and Engineers	98, 99	Radio Apparatus Corp.	137
Eddie Electronics, Inc.	147	Radio Craftsmen, Inc., The	131
Electro-Technical Industries	120	Radio Ham Shack Inc.	91
Electronic Expeditors, Inc.	144	Radio Kits Company	153
Electronic Instrument Co., Inc.	135	Radio Mail Orders	113, 124, 132
Electronic Sales Co.	142	Radio Parts Co.	105
Electronic Supplies	138	Radio Supply & Engineering Co., Inc.	108
Electronics Institute, Inc.	121	Radionic Equipment Company	152
Engineering Associates	119	Reeves Soundcraft Corp.	152
Esege Sales Co., Ltd.	146	Sams & Co., Inc., Howard W.	12
Espey Manufacturing Company, Inc.	133	Sangamo Electric Company	123
Fair Radio Sales	137	Senco Radio, Inc.	125
Federal Telephone and Radio Corporation	4th Cover, 16	Sonotone	72
Federated Purchaser, Incorporated	100	Soverign Television Co.	149
Feller Engineering Co.	150	Spartan School of Radio and Electronics	100
Franklin-Ellis Co.	141	Spellman Television Co., Inc.	99
General Electric Company	6, 26, 27, 65	Sprague Products Co.	143
General Electronic Distributing Co.	77	Stahl, Inc., Michael	88
General Test Equipment	113	Standard Radio & Electronic Products	102
Goodheart, R. E.	132	Standard Transformer Corporation	117
Greenlee Tool Co.	145	Sun Radio & Electronics Company, Inc.	153
Greylock Electronics Supply Co.	127	Sun Radio of Washington, D. C.	102
Hallcrafters Co., The	28	Superior Instruments Co.	92
Harvey Radio Company Inc.	147	Supreme Publications	23
Heath Company, The	67, 68, 69, 70, 71	Sutton's Wholesale Electronics, Bill	131
Henry Radio Stores	145	Sylvania Electric	15
Hiway Company	92	TAB	85
Hollywood Sound Institute, Inc.	129	Technical Radio Parts Co.	124
Hytron Radio and Electronics Corp.	3rd Cover	Technifax	151
Indiana Technical College	146	Telemarine Communications Co.	132
Instructograph Company	125	Television Assembly Co.	19
Instrument Associates	96	Telex, Inc.	127
Interstate Supply Co.	146	Thordarson	142
JFD Manufacturing Co., Inc.	136	Transvision, Inc.	10, 11
Jensen Industries Inc.	106	Tri-State College	125
Jensen Manufacturing Company	106	Triplett Electrical Instrument Company	28
Jerrold Electronics Corp.	84	Tyler Commercial College	89
Johnson Co., E. F.	104	Valparaiso Technical Institute	113
Klein, Manuel	142	Vertron Corp.	103
Leetrom, Incorporated	124	Walmar Distributing Co.	116
Leeds Radio Co.	121	Ward Products Corporation	90
Lehigh Television Company	111	Weller Manufacturing Company	8
		Wells Sales, Inc.	154
		White Radio, Guy	141
		Wholesale Radio Parts Co., Inc.	110
		Workshop Associates, Inc., The	24
		World Radio Laboratories, Incorporated	113

Mobile TV UNIT

(Continued from page 53)

reaches the home station through the use of telephone circuits. On most remote broadcasts, a crew of 10 or 11 men is needed. In addition, personnel are needed in the TV control room and at the transmitter at Radio City.

Before the new mobile unit was received, two portable cameras had to be transported to the scene on ordinary trucks. As they were the only cameras for television which were owned by WTMJ-TV, it was quite a problem for the engineers to set up the portable cameras for both studio and remote broadcasts. Now two studio-type RCA cameras for television work have been received, making more extensive programming possible. Until the new cameras arrived, studio and remote broadcasts could not be scheduled in the same broadcast segment.

In the mobile truck, the following special equipment for TV operation in the field is installed: A complete 7000 megacycle microwave transmitter and its four-foot parabolic antenna; three complete television camera chains with synchronizing generators and master monitor switching and power supplies; complete remote audio amplifiers, with cases containing six different types of microphones for various types of broadcasting; compartments for camera tripods, announcers' video monitor and view finders; camera cable, 500 feet, on reels, 250 feet of power cable, and 500 feet of microphone cable. A complete power distributing panel with power metering and voltage regulators.

In November, 1948, the mobile unit made its longest trip to do a remote broadcast. This was to Wrigley field in Chicago for the Green Bay Packer—Chicago Bear game. Most broadcasts from Chicago are network programs, but this particular one was exclusive with WTMJ-TV and, therefore, all operations had to be handled by the station. At any rate, the mobile TV truck proved itself in the test. —30—



BUILD AND SAVE WITH RADIO KITS

2-BAND RECEIVER

Enjoy both standard broadcasts and the logging of foreign and distant stations. 6 tube circuit of advanced design: RF amp, 12SK7, Converter 12SA7, IF 12SK7, Det and 1st Aud 10 12SQ7, Output 35L6, Rectifier 35Z5, 5" speaker. Tuning range 530 kc-1600 kc, 6 mc-16 mc, 110 volts AC-DC. Complete with handsome cabinet. Ask for **KIT MODEL 5-6X, \$17.45 only**.....



Signal Generator

150 Kc. to 34 megacycles on fundamentals. Can be extended to cover over a 100 megacycle range on strong harmonics. 110V AC power supply. 400 cycle oscillation may be used internally for modulating the signal or externally for audio testing purposes. Ask for **KIT MODEL 562, \$18.95 only**.....



VACUUM TUBE VOLTMETER

• 6SN7 bridge type voltmeter circuit
• 0-500 microamps DC 4 1/2" square meter
• 11 megohms DC, 6.5 megohms AC input resistance, .01 ohms to 1000 megohms in 5 ranges. Linear AC-DC volts 0-1000 volts, 5 scales, 6H6 balanced linear diode AC rectifier, 10% precision resistor. The perfect instrument for signal tracing and dynamic testing. Ask for **KIT MODEL \$23.95 012, only**.....

COMBINATION KIT for High Voltage and High Frequency Testing

Complete outfit includes Kit Model 012 plus two probes, High Frequency Probe up to 10 KV and High Voltage Probe up to 100 Mc and over. Ask for **KIT MODEL 012-X, only**.....



ALL KITS SOLD LESS SOLDER AND WIRE
Jobber and Export Inquiries Invited!
FREE—Send for Catalog P of all Radio Kits

RADIO KITS COMPANY

120 Cedar Street, New York 6, N. Y.

See RADIO KITS At These Leading Distributors!

ALABAMA
Birmingham.....Ack Radio, 223 N. 22nd St.

ARIZONA
Phoenix.....Radio Specialties, 401 W. Jackson

ARKANSAS
Little Rock.....Carlton Radio, 109-11 W. Ninth

CALIFORNIA
Inglewood.....Acorn Radio, 630 So. La Brea
Los Angeles.....Kierulff & Co., 820 W. Olympic
Los Angeles.....Radio Equip., 312 West Pico
Pasadena.....Empire Electronic, 37 E. Union St.
San Bernardino.....Geo. Hagley Co., 1216 D St.

CONNECTICUT
New Haven.....Ammrad Co., 920 Howard Ave.

FLORIDA
Tampa.....Tampa Radio Tele., 2706 Florida

GEORGIA
Atlanta.....Concord Radio, 265 Peachtree St.
Savannah.....Specialty Distrib., 223 E. Broughton

ILLINOIS
Chicago.....Concord Radio, 901 W. Jackson Blvd.
Chicago.....Newark Electric, 223 W. Madison

KENTUCKY
Lexington.....Kentucky Radio, 351 W. Short St.
Louisville.....Electronic Serv., 119 S. Sixth St.

LOUISIANA
New Orleans.....Allen Supply, 918 N. Claiborne

MASSACHUSETTS
Boston.....Foto Radio, 257 Huntington Ave.
Boston.....Radio Wire Tele., 110 Federal St.

MISSOURI
St. Louis.....Walter Ashe, 1123 Pine St.

NEW JERSEY
Jersey City.....Hallmark Elec., 592 Cummingsway
Newark.....Radio Wire Tele., 24 Central Ave.

NEW YORK CITY
Bronx.....Fordham Radio, 2260 Jerome Ave.
Manhattan.....Bonadio Radio, 89 1/2 Cortlandt St.
Manhattan.....Douglas Radio, 128 Greenwich St.
Manhattan.....Newark Electric, 242 W. 55th St.
Manhattan.....North Radio, 172 Washington St.
Manhattan.....Radio Dealers, 154 Greenwich St.
Manhattan.....Radio Wire Tele., 100 Sixth Ave.
Manhattan.....Rand Radio, 84 Cortlandt St.

NEW YORK STATE
Hempstead, L. I.....Island Radio, 412 Fulton
Mount Vernon.....Hadelco, 246 West 1st St.

PENNSYLVANIA
Philadelphia.....Penn Electronic, 5303 Frankford
Philadelphia.....Radio Electric, 7th & Arch St.
Reading.....Geo. D. Darby Co., 2nd & Penn St.
Sunnyvale.....Electronic Sales, 734 Market St.
Wilkes-Barre.....General Radio, 287 S. Main St.

TENNESSEE
Memphis.....Bluff City Distrib. Co., 905 Union Ave.
Memphis.....Memphis Sporting Gds., 162 N. Main
Nashville.....Curry's, 109 Sixteenth Ave. South

TEXAS
San Antonio.....Amateur Hdgtrs., 828 Brooklyn

VIRGINIA
Bristol.....Bristol Radio Supply, 31 Moore St.
Norfolk.....Ashman Distrib. Co., 807 Granby St.

WASHINGTON
Walla Walla.....Kar Radio, P.O. Box 878


If Kits Are Not Available at Your Local Supplier,
Write to Us Giving Supplier's Name

MULTI-SOCKETS!

CATALOG 300S



For single crystal holder with 1/2" spacing. Will also receive MOSLEY CAT. 300P PLUG for deadending 300 ohm line.

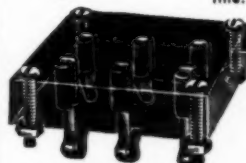

CATALOG 53

A three-way socket for mounting 3 crystals with 1/2" pin spacing side by side.




CATALOG 56 receives 6 crystals mounted side by side.

MOSLEY MULTI-SOCKETS are one-piece units that can be installed easily with the four screws provided.

MOSLEY CRYSTAL HOLDER ADAPTERS



(Catalog 5-75)
Fits 1/2" crystal holder to 1/4" spacing.

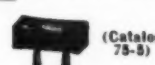

(Catalog 75-5)
Fits 3/4" crystal holder to 1/4" spacing.


FOR SALE AT YOUR JOBBER

MOSLEY ELECTRONIC SPECIALTIES

(W0FQY)

2125 LACKLAND RD OVERLAND 4 MO

New All-Triode 10W Hi-Fi Amplifier Kit!

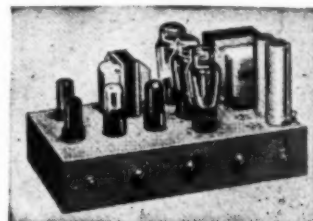

SUN RADIO AMPLIFIER, MODEL CR-10

Build This High-Quality, All-Triode, Self-Biased, High-Fidelity Amplifier For Only... **\$42.50**

From the design published by Consumers Research, Inc., of Washington, N. J.

Brilliant amplifier for use with FM/AM tuners and changers. Compare these specifications! Freq. Response: 20-15,000 c.p.s. ± 1 db. Built-in pre-amplifier and equalizer for use with magnetic cartridges. Hum level: 60-70 db. below rated output at radio input. Distortion: less than 2.5% at 10 watts; 2.5% at mid-frequencies at 11.8 watts. Gain: radio, 75 db.; phono, 97 db.; magnetic pickup, 117 db. at 50 c.p.s. Complete with all 7 tubes, components, punched chassis, hardware, etc., and simplified step-by-step instructions. Order now!

Laboratory-wired and tested.....**\$69.50**

SUN RADIO

AND ELECTRONICS COMPANY INC

122-124 DUANE STREET

New York 7, N. Y. BR 5-1840
2 BLOCKS NORTH OF CHAMBERS ST

RELAYS

FOR EVERY PURPOSE

Over a Million in Stock!

Whether you require large quantities of relays for production runs or single units for laboratory or amateur work, Wells can make immediate delivery and save you a substantial part of the cost.

Our capable engineering staff is prepared to offer assistance in the selection of correct types to suit your exact requirements.

Each relay is brand new, standard make, inspected, individually boxed and fully guaranteed.

The following list represents only a tiny portion of our relay stock. Write or wire us for information on types not shown.

STANDARD DC TELEPHONE RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-101	24V	1500	DPST (NO)	Auto. Elec.	\$1.35
R-102	24V	400	SPDT	Auto. Elec.	1.10
R-103	24V	400	3PST (NO)	Auto. Elec.	1.35
R-105	24V	600	3PST (NO)	Clare	1.20
R-106	24V	1300	3PST (NC)	Clare	1.25
R-152	12V	50	DPDT-SPST (NO)	Guardian	1.10
R-153	12V	200	SPDT-SPST (NO)	Stromberg	1.25
R-154	12V	200	SPST (NO)	Clare	1.20
R-155	12V	100	SPST (NO/NC)	Auto. Elec.	1.15
R-158	6V	50	4PST (NO)	Stromberg	1.10
R-159	6V	50	DPST (NO)	Stromberg	1.10
R-160	6V	12	3PDT-3PST (NO)	Auto. Elec.	1.05
R-161	6V	10	3PST (2NC-1NO)	Auto. Elec.	.90
R-121	150V	5000	2PST (NO) SPDT	Clare	1.65
R-123	150V	6300	SPDT (NO)	Clare	1.75
R-602	150V	6500	3PST (NO)	Clare	1.75
R-515	24V	750	SPST (NO)	Clare	1.25
R-517	12V	250	DPST (NO)	Clare	1.20
R-519	250V	14000	SPDT	Auto. Elec.	1.95
R-520	250V	14000	DPDT	R.B.M.	2.10
R-521	32V	1000	DPDT	Keilage	1.20
R-166	24V	DUAL 200	DPDT-SPST (NO)	Stromberg	1.59
R-168	24V	DUAL 200	4PST (NO)	Auto. Elec.	1.20
H-240	250-350V	40000	DPST (NO)	Auto. Elec.	2.95
H-241	48V	650	DPST-SPST (NO)	Clare	1.25

TYPE 18 DC TELEPHONE RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-109	24-48V	4000	SPDT	Auto. Elec.	\$1.50
R-110	24-32V	3500	SPDT	Auto. Elec.	1.50
R-112	90-120V	6500	SPST (NC)	Auto. Elec.	1.75
R-114	24V	500	4PST (NO)	Auto. Elec.	1.30
R-603	24V	400	DPST (NO)	Auto. Elec.	1.25
H-238	24V	150	DPDT-SPST (NC)	R.B.M.	1.25
H-239	24V	180	DPST (NO)	Auto. Elec.	1.25



SEALED DC TELEPHONE RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-125	24V	300	DPDT	Clare	\$2.75
R-126	90-120V	2000	DPDT	Clare	3.00
R-504	24-70V	2800	SPDT	GE-C103C25	3.00

V TYPE DC TELEPHONE RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-164	24-32V	1000	SPST (NO)	W.E.	\$1.20
R-512	24-48V	3500	DPDT	W.E.	1.30
R-513	12-24V	300	DPDT-SPST (NC)	W.E.	1.20
R-514	4-6V	60	SPDT	W.E.	1.05
R-526	6V	35	DPDT-SPST (INC-1NO)	W.E.	1.05

AC-STANDARD TELEPHONE RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-217	90-135V	—	NONE	Clare	\$0.95
R-213	5-8V	—	DPST (NO)	Clare	1.50
R-605	24V	—	3PST (NO)	Auto. Elec.	.95
R-606	24V	—	DPST (1NO-1NC)	Auto. Elec.	.95
R-607	24V	—	SPST (NO)	Auto. Elec.	.95



DIRECT CURRENT MIDGET RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-132	24V	300	DPDT	Clare	\$1.20
R-133	24V	300	NONE	Clare	.60
R-134	24V	250	4PDT	Clare	1.15
R-135	24V	300	SPST (NC)	Clare	1.15
R-137	24V	300	SPDT	Clare	1.15
R-138	24V	300	4PST (NO)	Clare	1.15
R-139	24V	200	4PDT	Clare	1.15
R-140	24V	280	SPDT	R.B.M.	1.15
R-141	24V	2800	3PST (NO)	R.B.M.	1.15
R-142	24V	400	DPDT	Allied Cont.	1.20
R-143	24V	280	SPST (NO)	R.B.M.	1.15
R-144	24V	250	SPST (NO)	Allied Cont.	1.15
R-145	24V	300	DPST (NO)	Allied Cont.	1.15
R-146	12V	125	DPST (1NO) (1NC)	Clare	1.10
R-147	9-14V	75	SPDT	Guardian	1.05
R-148	12V	100	DPDT-SPST (NC)	Price Bros.	1.10
R-149	6-8V	45	SPST (NC)	Clare	1.00
R-150	6V	30	SPST (NO)	E-Z Elec.	.95
R-522	2-6V	2	SPST (NO)	R.B.M.	.65
R-523	90-125V	6500	DPDT	Clare	1.90
R-222	12V	100	DPST (NO)	P.B.	.95
H-242	24-32V	300	DPDT	R.B.M.	1.20
H-243	24-32V	300	4PDT	R.B.M.	1.20



SENSITIVE DC RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-218	4-6V	1800	SPDT	Kurman 220C	\$1.95
R-220	75V	5000	SPDT	Allied Cont.	1.20
R-221	18-24V	5000	SPST (NO)	Allied Cont.	1.15
R-174	250V	5000	DPST (NO)	G.M.	1.85
R-175	350V	11000	DPDT-SPST (NO)	G.M.	2.95
R-176	24V	250	DPST (NO)	G.M.	1.50
R-177	24V	300	4PDT	G.M.	1.65
R-600	8-12V	500	SPDT	S-Dunn KS	2.10
R-507	24-48V	1000	SPDT-SPST (NC)	Guardian	1.15

TYPE 80 DC RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-169	24V	250	SPST (NO)	Allied Cont.	\$1.95
R-171	24V	230	DPDT	Allied Cont.	2.15
R-172	5-8V	30	DPDT-SPST (NO)	Allied Cont.	1.70
R-173	2-6V	5	SPST (NO)	Allied Cont.	1.25
R-529	24-48V	1000	DPDT	Allied Cont.	2.50

TYPE 8J DC RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-204	12V	45	SPST (NO)	Allied Cont.	\$1.15
R-205	24V	240	DPDT	Allied Cont.	1.25
R-224	12V	75	SPST (NO)	Allied Cont.	1.15
H-237	27V	230	DPDT	Allied Cont.	1.25

HEAVY DUTY KEYING RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-248	28V DC	150	SPST (NO) 10A	Guard 36471	\$1.05
R-244	75V AC	265	SPST (NO) 20A	Guard 1327	1.75
R-206	24V DC	150	SPDT-3 AMP	PAB KL	1.20
R-207	24V DC	210	4PDT-3 AMP	PAB KL	1.10
R-219	50V DC	1500	DPST (NO) 15A	PAB SP	1.25
R-217	115 AC	600	SPDT 10 AMP	St. Dunn IXAX225	1.25
R-525	24V DC	200	DPDT 10 AMP	Guard 34454	1.25
R-508	110 AC	600	SPDT 6 AMP	Guard 37189	1.95
R-506	24V DC	300	SPST (NO) 6A	—	.95
R-510	24V DC	200	3PDT 10 AMP	Guard 516983	1.05
R-604	24V DC	200	SPST (NO) 30A	St. Dunn B2A	1.25
H-608	115 AC	35	SPST (NO) 20A	St. Dunn IXAX225	1.05
R-620	12V DC	35	3PST (NO) 10A	Guard-BK2	1.35
R-223	28V DC	150	SPST (NO) 40A	Price Bros.	1.35
H-230	12-24V DC	80	DPST (NO) 10A	—	1.20
H-231	24V	230	DPST (NO) 5A	R.B.M.	1.15

DC-TYPE 76 ROTARY RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-197	9-16V	70	DPDT	Price Bros.	\$1.65
R-198	9-16V	125	DPDT (3NO) (3NC) SPDT	Price Bros.	1.65
R-199	24-32V	250	SPDT DPST (NC)	Price Bros.	1.65
R-200	24-32V	275	3PDT-SPST (NC)	Price Bros.	1.65
R-201	24-32V	250	DPST (NO) SPDT (NC) DPDT	Price Bros.	1.65
R-601	9-14V	60	SPST (NO)	Price Bros.	1.65



DIRECT CURRENT KEYING RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-199	12V	65	DPDT 10 AMP	Advance Elec.	\$1.15
R-191	28V	125	DPDT 10 AMP	Type 2000-A	1.20
R-192	12V	44	3PDT 10 AMP	Allied Cont.	1.35
R-193	5-8V	11	DPDT 10 AMP	Type NBS	1.05
R-194	24V	265	SPST (NO) 10A	Type 1027	1.05
R-195	6V	32	DPST (NO) 10 AMP	Type 1054SNW1	25
R-196	12V	50	DPDT 3 AMP	G.E.Co.	1.15
R-242	24V	170	DPDT 10 AMP	Guardian	1.15
H-236	5-8V	82.5	SPDT 2 AMP	Type 1253DEW	1.25
				Leach-HFM	8.05

CUTLER HAMMER HEAVY DUTY CONTACTORS



Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-178	24V DC	100	SPST (NO) 100A	6141N34A	\$1.15
R-179	6V DC	6.5	SPST (NO) 50A	6041H33A	1.00
R-180	12V DC	25	SPST (NO) 50A	604H308	3.25
R-181	24V DC	65	SPST (NO) 100A	6041H8B	3.65
H-232	24V	55	SPST (NO) 50A	Metal Cased	3.25
H-233	6V	15	SPST (NO) 50A	Type B6	1.15
H-235	24V	70	SPST (NO) 100A	Type B6	3.65

DIRECT CURRENT AIRCRAFT CONTACTORS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-182	28V	80	SPST (NO) 25 A	Guardian	\$1.85
R-183	24V	60	SPST (NO) 50 A	Allen Bradley	2.75
R-184	28V	50	SPST (NO) 100A	General Elec	2.95
R-185	24V	100	SPST (NO) 50 A	Leach 5055ECR	2.75
R-186	24V	132	SPST (NO) 50 A	Leach 7220-3	243.50
R-187	24V	100	SPST (NO) 50 A	Allen Bradley	2.95
R-188	24V	200	SPST (NO) 75 A	Allied Cont.	2.95
H-234	14V	45	SPST (NO) 30 A	—	1.85

ANTENNA CHANGEOVER RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-192	6-12V DC	44	2PDT 10 AMP	Allied-NBS	\$1.95
R-231	12VDC	100	DPDT 6 AMP	G.E.	1.90
R-256	24-32V DC	—	SPDT-SPST (NC)	Guardian	1.45
R-501	110 AC	4	DPDT (1KW)	G.E.	2.45
R-503	12-32V DC	100	SPDT-SPST	G.E.-500W	1.95

COMBINATION PUSH BUTTON AND REMOTE RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
H-244	12-24V DC	Dual-60	SPDT	CR2791-R106C8	\$1.65

ADJUSTABLE TIME DELAY RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-246	115 AC	—	SPST (NO) or (NC) 10 AMPS	R. W. Cramer	\$8.95
				1-120 Sec.	

DC MECHANICAL ACTION RELAYS

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-245	12V	25	4" Lever	G.M.	\$6.95
R-527	6-12V	200	2" Lever	—	.95

TYPE C.M.S. RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-511	24V DC	200	MICRO-SW. SPST (NO)	Clare	\$2.45

DC CURRENT REGULATOR

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-509	6-12V DC	40	SPST (NC)	G.E.	\$2.85

LATCH AND RESET RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-500	12V DC	10	DPDT-10 AMP	St. Dunn	\$2.85
				CX-3130B	

DC-ROTARY STEP RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-621	6-12V	10	3 POLE 23 POSITION	W.E.	\$10.95

DC-RATCHET RELAY

Stock No.	Operating Voltage	Coil Resistance	Contacts	Manufacturer	Net Each
R-230	5-8V	2	SPDT-SPST (NO)	Guardian	\$2.15

Special Sample Engineering Offer

